

ELECTRONICS

Australia

HIFI NEWS



MAY, 1975
AUST 80c* NZ 80c



**LOW COST SOLAR
CELLS: HOW SOON?**

PAL-S DECODER

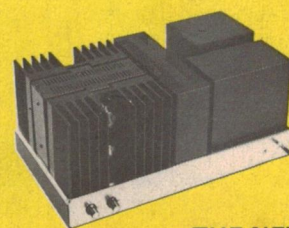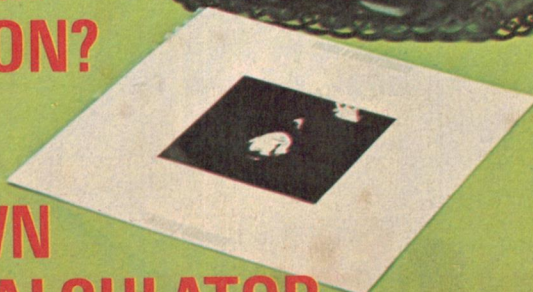**BUILD YOUR OWN
SLAVE FLASH, CALCULATOR**



**THE NEW
POWER FET AMPLIFIERS**

Now, Sony gets it all together for youbeautifully.

SCORPIO[×]. . . The Supreme Sound System.

A new high in high-fidelity — designed to grace the finest of homes.



The Scorpio System

Powerful Integrated Amplifier — TA 1130. Offers 200 watts/8 ohms I.H.F. constant power, direct-coupled circuit to cut out noise and distortion. Rich, smooth sound from many sources — player, tuner, tapes, auxiliaries. Turnover switches retain highs and lows at soft levels. Frequency from 20 Hz.-200 kHz. Extremely low signal-to-noise ratio. Harmonic distortion less than 0.05% at 1 W output.

Photo-Electric Return Turntable — PS 5550. The ultimate automatic turntable, activated optically for convenience and flawless reproduction. DC Servo motor is rumble-free. Amazingly low wow and flutter.

Ultra Linear Speakers — SS 7330. Designed on Sony's unique new system that delivers powerful sound with incredible clarity. Damped Bass Reflex 3-way, 3-speaker type, front panel controls. Range 40-25,000 Hz.

MATCHED OPTIONS SHOWN: Cassette Deck — TC 177SD. First cassette deck to rival open reel. Dolby*, 3 Ferrite heads. 20-20,000 Hz. with FeCr tape.

Tape Recorder — TC 755. 3 motor. Closed loop, dual capstan, 3 Ferrite heads. 20-30,000 Hz. with SLH tape.

Stereo Tuner — ST 5066. For higher quality FM/AM music. **Headphones DR15.** High-fidelity, light, only 300 g. 20-20,000 Hz. **Furniture Unit.**

[×]One of Sony's seven new Zodiac Hi-Fi Systems. See them at your dealer, soon.

*"Dolby" is a trade mark of Dolby Laboratories.

SONY
for particular people




ELECTRONICS Australia

Australia's largest-selling electronics & hi-fi magazine

VOLUME 37 No 2



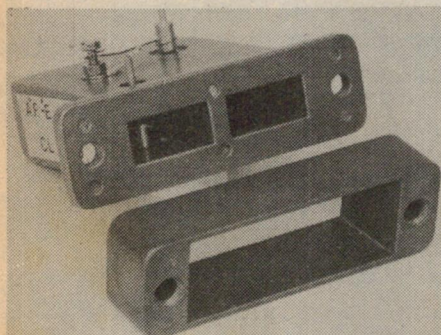Developed in our laboratory, this versatile windscreen wiper control unit is simple to construct and can be fitted to almost all types of cars. Full constructional details commence on page 34.



This 10GHz twin transmitter/receiver Doppler radar module recently released by Philips Elcoma is suited to a wide range of applications. To illustrate just one of these applications Elcoma made up a simple intruder alarm, the details of which are provided in our article on page 64.

On the cover

Our cover this month depicts a selection of high quality Yamaha stereo equipment as distributed in Australia by Rose Music Pty Ltd, 17-33 Market St, Melbourne. Inset shows one of the new generation stereo amplifiers using power FET transistors in the output stages. Details of this new breed of power amplifier are given in our feature article commencing on page 14.

CONTENTS — MAY 1975

world of electronics and hi-fi


- 3 Editorial: Colour facts and fancies
- 9 Hi-Fi News:
 - Spring reverb - with a difference — Grado CD-4 compatible phono cartridges — New Nakamichi portable cassette recorder*
- 14 Power FETS usher in a new breed of Hi-Fi amplifier
- 21 Review: Technics RS-376-US stereo cassette deck
- 23 Review: Kenwood KP-1022 player system
- 28 Solar cells: the promise of sunshine electricity
- 33 Frequency calibration using a colour TV set
- 62 Forum: Should Australia have a full-scale Citizens Band?

projects and technical

- 34 A control unit for intermittent wiper action
- 40 Novel tapered column for "super bass" response
- 44 Building your own digital calculator — a guide
- 48 Light trigger for slave flashguns
- 51 What's new in solid state: More CCD chips, and another LSI clock
- 54 Design for a PAL-S colour TV receiver — 2
- 64 Using the Philips 10GHz Doppler module
- 70 The serviceman: How to win friends — and lose money!
- 72 A full ASCII-type input keyboard for EDUC-8
- 81 Circuit and design ideas:
 - LEDs monitor supply voltage — Motor reversing using silicon diodes — 100-hour timer uses plating cell*
- 94 New products:
 - General Electric TC20T1 colour receiver — Portable DMM/CRO combination — "Zippy" boxes — Flyback transistors — Photo-etched panels — New plastic case range — Degaussing wand, battery charger from A & R Soanar*

regular features

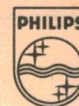- 24 News Highlights
- 84 Record reviews — classical
- 86 Record reviews — devotional, popular, jazz
- 92 Book reviews
- 99 The amateur bands
- 102 Shortwave scene
- 105 Information centre
- 109 Marketplace — classified
- 112 Index to advertisers
- 107 Notes and errata



If it moves, Doppler can detect it.

low cost—wide range—high reliability

Doppler miniature radars, for the local detection of moving objects, can be readily designed and manufactured with our microwave modules.

A typical example is the twin cavity X-band Doppler transmitter-receiver, CL8960. It incorporates its own antenna, yet it is small enough to be held in the palm of your hand.

Our range of components and sub-assemblies for Doppler systems permit their use in a variety of applications:

- The measurement of presence, speed, vibration, direction, distance, rotation—in many facets of industry
- Anti-shoplifting, fire detection, intrusion alarm and allied security operations
- Police radar, traffic light co-ordination and most areas of electronic traffic control
- Medical applications including remote patient monitoring

There are more than 50 Doppler devices available from Elcoma, in these types:

- | |
|---|
| (1) Gunn oscillator sources
CL....series 8.0-12.4GHZ 3.0-100.0MW
mechanical & varactor tuning |
| (2) Gunn oscillator & mixer cavities
CL....series 9.47-10.687GHZ 8.0MW
self mixing and twin cavity |
| (3) Mixer/detector cavity
CL75 series 9.35-10.687GHZ
Schottky diode detector |
| (4) X-band mixers
CL73 series 9-12.7GHZ
SMA connectors |
| (5) X-band coaxial circulators
2722-162....series 7.0-12.7GHZ
SMA connectors |
| (6) Microwave diodes
CXY....series Gunn oscillators 6.0-450.0MW
silicon Schottky detectors |

For further information contact ELCOMA
Electronic Components & Materials
Phone Sydney 42 1261 or 42 0361

To ELCOMA, P.O. Box 50,
Lane Cove, N.S.W. 2066.

Please supply me with more information on your Doppler systems. I am particularly interested in.....
(type of application)

Name

Organisation

Address

Postcode Phone

153 0091

ELCOMA



Editorial Viewpoint

Colour facts and fancies

Not surprisingly, there has been a dramatic increase in colour TV promotional activity since regular colour transmissions began in March. Most of it has been initiated by the two main vested-interest groups: the broadcasters and the set marketers. At times it has been hard to decide which group has been the more frenzied—the former with their attempts to whip up viewer demand, or the latter with their attempts to build, borrow or import enough sets to satisfy the demand!

I suppose it was inevitable that we would get a spate of dubious and misleading claims and assertions during this period, despite the recent introduction of legislation designed to curb such abuses. The main effect of the legislation seems to have been to force those making claims to be more vague and ambiguous.

For example one of the leading manufacturers has run many times an advert claiming that its sets produce "the most natural colour in the world", despite the fact that they employ virtually the same colour kinescopes and PAL-D circuitry used in many others. Another manufacturer claims that its sets use "a delta-mask tube, for the picture the others would like to have", making a virtue out of a tube technology now generally acknowledged to be obsolescent. Still another advertisement proclaims proudly that an imported set uses the PAL-bypass system for true-to-life colours!

Some of the broadcasters haven't been entirely sincere, either. I've almost lost count of the comments by announcers or comperes implying that the vast majority of viewers are already viewing in colour. This despite the fact that as yet fewer than 5% would be in this position. This is either wishful thinking, or a deliberate attempt to exert pressure on viewers by setting up a fictitious majority of "Joneses" against which one should supposedly be competing.

But perhaps the most misleading story of all is apparently being propagated by salesmen in some retailers, and also in modified form by some hiring firms. Within 5 years, so the story goes, all colour TV transmissions are to be shifted into the UHF band, so that any colour set without a UHF tuner will become useless.

Presumably this quite false and misleading story stems partly from a vague and distorted awareness of ABCB planning and advice concerning future extension of TV broadcasting into UHF channels, and perhaps partly from "analogy" with the UK change from VHF to UHF.

The benighted salesmen peddling the story are apparently unaware that our situation is quite different from that in the UK, where they needed to change both the picture transmission standards and the band. In our case there is no intention of shifting all TV broadcasting into the UHF band, merely the provision to expand into it when necessary. And in any case, when the time comes, virtually any receiver may be adapted for UHF reception by the addition of a low-cost converter.

I hope that readers of EA will try to counter the misleading tales and rumours, where possible, by suitable reference to facts. No firm, or industry for that matter, can survive for long by promoting falsehoods.

—Jamieson Rowe

EDITOR-IN-CHIEF

Neville Williams
M.I.R.E.E. (Aust.) (VK2XV)

EDITOR

Jamieson Rowe
B.A. (Sydney), B.Sc. (Technology, NSW)
M.I.R.E.E. (Aust.) (VK2ZLO/T)

ASSISTANT EDITOR

Philip Watson
A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

PRODUCT REVIEWS

Leo Simpson

TECHNICAL PROJECTS

David Edwards, B.E. (Hons, Tasmania)
Ian Pogson (VK2AZN/T)

GRAPHICS

Robert Flynn

PRODUCTION

Ross Tester

ADVERTISING MANAGER

Selwyn Sayers

CIRCULATION MANAGER

Alan Parker

ON SALE THE FIRST MONDAY OF EACH MONTH.

Printed by Dalley-Middleton-Moore Pty Ltd, of Kent St, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

*Recommended and maximum price only.

Editorial Office

12th Floor, 235 — 243 Jones Street, Broadway, Sydney, 2007. Phone 2 0944. Postal Address: PO Box 163, Beaconsfield 2014.

Advertising Offices

Sydney — 57-59 Regent St, Sydney 2008. Phone: 699 3622.

Representative: Mike Avey.

Melbourne — 425 St Kilda Road, Melbourne, 3004. Phone: 267 3800.

Representative: Noel Fitzpatrick.

Adelaide — Charles F. Brown & Associates Ltd, 429 Pulteney Street, Adelaide 5000.

Representative: Tom Duffy 23 1657.

Perth — 454 Murray Street, Perth 6000.

Representative: Jack Hansen. 21 8217.

Subscriptions

Subscription Dept, PO Box M204, Sydney Mail Exchange 2012.

Circulation Office

21 Morley Ave, Rosebery, Sydney 2018. Phone 663 3911.

Distribution

Distributed in NSW by Sungravure Pty Ltd, 57-59 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in

Western Australia by Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 22 Argyle St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.


Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice to patent rights.

All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.

The name's the same, just the style's been changed.

From *SANWA* to **sanwa**

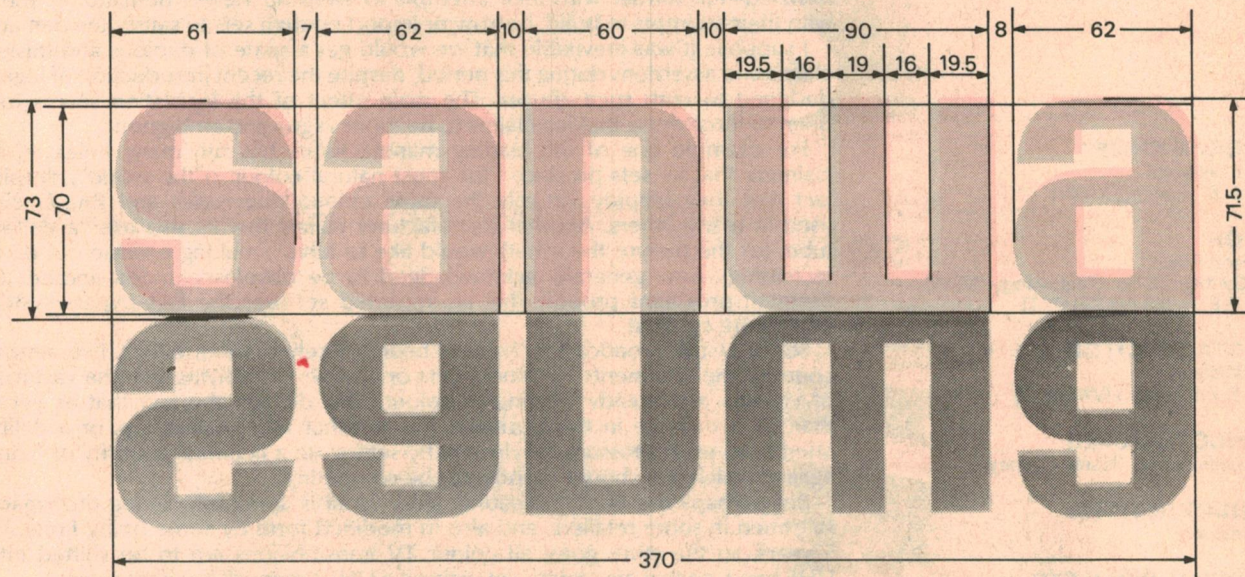


Why the change?

Because besides being more attractive, we think the new style presents a sharper image of precision. And precision is what Sanwa is all about.

For thirty years now we've been manufacturing precision measuring instruments. For customers throughout the world (in over a hundred countries, so far). For service engineers, researchers, radio hams—in fact for all kinds of people and companies involved in electronics.

Seventy per cent of all multimeters sold in Japan carry the Sanwa brand. Which isn't really surprising, since Sanwa multimeters have exceptional built-in capabilities. Versatility is a standard feature. So is sensitivity. And there are more than twenty-five models to choose from.

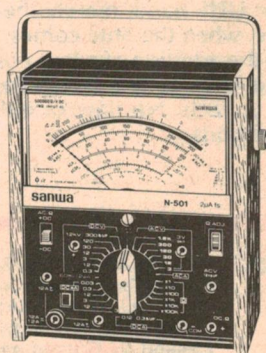Sanwa: the name that's synonymous with precision.



sanwa
MULTIMETERS

- BRISBANE 52 7255 • HOBART 23-1841 • LAUNCESTON 31-3300
- MELBOURNE 69-0151 • NEWCASTLE 61-4077 • SYDNEY 648-1711
- WOLLONGONG 29 4137

Introducing
**Ferric Oxide's
finest
hour...**




...hour and a half, and two hours

New BASF LH Super Cassettes with finer, more highly refined ferric oxide particles to give a 50% increase in volume without distortion.

Introducing a new standard of recording for all cassette recorders and decks without a CrO₂ bias switch. BASF LH Super cassette tape represents the ultimate in ferric oxide tape technology. Utilising a pure Meghemite oxide as well as a totally new binder system, LH Super features higher magnetic density and improved particle orientation.

This means more magnetic energy from the same tape surface area. The result: 50% increase in volume without distortion, across the full frequency range. An added 4 dB of low frequency, distortion-free dynamic output. A higher level of high reproduction is attainable flat to 20 kHz with a lower compression factor.

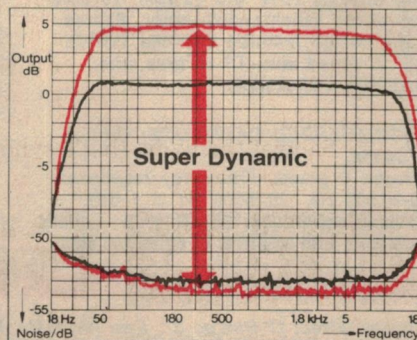Low Noise characteristics are even lower than standard Low Noise tape.



Performance specifications of the higher quality cassette decks are exceeded, the reproduction of any recorder is improved.

No special bias switch is required. BASF LH Super provides professional results with standard bias settings found on all cassette recorders and decks.



BASF
the best in
cassette sound

® BASF Aktiengesellschaft, 6700 Ludwigshafen/Rhein, Federal Republic of Germany.


Sole Australian Distributors: MAURICE CHAPMAN & COMPANY PTY. LTD. Sydney: 276 Castlereagh Street, Sydney 2000. Melbourne: 146-150 Burwood Road, Hawthorn, Vic. 3122. Brisbane: 123 Abbotsford Road, Mayne, Qld. 4006. Agents:—Newcastle: W. L. Redman & Co. Pty. Ltd.; Canberra: Sonney Cohen & Sons. State Distributors:—Adelaide: Neil Muller Pty. Ltd.; Perth: M. J. Bateman Pty. Ltd; Launceston: P. & M. Distributors; Darwin: Pfitzners Music House.

BA4472

ELECTRONICS Australia, May, 1975

5

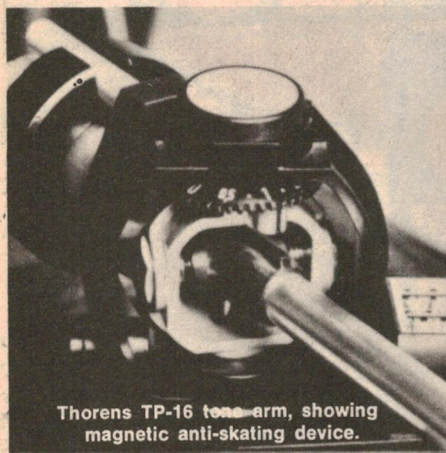there's no point trying to rumble a THORENS rumble.




Thorens TP-16 tone arm, showing magnetic anti-skating device.



Typical Thorens belt drive assembly.



Thorens model TD-125 Mk. II.

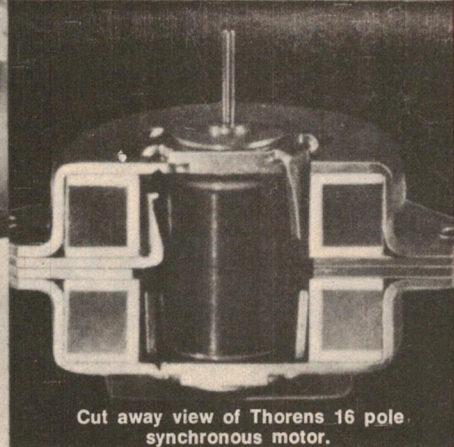

Cut away view of Thorens 16 pole synchronous motor.

THORENS

Detecting a Thorens rumble is nigh impossible; after almost 50 years continuing development Thorens adhere firmly to the belt drive principle. This policy is endorsed by the numerous reviewers and dedicated audio enthusiasts — *all over the world* — who use Thorens turntables in preference to all others. It's not surprising to find Thorens regarded as Europe's finest turntable.

Three models are now available throughout Australia:—

THORENS TD-125 AB Mk. II ELECTRONIC TRANSCRIPTION TURNTABLE

A precision instrument with electronic speed control, three speeds (16, 33 $\frac{1}{3}$, 45 rpm), and a run-up time of just one

second. Incorporates the TP-16 tone arm with its unique magnetic anti-skating bias adjustment.

RECOMMENDED CARTRIDGE: Ortofon M 15 E SUPER.

Weight: 5 grams. **Frequency response:** 20-20,000 Hz. (20-10,000 Hz \pm 1 dB). **Channel separation:** 25 dB. Elliptical stylus.

THORENS TD-160C TRANSCRIPTION TURNTABLE

Two speeds, 33 $\frac{1}{3}$ and 45 rpm. 16 pole two phase synchronous motor. Shares many design features with the TD-125 Mk. II. Fitted with TP-16 tone arm, magnetic anti-skating.

RECOMMENDED CARTRIDGE: Ortofon F Series.

Weight: 5 grams. **Frequency response:** 20-20,000 Hz. (20-8,000 Hz \pm 1 dB). **Channel separation:** 25 dB. Four models available, with elliptical or spherical styli.

THORENS TD-165C TRANSCRIPTION TURNTABLE

A budget priced Thorens turntable, sharing many design features with other models. 16 pole synchronous motor. Fitted with TP-11 tone arm, plumb-bob anti-skating device. Two speeds, 33 $\frac{1}{3}$ and 45 rpm. Magnetic cartridge supplied, with diamond stylus.

The combination . . . THORENS and ORTOFON . . . is very hard to beat, when it comes to quality sound reproduction. They're both great names from Europe, the source of much fine music, and equally fine audio equipment. Listen to the THORENS/ ORTOFON combination at your favourite specialist hi-fi store!

RIA-TO-375




Australian National Distributors:

RANK INDUSTRIES AUSTRALIA Pty. Limited.

Sydney Office: 12 Barcoo St., East Roseville, N.S.W. Tel. 406 5666*
Melbourne Office: 68 Queensbridge St., South Melbourne, Vic. Tel. 62 0031*
Canberra Office: 25 Molonglo Mall, Fyshwick, A.C.T. Tel. 95 2144*
Adelaide Office: 2 Bowen St., Kensington, S.A. Tel. 332 4288
Brisbane Office: 14 Proe St., Fortitude Valley, Qld. Tel. 52 7333
Perth Office: 27 Oxford St., Leederville, W.A. Tel. 81 4988
INTERSTATE REPRESENTATIVES: N.T. Pfizner's Music House, Smith Street, Darwin. Tel. 3801.

FERROGRAPH RTS2

The complete audio test unit

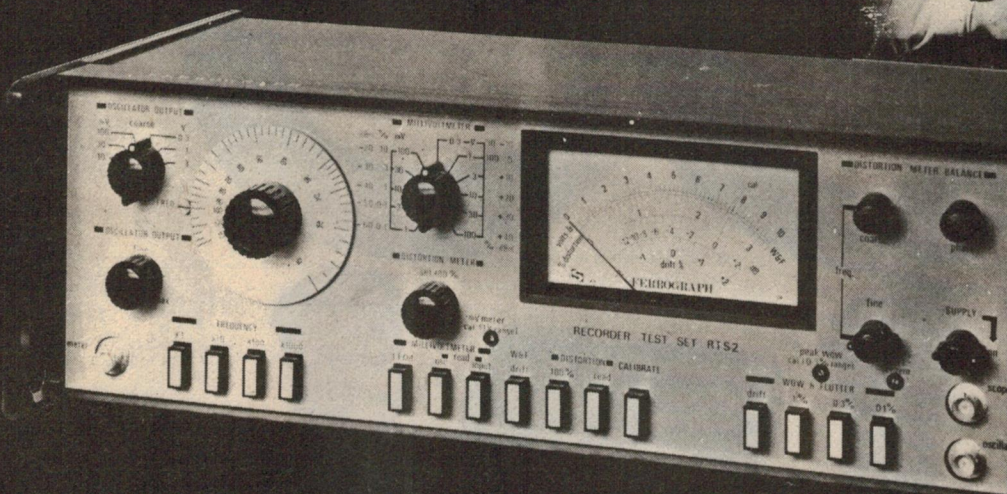

...and the alternatives

Save time and temper. You don't have to work with a maze of wires and dials and humloops any more.

The RTS 2 the "all in one" audio test set provides the complete answer.

Now you can check frequency response, signal noise ratio distortion, cross talk, Wow & Flutter, Drift, Erasure, Input Sensitivity, Output Power and Gain, all on the one instrument and the one pair of leads!

All these measurements can be made by pushing buttons and twisting knobs.

You don't even have to change a lead, let alone an instrument!

And at \$925.00 (excluding sales tax) everyone can afford the RTS 2.

Distributed throughout Australia by:

Leroya Industries PTY. LTD.

Head Office: 266 Hay Street, Subiaco, Western Australia 6008. Phone 81 2930.


NSW Office: 100 Walker Street, North Sydney, NSW 2060. Phone 922 4037.

VICTORIA Office: 103 Pelham Street, Carlton, 3053. Phone 347 7620.
also

Jacoby Mitchell Ltd. All States.




LER 051

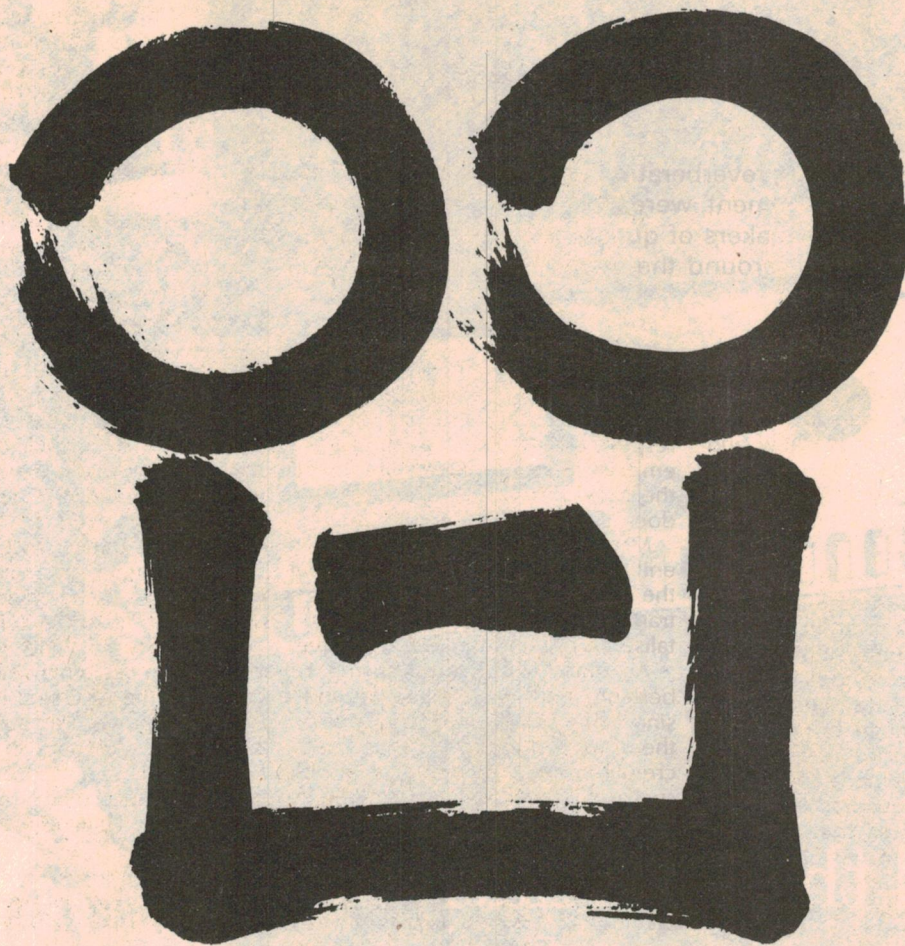

AKAI. It's the reel to reel thing.

PKB70550

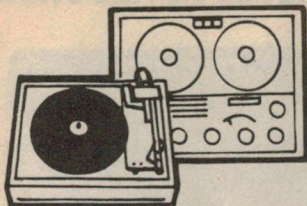

Hi Fi News

Spring reverb—with a difference!

A revival of interest in spring reverberation units for hifi systems would seem a most unlikely development, were it not for one thing: the interest is being sparked by AKG, makers of quality microphones and a company known and respected around the world.

A few months ago, AKG in association with Philips, hosted a party of internationally known hifi writers and critics, in order to show off various new and interesting product lines. Curiously, one that grabbed a large share of attention was a spring reverberation unit! It happened this way:

Without being forewarned the writer/tourists were invited by AKG engineers to listen to a good quality but otherwise normal stereo system playing the Bruckner 7th Symphony. It was pleasant but not in any sense spectacular.

Then the AKG engineers brought into action loudspeakers in the rear corners of the room, in what seemed superficially to be a conventional quadraphonic set-up. The difference was that the rear loudspeakers, in this case, were being fed with front signals, delayed 30 milliseconds in an AKG digital delay system. The extra, delayed signal lent a new perspective to the overall sound but, while the audience voted it better than straight stereo, it was still hardly sensational.

Next, the engineers cut out the digital delay unit and substituted AKG's torsion transmission line (TTL) which happens to be a fancy name for a spring reverberation unit. As a unit, it was obviously a good one and its 2.5 seconds delay gave a different perspective—but again hardly sensational.

Then both units were cut in, giving both short and long delay and the immediate effect was voted as being acoustically little short of sensational. To quote Bert Whyte of "Audio" magazine: "... the walls of the room did indeed seem to fall away, giving a tremendously enhanced concert hall perspective to the sound. This was pseudo quadrophony of a very high order, and it was hard to believe that a stereo recording could be processed to achieve such a thrilling and very desirous sound. Why, this would revitalise even the oldest of stereo recordings."

The overall effect of the demonstration was apparently to produce a batch of hifi enthusiasts, with a healthy new respect for synthetic reverberation, and embryo plans for getting their hands on the necessary (and expensive) units to doctor their own music systems.

More than anything else, the collective enthusiasm must be seen as a tribute to the designers of the new AKG torsional transmission line, in their ability to revitalise an old and limited technique.

As many will know, spring reverberation units have been around ever since the Hammond company added them to electronic organs. Used discreetly under the control of the player, such units can add a welcome reverberant quality to the otherwise bland

sound of a typical electronic organ used in a typical living area.

Conventional organ spring units range from about 20 to 50cm in length and contain two deliberately different spiral springs anchored between pairs of magnetic transducers. Signal is fed to the springs at one end, then picked up at the other, amplified and fed to loudspeakers. Some of the simpler reverb units have only a single spring.

While the makers of such units try to minimise and disperse bandpass and resonance effects, they still represent a problem—tolerable only if the reverberated signal is kept subordinate to the main signal. If the reverberation system is too prominent, the sound takes on a quite artificial quality which has been described eloquently as "boing"!

About 15 years ago, STC Australia tried to capture a slice of the local stereogram market with a model which featured in-built reverberation. The venture proved a failure commercially but it was a bonanza for local organ enthusiasts who were presented with an oversupply of excellent Hammond/Rola reverb units at a fraction of their normal market value.

What made the difference between a bad idea for STC and a potentially good one for AKG?

Two things: AKG used reverberation to project ambience from behind the listener, rather than via the front loudspeakers. And AKG have a very carefully engineered (and very expensive) unit which seemingly earns its fancy title.

In the AKG unit individual coils of the two springs are bent, or pushed together, or spread apart in a statistically determined way, to prevent the build-up of resonance effects in any one frequency region. This looks after the response up

GRADO CD-4 COMPATIBLE PHONO CARTRIDGES

The F+ series of pickup cartridges is Grado's answer to the contention that no single cartridge can do justice to CD-4 records as well as to ordinary 2-channel and 4-channel matrix discs. Grado claim that their F+ series cartridges have uniquely low mass and high compliance, making them much less reliant than normal on special stylus shapes to track frequencies above the audible range. In addition, they have a lower inductance than normal, making them much less

sensitive to the effects of cable capacitance and amplifier input impedance.


The least expensive in the series are the "Professional" types FTR+ and the FTE+, available respectively with spherical and elliptical styli; Grado claim that they are more than competitive with other 40kHz cartridges on the quality market, intended for arms needing a playing weight of 2-3 grams.

The FCR+ and FCE+ are selected units from the Professional production run, for top-of-the-line performance.

The "Flux Bridger" models FTR+1 and FCR+1 have a different internal generator system, a response to 50kHz and a normal tracking weight of 1-2 grams.

Above them again in the range is the "Super Flux-Bridger" series F3E+, F2+ and F1+, all with elliptical diamond stylus and a recommended tracking weight of 0.75 to 2 grams.

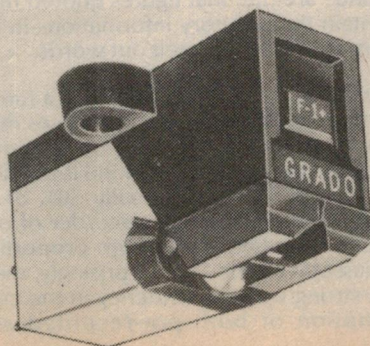For further information: H. Rowe & Co Pty Ltd, in all capital cities or at 127 Victoria Road, Marrickville 2204.



to about 1kHz.

To produce a similar effect at the higher frequencies, the wire is dented by distributed spot etching which produces thousands of discontinuities along its length. Something like 20% of the wire is removed by this treatment but the end result is a reverberated sound which is reportedly extremely natural and notably free from traditional spring reverb "boing"!

But there is a catch: Whereas Hammond style reverb units and scaled-down copies have commonly changed hands for a few dollars a time, the AKG torsional transmission line has a current price tag of some hundreds of dollars. At this price, they might be a proposition for commercial concerns reworking old recordings but they're hardly a proposition for individual quadraphonic enthusiasts.

But the thought is there. If AKG could cause a group of hard-bitten hifi writers to sit up and take notice with short and long time delayed signals fed into the back channels, it must pose a challenge to local enthusiasts to achieve a similar reaction with the limited means—and dollars—at their disposal!

"SHARP" CASSETTES: The latest radio/cassette players announced by the Sharp Corporation are sharp by design as well as by name. Their model GF-77M has a wide band tuner capable of covering adjacent television sound channels as well as the full international FM band. What is more, it is possible to set it up so that it will record a program via the FM facility, while the user is actually listening to an AM station. The reverse is also possible. For good measure, it incorporates provision for microphone mixing, full auto-stop facilities and a "clock system" counter which indicates the amount of unrecorded tape.

The Sharp model GF-11M contains the APSS facility, which stands for Automatic Program Starting System. With this system, the transport mechanism will operate in fast forward mode and stop automatically at the head of each new item, presumably triggered by the silence break in between. This model also has de-luxe audio features such as independent bass, treble and loudness controls, microphone mixing, high-output 2-loudspeaker system, automatic or manual recording facilities; metering for tuning, recording level and battery voltage; auto-stop provision, pause control and "sleep" switch.

HIFI ADVERTISING: Prompted by huge numbers of complaints from consumers, the U.S. Federal Trade Commission came out with a strict set of rules governing the way in which hifi equipment specifications must be determined and presented to the public. The objective was to rule out fancy descriptions and artificially jacked-up figures.

The industry generally welcomed the

NEW NAKAMICHI PORTABLE CASSETTE RECORDER



Having gained a great deal of attention with their super quality 3-head cassette decks for professional and domestic use, Nakamichi have now released a high quality portable deck—again with ambitious specifications. It is a 2-head machine with a response to 17kHz (+ and -3dB), a signal/noise ratio better than 60dB (Dolby in), harmonic distortion 2% (typical), and a wow/flutter of 0.13% WTD peak. Identified as model 550, it

can operate from internal dry cells, car battery or mains supply, internal regulation taking care of any voltage variations. It has the usual tape travel controls but the indicator and cueing facilities, level meters and such like are in line with professional standards. Dynamic range of the microphone input circuits is 120dB. For further information: Nakamichi Sales, Magnecord International Pty Ltd, 276 Castlereagh Street, Sydney 2000.

measures but there were many complaints that the F.T.C. had gone too far and demanded testing procedures that were to the disadvantage of amplifiers which had genuine qualities to offer, such as an enormous reserve of peak power to cope with transient peaks. But the Commission has been adamant (some called it stubborn) and the rules stand.

The major problem at the moment is not with major manufacturers or the professional journals, all of whom are close enough to the action to know what is right and wrong. It is with retailers, advertising agencies and newspapers or non-professional journals who remain blissfully unaware of the Commission's crack-down.

At the moment, the authorities are being "understanding" about breaches but a tougher period is ahead. Anyone who offers hifi gear simply has to learn that claims like "super power" and "big sound" are out; that figures quoted must contain the statutory information—in the form specified—in spelt out words.

COPYING RECORDS: If there is a furore in America about "pirate" cassettes marketed outside copyright obligations, another one of a different kind is building up in Japan. There, virtually 50% of all households own a tape recorder of one kind or another, with a high proportion of cassette radios. Not surprisingly, there is a strong upward tendency in the consumption of both pre-recorded and



blank cassettes. Long-playing discs are still doing well also but sales of single discs are faltering badly by comparison.

Record manufacturers are concerned by this shrinking one-time lucrative market and are blaming copying by private individuals, off-air, or off borrowed discs. Traditionally in Japan, as in many other countries, recording of copyright material for individual use has been tolerated and conceded "legal" status. But mass infringement of copyright by individuals poses a challenge of a different order and pressure is mounting for a more stringent interpretation of the law. First obvious target would be listener groups or cooperatives who buy individual recordings, which are then passed around.

NON-DIAMOND STYLUS: Prompted by the cost and reliance upon imports of quality diamonds, Toshiba and Nagaoka have jointly developed a new, long-life, low-cost stylus which is being marketed under the name "Ultra Extend Stylus". The stylus is based on artificial "corundum" crystal whose main ingredient is aluminium oxide. Under X-ray examination, the direction of the crystalline structure can be identified and controlled so that it exhibits the greatest possible resistance to abrasion.

Information about the physical shape of the new stylus is sparse at this stage but it would appear to be multi-radial and designed to play both 2-channel and 4-channel records.

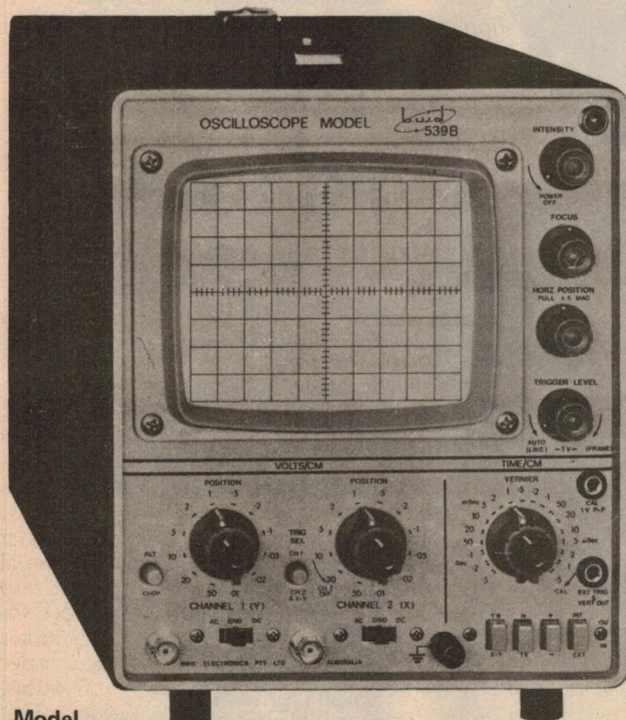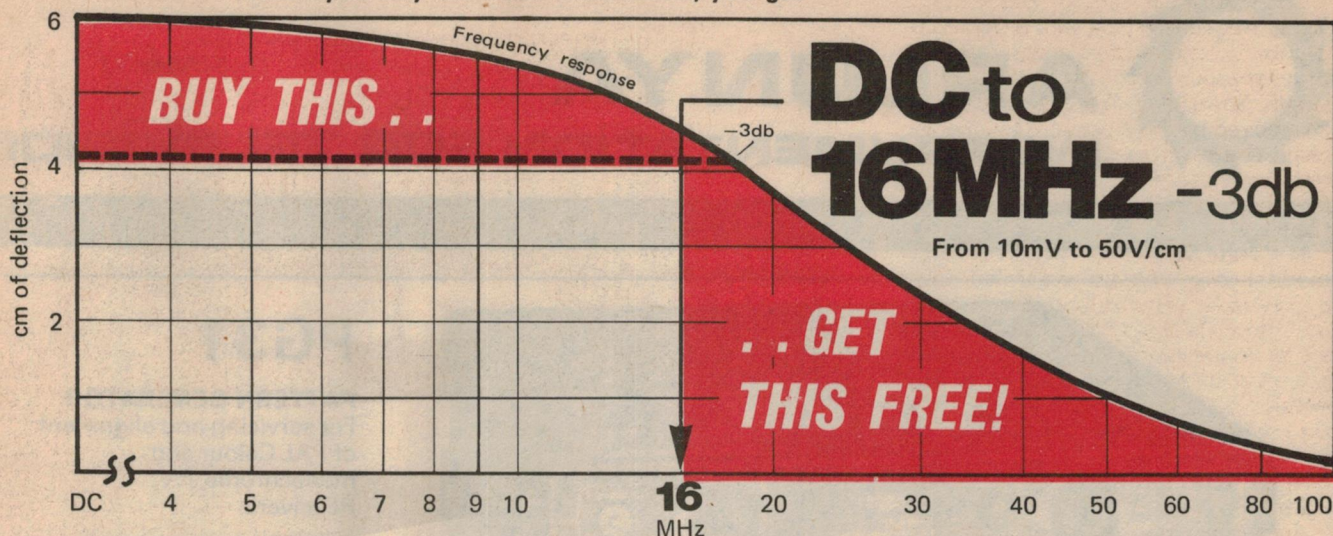When you buy the Dual Trace 539B, you get



Model

539B

DUAL TRACE
OSCILLOSCOPE

B.W.D. ELECTRONICS PTY. LTD.

329-333 Burke Rd., Gardiner, Vic., 3146

Phone: 25 4425

N.S.W.: 929 7452

INTERSTATE DISTRIBUTORS

S.A.: 269 1244

W.A.: 25 3130

QLD.: 52 7255

TAS.: 23 1843

EXPORT
AWARD



Winner of
Award for
Outstanding
Export Achievement

1955/1975 20 YEARS OF AUSTRALIAN
DESIGN INNOVATION

This is the tip of the performance range. Like the iceberg, there's a lot below the surface... and when you buy a bwd539B for its performance to 16MHz, you get the measuring capability to beyond 50MHz for nothing.

These are just some of the features:

- Sensitivity: 10mV/cm DC to 16MHz
≈ 30mV/cm at 30MHz
≈ 100mV/cm at 50MHz
≈ 500μ V/cm 3 Hz to 30kHz cascaded
- Time Base Range: 100n Sec to 2.5 sec/cm
- Trigger Range: <5Hz to beyond 30MHz
- TV Trigger, Identical X-Y, 3.3KV EHT
- 8 x 10 cm display,

and it's Australian designed and manufactured.

*The brochure gives you a full page
of specifications. Send the coupon.*

MB7503

B.W.D. Electronics Pty. Ltd.,
P.O. Box 123, Glen Iris, Vic., 3146.


Please let me have full details
on the bwd539B oscilloscope.

Name

Position

Company

Address

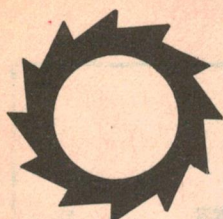

ARLUNYA

INSTRUMENTATION FOR TELEVISION



PG31

PATTERN GENERATOR

For servicing and alignment of PAL Colour and monochrome T.V. Receivers.

Gives the features most technicians want in a colour generator at a very keen price.

\$390 FIS PLUS TAX




PG 100E

PATTERN GENERATOR

For servicing and alignment of PAL Colour and Monochrome T.V. Receivers.

A pacesetter colour generator for workshop, factory and field use.

\$560 FIS PLUS TAX

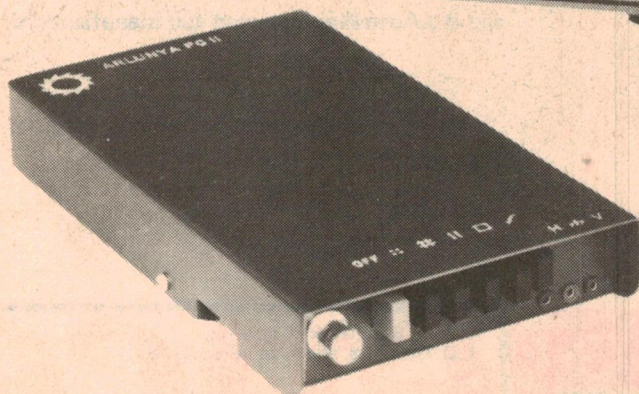

PG11 and PG11v

POCKET PATTERN GENERATORS

Small Lightweight monochrome generators for static and dynamic convergence, grey scale tracking and purity alignment of PAL colour receivers.

Battery operated (mains adapters available) ideal for installation and first line house call servicing.

\$165 FIS PLUS TAX

ARLUNYA ALSO HAS FM ALIGNMENT INSTRUMENTATION

Designed and Manufactured in Australia by

ARLUNYA PTY. LTD.

P.O. Box 113, Balwyn, Victoria, 3103, Australia.
Telephone 836 6533 (area code 03).
Telegrams or cables, Arlunya Melbourne, Australia.

SEND THIS COUPON OR WRITE FOR YOUR COPY OF OUR TELEVISION INSTRUMENTATION BROCHURE.

NAME

TELEPHONE NO.

ADDRESS

..... POST CODE

wharfedale

Wharfedale's 45 years experience is AUDIBLE in the 1975 models.



Many high fidelity Wharfedale speakers manufactured over twenty years ago are in daily use right now . . . but of course, Wharfedale technology has always been most advanced. It's no surprise to find Wharfedale still the most highly regarded speaker manufacturer in the U.K. — *with over 45 years experience!*

With the advent of stereo, smaller enclosures became desirable — and again Wharfedale pioneered the design of really effective small speaker systems based on the infinite baffle principle. With Wharfedale "know-how", drive units were designed specifically for smaller systems. The Wharfedale "Lintons" and "Dentons" are probably the most satisfying small systems available today.


In Australia today three particular Wharfedale speaker systems enjoy an ever growing demand — they're reasonably priced and completely compatible with all transistorised amplifiers. Listen to the audible difference Wharfedale experience makes when you visit your hi-fi specialist store — *and compare the performance!*

With a frequency response of 55-17,000 Hz. ± 3 dB. and a power handling capacity of 20 watts DIN, the compact "Linton 2" features a specially designed and sensitive 20 cm bass/mid range reproducer and a 5 cm high frequency unit. Size is only 48 x 25 x 24 cm. Ideal for floor or shelf. In teak and walnut finishes

Features a very even frequency response from 45-17,000 Hz. ± 3 dB. and extends well beyond these figures. Handles 30 watts DIN with ease. Incorporates a 30 cm bass reproducer and a 5 cm mid-range treble unit, with crossover at 1500 Hz. Size is 53.5 x 37 x 26 cm. In teak and walnut finishes. For floor or shelf mounting.

A superior 3 way speaker system, measuring 61 x 35.5 x 30.5 cm and featuring a 30 cm bass reproducer, 13 cm mid-range speaker and a 2.5 cm dome tweeter. Will handle 50 watts DIN. This particular system provides the smoothest frequency response ever available in a Wharfedale enclosure — from 45-20,000 Hz. \pm only 3 dB. The "Dovedale 3" is popular with musicians, and those music lovers with most discerning hearing. Available in teak and walnut finishes — designed to blend with any period or style.

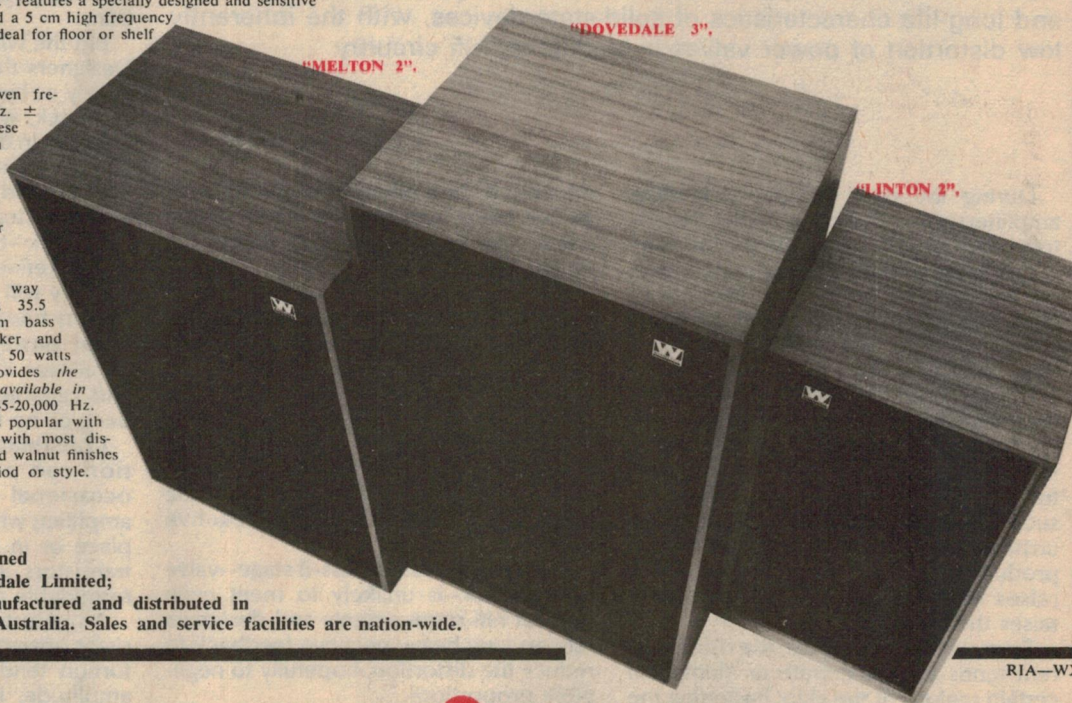Wharfedale speakers are designed in the U.K. by Rank Wharfedale Limited; these fine reproducers are manufactured and distributed in Australia by Rank Industries Australia. Sales and service facilities are nation-wide.



RIA-WX3

experience

Australian National Distributors:

RANK INDUSTRIES AUSTRALIA PTY. LIMITED.



Sydney Office: 12 Barcoo St., East Roseville, N.S.W. Tel. 406 5666*

Melbourne Office: 68 Queensbridge St., South Melbourne, Vic. Tel. 62 0031

Canberra Office: 25 Molonglo Mall, Fyshwick, A.C.T. Tel. 95 2144*

Adelaide Office: 2 Bowen St., Kensington, S.A. Tel. 332 4288

Brisbane Office: 14 Proe St., Fortitude Valley, Qld. Tel. 52 7333

Perth Office: 27 Oxford St., Leederville, W.A. Tel. 81 4988

INTERSTATE REPRESENTATIVE: N.T. Pflitzer's Music House, Smith Street, Darwin. Tel. 3801.

ELECTRONICS Australia, May, 1975

13

Power FETs usher in a new breed of HiFi Amplifier

Fig. 5.

As we indicated in our March issue, the emergence of commercial field effect power transistors—power FETs—is likely to have an important bearing on the future design of high fidelity amplifier systems. Power FETs would appear to combine the ruggedness, convenience and long-life characteristics of solid-state devices, with the inherently low distortion of power valves in traditional hifi circuitry.

by NEVILLE WILLIAMS

During the past decade, solid-state amplifiers using ordinary bipolar transistors have come to dominate the hifi market offering, as they do, high power output and ostensibly excellent results from units that are far more reliable, compact and cooler running than would ever have been possible with valve technology.

It is undoubtedly a tribute to designers that they have achieved these plus factors in the face of considerable difficulties, most of them originating with the bipolar transistors used in the output stage. All such transistors are inherently thermally unstable: a rise in temperature tends to produce a rise in current, which further raises the temperature, which further raises the current, etc.

To make matters worse, the rising current tends to concentrate or "lump" in certain regions of the chip, hastening the process towards self-destruction.

To safeguard the transistors, designers have to provide generously proportioned heatsinks along with thermal and direct current feedback—adding considerably to design and circuit complexity. But that is not the end of the matter.

As further insurance against temperature rise, designers have opted almost universally to operate the output transistors in class-B mode, with a quiescent current of only a few milliamps. In so doing, they have to face up to non-linearity in the crossover region where the output current is being transferred, on successive half cycles, from one transistor to the other. The problem can be

minimised but rarely eliminated altogether, being further complicated if transistors are used in parallel to up the power rating.

The end result is an output system which, apart from thermal and DC complications, has two potential sources of distortion, characteristic of all class-B audio amplifiers: (1) drivers which have to deliver significant power into a low and non-constant impedance and (2) output devices which pass in and out of conduction on each alternate half cycle—this into a complex, highly reactive load!

In its natural state a class-B stage—valve or transistor—is unlikely to meet even modest hifi requirements and designers rely on very heavy negative feedback to reduce the distortion, hopefully to negligible proportions.

To be fair, it must be admitted that

the distortion figures for modern, quality amplifiers are indeed very low. As a bonus, output impedance is also low and frequency response notably flat way beyond both ends of the audible spectrum.


But the whole approach has its critics. Designers themselves would prefer not to rely as heavily as they do on negative feedback, with its tendency to be least effective in the crossover situation where it is most needed. They would prefer, if they could, to produce a system which is intrinsically good "as-is"—without feedback—then use feedback as an added refinement.

Many will recall that this was the philosophy towards the end of the valve era, when power triodes and pentodes in ultralinear configuration were popular and capable of excellent results, feedback or no feedback.

Confirmation for this "boffin" conviction can probably be found in the occasional super-quality solid-state amplifier, which shows up in the marketplace or in the literature, using bipolar transistors in class-A—despite the very formidable design difficulties involved.

An unfortunate aspect of class-B transistor operation is that the crossover distortion tends to have a fairly constant amplitude, irrespective of signal level. When compared with the total signal at

Fig. 1: Illustrating the basic principles of a small-signal N-channel FET. The long, narrow channel produces drain output impedance curves similar to those of a pentode valve, not well suited for an audio output stage. The new "vertical" configuration lowers output impedance and increases dissipation.

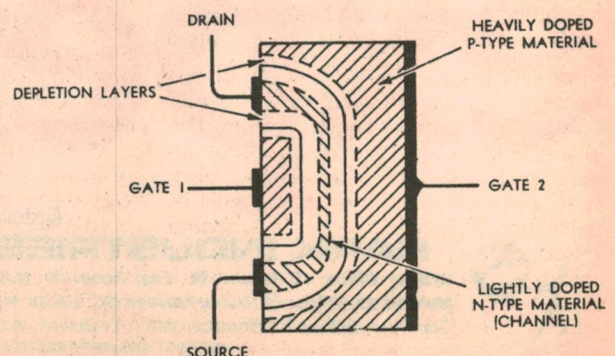

full power, the distortion content may be very small, so that formal tests yield a commendably low THD (total harmonic distortion) reading. But this is a rather artificial situation.

In everyday use, high fidelity amplifiers operate on program material far below their maximum power rating; on soft passages, the output may diminish to a fraction of a watt. Critics maintain that, compared with output of this order, a constant amplitude of crossover distortion may represent an unacceptable THD percentage, being rendered the more objectionable by the presence of higher order harmonics, resulting from the "switching" action.

They maintain that the distortion can be discerned in some circumstances, being evident as a subtle harshness, particularly in low level sound.

If admitted as a significant problem, crossover distortion would seem to be interlocked with loudspeaker efficiency—with sensitive systems at a disadvantage, because every extra dB of sensitivity would expose an extra dB of the constant amplitude distortion. It leads to speculation as to whether insensitive systems may have been preferred on occasions, not for their intrinsic merit, but because they helped bury a distortion problem!

While it is difficult to debate or quantify the subjective effect of distortion, one thing is certain: with high quality valve amplifiers, distortion tends to diminish both in absolute amplitude and percentage as the operating level is reduced, being at its lowest in soft musical passages, and with a minimum of objectionable high order harmonics. What is more, the use of a sensitive loudspeaker system helps matters further, because it allows the amplifier to operate at an even lower power level, while, of course, ensuring higher acoustic output on peaks.

In all this, there is unlimited scope for claim and counter-claim but, in the highly subjective and emotional world of hifi sound, the arguments provide a very favourable climate for the introduction of a new device which promises to combine the best of both technologies—the convenience, efficiency and durability of solid-state with the low intrinsic distortion of the almost proverbial class-A valve output stage!

That device is the power field effect transistor; for short, the power FET. It is being heralded by some as a device that looks like a transistor but acts like a valve!

While it is natural to draw comparisons between power FETs and power triode valves, the theme can be overdone. The power FET is not the outcome of an attempt to produce a solid-state valve. It is a device in its own right, with its own special advantages, which would probably end up in the same kind of circuitry, even had valves never existed. It just so happens that the two lend themselves to similar circuit application, and on this basis, comparison is valid.

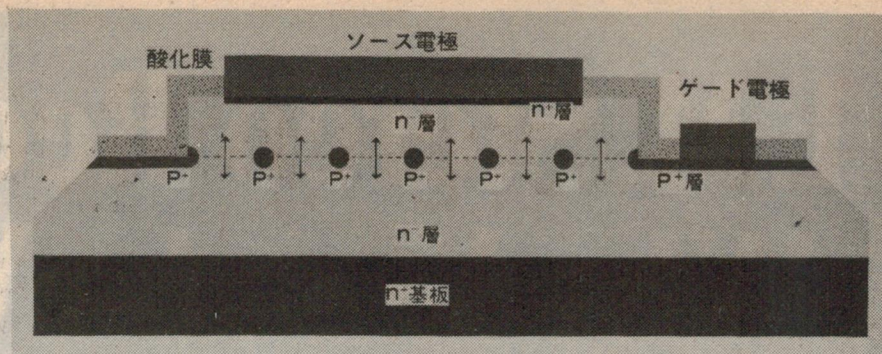


Fig. 2: Supplied to E.A. by Yamaha—complete with Japanese labels—this diagram illustrates the principles of the new "vertical" power FET, in this case N-channel. A lattice of positively doped material is implanted in N material acting as a gate. The N material above the lattice (as depicted) forms the source; that within the lattice (arrowed) the multiple channels; and that below, the drain. The dark regions at top and bottom are the heavily doped "contact" zones for source and drain.


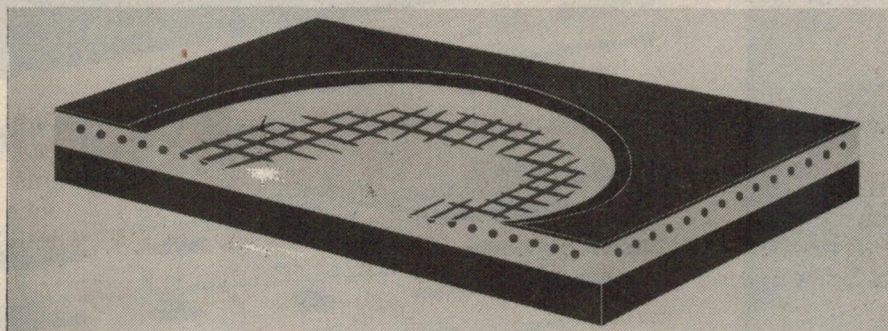


Fig. 3 (above) is an artist's sketch of what a power FET chip would look like if a hollow were ground in the top, through the contact and source zones, through the gate lattice into the drain. Fig. 4 (right) is an actual microphotograph of a chip which has been subjected to this treatment.

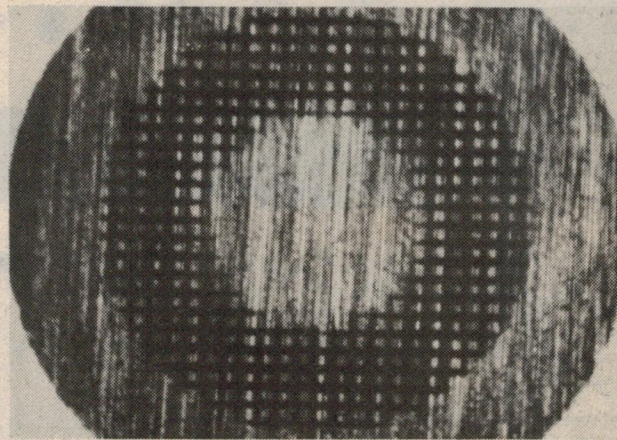

In a valve, current flows across the vacuum between a cathode and anode, the quantity of current being controlled by the intervening grid. The grid does not normally draw significant current, so that the input impedance to the stage is high and constant. As a result, while the preceding amplifier stage(s) must provide an adequate signal voltage, they can operate as straightforward low-distortion voltage amplifiers.

More importantly, it is convenient to operate a valve output stage under class-A or class-AB1 conditions, with both valves drawing substantially normal current, irrespective of the amount of signal being handled. Under dynamic conditions, both valves contribute to the output over the cycle and there is little or no discontinuity in the flow of output


signal current.

With a non-critical drive requirement, no output current discontinuity and with the push-pull connection substantially cancelling even order harmonics, the intrinsic or "as-is" distortion of such an output stage is quite low. It can be made even lower by the use of negative feedback, without ever needing to use so much feedback that it begins to endanger stability.

There is every reason to believe that the new FET power transistors can accommodate to this kind of circuitry with important additional advantages: (1) Being a low impedance device, they can operate directly into loudspeaker voice coils and (2) they can be used in circuit configurations not practical with valves.

As opposed to bipolar types, field ef-

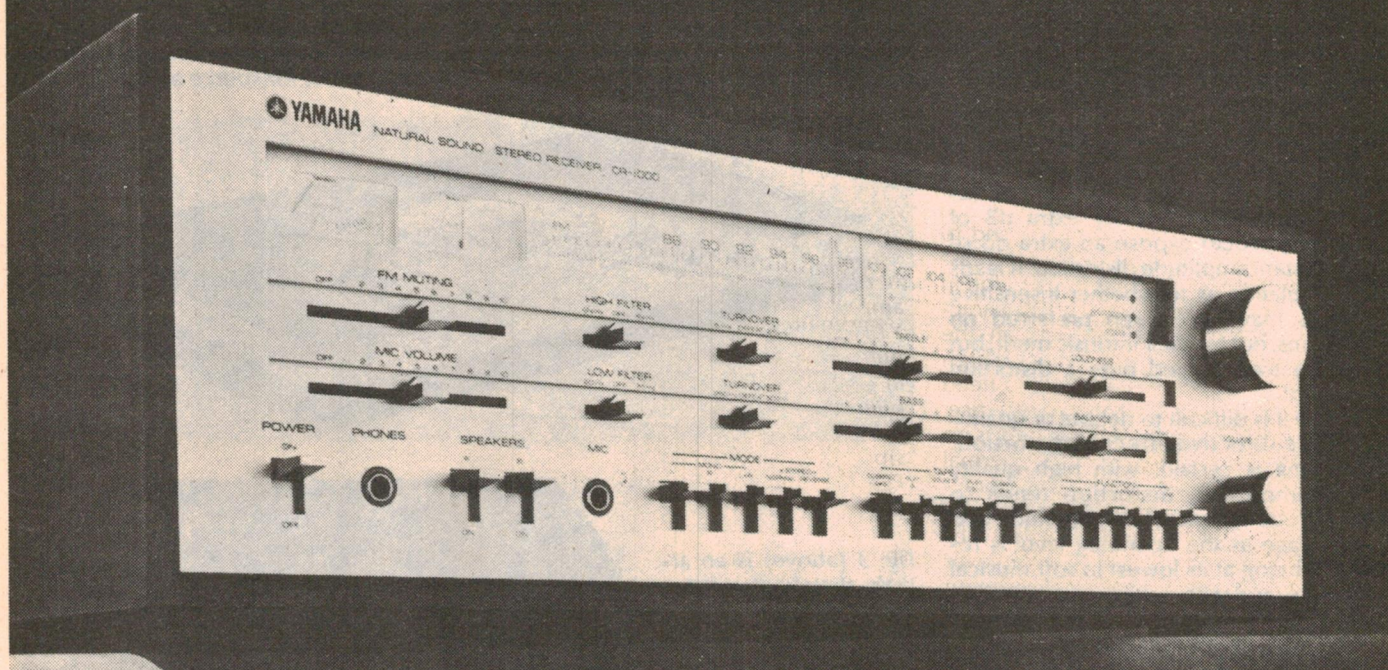F.M. Stereo Reception, Why Yamaha Waited.



Australia, wisely, has adopted International Standards and Specifications for F.M. Transmission and it would not be difficult for any competent manufacturer to design and produce an F.M. Receiver to meet these specifications.

But receiving a F.M. signal is one thing. Converting that signal into an almost perfect reproduction of the transmitted sound is another.

So Yamaha waited. And whilst they waited they worked — hard.

It soon became evident that there were many international brand name F.M. Receivers which could receive an F.M. signal perfectly. But there was something lacking between Reception of the signal and subsequent conversion into Sound.

And here is where Yamaha took a giant step ahead.


F.M. Tuner the Secret.

Each of the new Yamaha Stereo FM/AM Receivers feature —

Yamaha Exclusive Auto-Touch Tuning.

To select your desired F.M. Station, you simply touch the Tuning knob and the built-in AFC (Automatic Frequency Control) circuit shuts itself off for accurate tuning.

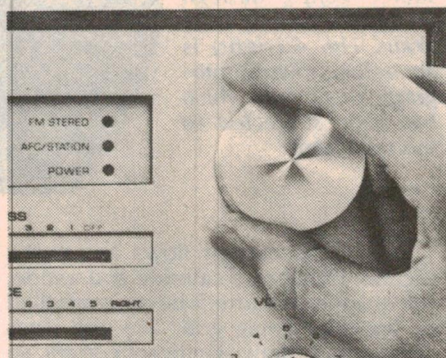Once you have "tuned in" the station, this AFC circuit activates as soon as you release the knob, guaranteeing steady, drift free reception regardless of fluctuations in the power supply voltage or changes in the temperature of the tuner circuitry.



Permanent Light-emitting Diode Indicators for Power, F.M. Stereo and AFC/Station.

Yamaha has used LED (Light Emitting Diode) lamp indicators for power, automatic switch-over from FM Mono to FM Stereo reception, and the automatic AFC/Station selection. These lamps last a lifetime. The AFC/Station indicator glows in half-brightness when a station is tuned in; it changes to full brightness as you release the Tuning Knob, indicating that the AFC circuit is working.

For brochures giving you full details and specifications of the new range of Yamaha Stereo FM/AM Receivers with Dual Tuning Meters and Mic Mixing — CR 400, CR 600, CR 800, CR 1000 — complete and post the coupon on this page.

**TO ROSE MUSIC PTY. LTD.,
17-30 MARKET STREET,
SOUTH MELB., VIC. 3205**

Please send me details of the new Yamaha Stereo FM/AM Receiver.

NAME

ADDRESS

State Postcode

Another Rose Music sponsored product.



Yamaha natural sound.

GL&C/160RM

A NEW BREED OF HIFI AMPLIFIER . . .

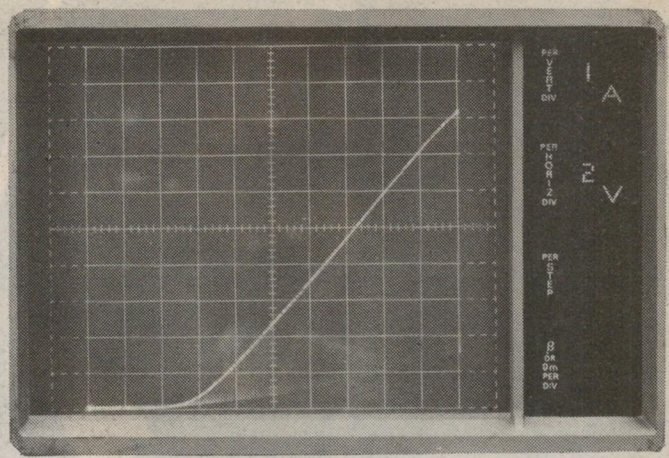
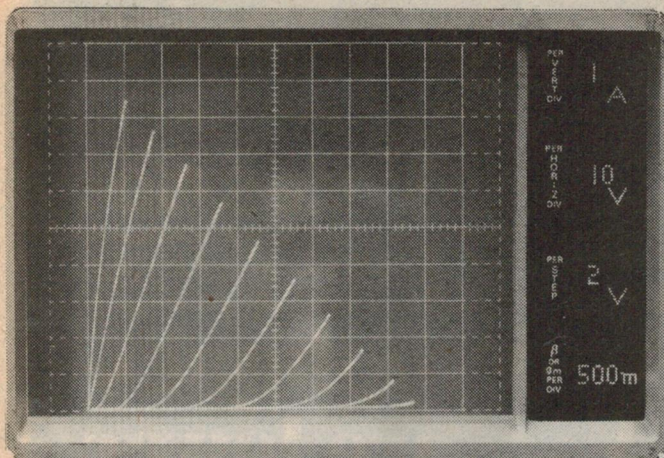


Fig. 6 (above) is an oscilloscopic plot of a family of drain curves for a typical Yamaha power FET. The resemblance to a power triode plate family is apparent. Fig. 7 (top right) is a linearity plot for a power FET.

fect transistors, large and small, tend to be thermally self-protecting, as increasing temperature produces a reduction in the current through them. The characteristic is particularly important in the new breed of FET intended for high power applications; while they still need heatsinks to combat temperature rise, circuit configuration and complexity is no longer dictated by the fear of thermal runaway. It becomes much more practical to operate a FET output stage under class-A or -AB conditions, thereby obviating the basic problem of crossover distortion, as well as cancelling even order harmonics.


Nor is it just a matter of quiescent current and elimination of crossover distortion. As we shall see later, the new power FETs have an intrinsically low output impedance, the counterpart of a power triode. As such, they are much more compatible with a reactive (e.g. loudspeaker) load than a bipolar transistor or a pentode valve.

As far as drive requirements are concerned they suffer the drawback that they exhibit high input capacitance, typically reckoned in thousands of pF. Thus, while the pre-output drivers do not have to cope with a non-linear load, as for a class-B stage, they do have to operate at quite low impedance and therefore draw significant current. The drivers most favoured seem to be smaller scale power FETs.

As with any class-A or -AB system, the power supply must be capable of supplying a consistently high current, more or less independent of output level. However, because the current is constant and because power FETs tend to be self-protecting, the need for supply regulation is either reduced or eliminated.

Details aside, however, power FETs would seem to offer to designers an important new approach which exhibits lower intrinsic distortion, relying much less on negative feedback to correct any

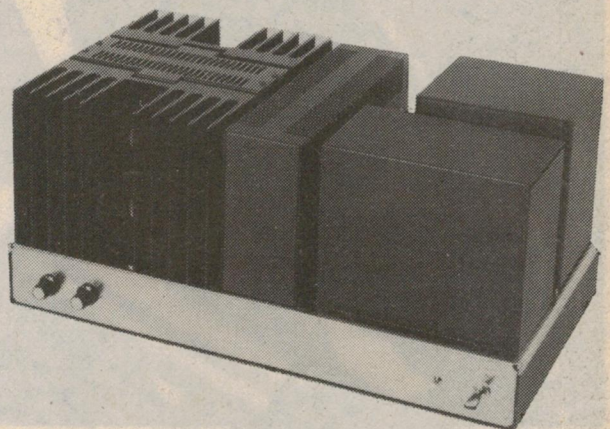A Yamaha basic power amplifier using a pair of YT304 power FETs in the output of each channel, in a single-ended push pull configuration. They are preceded by four smaller YT405 power FET drivers.



shortcomings.

While power FETs are a relatively new development, the basic concept of the field effect transistor is quite old. It was first suggested in 1928 by American engineer Julius E. Lilienfeld, and patented in 1930. The first commercial germanium field effect transistor was developed in 1958 by the Polish scientist Stanislaw Tetzner in the laboratories of the French firm Compagnie Francaise Thompson-Houston. A silicon version produced by the American firm Crystalonics Inc, two years later, set the stage for commercial exploitation.

Small signal FETs have been used for some years in the front end of VHF TV, FM and communications receivers, but high power development and application proved more elusive. It is only in the last few months that they have emerged in significant commercial quantities.

Most of the recent activity in power FETs has flowed from the work of Professor Junichi Nishizawa, of Tohoku University, under commission from the Japan Technology Development Foundation. Commenced in 1969, it was taken up by companies like Nippon Gakki (Yamaha), Nippon Electric and Sony, who produced their own versions. Sony in particular are using the term "N-FET".

Equipment manufacturers also began developmental programs and the period 1973/4 saw the unveiling of prototype FET amplifiers by such companies as

Matsushita, Trio/Kenwood, Pioneer, Toshiba, JVC and Sharp. The current year should see the commercial release of quite a few big-name amplifiers with class-A FETs in the output stage—and more arguments as to whether the valve has at last been successfully challenged in the purist domain!


The basic principles of ordinary FETs have been covered in detail by Editor Jim Rowe in the "Electronics Australia" handbook "Fundamentals Of Solid State".

Fig. 1, taken from this book, illustrates the structure and operation of a small signal silicon N-channel junction FET. Produced by ordinary etching, diffusion and allied techniques, a U-shaped channel of lightly doped N-type material is enclosed between the body of the chip and another smaller region, both of heavily doped P-type material. Because current carriers tend naturally to retreat from P-N junctions, the U-channel tends to become isolated electrically from the P-type regions by two depletion layers shown as clear white.

In these circumstances, when source and drain are connected to an external circuit, current can flow through the isolated N-channel, just as it would through a resistive path. But it is not an ordinary resistive path. If the two P-type regions are joined together and biased progressively more negative with respect to source, the depletion layers will widen



Prices on

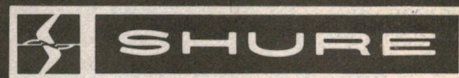

microphones
are lower
than you
think!

SM53
Unidirectional
Dynamic
Microphone

Shure microphones — used by Paul Anka and other famous artists in show business — are recognised as the most dependable travelling companion any entertainer can have.

565 SD
Unisphere I


Shure microphones are the lowest cost single item in the average system — yet their function is critical. In truth, your system can be no better than the microphone that originally converts sound waves into electrical impulses. In general, unidirection cardioid mikes are the most expensive; however, some omnidirectional and bidirectional models can cost about the same. Where quality is first and foremost, we recommend ribbons or dynamics.

515 SB
Shure
Unidyne B

ALL SHURE PROFESSIONAL MIKES USE SWITCHCRAFT AUDIO CONNECTORS.

Ask your dealer about the new prices.

545
Unidyne III

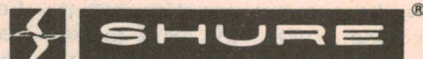

AUDIO ENGINEERS P/L	AUDIO ENGINEERS (Vic.)	RON JONES PTY. LTD.	ATHOL M. HILL P/L	AUDIO ENGINEERS (S.A.)
342 Kent Street, SYDNEY 2000 N.S.W.	2A Hill Street, THORNBURY 3071 Vic.	57 Castlemaine Street, MILTON 4064 Qld.	1000 Hay Street, PERTH 6000 W.A.	37 Market Street, ADELAIDE 5000 S.A.

AE089/FP

and gradually reduce the thickness of the N-channel, ultimately depleting it completely of carriers and interrupting current flow.

There is obviously a close parallel between the action of the gate in a FET and grid in a thermionic valve.

For reasons which are fully explained in "Fundamentals of Solid State", the type of FET illustrated in Fig. 1 has output characteristics which resemble those of a pentode valve—fine for RF applications but undesirable for an audio power output device, operating into a reactive load. In addition, the structure cannot easily be modified to cope with high currents, as for a high dissipation device.

The configuration which followed from Professor Nishizawa's work is illustrated in Fig. 2, which we reproduce directly from the material supplied to "Electronics Australia" by Nippon-Gakki (Yamaha). Instead of the current flowing between source and drain parallel to the surface of the chip, it flows at right angles to the main planes, leading to the previously mentioned description "vertical FET" or "V-FET".

As indicated in Fig. 2, the lightly doped N-type drain covers the total area of the chip, allowing heat to be conducted away from it quite freely.

Implanted in the upper surface of the drain is a closely spaced lattice or grid of heavily-doped P-type material which serves as the gate. The layer of N-type material continues through this and above it, to become the source, at the top of the chip.

With this structure, current flowing between source and drain must pass through the holes in the lattice so that, in effect, there are as many channels—and as many parallel connected FETs—as there are spaces in the lattice.

If the lattice (gate) is biased progressively more negative with respect to source, the paths through it will be progressively depleted and narrowed, leading to an ultimate current cut-off. The analogy with a thermionic valve is most obvious.

With this structure, the current density and distribution remains as uniform throughout the chip as the manufacture will allow.

No less important, the very short channels, as compared with the kind of construction in Fig. 1, minimises "pinch-off" as a by-product of the IR drop (see "Fundamentals of Solid State Fig. 8.2") and this produces a family of drain (cf plate) curves very similar to those of the triode power valve.

Fig. 3 further illustrates the structure of a vertical power FET, being an artist's depiction of what would be exposed if a hollow was ground in the top of the chip—through the source contact surface layer, through the source region, through the gate mesh and into the drain region at the deepest point.

Fig. 4 is an actual microphotograph of a chip which has been ground in this way.

Fig. 5 shows a group of Yamaha vertical FETs—looking exactly like any other power transistor. Device information is sparse at this stage but the range would appear to include N-channel FETs as already discussed, their P-channel counterparts and others intended for lower power or voltage amplification. Typically, the power FETs would appear to have an amplification factor (μ) of about 5 with very low output impedance, while the voltage amplifiers have a μ of 50 and, of course, much higher drain impedance.

Vertical FETs produced by other manufacturers differ in structural detail, probably because of patent situations, and individual preferences and facilities. Sony, for example, use an oxide layer for

supply is used: plus and minus 85V and minus 200V.

The output transistors operate under class-AB conditions but the quiescent current is still high—which is not surprising when it is considered that the output device dissipation is reckoned in hundreds of watts. Even so, the designers have found thermal protection to be quite superfluous. The protection circuitry which is included is there to guard against actual circuit malfunction, and will break the amplifier/speaker connection if a DC potential greater than 2V appears at any time across the voice coil terminals.

Preliminary figures for the amplifier suggest a power output of 150W RMS per channel into 8-ohm loads, over the



This Sony model TA-8650 integrated amplifier uses 6 smaller V-FETs (3 + 3 parallel) in a complementary output circuit to produce an output of 80W RMS per channel into 8 ohms. IM distortion and THD at the 1W level is .05% or less at 1000Hz. THD is 0.1% or less at rated output 20Hz to 20kHz. Response is ± 20 dB from 10Hz to 100kHz.

additional isolation of the gate lattice.

Fig. 6 shows an oscillographic plot of a family of drain curves for a Yamaha power FET. The vertical current scale is 0-10A, the horizontal voltage scale 0-100V, and the plots for gate potentials in 2V steps from zero bias on the left to a maximum of -18V. A cursory examination of the curves in the likely working point zone suggests an amplification factor of 5, a natural output impedance of 5 ohms, and a mutual conductance of 1.25A/V.

Fig. 7 shows drain current (vertical 0-10A) plotted against gate voltage (horizontal 0-20V).

As mentioned earlier, prototype amplifiers using power FET output stages have been shown by a number of Japanese companies. Sony have exhibited advance models in Australia and, by the time this appears in print, FET equipped Yamaha amplifiers should be available.

Preliminary information on a typical Yamaha main amplifier indicates that the output transistors are in a conventional single-ended push-pull configuration, directly coupled to the loudspeaker. The FET drivers are also directly coupled, with a "newly developed biasing method . . . 5 patents pending . . . which permits stable circuit operation even without a stabilised power supply". A triple power

band 20-20,000Hz, with both channels driven. At the 100W level, distortion at 1kHz is given as 0.01%, and not more than 0.03% at any other frequency within the abovementioned band. Frequency response is quoted as within ± 0 to ± 1 dB from 5Hz to 100kHz.

These are impressive figures by any standards, the more so when it is remembered that distortion should diminish with output.

While class-A FET output stages could be scaled for a wide range of power levels, it seems certain that they will come in first at the top end of the market—lots of watts and lots of dollars! But if FET production climbs, as expected, and device costs diminish towards that of comparable bipolar types, the technology will probably spread downward.

Will power FETs revolutionise amplifier design? They probably will, but whether they will revolutionise hifi listening is quite another matter. Good conventional amplifiers probably contribute less to distortion than any other link in the reproduction chain, and the result of improving the already-strongest link may not be all that apparent.

But that doesn't seem to alter the fact that enthusiasts still seem to aspire after the perfect amplifier!

If everything you wanted to know about Hi-Fi seemed too complicated, Sony has a beautiful answer for you.



The Taurus System^x

Refined Stereo Amplifier — TA 1055. Powerful 70 watts/8 ohms I.H.F. constant power, direct-coupled. Versatile facilities for wide range of sources. High filter and loudness controls for better listening. Frequency 10-60,000 Hz. Superior signal-to-noise ratio.

Outstanding Auto-Return Player — PS 5100. High quality synchronous motor. Belt drive magnetic cartridge.

Ultra Linear Speakers — SS 7100. Powerful yet compact, 2-way, 2-speaker infinite baffle system. Woofer 20 cm, tweeter 2.5 cm. Frequency 60-20,000 Hz.

MATCHED OPTIONS SHOWN: Cassette Deck — TC 134SD. High quality Dolby*, Ferrite head. 30-17,000 Hz. with CrO₂ tape.

Reel-to-Reel Deck — TC 377. A big performer for your hi-fi sound system. 3-head

stereo deck in slant front with Sony's new Ferrite heads.

Stereo Tuner — ST 5066. For higher quality FM/AM reception.

Stereo Headphones — DR11. Tone and volume controls. 50-18,000 Hz. Black or yellow.

Furniture Unit.

^xOne of Sony's seven new Zodiac Hi-Fi Systems. See them at your dealer, soon.

*"Dolby" is a trade mark of Dolby Laboratories.

SONY

for particular people

Technics RS-676-US stereo cassette deck

A recent development in stereo cassette decks is the appearance of decks with all controls on the vertical front panel, along with an opening for front-loading of the cassette. An interesting example is the Technics RS-676-US stereo cassette deck, which features solenoid control.

It now seems as though stereo cassette deck buyers are presented with two broad choices: a cassette deck with all major controls and the cassette well on the top surface, or those with all facilities on the front panel and nothing on top.

These latter machines have the advantage that they can be installed behind the front panel of a furniture cabinet together with FM tuner, amplifier and so. The inevitable clutter of connecting wires is right out of sight.

On the Technics RS-676-US, cassettes are frontally loaded by opening the hinged window and placing the cassette on a horizontal platform which is then depressed into the operating position. Pushing the eject button raises the cassette platform and flips the hinged window partially open.

An internal light and a mirror set at 45 degrees makes the cassette visible, provided the viewer has his head at window level. A worthwhile addition would be a light behind the cassette, so that the viewer can judge the progress of the tape. With the present system, there is no way of knowing whether the tape is

near end or start, without removing it to look.

Next to the cassette window are the six push-bars for solenoid control of the tape transport. These push-bars have a delightfully light action and a fast response. When the Record, Play or Pause controls are actuated, they are lit up from behind to show the operating mode of the deck.

As on many other decks, the RS-676-US has a memory rewind feature which enables it to return the tape to a preset 'OOO'. But in this case it then goes one better by automatically shifting into Playback mode.

Automatic sensing is provided, for Cr02 cassettes which have the detection recess adjacent to the recording knock-outs. Older Cr02 cassettes without the detection recesses are catered for by flipping the Tape Select lever to the appropriate position.

Having the frontal loading system for the cassettes means that the heads are not as accessible as on most conventional decks. When cleaning the heads and capstan you really need a dentist's


inspection mirror to do the job properly.

As might be imagined in a machine using solenoid control, the transport mechanism is quite complex, employing at least ten micro-switches, three relays and three solenoids (there may have been a few others hidden away). Two motors are used; one drives the large capstan flywheel while the other drives the cassette spools and the revolution counter. Both motors are DC but the capstan motor is not the direct drive type as used in the RS-276-US (reviewed in "Electronics Australia" November 1973) and the RS-279-US models by Technics.


Apart from the solenoids used to control the transport mechanism, there are two large solenoids which operate multi-pole slide switches—for the record function and for the circuit changes necessary for Cr02 tape.

One of the reasons for having relays involved in the control circuitry for the tape transport is that the RS-676-US can be operated by an optional remote control (hand-held), which comes with a long cable connecting to the rear of the unit via a 12-pin plug. This is one of the highly desirable functions that is only made possible by solenoid operation of the transport. Remote control is particularly handy during recording.

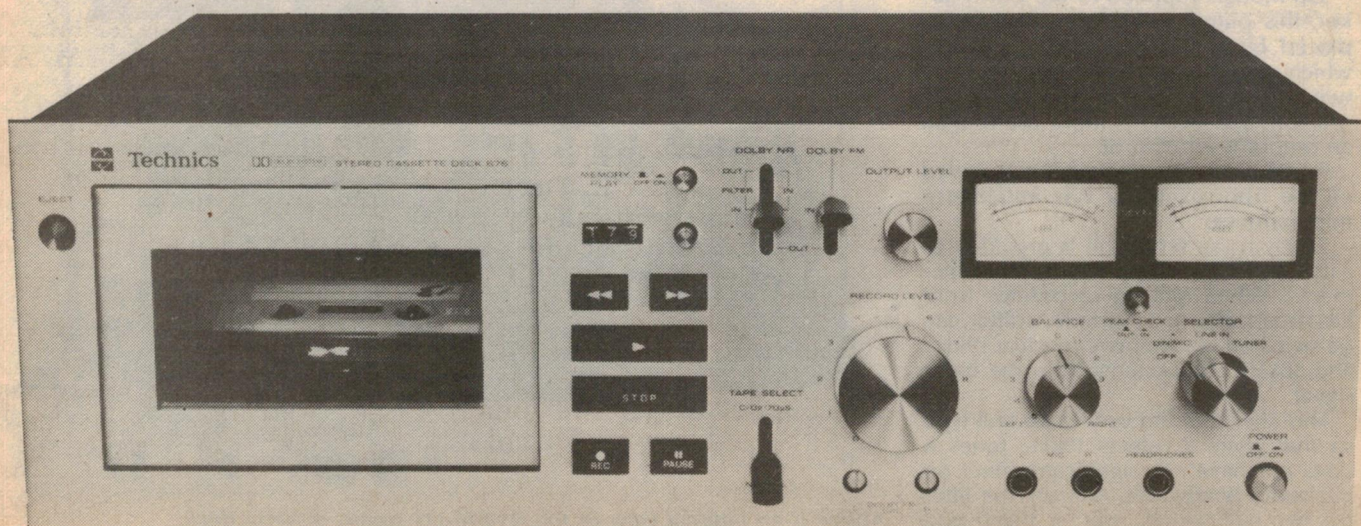A large knob provides control of the recording level together with a Balance



Technics RS-676-US stereo cassette deck

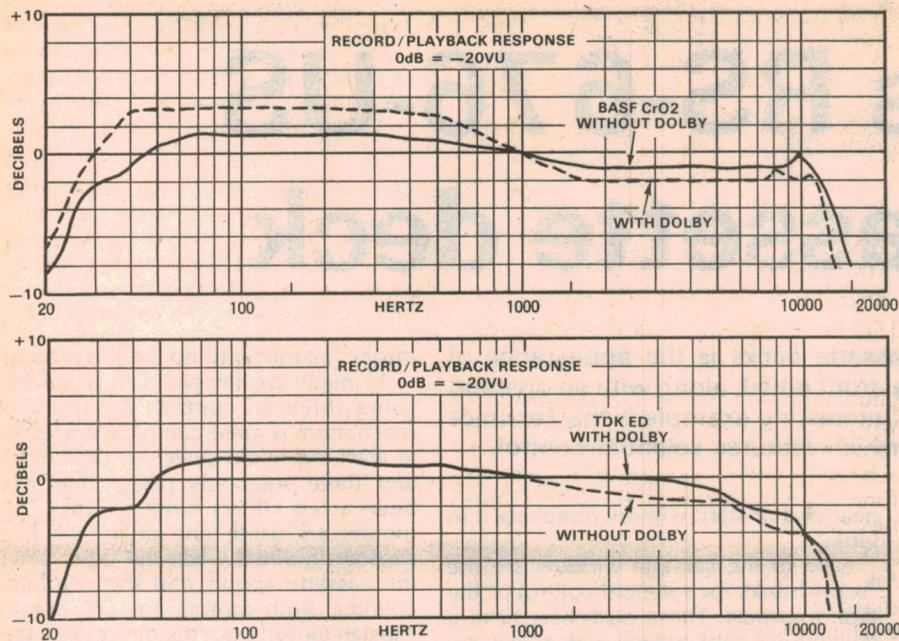

control knob to adjust the relative levels of the two channels. An input selector knob provides a choice of mic, line or tuner inputs.

An interesting feature of the level meters is that they have a push-button which converts them from VU characteristic to peak-reading. When the peak-reading mode is selected, a more accurate response to sharp transients is obtained. As worthwhile as this system is, we are still of the opinion that supplementary LED overload indicators are the final refinement for distortion-free recordings.

Adjacent to the recording level meters is a small knob which controls the output from the Line Out jacks on the rear panel. No level control is provided for the headphone socket.

On models supplied to the USA market, this output knob is apparently replaced by a pair of concentric knobs which, together with the input selector switch, provide mic/line mixing. In our opinion, this facility is more useful than an output level control.

Two 6.5 mm jack sockets are provided on the front panel for low impedance microphones.

Dolby noise reduction is provided as a matter of course, but with a few refinements. When making recordings from FM broadcasts, for example, a filter can be switched in to remove residual 19kHz and 38kHz components from the tuner signal.

This filter is of the very sharp null type so that while it rejects 19kHz tones it does not have any significant effect on the audio bandwidth. Actually the filter has two null circuits, one for 19kHz and

one at 38kHz. The latter is always in circuit.

Circuitry is also provided for recording Dolbyised FM broadcasts but this is likely to be of little interest to Australian buyers for some time to come.

Wow and flutter is quoted at less than 0.15% DIN. We measured a best result of 0.2% DIN but we found this depended to quite an extent on the vagaries of the particular cassette used.

Cassette rewind time was quite fast at about 65 seconds for a C-60 tape.

Record/playback response was checked using a variety of tapes, with and without Dolby, and the results are shown in the graphs. As can be seen, there is relatively little loss in highs when Dolby was switched in.

Quite a dramatic improvement in signal to noise ratio was obtained when Dolby was switched in. Typically, the unweighted figure obtained for low noise ferric tape was minus 48dB with respect to OVU and this improved to 53dB with Dolby.


We also made some tests using Ferrichrome tape but found that the bias conditions did not seem to be quite right to get the optimum results.

Radar and RF interference was not noticeable at any time and the reproduction was at all times free of switch clicks and other extraneous noises. Sound quality is excellent and is certainly among the best available from cassette machines.

But clearly, the major attraction of this machine is its operating refinement. Its solenoid control is one of the best we have tested on any deck.

One point though, the unit cannot be stacked on top of other equipment with large transformers — hum increases markedly.

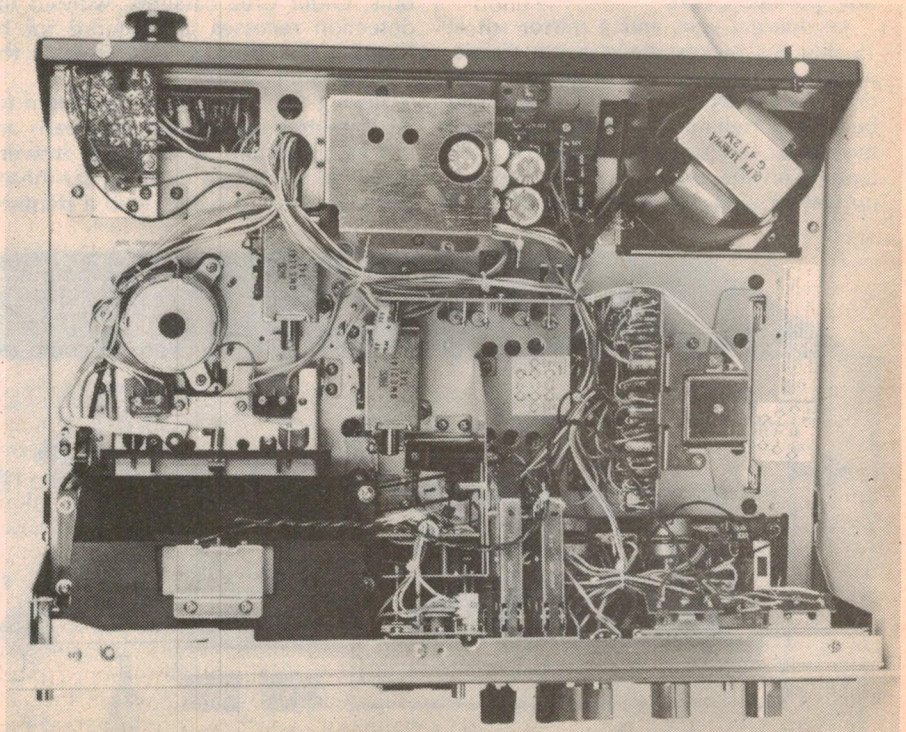Recommended retail price of the Technics RS-676-US stereo cassette deck is \$569.00 including sales tax. For further information on Technics products, contact your high fidelity retailer or the Australian distributors, Haco Distributing Agencies Pty Ltd, 57-69 Anzac Parade, Kensington, NSW 2033. (L.D.S.)



Above is an internal view of the RS-676-US stereo cassette deck.

Kenwood KP-1022 Player System

In spite of the widespread popularity of automatic turntables, there is apparently still a sizable market for manually-controlled units. Some people like them for their simplicity and others for their lower price. For these people, the Kenwood KP-1022 is worthy of consideration.

Like many turntables these days, the Kenwood KP-1022 is marketed as a complete package deal. It is supplied with arm, magnetic cartridge, wooden platform and tinted perspex cover.

From the point of view of some enthusiasts who may wish to build the unit into a furniture cabinet, having to buy the perspex cover as part of the purchase deal will be regarded as a disadvantage. They would still have to buy the timber platform though, because of its suspension system.

Unlike other turntables, the KP-1022 is mounted directly onto its timber base which is provided with four large conical suspension points. While possibly not as attractive, these would appear to provide better acoustic isolation than the suspension on other units.

Measurements of the platform are 350mm (deep) by 445mm (wide). Clearance required at the rear of the unit is approximately 85mm, while the unobstructed height required above the mounting shelf is 435mm.

Three simple controls are provided for operation of the turntable. A toggle lever on the left-hand side selects the speed, either 33 or 45 rpm. On the right-hand side, a lever with a very light action actuates a micro-switch to start or stop the turntable motor. Near the arm pivot is the cueing lever which is damped to provide gentle lifting and lowering of the tone-arm.

Since it is a manually controlled unit, there is no automatic stop or lift-off at the end of a record.

The platter is a 300mm diameter aluminium alloy diecasting driven around an inner rim by the usual flat rubber belt, from a 4-pole synchronous motor with a stepped pulley. The motor windings are connected in parallel or series by a slide-switch for 110VAC or 240VAC operation. This means that there is no power transformer as fitted to some other units, and consequently there is less likelihood of hum induced into the cartridge or pick-up leads.

The chromed tubular arm is S-shaped in the usual manner and is balanced lon-

gitudinally by a rotatable counterweight which also provides the vertical tracking force setting. Anti-skating is provided by a hanging weight system which applies force to a calibrated lever on the arm pivot.

A moving magnet cartridge, type V-39 Mk 2, is fitted. It has a 0.5mil conical diamond stylus and a recommended tracking force of 2 grams.

In use, we found the turntable

At right is the Kenwood KP-1022 shown with tinted perspex cover removed.



operated smoothly and quietly and is virtually free of rumble, wow and flutter. Kenwood rate wow and flutter at less than 0.07% (WRMS). We measured it at 0.15% weighted according to DIN 45507, which is a good result. The main turntable bearing was quite free. With the belt removed and then spun up to 33 rpm, the platter took 75 seconds to come to a halt.

Vertical tracking forces were found to be within 5% of the calibrated settings and anti-skating settings seemed to be very close to optimum. The arm appeared to have quite low bearing friction in its pivots and would be suitable for cartridges with tracking force recommendations of less than 2 grams.

At the recommended tracking force of 2 grams, the cartridge tracked the plus 16dB band of the W&G 25/2434 test record with no audible distortion, a good result. Cartridge output was 3.4mV at 50mm/sec, which is a little above the specification.

While in some respects the performance specification is fairly exact, the claim for frequency response is vague with a rating of 20Hz to 20kHz and no tolerance quoted. Using a 56k load, we measured the frequency response at plus or minus 3dB between 20Hz and 20kHz. Channel balance was within 1dB over the whole range and separation was an even minus 22dB in both directions and quite symmetrical in both directions.

From the above results, one could judge the cartridge as being a good unit with typical middle-of-the-road performance. But the waveform at frequencies between 4kHz and 10kHz had to be seen to be believed. To say that it was irregular would be an understatement. And no amount of fiddling with the various arm adjustments had more than a slight effect on it.

Sound quality on music signals tended to be harsh and definitely not as pleasant as one expects of a typical magnetic cartridge. As far as the cartridge was concerned, we were not happy. At the very least, one must cast doubts on the quality control of the particular sample tested.

Of course to keep this review in perspective, one must realise that the KP-


1022 turntable is a relatively low-priced unit from the Kenwood line.

Since the total cable capacitance in each channel is less than 100 picofarads, it is possible to substitute a cartridge for CD-4 (or UD-4) records.


And we are pleased to note that a three-pin plug and three-core flex was fitted for the mains connection.

In summary, the Kenwood KP-1022 is a well-finished unit with no unnecessary frills. With its mechanical simplicity it should give a lifetime of troublefree service. But if your dealer gives you the option of upgrading to a better cartridge for a few dollars more, we suggest you take it.

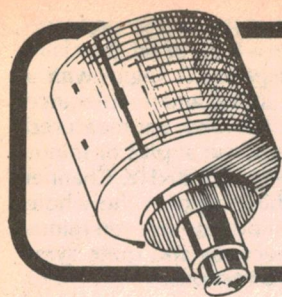Suggested retail price of the Kenwood KP-1002 is \$139.00 including sales tax. Further information on the unit can be obtained from hifi retailers or from the Australian distributors for Kenwood, Jacoby, Mitchell & Co Pty Ltd, 215 North Rocks Road, North Rocks, NSW 2151. (L.D.S.)



News Highlights

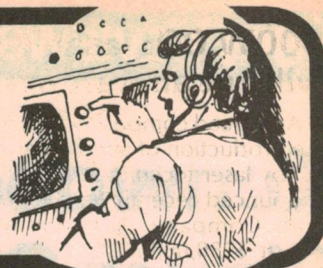

Video disc contenders prepare for battle

Following the flurry of publicity about two years back, the most conspicuous factor concerning the various forthcoming video disc systems has been the deafening silence from the development companies. In mid-March, however, the three principal contenders in the home video stakes emerged from hibernation to face consumers in Europe and the USA.

Notable among these was the German Telefunken company which began selling its TED mechanical videodisc player in Germany on March 17. Jointly developed by Telefunken and British Decca, the TED video player has been designed in both NTSC and SECAM versions as well as the PAL colour version. However, no US demonstration is scheduled at this date.

In Germany, the TED video player is to be distributed through some 1,000 radio-television dealers and department stores. Retail cost is around the \$650 mark—less than half the price of a videotape recorder, according to Telefunken. The TED discs, which offer 10 minutes of colour programs, will retail for about \$4 or more, and will include an initial repertoire of 50 titles. It is expected that some 350 titles will be available by the end of the year.

On the same day as the Telefunken release, Philips and MCA were scheduled to start a round of demonstrations in New York of a modified VLP player which can accommodate both rigid (Philips) and flexible (MCA) discs. Philips and MCA recently signed an agreement under which Philips is to manufacture and market the modified VLP player, while MCA will manufacture and market much of the video disc program material.

The agreement is an important one from the Philips viewpoint as MCA has access to a wide variety of entertainment material, including the Universal Pictures film library. In addition, Philips will also gain the rights to MCA's lower cost flexible disc which uses about 1/10 the plastic of the Philips VLP disc, and which can be duplicated on a rotary press. Feature film albums selling through ordinary record shops for about \$10 are predicted.

Prime advantage of the Philips/MCA VLP player over the Telefunken TED system is its extended playing time—45 minutes as compared to ten minutes.



The Philips VLP player—a serious contender in the home video stakes.

Signal pick-up in the VLP player is by means of a laser beam which scans information encoded into spiral tracks on a reflective metallised disc. For a more detailed technical description of the VLP player, readers are referred to the November 1973 issue of "Electronics Australia."

The Philips/MCA deal effectively narrows the video disc competition in the US to two systems, the other being the RCA capacitive pickup system known as "SelectaVision." Details of the RCA system were released towards the end of February when the company announced plans to set up a permanent "SelectaVision VideoDisc" demonstration in New York about the end of March. Previously, the RCA system had been demonstrated only to other manufacturers in order to attract licensees.

The RCA capacitive video system is similar in many respects to a conventional record player. Program storage is on metallised discs, and takes the form of a series of transverse slots of varying width and separation etched into a pre-cut groove by an electron-beam recording system. The discs are two-sided and provide a total playing time of some 60 minutes.

Signal pick-up is by means of a sapphire stylus containing a thin metal elec-

trode. This stylus rides in the groove, the electrode detecting the relief pattern by changes in the capacitance between its tip and the metallic coating on the record surface.

As with RCA, Philips and MCA are currently courting licensees, especially Zenith in the US and Thompson-CSF in France. Most of Zenith's work has been in the optical disc area, its prime system being essentially an NTSC version of the transmissive system developed by Thomson-CSF. Observers believe that both companies will move into the Philips/MCA camp if agreement can be reached on standardised software for use in both reflective and transmissive optical systems.

However, Zenith has also been working on an electrostatic-capacitance disc pick-up system similar in principle to the RCA system. At this stage, then, Zenith must be listed as uncommitted, but leaning strongly towards the optical system.

Giant Japanese manufacturer Matsushita is being wooed ardently by both camps. Probably the world's largest TV maker, it provides the key to the Japanese market and must be considered a major factor in the US battleground. As Matsushita goes, so go Panasonic, Quasar and JVC.

(continued on page 25)

500W CO₂ laser will cut aircraft parts

Advanced composite materials used in the production of aircraft parts are to be cut by laser techniques under a contract announced recently by the Hughes Aircraft Company. The contract, worth about \$750,000, was awarded to the Hughes Aircraft Company by McDonnell Douglas, and calls for the development of a numerically controlled laser cutter for delivery by the end of the year.

Hughes laser-cutters have already found wide application in the garment industry and the shoe industry, where they are used for cutting out patterns. McDonnell Douglas says that the new system will be similar to the models used in the abovementioned industries in that it will use a small computer to store cutting information, a linear motor positioning system, and a high powered laser. The laser itself will be a 500W carbon dioxide model.

The new laser cutter will be used in the production of aircraft parts which are subject to high stress factors. These often contain boron fibre and carbon fibre reinforcement, and are hard to machine satisfactorily using conventional methods. The laser system should therefore offer considerable advantages over the old methods, both in terms of speed and cost. Waste of expensive material should also be considerably reduced, and cutting accuracy improved.

Video disc contenders prepare for battle . . . ctd

Politically, Matsushita has good reason to go either way, having joint bonds with both Philips and RCA. On the Philips side of the ledger is its joint ventures with Matsushita in Japan (involving the manufacture of semiconductors and picture tubes) and in Europe (batteries). Counter to this is Matsushita's alliance with RCA in promoting the CD-4 quadrasonic sound system.

RCA's main advantage at this stage is the fact that it is probably some 12 months ahead of the Philips/MCA group, and the RCA strategy is now geared to speed. In addition, the SelectaVision system uses relatively conventional components compared to the VLP player which requires the production of laser signal pick-up units and specialised servo systems. RCA feels that this factor will place the company in a favourable position as regards cost, although admittedly their system is less versatile than the Philips/MCA VLP system.

What this means in terms of marketing dates is difficult to forecast at this time. What it does mean is that the Australian consumer is unlikely to see a video disc system here for at least two years—unless a decision is made to market the Telefunken-Decca TED system.

Flat screen video communications system

An experimental flat-screen video system that transmits handwriting, reproduces pictures, and can be used to communicate directly with a computer has been demonstrated by scientists at Bell Telephone Laboratories, Holmdel, New Jersey.

The system consists of a commercially available plasma panel display (modified by Bell scientists), electronic control circuitry, and a special pen called a light pen. Plasma panels are made up of thousands of tiny neon-gas cells arranged in vertical and horizontal rows. These cells glow when energised by an electric current.

In the Bell Labs' system these cells are selectively turned on or off to produce an image. Message transcription is effected by means of a light pen which acts as a pencil or pointer. Images placed on a sending panel by this means can be transmitted to a distant receiving panel over telephone lines.

A unique part of the Bell Labs' development is the method used to



achieve the grey tones necessary for picture or facsimile reproduction. Gradation in tone is obtained simply by altering the density of cells turned on over a given area of the panel.

Atomic plants may burn radioactive wastes

A nuclear fission energy system, capable of eliminating a significant amount of its radioactive wastes by burning them, shows considerable promise, scientists and engineers*from NASA report.

A study of the system, a theoretical investigation conducted by computer analysis, is based on use of gaseous fuel nuclear reactors. Gaseous core reactors using a uranium plasma fuel have been under study and development for space propulsion by NASA for several years.

A major atomic energy headache in recent years has been the various long-lived high-level radioactive wastes produced in the fission process. Some of these wastes have a half-life of many thousands of years. One solution to this

problem may be to transform such radioactive wastes into harmless materials by bombarding them with neutrons.

The unique characteristics of gaseous fuel reactors make them especially suited to burn up nuclear waste materials, as these reactors have a large neutron population. The fuel, a gaseous compound of uranium, can be readily circulated and returned to the reactor to burn up radioactive materials produced in the fuel.

Computer analysis showed that a gaseous fuel reactor, after three years of operation, can establish a balance in rates of production and elimination of these waste products. Once this equilibrium has been established, no additional long-lived radioactive wastes will be produced.

Post Office approves push-button dialler

The Australian Post Office has approved a new telephone number dialling device that provides push-button dialling. Designated the SpheriCall, the new device is to be marketed in Australia by Philips TMC Ltd.

SpheriCall is based on the latest MOS-LSI technology and adds the speed and convenience of press-button dialling to an ordinary rotary dial telephone. It features a "try again" facility at the press of a button, and a memory in which the 10 most frequently used numbers (up to 18 digits long) can be stored. Any of these numbers can then be called automatically simply by pressing the appropriate button.



The unit is used with a normal telephone, and requires no internal modifications to existing telephone equipment. It is expected to win widespread acceptance in Australian business commerce, and even in private homes.



A screwdriver and about ½ an hour is all you need to build this 40 watt Philips speaker system.

Philips make it easy and inexpensive for you to own a professional speaker system. Assemble it yourself in about 30 minutes and you have 40 watt (RMS) capacity speakers to complement your hi-fi gear.

The AD8K40 Speaker Kit includes:

- 2 pre-cut, pre-finished wood grain cabinet enclosures with pre-painted baffle boards.
- 2 mounted grill cloths with pre-painted baffle boards.
- 2x8" woofers.
- 2 x1" dome

- tweeters
- 2 x 2 way crossover networks with leads and fastons fitted.
- Innerbond lining
- Wood screws.
- Wood glue
- Caulking compound.

Plus full assembly instructions. Check the column opposite this page for the dealer nearest you, or send coupon for a free brochure.

ELCOMA

To: ELCOMA, P.O. Box 50,
Lane Cove, N.S.W. 2066.
Please send me your fully
illustrated brochure on the Philips
AD8K40 Speaker Kit.

Name

Address

Postcode

153 89

Philips Stereo Speaker Kit now available from:

QLD:
GIPPS ELECTRONICS,
12 Douglas Street, MILTON 4064.


NSW:
PANTEK INDUSTRIES,
King Georges Rd., BEVERLEY HILLS.
EDGE ELECTRIX, 34A Burwood Road,
BURWOOD 2134.
RADIO DESPATCH SERVICE,
869 George Street, SYDNEY 2000.

ACT:
DURATONE HI-FI, 3A Botany Street,
PHILLIP, ACT 2606.

VIC:
J. H. MAGRATH & CO.,
308 Lt. Lonsdale Street, MELBOURNE
3000.
GEORGE HAWTHORN ELECTRONICS,
966-968 High Street, ARMADALE
3143.
LAWRENCE & HANSON GROUP,
142 Dorcas Street, MELBOURNE &
BRANCHES.
RADIO PARTS GROUP, 562 Spencer
Street, WEST MELBOURNE 3003,
1103 Dandenong Road, EAST
MALVERN 3145.
BALLARAT ELECTRICAL SUPPLIES,
5 Ripon Street, BALLARAT 3350.
TELEPARTS, 55 Fyans St West,
NEWTOWN (GEELONG) 3220.

SA:
GERARD & GOODMAN,
192 Rundle Street, ADELAIDE 5000.
SOUND SPECTRUM, Regent Arcade,
101 Rundle Street, ADELAIDE 5000.
WOOLLARD & CRABBE, 176 Wright
St., ADELAIDE 5000.

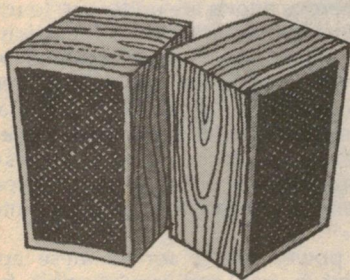WA:
ATKINS CARLYLE, 1-9 Milligan
Street, PERTH 6000.
V.A.E.A., 331 Charles Street, NORTH
PERTH 6000.
WILLIS TRADING CO., 445 Murray
Street, PERTH 6000.



ELCOMA

153.90

NEWS HIGHLIGHTS

New scientific calculator range


Novus, the Consumer Products Division of National Semiconductor Corporation, has introduced 14 new calculators in the USA to form the broadest range of portable calculating power available from a single manufacturer.

The new calculator range, unveiled at the Winter Consumer Electronics Show in Chicago, included five personal calculators for general consumer and business uses, five advanced calculators dedicated to a variety of professional computation tasks, and four 100-step "learn mode" programmable calculators.

The new Novus models have been introduced progressively into Australia over the past few months commencing with the model 850 and model 4510. The model 850 is an 8 digit floating decimal point machine with algebraic logic retailing at \$19.95. This joins the existing Novus 650, 950, 820 and 823 at the consumer end of the market.

The model 4510 Mathematician was the first of the Novus "Professional" models to be introduced. It is an electronic slide rule featuring RPN logic, a 3 level stack, separate accumulating memory and a full range of arithmetic, trigonometric and logarithmic functions, square root, reciprocals etc. The 4510 retails for \$79.95.

Following the model 4510 Math-

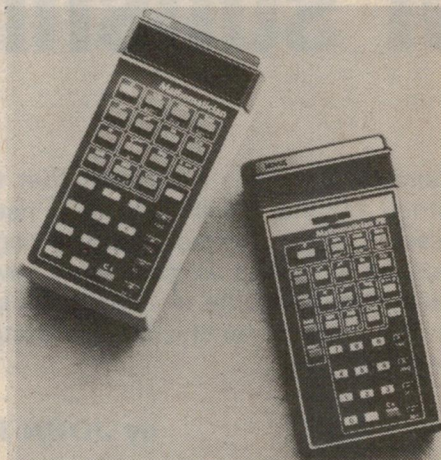

ematician, several additional dedicated professional models including the 4520 Scientist, 6010 International Computer, 6020 Financier and 6030 Statistician were introduced. These models are preprogrammed to provide the functions and formulae their names imply. The prices of these models will range from around \$100 for standard versions to \$179.95 for 100 step keyboard programmable versions.

For further information contact Novus, NS Electronics Pty Ltd, Cnr Stud Rd & Mountain Hwy, Bayswater, Victoria 3153.

New Manpack radio for US Marine Corp

A new, virtually-automatic Manpack radio that provides the use of 280,000 high-frequency-band channels to communicate over distances of hundreds of miles is being produced by Hughes Aircraft Company. Known officially as the AN/PRC-104, the new unit is designed to lighten the burden of a combat radioman, and to provide the highest degree of flexibility in tactical communications.

Hughes' ground systems group in Fullerton, California, will build about 5,000 of the new radios for the US Marine Corps under a \$22 million contract recently awarded by the US Naval Electronics Systems Command, according to Sam A. Stameson, Communications and Radar Division Manager.

The radio has so many automatic features that it is virtually a "hands-off" set. "The radioman simply goes into the transmit-receive mode, selects his frequency, and hits the press-to-talk switch. The antenna is tuned, the set is aligned, and the transmitter comes up full power, all automatically," Mr Stameson said.

Hughes' Manpack project manager Donald Q. Hall said the PRC-104 employs advanced circuit design and mi-



cro-miniaturised solid state devices to achieve high performance and ruggedness in an extremely small package. The radio, with its battery, forms a package only 12½ inches wide, 11½ inches tall and 2½ inches thick. Each unit weighs only 12½ pounds, including the battery pack.

Output power of the AN/PRC-104 transceiver is 20 watts, whilst average power consumption is somewhat less than five watts. Typical operational conditions call for a range of 50-300 miles.

—George E. Toles.

Solar cells: the promise of sunshine electricity

Spurred on by the realisation that the world supply of fossil fuel is limited and that it will continue to rise in price, the pace of solar energy research in the United States is beginning to quicken. Much of this research is aimed at producing low cost solar cells for converting sunlight directly into electricity. This article takes a brief look at solar energy research in the United States, and presents a timetable for the future.

by JOHN R. FREE

Sunlight glistened from thousands of solar cells on a rooftop near Washington, DC. I was looking at the most powerful solar cell array assembled for terrestrial use in the world. But its 1000-watt power rating seemed modest for this claim. Mitre Corporation, an engineering firm studying solar cell systems, had paid \$30,000 for 20 panels of cells.

That's \$30 a watt, typical for solar-cell power today, and the main reason larger arrays aren't delivering tens of kilowatts or megawatts to homes and buildings. Costs quickly become astronomical. What's kept solar cell prices so high over

the years has been technological limitations and a small, specialized market. Solar cells, priced at \$200 to \$600 a watt, have been used primarily in space vehicles and satellites, where they must be used regardless of price.

But now, with energy scarcities becoming critical, there's a growing effort to reduce solar-cell costs and bring cell power down to earth. Industry, government, and academic experts I've visited and questioned are optimistic that manufacturing costs for cells can be shaved to fifty, then thirty cents a watt during the 1980s. At these prices, cell systems for homes, schools, shopping centres, industrial plants, and utility power networks are practical.

One irrefutable fact makes Joseph Lindmayer of Solarex Corporation hopeful: silicon—now used for most solar cells—is the second most abundant element on earth next to oxygen. (Sand is mostly silicon dioxide.) "Between the abundant resources of silicon and light," Lindmayer told a US Senate subcommittee, "we have only technological difficulties in making the systems work economically."

Happily, a string of developments suggest these difficulties can be solved:

- A breakthrough process called edge-defined film-fed growth (EFG) promises low-cost cells made from continuous silicon ribbons;

- Oil companies are pumping vital funds into EFG development and the improvement of cadmium-sulphide (CdS) solar cells;

- Spinoffs from space research are boosting cell efficiencies and suggesting ways to automate production;

- Manufacturers of purified silicon are exploring ways to trim raw-material costs;


- Systems to store solar energy for round-the-clock use are being designed and tested; and

- Techniques are being studied to boost solar-cell power enormously by concentrating sunlight.

Quickening the pace of solar energy research is the realization that our supply of fossil fuels is limited and that they will continue to climb in price. As a result, the US Government is planning a billion-dollar effort to tap the sun's energy. "It appears possible that by the year 2000, solar-energy systems might be capable of supplying 5 to 10 percent of the total US electricity requirement," says John Sawhill of the Federal Energy Office.

Numerous efforts are underway to use solar energy: solar heat-to-electricity power plants; wind power created by solar heating; solar heated/cooled homes and buildings; and even generators powered by differences in ocean temperatures. Researchers are also studying chemical processors to convert solar energy stored in vegetation into fuels.

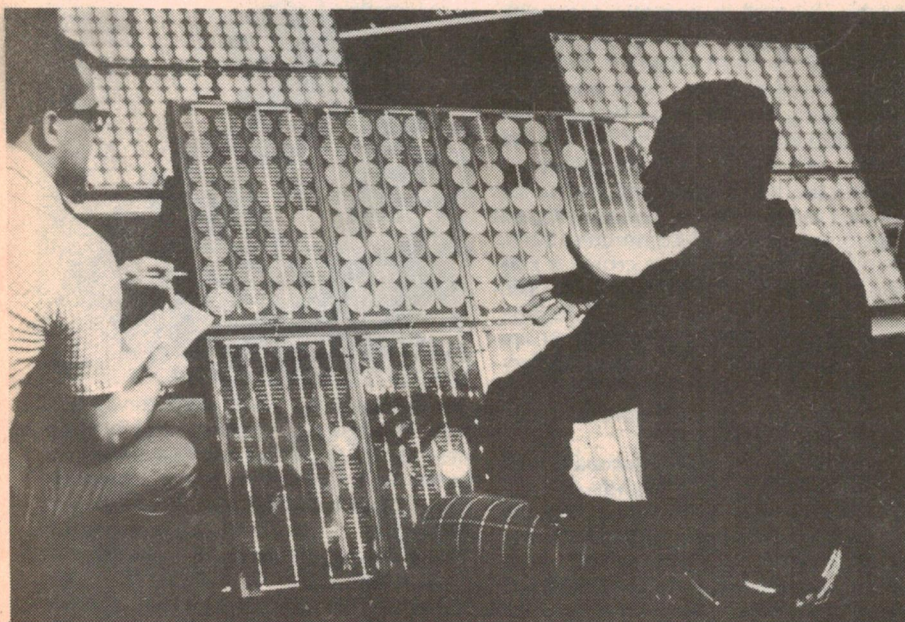The power source for all these approaches is free and inexhaustible by human time scales. In the US, the Sun beams a daily, all-weather average of 194 watts on each square metre of land. Ordinarily, each day, the roof of your house



These glittering solar cell panels each produce 50 watts of peak power. Twenty such panels, mounted on top of the Mitre Corporation building in Washington DC, are used by Mitre Corporation as the basis for an experimental 1kW system.

receives three times more energy from sunlight than the energy you consume by heating, cooling, or other electrical usage.

But solar cells have a special advantage. Using what is called the photovoltaic effect, they convert light directly into electricity. There is no physical movement involved, no heat-to-steam step, no air pollution and no noise.

Cells, of course, have disadvantages, too. Like other solar energy systems, their dependence on sunlight mandates an energy storage system, such as batteries. Efficiency of solar cells (input versus output power) may be limited to about 23 percent. And for widespread use, the DC output of cells must be converted to AC.

Also, a large land area is needed: one square mile of 12-percent-efficient cells delivers an average of 50MW power. (Cells are rated for their peak output—when the sun is brightest. Average power, figured over 24 hours, is about one-fifth peak power.) Right now, though, the biggest obstacle to solar cell systems is cost.


The manufacturing process used today is primarily responsible for the high price of silicon cells. Solar cells were developed at Bell Labs during the early 1950s. Researchers found that to make efficient cells, the jumbled polycrystalline structure of purified silicon must first be converted into the orderly, all-in-a-line structure of single-crystal silicon. They turned to the Czochralski process.

This crystal-growing technique, invented in 1923, provides single-crystal silicon in the form of cylindrical ingots two or more inches in diameter. Producing these ingots, however, is time-consuming and costly. One batch of silicon must be melted for each ingot. A pinch of boron, phosphorus, or another impurity converts the purified silicon (a poor electrical conductor) into a semiconductor.

Then, a silicon seed crystal is lowered into the 1,420°C liquid and an ingot is "grown" by twirling and pulling the seed upward at a few centimetres per hour.

But, once an ingot has been painstakingly grown, up to three-quarters of it must be destroyed to produce solar cells. During a tour of NASA's extensive research facilities at the Cleveland Research Center, I saw why. A circular diamond saw, which looks much like its cousin at your meat counter, zips slices from icicle-like silicon ingots as easily as it would cut through butter. The silicon slices are only 0.25-0.30mm thick. But since the saw blade is also this thick, much of the ingot becomes sawdust. Rectangular cells, used for compactness in space, waste still more silicon.

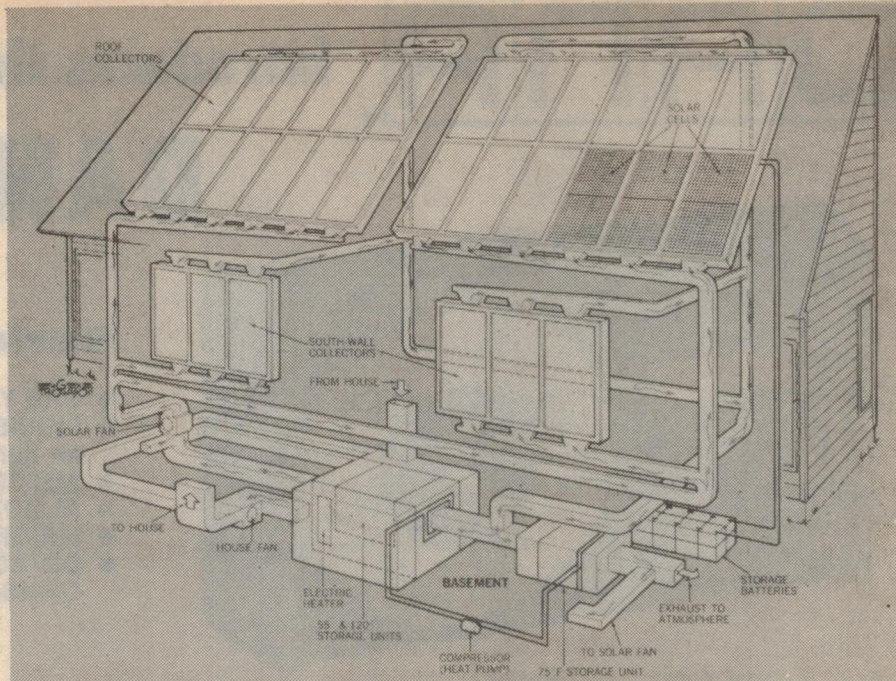Grinding and polishing these silicon wafers pushes labour costs higher. Wafers are then baked in a chemical atmosphere that diffuses another semiconducting layer into one surface. Finally, electrical terminals are attached and the wafers are wired into solar panels.



Solar One house at the University of Delaware "harvests" sunlight into both heat and electricity, and will ultimately obtain 80 percent of its energy needs from the Sun. The 45° angled roof has 24 solar panels, three of which are covered with cadmium-sulphide (CdS) solar cells. Six additional panels are on the south wall. DC electricity generated by the solar cells is used to charge an 18kW/hr battery system for lighting and resistive type appliances. A DC to AC inverter is planned for motor-driven devices. Heat energy generated in the cells is collected by air circulating beneath the cells. This hot air passes through ductwork into a basement storage system using eutectic salt bins. The heating cycle is supplemented by a heat pump which can also be used to collect cool air at night, further chilling it to freeze another eutectic salt for the air-conditioning system.

Automating some steps should bring costs down to \$5 a watt with Czochralski ingots in a few years. That's still too expensive for large scale applications, but reduced prices would increase solar cell use.

Solar cell costs can be effectively trimmed another way. At Solar Power's small plant near Boston, president Bob Willis demonstrated how a cell's power can be boosted several times—or hundreds of times. Standing on a roof, I saw several test cells covered with dome-shaped plastic lenses. By concentrating sunlight on a cell, Willis explained, its current output can be increased in proportion to the light collected. Most manufacturers are also experimenting with mirror concentrators and thin Fresnel plastic lenses.

Sunlight concentrators look like a promising way of reducing costs (fewer cells are needed), but there are tradeoffs. "One advantage of solar cells is that you don't have to do anything to them," says Dan Bernatowicz, who directs solar research at NASA's Lewis Center. "They just sit there and generate power for years and years."

This advantage of unattended, long-lived operation could be lost if large concentrators are used, Bernatowicz feels. The reason: exotic devices needed

to remove excess heat from cells may break down. Similarly, mechanisms for tracking the sun throughout the day could fail. Bernatowicz thinks seasonal tracking (periodically shifting cell panels by hand) might be more practical.

The role that concentrators or tracking mechanisms might play in large-scale systems is undetermined. But most experts believe the key to cost cutting lies in the cell-manufacturing process itself. And now there's a process called edge-defined film-fed growth (EFG) that appears to offer great promise.


EFG, which provides long ribbons of single-crystal silicon, resulted from a joint venture by Tyco Laboratories and Harvard University. Mobil Oil Corporation recently agreed to provide up to \$30 million to develop EFG jointly with Tyco over several years.

Originally, EFG was developed to speed the growth of single-crystal sapphire, used for microcircuits and in other industrial applications. When a die is lowered into molten silicon or sapphire material, the liquid rises through its centre by capillary action. The material flows only to the top edge of the die whose shape determines whether a tube, square, ribbon, etc., is formed. A seed crystal pulls the solidifying material upward; one thin dimension must exist to

DANA

introduces the


DANAMETER

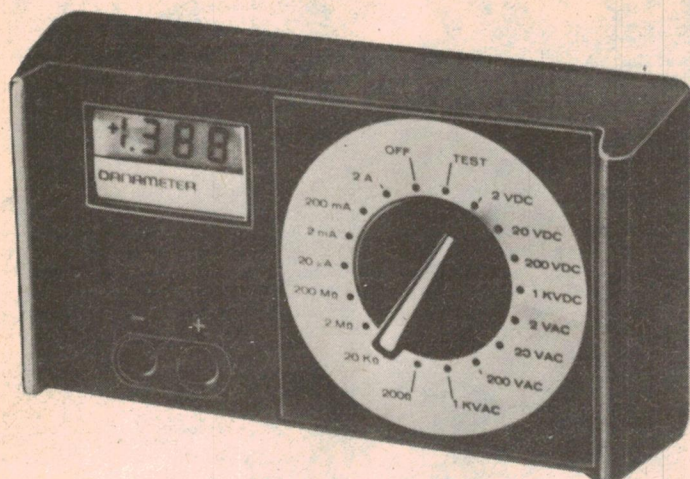


Series 2000

- ONE YEAR BATTERY LIFE
- LIQUID CRYSTAL DISPLAY for quick, clear readout
- AUTOMATIC POLARITY
- ALMOST INDESTRUCTIBLE
- WEIGHS ONLY 1 lb (453.59 g)
- DC/AC VOLTS, DC CURRENT, OHMS, R.F. & H.V. OPTIONS


4-DIGIT VOLTMETERS

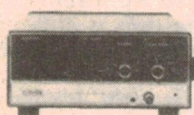

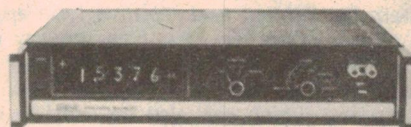Series 4300 • Unbreakable—rugged construction • 4-digit led readout with insignificant zero elimination • 100% overranging • On-line or battery operated • Exclusive battery sensor and protection • Automatic display intensity control • Protection against incorrect range and mode combinations • Overload high voltage protection in all functions.




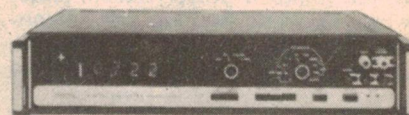Series 4700A • Economical 4-digit multimeter • 5 DC ranges with 10 μ V resolution • 4 AC ranges over wide bandwidth—40 Hz to 100 kHz • 6 K Ω ranges with 10 milliohm resolution • 0.01 DC accuracy • Autoranging—all functions, all ranges • 100% overrange • Solid-state isolated digital output and programming • High voltage overload protection.



Series 4800 • 100% overranging • Systems oriented 4-digit Voltmeter • Ultrafast AC, mV & ohms measurements • 0.005% DC accuracy—1 μ V resolution • More than 18 DC readings per second • High accuracy, distortion insensitive AC converter • Four wire ohms—9 ohm ranges.


5-DIGIT VOLTMETERS

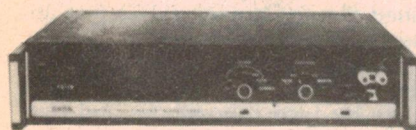

Series 5000 • Economical 5-digit Voltmeter • 100% overranging • Four-wire—four quadrant—autopolarity DC/DC ratio • 0.005% DC accuracy • Full systems capability • Switchable filter plus integrator • 1 milliohm resolution • Delayed dual slope.



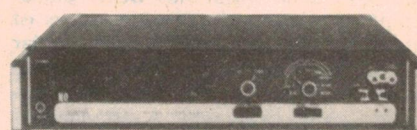Series 5800A • High performance 5-digit Voltmeter • 0.003% DC accuracy • 100 dB normal mode rejection • 0.1 microvolt resolution • 9 ohm ranges (auto-ranging 1 ohm to 100 megohm full scale) • Fast RMS AC measurements • AC/AC, AC/DC, DC/AC ratios • 125 DC and 10 AC readings/second • Systems compatible (8-command modes).



Series 5900 • 0.001% DC accuracy • High performance 5-digit Voltmeter • 100 dB normal mode rejection • 60% overrange • True four-wire ratio • 20/100 readings/second • 0.003% ohms accuracy.

DANA

Others measure by us.

Distributed by:

JACOBY MITCHELL

215 North Rocks Road, North Rocks, N.S.W.
2151. Phone: 630 7400
OFFICES: Melbourne 44 5021 • Adelaide
293 6117 • Brisbane 52 8266 • Perth 81 4144

The Promise of Sunshine Electricity

enable heat to dissipate quickly. In contrast, thick Czochralski-grown ingots lose heat slowly and take much longer to crystallize.

What makes Mobil bullish on EFG is the phenomenal rate at which silicon can be produced. This year Tyco pulled a six-foot-long ribbon from a crucible of molten silicon in one hour. The ribbons can be converted into solar cells without costly grinding and polishing.


"The next major step is to produce a ribbon 50 to 100 feet long," says Tyco's A. I. Mlavsky. That step, which Mlavsky believes will occur before mid-1975, will be a significant EFG milestone.

Standing near one of Tyco's single-ribbon EFG lab machines, however, I found the numbers involved in this engineering scaleup to be staggering. According to one estimate, to produce

tion-type silicon cells are being investigated, too. IBM recently brewed up an 18-percent-efficient gallium-arsenide cell. Gallium is nearly as abundant as lead. Schottky-barrier devices—thin semi-conducting layers with an ultra-thin metal coating—are also showing promise.

Next to silicon-based cells, however, the most intensely studied devices involve thin films of cadmium sulphide combined with copper sulphide and other compounds. Solar Energy Systems, associated with the University of Delaware's Institute of Energy Conversion, is setting up lines to fabricate cadmium-sulphide (CdS) cells with \$3 million backing by Shell Oil Corporation.

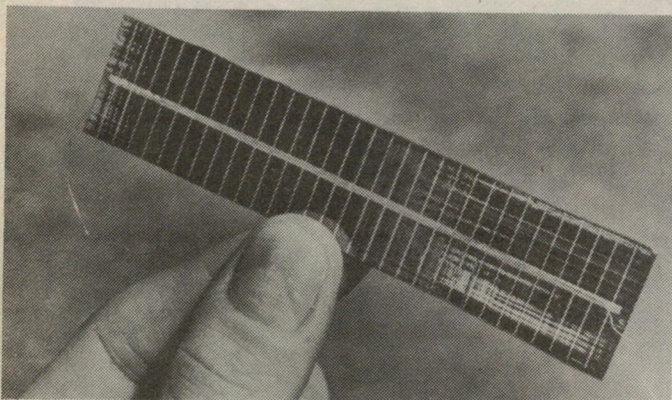Although CdS cells are less expensive and simpler to manufacture than silicon cells, they have several disadvantages by comparison. Their efficiency has been



Developed by Tyco Laboratories, this experimental solar cell is made from silicon ribbon grown by the EFG process.

4000 MW (about one percent of US generating capacity today), would require 80 square miles of 12-percent-efficient solar cells and about 100,000 tons of silicon. That translates into 40,000 ribbons growing simultaneously for one year, according to Motorola's I. A. Lesk.

Another ribbon process, called dendritic-web growth, was developed during the 1960's at Westinghouse. In this technique, wire-like seed crystals, which act as ribbon edge supports, are used to pull silicon from the melt. "It's like a couple of wires with a bridge across the top being immersed in a soap solution," says Raymond Seidensticker of Westinghouse. Although web-process ribbons were being wound on spools years ago, most authorities believe the process isn't economical enough for mass production.

Some researchers are trying to form extraordinarily thin films of silicon—millionths of an inch thick. Although thin-film polycrystalline cells would be cheap compared with single-crystal forms, the efficiency hangup must be solved. So far, polycrystalline efficiency has been limited to about one percent. Without improvement, such arrays would require enormous land or rooftop areas.

A wide variety of alternatives to junc-

limited to less than eight percent, and they deteriorate rapidly when exposed to air.

Nevertheless, carefully encapsulated CdS cells have been used to collect data from Solar One, the solar home built by the Institute. So far, only three CdS panels have been installed on Solar One. The use of NASA reject cells has also limited overall efficiency to 2.5 percent (340 watts peak).


According to physicist Karl Böer, data gathered during two winter and spring days shows that a completed CdS roof panel would provide from 26 to 43 percent of the home's electrical needs. The eight-percent cells Böer anticipates from Solar Energy Systems could supply some 87 percent of Solar One's requirements.

Mitre is also collecting data from its 1kW system, and is designing a 1MW system. Part of the electricity generated by the 20 rooftop panels will produce hydrogen and oxygen from water; fuel cells will help provide power when the sun is not shining.

Results from these and other working systems—combined with low-cost cells developed in coming years—will provide the technology to conserve billions of dollars' worth of fossil fuels.

Timetable leading to large-scale terrestrial applications of solar cells

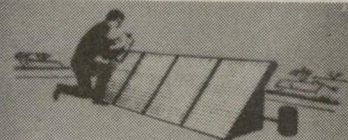1975 Data-collection network established to measure sun's intensity throughout U.S.




1976 Solar arrays tested at several sites. Central-station cost limits determined.

1977 Lower-power systems designed. Technology for \$5/watt (peak) cells attained.

1979 Low-power system installed. Technology shown for \$0.50/watt (peak) cells.



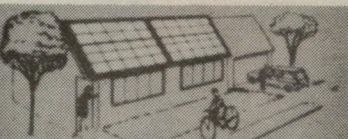
1981 Pilot line completed to manufacture arrays using \$0.50/watt (peak) cells.



1982 Solar-cell systems from 10 kw to 1 Mw installed in homes, schools, etc.

1985 Medium-power 10-Mw systems built for communities and large industrial plants.

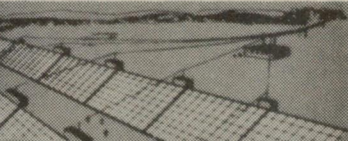1986 Pilot-line completed to manufacture \$0.30/watt (peak) solar-cell arrays.



1990 Giant solar-cell systems (100 Mw or more) provide power to towns and utilities.

Here at last is reliable, rechargeable power, power to deliver high currents at stable voltages... compact, rugged and long lasting. Plessey SAFT Batteries offer the most versatile, maintenance free power source available. Portable power for consumer, industry and military applications ranging from tooth-brushes to transceivers... shavers to satellites... missiles to medical instruments.

Plessey SAFT nickel cadmium batteries give

a long useful life with constant power and are rechargeable many times.

Technical literature and our technical advisory service are available on request.


Plessey
SAFT

Made under licence from
Société des Accumulateurs Fixes
et de Traction by

Plessey Australia Pty Limited
Components Division
Box 2 PO Villawood NSW 2163
Telephone 72 0133 Telex 20384

MELB. Zephyr Products Pty Ltd 56 7231
PERTH H.J. McQuillan Pty Ltd 68 7111
ADEL. K.D. Fisher & Co 223 6294
BRIS. L.E. Boughen & Co 70 8097
N.Z. Henderson (N.Z.) 6 4189

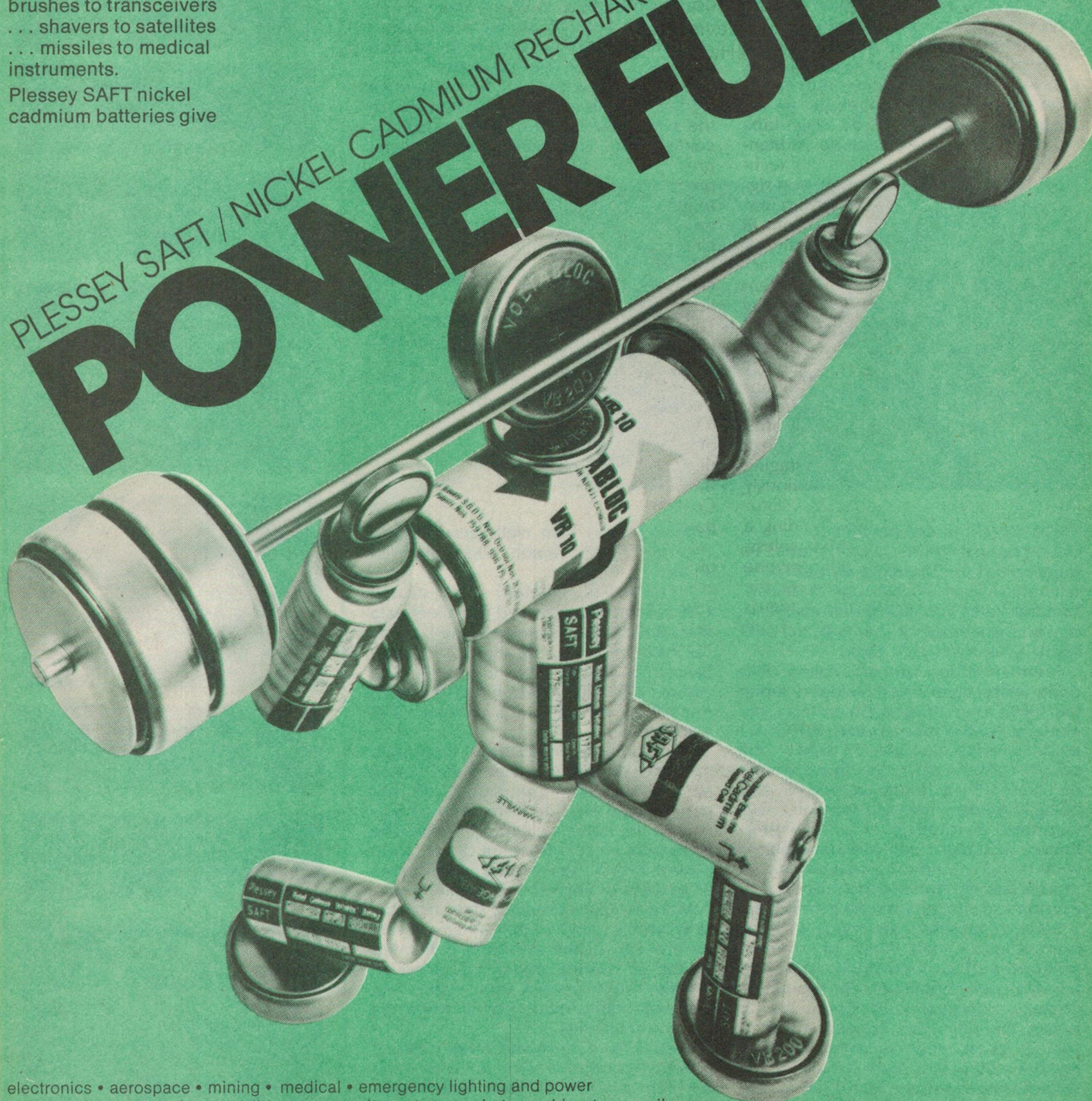PLESSEY SAFT / NICKEL CADMIUM RECHARGEABLE BATTERIES
POWER FULL!



electronics • aerospace • mining • medical • emergency lighting and power
• process instrumentation • appliances • security systems • photographic • toys • railways •

AC 37/R1 HOLT

Frequency calibration using a colour TV set

Numerous occasions arise when it is desired to calibrate an oscillator against an accurate frequency reference. Most Americans have such a reference sitting in their lounge room—the colour TV set. The US National Bureau of Standards has devised several methods for calibrating an oscillator against the 3.58MHz colour burst signal as transmitted by the four major networks.

Researchers at the Boulder laboratories of the National Bureau of Standards have developed a series of techniques which use network television signals to calibrate oscillators with accuracies approaching a part in 10^{11} , in 15 minutes or less of measurement time.

This combination of speed and accuracy exceeds that of any other system of frequency calibration available today and accomplishes it at relatively low cost. For example, short wave radio broadcasts can achieve only 1×10^{-7} accuracy (a part in 10^7) if propagation conditions are favourable, and low frequency broadcasts can provide 1×10^{-10} only after one day of averaging or 1×10^{-11} in a week of averaging. Such long averaging times for high accuracy are obviously inconvenient and, when the oscillator under test has a drift rate exceeding a part in 10^{10} per day, they become useless.

The new techniques permit anyone with a colour TV set to "borrow" the networks' atomic frequency standards for his test. All four major networks in the USA (ABC, CBS, NBC and PBS) use rubidium-controlled oscillators to create

the 3.58MHz frequency that forms the colour burst signal. This stable signal is present in all network-originated colour programs, and when a TV set is tuned to a live network program (not delayed on tape by the local station), the TV set's circuit is locked to this frequency.

NBS measures the networks' frequencies regularly and publishes their relationship to the NBS standard frequency. Thus, a user can calibrate his own oscillator in terms of the NBS standard by using TV.

There are several ways to extract this frequency from the TV receiver and use it to calibrate another oscillator. In order of increasing complexity, four techniques developed at NBS are: the "RF Colour Bar Comparator," "Video Colour Bar Comparator," "Digital Subcarrier Comparator" and "Digital Offset Computer."


The "RF Colour Bar" technique requires no modification to the TV set and achieves 1×10^{-9} accuracy in less than 5 minutes of measurement. For a parts cost of less than \$50, a small electronic circuit can be built which creates a vertical rainbow coloured bar on the TV

screen when attached to the antenna terminals. When the oscillator under test is plugged into the circuit, the bar moves across the screen at a rate proportional to the difference between the tested frequency and the network frequency. When the difference is small, the motion is very slow, and the bar changes colours at a rate proportional to the difference. The test oscillator must have a frequency of $(5/N)$ MHz when $N = 1, 2, 3, \dots$. By timing the number of seconds required for the colours to change from red through blue, green and back to red, the difference between frequencies can be calculated.

The "Video Colour Bar" technique is very similar, except that the colour calibration signal is injected into the chroma circuit instead of the antenna terminal. This requires the addition of a resistor and two capacitors to the TV circuit, but does not interfere at all with normal program reception. The advantage is an improvement in the appearance of the colour bar, which improves the resolution of the measurement. This version permits 1×10^{-10} accuracy in 5 minutes.

The third version requires more elaborate circuitry and provides greater accuracy. Called the "Digital Subcarrier Comparator," it generates a narrow vertical line that proceeds slowly across the screen and then snaps back rapidly, acting as an analog indicator of the phase difference between the frequency being tested (or adjusted) and the reference signal from the network. At the same time, the period of one cycle of this phase difference is indicated by a 4-digit counter. Accuracy to one part in 10^{10} is possible in $1\frac{1}{2}$ minutes of measurement time, or 2 parts in 10^{11} in about 15 minutes.

The most accurate and easiest-to-run is the fourth technique which is almost completely automatic. The circuits developed by NBS take a series of averaged readings, automatically compute the difference between test oscillator and reference signal and display the difference in 10 four-digit numbers on the TV screen. The numbers are averaged by the operator to obtain an accuracy approaching one part in 10^{11} in 15 minutes.

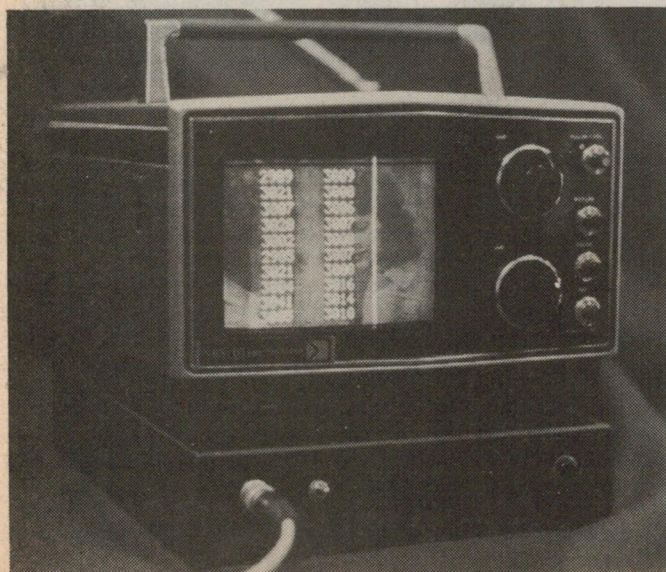

A typical readout obtained using the digital offset computer technique. The current 10 samples of frequency difference are displayed in the left hand column, while the averages of 10 groups of 10 samples each are displayed in the right.

Reprinted from "Dimensions", by arrangement with the US National Bureau of Standards.

A control unit for intermittent wiper action

In this article we present full constructional details of a simple type of intermittent windscreen wiper control, which uses a minimum of parts, and can be fitted to almost all types of cars. Fitted with push button control, our Variable Delay Wiper will make a neat addition to your dashboard.

by DAVID EDWARDS

Almost anyone who drives a car must have found themselves in the situation where it is raining hard enough to need to use the windscreen wipers, but not hard enough to need them on continuously. As a result, one has to constantly reach for the wiper switch, turning them on and off as the need arises. This can be very tiring on a long trip, and must reduce the driver's concentration, so vital to a safe journey.

Two-speed wipers do help to alleviate this problem, but do not entirely cope with all weather situations, particularly when it is only just raining, and a wipe every few seconds or so is all that is needed. The Variable Delay Wiper control described in this article is designed to overcome this problem, in a simple, reliable and economical way.

One of the main features we have incorporated into the controller is that it should fit all makes of cars without modifications, yet at the same time be simple to build and operate. In its basic form, our controller is suitable for both positive and negative earth cars, for single and dual speed wipers, and for wound field and permanent magnet motors, including those with dynamic braking.

The second major feature we have incorporated into our design is inherent safety. When the controller is not being used, the wipers are controlled by the main wiper switch, exactly as standard. To use the Variable Delay Wiper, the main wiper switch is turned off, and the Variable Delay Wiper turned on. If during intermittent operation, it is required to use the wipers normally, operation of the main wiper switch will achieve this.

As presented in this article, the controller is only suitable for use with 12V cars. However, only one component (the relay) need be changed to enable use with 6V vehicles. This controller cannot be used in cars which are already fitted with continuously variable wipers. (These cars probably have a completely satis-

factory system anyway!)


In order to make the controller applicable to all cars, we have not used a completely solid state design, but incorporated a relay as the output device. This serves four purposes: it functions as a power amplifier; it provides isolation between the electronics of the controller and the wiper circuitry; it makes possible the control of most types of wipers; and it ensures that normal operation of the wipers will be possible in the event of a failure of the controller.

found that this does not give satisfactory control, due to the nature of the effect being controlled.

When the volume control of a radio is varied, the change in level of the sound is detected by the ears, processed by the brain, and applied to the hands controlling the volume. This is a stable system, as any tendency for a too drastic change is immediately perceived and acted on. Of course, this requires a little practice, but this is usually easily mastered.

This system achieves stability because of the speed with which the brain can act on the information that the change is too large, and use it to control the hand. Unfortunately, there is a time delay inherent in the use of this system to control our variable delay wipers, and we can no longer achieve stable operation.

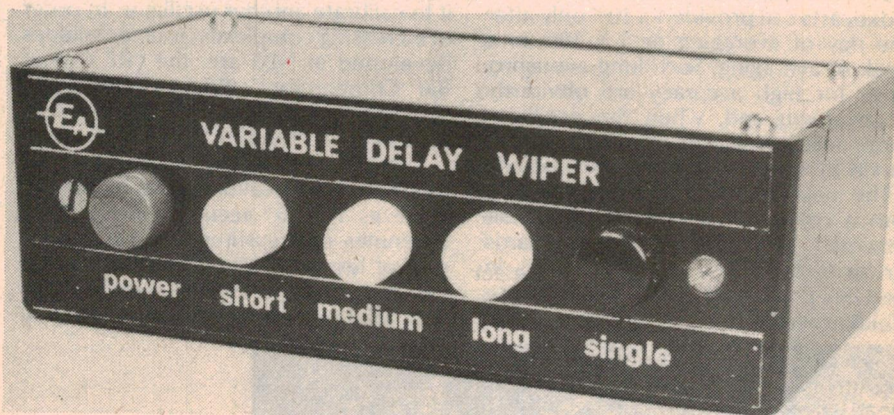This delay arises because we are trying to control a delay. Suppose that our control is set to give a ten-second delay



The completed prototype, housed in a plastic case.

This last feature arises because the relay, in the unoperated position, does not alter the original circuitry of the main wiper control switch in any way, so that if a failure does occur, the circuitry will not be changed. If the failure is such that the relay remains energised, it is only necessary to turn off the Variable Delay Wiper to de-energise the relay.

There is of course a possibility that the relay could mechanically jam in the operated position, but the chances of this occurring should be very remote.

The conventional way of varying the delay rate of the wipers is via a potentiometer, in the same way as the volume of a radio is varied. However, we have

between wipes, and it has just finished a wipe. The next wipe is not due to commence for about ten seconds, but we decide to increase the wiping rate to one every five seconds. If we give the control pot a nudge in the correct direction, nothing happens, at least not immediately. There is no signal to tell our brain what the effect of the nudge was.

Figuratively speaking, we are floundering in the dark, so to get some sort of response, we give the pot a much larger nudge. This produces a wipe almost immediately, but we then discover that we have increased the wiping rate to one every two seconds. This was not the intended effect.

The three interlocked switches, S2, S3 and S4, are wired so that the three trim pots are normally shorted. Thus when S2 is pushed, the 10k trimpot is placed in series with the 4.7k limiting resistor, when S3 is pushed, the 47k trimpot is selected, and when S4 is pushed, the 220k trimpot is selected.



The single wipe facility is obtained by forcing the 220uF capacitor to full charge. This corresponds to a voltage of two-thirds of the supply voltage, and is achieved by means of a low impedance resistive divider formed by the 180 ohm and 82 ohm resistors. As this divider puts a considerable load on the supply rail, it is only connected when required.

Note: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with high ratings may generally be used, providing they are physically compatible. Components with lower ratings may also be used in some cases if available, providing ratings are not exceeded.

AWA

world's finest public address equipment!

**Guaranteed quality . . . guaranteed after-sales
service throughout Australia!**

TOA — the world's best equipment and AWA,
Australia's leading electronics organisation
. . . the unbeatable combination for the
highest standards of public address
equipment and systems around Australia.

TOA delivers highest efficiency, long life and
a greater carrying power to greater ranges
under ideal or difficult conditions. And it's
backed by AWA's Australia-wide sales and
service network.

Distributed throughout Australia by
AMALGAMATED WIRELESS
(AUSTRALASIA) LIMITED — Ashfield Division

SYDNEY phone 797 5757
NEWCASTLE phone 2 5166
CANBERRA phone 95 3431
BRISBANE phone 44 1631
MELBOURNE phone 560 4533


ADELAIDE phone 272 2366
PERTH phone 71 0888
HOBART phone 34 3836
LAUNCESTON phone 31 5466

*Additional information is available on request
from any of the above branches.*



AWA

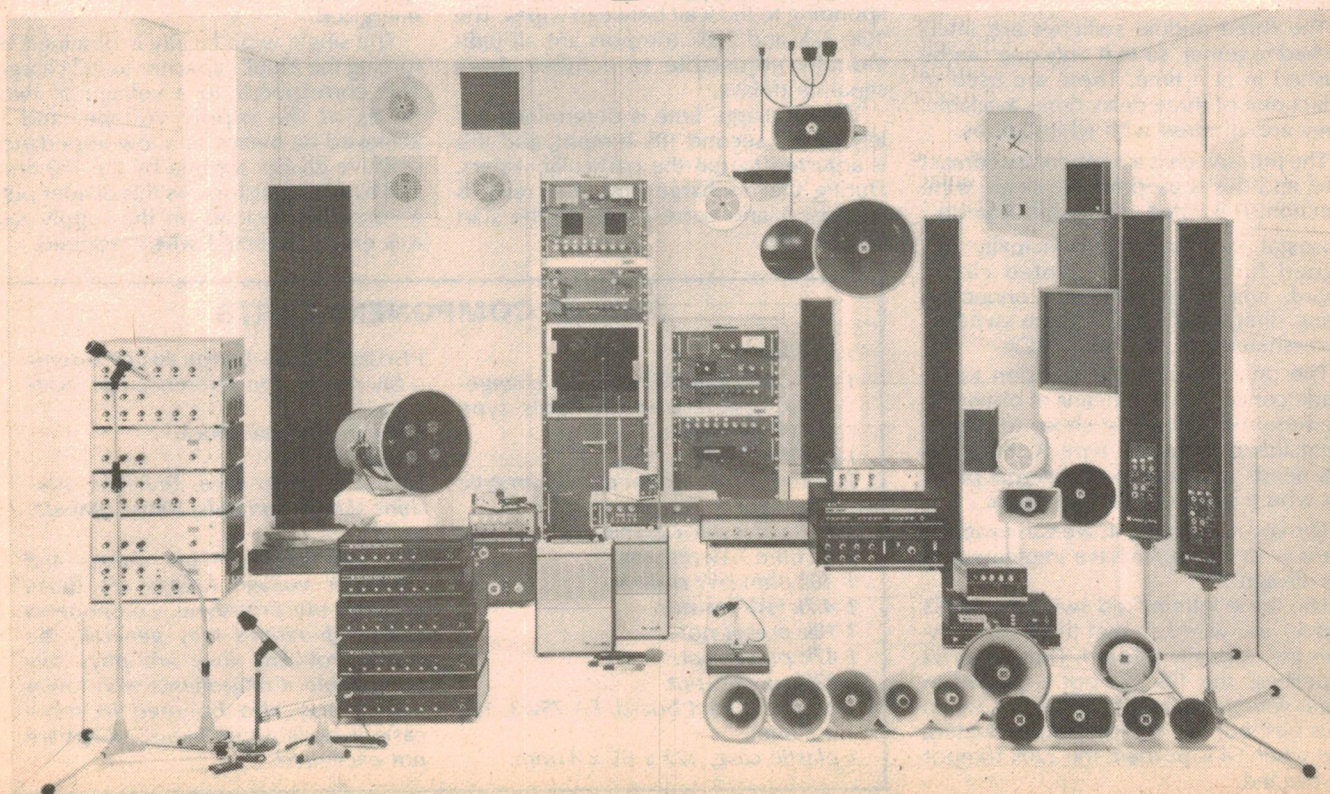**World's finest
Public Address
equipment**



Variable Delay Wiper

Such a low impedance divider is required to ensure that the capacitor is charged almost immediately.

It is necessary to filter the supply voltage to prevent ignition transients and surges due to load changes on the car electrics from falsely triggering the timer. This is achieved by the 1uF capacitor. In extreme cases, it may be necessary to fit a 1000uF electrolytic capacitor as well.

Before describing the construction of the unit, we will digress and give a short explanation of the various types of electric wipers commonly fitted to cars. Table 1 is a list of the more common types, and their identifying characteristics.

The earliest types of motors employed a wound field, and these were characterised by a good self-braking action. All that is required to control them is a simple on-off switch. Self parking is achieved by using a second, mechanically linked switch in parallel, which keeps power applied until the parking position is reached. Fig. 2 is a schematic diagram of such a system.

However, the more recent type of permanent magnet motor does not have the same braking characteristics, and it is necessary to apply dynamic braking by placing a short across the armature. Fig. 3 is a representative schematic circuit for these types of motors.

In the on position, the wiper motor is connected directly to the 12V supply. As the motor rotates, it operates a synchronised change-over switch. In the diagram, this switch is shown in the self-parking position, and it can be seen that there is a short directly across the motor armature.

When the wipers are turned off, the armature is earthed via the "B" contact on the wiper switch, and by the cam-actuated switch, so that the motor continues to operate. However, when the cam-actuated switch operates, it shorts out the armature, bringing the motor, and hence the wipers, to a stop. The cam is

TABLE 1: Windscreen Motor Systems			
No. of speeds	Type of Motor	No. of wires to switch	System code
1	wound field	2	1
1	wound fld, not self-parking	2	1a
2	wound field	3	2
1	permanent mag.	3	3
2	permanent mag.	4	4
cont. variable	not suitable for use with our timer		

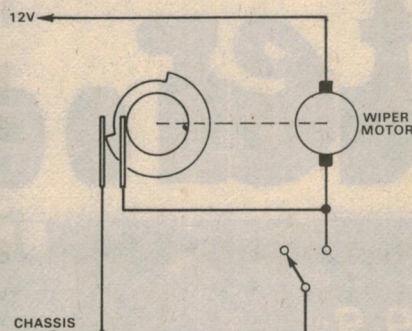


FIG. 2 SELF PARKING WOUND FIELD TYPE MOTOR SHOWN IN PARKED POSITION

A list of the most common types of windscreen wiper motors is given in Table 1

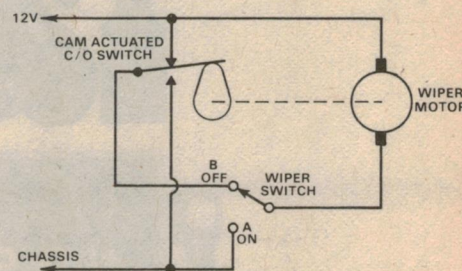


FIG. 3 TYPICAL PERMANENT MAGNET MOTOR SHOWN IN PARKED POSITION

arranged so that this occurs at the bottom of the windscreen.

For all types of motors, our relay must act in a parallel fashion, so that it will turn on the wipers when the main switch is turned off, but not interfere when the main wiper is turned on. In order to do this, it is essential to use a relay with break before make contacts, such as the one specified in the parts list.

With all types of two-speed wipers, we recommend that in the intermittent mode, the slow speed is used. This will help to minimise the current through the relay contacts on switch on without seriously affecting the wiping action.

Construction of the unit should be relatively easy, as most of the components are mounted on a printed circuit board. The first stage is to mount the switch assembly on the PCB. This must

be fitted with the momentary contact switch on the right hand end, as shown in the photographs. Do not push the switch right down onto the PCB, as otherwise there will not be enough clearance above the relay.

When fitting the remaining components, take care to fit them with the correct polarity. The two trimpots on the right hand end must be fitted so that their wipers do not touch, as shown in the photograph. PCB pins can be fitted to the relay outputs, as well as the power supply points.

The PCB and switch assembly is held into the plastic case by two countersunk machine screws, in conjunction with nylon spacers. We used extra nuts to lengthen the spacers, as this gave a better appearance from the front. Before fitting the PCB, drill five clearance holes for the wires to the terminal block, and fit and wire it.

The suppression components, which are not fitted onto the PCB, can be wired directly between the negative supply input and one of the tags on top of the power switch. Our photograph shows how we fitted the 1uF capacitor. If needed, the 1000uF electro. can be fitted in a similar manner, or it can be wired directly across the terminal block.

Once construction is complete, the unit can be installed in the car. A small bracket must be made, to hold the case to the underside of the dashboard. We have left the details of this to the individual constructor, as it will have to be made to suit each individual car and mounting point.


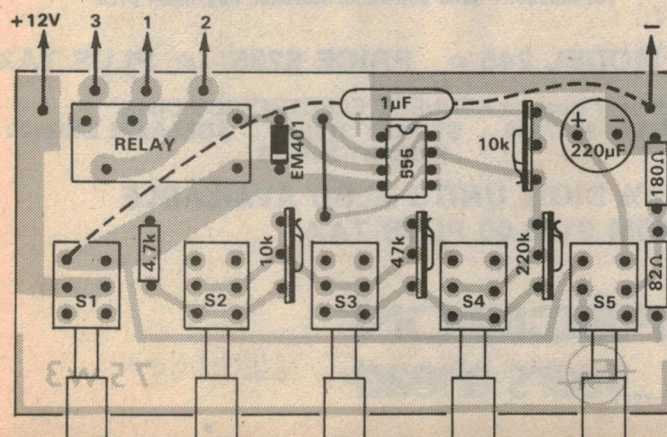


FIG. 5

The component layout for the Variable Delay Wiper control. For greater reliability, fixed resistors may be wired in place of the trimpots once the values of these are known.

10,000 meters later...

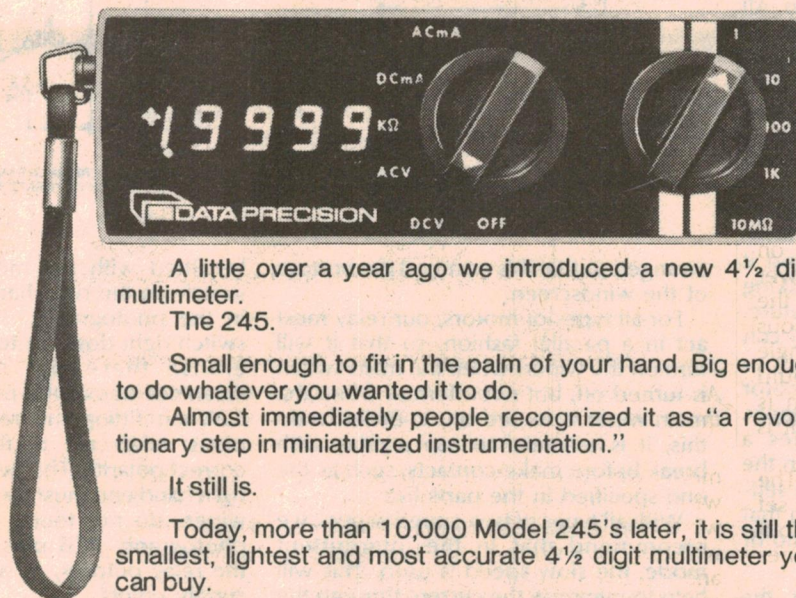

A little over a year ago we introduced a new 4½ digit multimeter.
The 245.

Small enough to fit in the palm of your hand. Big enough to do whatever you wanted it to do.

Almost immediately people recognized it as "a revolutionary step in miniaturized instrumentation."

It still is.

Today, more than 10,000 Model 245's later, it is still the smallest, lightest and most accurate 4½ digit multimeter you can buy.

Model 245 is a rugged, truly miniature, laboratory quality 4½ digit multimeter that measures AC volts, DC volts, AC current, DC current and resistance with .005% resolution and a basic accuracy of $\pm .05\%$ with 100% overranging.

DC Volts, 1 volt to 1000 volts full scale, 100 μ V resolution.

AC Volts, 1 volt to 500 volts RMS full scale, 100 μ V resolution, 30 HZ-50kHz.

DC Current, 1 ma to 1 A f.s., 1 μ A resolution.

AC Current, 1 ma to 1 A f.s., 1 μ A resolution, 30 HZ-50kHz.

Resistance, 1 K Ω -10M Ω full scale, 100 milliohms resolution.

To get your hands on this remarkable instrument, simply contact your local sales representative for immediate delivery.


KENNEDY ELECTRONICS PTY. LTD.

142 Highbury Road Burwood, Victoria, Australia 3125

☆ **MODEL 245** ☆ **PRICE \$235** ☆ **PLUS TAX**

Call your nearest KENNEDY ELECTRONICS Office
MELB. 2887100 SYDNEY 318243 ADELAIDE 2232420
HOBART 345175

☆ **3½ DIGIT UNITS ALSO AVAILABLE**
FROM \$150.00 PLUS TAX

 **DATA PRECISION**
...years ahead

Variable Delay Wiper

The next step is to complete the wiring to the electronics. First check to see if the wiring has a positive or a negative earth. If the car has a positive earth, connect the positive supply lead to some convenient earth point. It is a good idea to check with an ohmmeter that the point chosen is in fact connected to the main metalwork of the car, particularly in cars using plastic materials for the internal fittings.

If the car has a negative earth system, connect the negative supply wire to an earth point. The remaining supply wire (negative for a positive earth car, positive for a negative earth car), must be connected via the ignition switch. If your car has an accessories position, then connect this wire so that the unit will operate in this position.

Perhaps the most convenient place to connect the wire is near the fuses. Take care to connect the wire so that the unit is protected by the fuse. Connect a voltmeter between the proposed take off point and chassis, being careful to observe polarities. When the fuse is removed, the voltage should fall to zero.

It will now be possible to check the operation of the electronics. Switch on the motor, and press the timer power switch. It should be possible to hear the operation of the relay, as the various buttons are pressed. When the single button is pressed, the relay should operate for as long as the button is pressed, and for a short time after it is released.



The trimpots can now be adjusted. The 10k one nearest the 220uF electro is set to give the relay an on time of about half a second, and the remaining ones so that suitable delays are obtained.

The next step is to connect the wipers into the circuit. First ascertain what type of wipers are fitted. Table 1 is a list of the more common types. Fig. 4 gives the coding scheme we have used for the relay contacts.

We will consider system No.1 first. This type is usually fitted to early model English cars, and uses a wound field type motor with self parking facilities. There are two wires connected to the wiper switch, which is a single pole type. Connect the normally open relay contacts (2 & 3) in parallel with the wiper switch.

System No. 1a is very similar, but does not have self parking facilities. Our wiper control can be used with these wipers. Connect the normally open relay contacts (2 and 3) in parallel with the wiper switch, and adjust the on time of the relay so that the wipers give only one wipe. It will be found that this cannot be done exactly, due to the loading effects of the windscreen on the motor, but satisfactory operation can be obtained.

System No. 2 has a wound field type

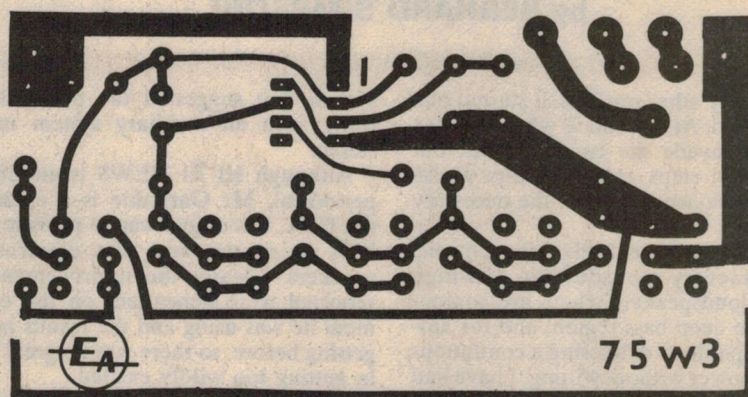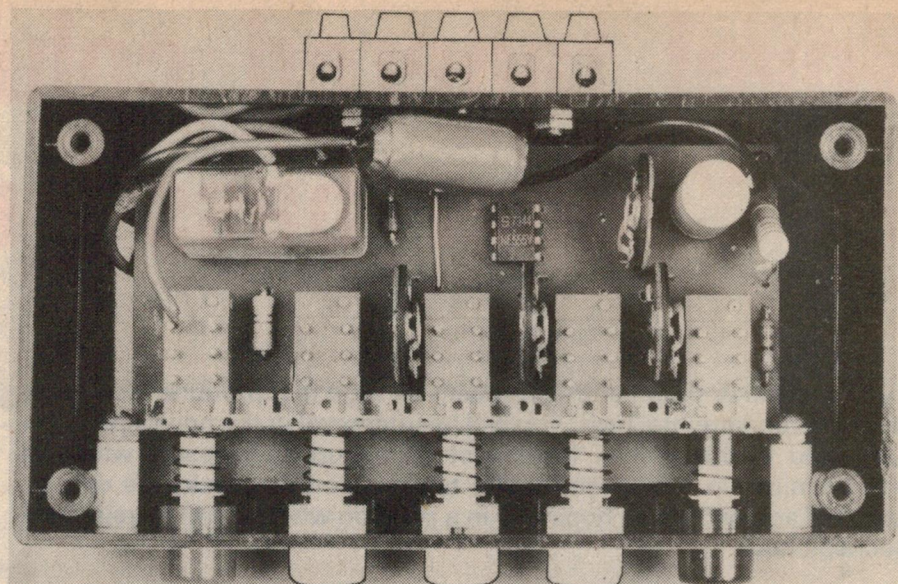

An interior view of the completed prototype is shown at top. Directly above is the printed circuit board pattern, shown actual size to facilitate tracing.

motor, with two speeds. There are three wires to the wiper switch. Turn the wipers on, and find and mark the wire which stops both fast and slow speeds, and the one which affects only the slow speed. Connect the normally open relay contacts (2 and 3) in parallel with the two marked ones.

System No. 3 uses a permanent magnet motor fitted with dynamic braking. There are three wires connected to the wiper switch. Identify the ground wire, i.e., the one connected to the car chassis, and mark it "A". Turn on the wipers, and find one of the two remaining wires which does not affect the operation of the wipers. The correct wire is the one which prevents the self parking facility from working. Without this wire connected, the wipers should not self park. Mark this wire "B".

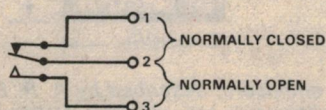


FIG. 4 RELAY CONTACTS SHOWN IN UNENERGISED POSITION

Fig. 4: the coding scheme used for the relay contacts (see text for connections).

Cut wire "B", and connect relay contacts 1 and 2 across the break, with contact 2 nearest to the switch. Contact 3 is then connected onto the earth wire "A".

The last system to be considered is No. 4. This uses a permanent magnet motor with dynamic braking, but has two speeds. The procedure is very similar to that used for No. 3. Identify the earth wire, and mark it "A". Turn on the wipers in the slow speed position, and find one of the three remaining wires which does not stop the wipers, but does stop the self parking when disconnected. Mark this wire "B".

Cut wire "B", and connect relay contacts 1 and 2 across the break, with contact 2 nearest to the switch. Contact 3 is then connected onto the earth wire "A".

Having completed installation, the unit can be given a final checkout, and if necessary the trimpots readjusted. Turn on other electrical devices fitted to the car, such as the headlights and turn indicating systems, and check to see if the timer is being triggered by the resultant pulses. If so, it may be necessary to fit a 1000uF electrolytic capacitor across the supply lines.

Novel tapered column for "super bass" response

If you're a hifi or organ enthusiast with an urge to reproduce the lowest octave of fundamental bass, you will be interested in the novel approach suggested in this article. Instead of taking up floor space, which is at a premium in most homes, the tapered column enclosure can be mounted against a wall, hopefully in a position where it will be relatively inconspicuous.

by **BERNARD SIMPSON***

Like many other projects, it started one wet weekend. At least that's when the idea started to invade the consciousness, but the practical steps awaited many weeks and a chance acquisition of the necessary components.

I have always been fond of organ music, the satisfactory reproduction of which calls for loudspeakers which are competent in the deep bass region, and for amplifiers capable of delivering a continuous block of power without wilting. I have had good results with my systems over the years, in stereo and more lately in the various kinds of four-channel that have come along. Even musicians who are organists have commented favourably, and that's good enough for me.

I do have the advantage of a room of reasonable size, where the dimensions are not inhibitive of deep bass reproduction. I did calculate the eigen tones some years ago, and whilst I do not remember all the figures, I do remember the lowest one was down towards 20Hz. This, together with loudspeakers of very good quality, has produced very satisfactory results.


But human beings are always striving for better things, even if instinct suggests there may not be much more to achieve. Besides, any of us, however hardened by years of experiment, can still get fired up reading about the adventures of others. And that is what happened to me.

I was turning over some old photocopies made on the basis of "I might want to refer to that one day", when I came across an item "The Super Woofer", by Nate Garfinkle, HI FI NEWS, July 1969. The article discussed briefly an exercise in which the deep bass was lifted by using a suitable loudspeaker and enclosure, whilst limiting the frequency range of the auxiliary system by the use of a low pass filter with a cut off at about 70Hz. The author used a combined channel system with one loudspeaker for the auxiliary

system, but suggested the possibility of using such an auxiliary system in full stereo.

Although HI FI NEWS is an English periodical, Mr Garfinkle is a citizen of the USA. His object was to provide deep bass to accompany two electrostatic speakers. Clearly the improvements he reported were dependent on the equipment he was using and the results he was getting before, so there was no great point in getting too wildly excited.

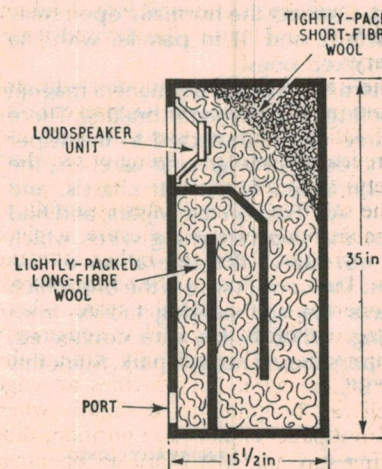Some points were noted: An electronic low-level low-pass filter was used to avoid large inductors. The loudspeaker/enclosure combination used must be inherently capable of real bass performance. The author mentioned he would have liked to have used a KEF B 139 in an arrangement similar to that described by



This enclosure, described by A. R. Bailey in "Wireless World" (Oct 1965) has been the subject of much argument but it has one thing in its favour: it works! It was the starting point for the vertical column described here.

Dr. A. R. Bailey in "A Non-Resonant Loudspeaker Enclosure Design", WIRELESS WORLD, October 1965, but the B 139 (at that time) was not available to him in the USA. It goes without saying that a quick scabble around produced the WIRELESS WORLD article, and also a very interesting letter on the subject from E. A. Harman, published in the December 1965 issue.

The combination of the Bailey enclosure and the B 139 was clearly the kind of design required if the auxiliary bass channel was to be tried. Furthermore, there was the interesting possibility for the experimenter in varying the density of the medium inside the enclosure. However, remembering that many homes are shared by wives, the Bailey enclosures are not tiny. A saving thought was that if the enclosure were only for auxiliary bass, location in the room would not be determined by the usual speaker placement considerations.

At this stage, as so often happens, the idea passed off centre-stage into the subconscious. It received a shock revival one Saturday when, scanning the hifi ads in the morning paper, I saw someone offering a pair of B 139's "new in cartoons" at a very attractive price. A quick use of my horseless carriage led to the translation of these two goodies into my possession. And having bought them, obviously I had to use them. But how?

No one is going to be interested in all the thought processes, so suffice it to say that a solution was found. There is a corner space in my listening room between a door and a wall, where nobody ever goes. Something placed there would be virtually invisible. At this stage I had a space which did not fit two of Dr. Bailey's enclosures.

But these enclosures are folded—how about unfolding them? A scaled-up sketch of the enclosure was made so that such things as mean path length through the enclosure could be checked. A few simple calculations confirmed the major dimensions and ironed out errors arising from scaling up a very small drawing. A straight, tapered tube was then drawn up embracing the important dimensions. After some fiddling with sizes to provide a cross-sectional area tube to accept the B 139, a double side-by-side tapered tube was drawn up, which could just be accommodated in the space available.

There are a couple of points about this

Ever an enthusiast, the Author built up a twin column with two loudspeakers, one for each stereo channel. For the ordinary domestic scene, a single channel would be adequate, fed with signals taken from both channels. The enclosure needs to be very solidly constructed but the method of assembly can be varied to suit facilities. Dimensions are not highly critical and other high performance woofers could be utilised.

*6 Eden Avenue, Turramurra 2074. Bernard Simpson was formerly editor of "Radiotronics" and is a well known writer on hifi topics.

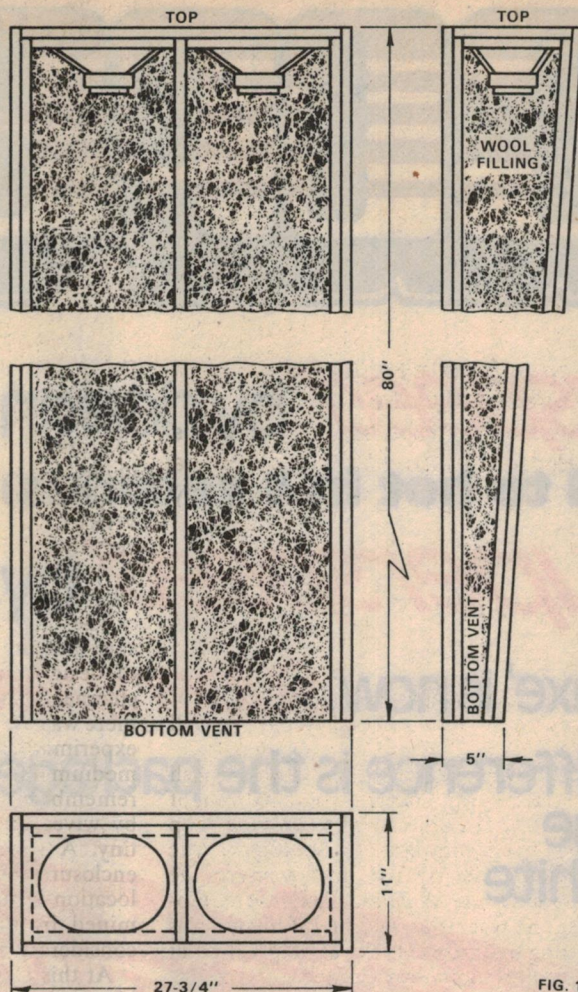


FIG. 1

double enclosure. One is that the simple construction brings the speakers into a position where the axis through the coil is vertical. The literature has some criticism of this orientation of speakers, claiming that the cone will sag. Maybe it will, but it is good enough for experiment—modification to turn the speakers onto a horizontal axis could come later.

The second point is that the "port" ends of the tubes are adjacent. This has been claimed by some to have a mutual augmentation effect. I have no strong feelings on this, as the two speakers are usually not reproducing exactly the same material, and theories could be down the drain.

The double enclosure finally constructed is sketched in Fig. 1. Construction is of 3/4" chip board and 1" x 1" D.A.R. soft wood. Obviously the detail could be varied to suit circumstances. The tubes must be airtight at the seams. This calls for accurate cutting and fitting of the two sides and the centre divider in particular. Various sealing substances are available and have received mention in articles on building enclosures. Working and fitting to fairly close tolerances, one of my favourites for many years has been a liberal application of BOSTIK shortly before assembly. The assembly method used was gluing and screwing.

My enclosure was constructed so that

the sloping panel covering the two tubes, which was to be the front of the unit, was placed into position and screwed down last, after the wool was packed in. The entire enclosure was affixed to a wall with the openings clear of the floor. It is not easy to make such a tall unit free-standing, but a way could surely be devised if necessary.

The opening at the bottom of the enclosure needs provision to prevent the wool filling from coming out, and also to prevent bugs (of the flying or crawling variety) from getting in.

The solution is easy. After assembly of the main body of the enclosure, a piece of fly wire, of the metal rather than the plastic kind, is affixed to the bottom across the openings. Towards the front, where it is to meet the front panel, the edge may be turned up. This not only stiffens the edge of the wire, but provides an edge which can be compressed slightly when the front panel is placed in position, thus making sure that there are no openings left past the wire.


I use a kg. of raw, long-fibred wool (fibres about 10cm. long) for each tube, a total of 2 kg for the project. This amount is within the range suggested by Dr. Bailey and confirmed by Mr. Harman.

Supplies of suitable wool are much more readily available in Australia than

QUAD

50 E

PROFESSIONAL power amplifier

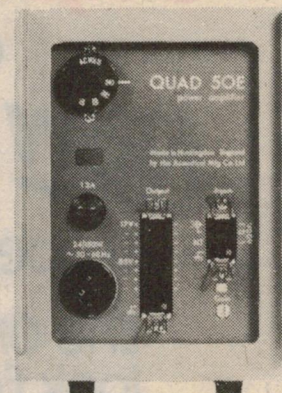

A single channel mono amplifier designed for Broadcast, Recording and other applications in the Audio Industry.

The multiple output windings of the Quad 50 terminate in a multiple output socket on the amplifier. Choice of matching is obtained by various connections in the output plug which is part of the installation itself. Quad 50 amplifiers may, therefore, be moved from one application to another without adjustment. With the exception of output impedance, the performance of the amplifier is identical with any output configuration.

The standard of quality is of the highest order and with any complex input, distortion falling within the useful part of the audio range will not exceed a small fraction of one percent. Overloading with any load will not significantly affect long time constants, ensuring immediate recovery and minimum distortion resulting from such overload.

Brief specification:—

POWER RESPONSE:

—1 dB at 30 Hz and 20 kHz ref to maximum output

DISTORTION:

40 Hz < 0.35% } any level
1 kHz < 0.1% } up to
10 kHz < 1.0% } maximum output

OUTPUT SOURCE IMPEDANCE:

0.5 Ω in series with 25 μH for 5.5 Ω connection.

Others in direct proportion.

HUM & NOISE:

Better than 80 dB referred to full output.

FREQUENCY RESPONSE:

Unbalanced input:

—1 dB 30 Hz and 20 kHz ref: 1 kHz.

600 Ω bridging:

—2 dB 30 Hz and 20 kHz ref: 1 kHz.

INPUT LEVEL:

0.5 V for full output, balanced or unbalanced

Preset adjustment for higher levels.

INPUT IMPEDANCE:

Unbalanced:

14—50 K Ω depending on preset gain.

600 Ω bridging:

< 14 K Ω in parallel with 50 H.

STABILITY:

Unconditionally stable with any load.

Price and full particulars obtainable from the Australian Agent:

British Merchandising Pty. Ltd.,
49-51 York Street, Sydney.
Telephone: 29-1571.



Superspeed by design
(cold to hot in 5 seconds)


Now *Superspeed* by name

'Scope Deluxe' is now *Superspeed*
the only difference is the package
look for the
Red and White
carton



'Miniscope' is now
Mini Superspeed

look for the
Black and White
carton

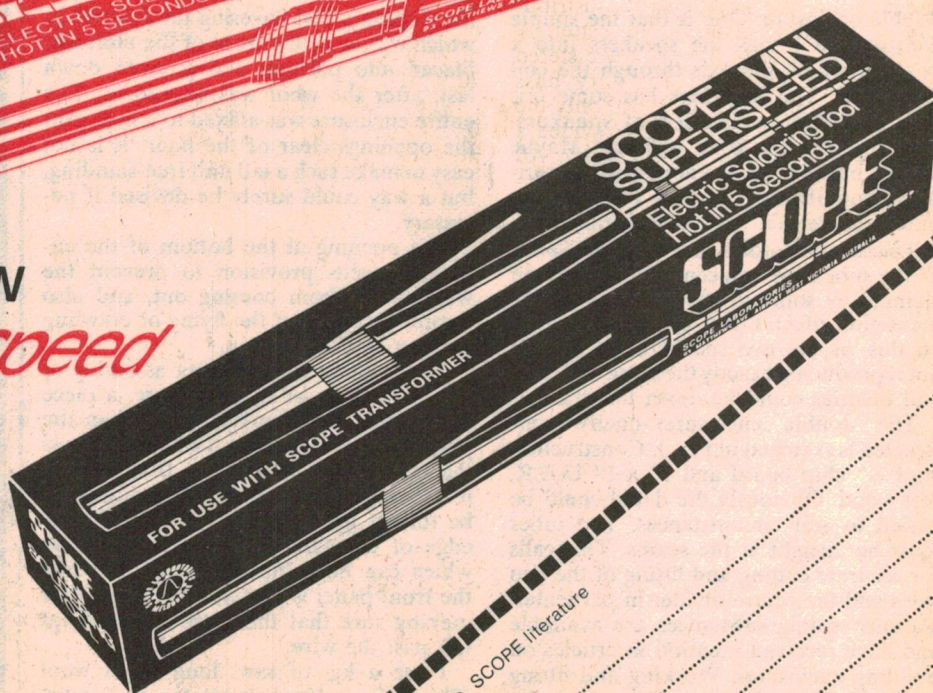

IRH COMPONENTS DIVISION
NATRONICS PTY. LIMITED

The Crescent, Kingsgrove, N.S.W. 2208

Please Post free SCOPE literature

NAME

ADDRESS

CITY

POSTCODE



"SUPER BASS" RESPONSE

Dr. Bailey found in England. I got mine from a specialist spinning/weaving supplies shop. The biggest task apart from the basic carpentry was preparing the wool. There was some vegetable matter to be removed, and a few soiled areas to be cut off. The whole of the wool was then pulled and teased out into an enormous fluffy, homogeneous mass, and fin-

completeness, my version is shown in Fig. 2, two filters being needed for two channels. I tapped off two channels from my "front" amplifier after the tone controls, through the two low-pass filters and into the auxiliary input of the spare amplifier, with preset level adjusting controls.

By setting the auxiliary bass amplifier tone controls top "flat", the whole "front" area of the sound was then controlled by the tone controls on the "front" amplifier. Incidentally, the filter draws only a few milliamps, so that it can be energised from

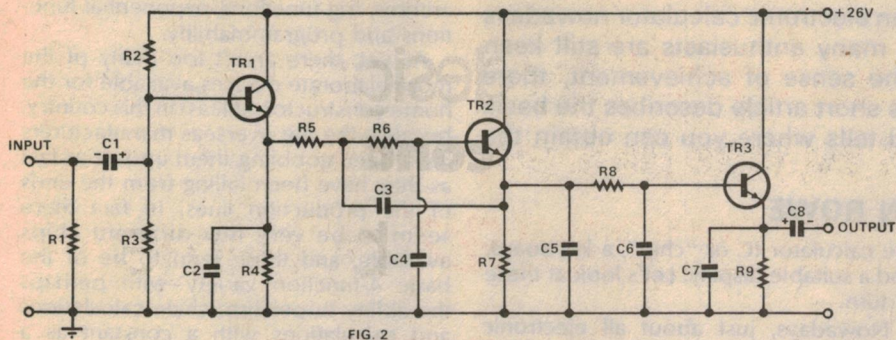


FIG. 2

Fig. 2: Low-pass preamplifier used to segregate low frequency signals. If common to stereo channels, isolating resistors would be necessary.

ally packed into the tubes.

In working with this wool it became clear why Dr. Bailey used wool in preference to other materials. The springy-ness of the fluffy mass is astonishing, whilst its homogeneity when treated in this way is superior to that of other possible materials I know. It is worth recalling, as pointed out in Mr. Harman's letter, that the function of the filling material is effectively to increase the density of the sound-transmitting medium in the tube, and therefore the more even the distribution of the filling material, the better.

I was fortunate to have a spare stereo amplifier to drive the auxiliary bass speakers, so that there remained only the low-pass filter. Mr. Garfinkle provided a design which was quite satisfactory. All I had to do was to copy it using locally-available components. For the sake of

virtually any convenient source.

Listening results? Well they can be dreadful with any augmentation system unless it is used intelligently. There is an initial temptation to wind up the auxiliary bass too far, particularly if the other speakers in the system have not been doing so well in the deep bass region. Careful adjustment produces a subtle but satisfying result, at times a matter of feel rather than hearing.

The improvement depends on what one started off with, and is obviously available only on program material containing significant amounts of information below 70Hz.

Those who want more deep bass but find a couple of B 139's inhibiting may prefer to go along with Mr. Garfinkle and use one of everything driven by combined channel information. This single channel signal is easily derived from the two "front" stereo signals using a simple resistive network.

There are obviously several variants available on the electronics side, dependent for example on what amplifiers are available.

A word may be appropriate regarding the wool filling. I was not at first certain about the use of raw wool on a long-term basis, although it is no problem for experimenting. Scoured wool in the condition it must reach immediately prior to spinning would presumably be satisfactory, but I have not been able to locate a supply of the size required. In any case it would then be necessary to pack in a greater weight of scoured wool to produce the same effective density inside the tubes. However, enquiries have suggested that there is no long-term problem with the raw wool when the loose dirt and vegetable matter has been removed as described.

PARTS LIST FOR L.P. FILTER

(For one channel, duplicate for full stereo)

CAPACITORS

C1, C8	10uF elec., 25 VW
C2, C5, C7	0.001uF poly.
C3	0.27uF poly.
C4	0.068uF poly.
C6	0.15uF poly.

RESISTORS

(All ½W, 10%)

R1	470K
R2	68K
R3	82K
R4	5.6K
R5, R6, R8	15K
R7, R9	10K

SEMICONDUCTORS

TR1, TR2, TR3 BC184L or equiv.

New Release!..

'FERROGRAPH' SUPER SEVEN



The latest Ferrograph Super Seven Tape recorders maintain the famous Ferrograph standards of outstanding audio quality and mechanical durability.

The most obvious improvement of the Super Seven is the 10½" spool capacity. In addition new spooling motors, electrical tape tensioning, and extensive redesigning make the Super Seven the obvious choice for those who are serious about recording.

The following variations are available:—

- *With or without output amplifiers
- *With or without "Dolby B"
- *1½, 3½, 7½ ips OR 3½, 7½, 15 ips
- *Half track stereo OR quarter track stereo

For full details please return the coupon below to:—

LEROYA INDUSTRIES PTY LTD
 266 Hay Street,
 SUBIACO
 Western Australia 6008

Please send me full details of the
 Ferrograph Super Seven Series Tape
 Recorders.

NAME

ADDRESS

Postcode

LER 081

Building your own digital calculator—a guide

Although the cheapest way of getting an electronic calculator nowadays is to buy one completely assembled, many enthusiasts are still keen to build up their own. Apart from the sense of achievement, there is of course the educational value. This short article describes the basic operation of a modern calculator, and tells where you can obtain the parts needed to build one up.

by JAMIESON ROWE

Let's be realistic—if you want a cheap electronic calculator, building one yourself is not the way to get one. Nowadays, you can buy quite a nifty little 4-function pocket model for less than \$20, from most department and bargain stores. So there's no money incentive in building one yourself, just the reverse in fact.

There isn't a great deal of educational value in building up a modern calculator, either. Virtually the only practical approach is to use one of the modern LSI (large-scale integration) calculator circuits, which typically comprises one large IC (integrated circuit) together with a few minor components, a keyboard and a display. All the real operation takes place inside the "black box" IC, so that you don't really learn very much from connecting it up.

But despite these sobering realities, there are undoubtedly quite a few people who do still want to build one, judging by the number of letters we get from readers asking for information on circuits and parts availability. We can only assume that it is for the sense of achievement—who said the amateur spirit had died?

If you're one of the hardy souls who do indeed want to build their own calculator, then, this article has been written for you. We hope it will help answer your questions, and give you all the basic information you need.

The basic items you'll need for either a pocket calculator or a desk type are

the calculator IC or "chip", a keyboard, and a suitable display. Let's look at these in turn.

Nowadays, just about all electronic calculators are based on the "one-chip" concept, with a single LSI device performing all of the basic calculator functions. The device is usually in a large DIL (dual-in-line) package, with anything from 24 to 40 pins, and represents the most expensive single item required—typically it will cost around \$20-30.


Almost every semiconductor manufacturer has produced one or more such calculator chips, while those who have specialised in the field have produced an almost dazzling array of devices ranging all the way from simple 4-function chips to quite elaborate and costly items offering multiple memory registers, log-

arithms, trig functions, exponential functions and programmability.

As yet, there aren't too many of the more elaborate devices available for the home constructor, at least in this country, because the big overseas manufacturers have been gobbling them up just as fast as they have been falling from the ends of the production lines. In fact there seem to be very few different chips available, and these tend to be of the basic 4-function variety—with perhaps the ability to perform chain calculations and calculations with a constant as a bonus.

One chip which does appear to be in good supply is the C-550, made by General Instrument Microelectronics. This is available from the local GIM agent, General Electronic Services, whose address is 99 Alexander Street, Crows Nest, NSW 2065. It costs \$20 plus tax (15%).

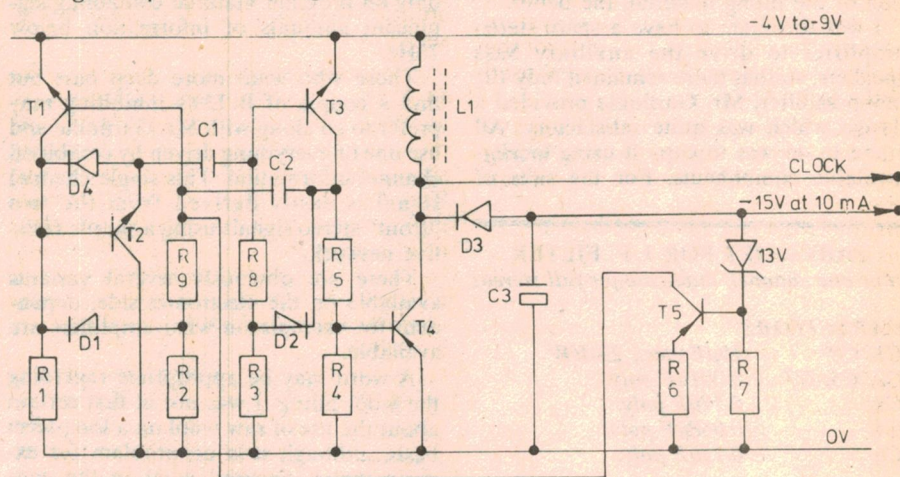The C-550 is a MOS device in a 24-pin ceramic DIL package. It is designed to perform the four normal arithmetic functions, with additional features such as chaining, constant storage, integral powers, and floating point on entry and result. It is designed to work into an 8-digit display unit, although the internal



- R1. 3K9
- R2. 68K
- R3. 22K
- R4. 1K
- R5. 1K5
- R6. 2K2
- R7. 6K8
- R8. 2K 2

- R9. 2K 2
- C1. 570PF
- C2. 470PF
- C3. 1MFD
- L1. 35T ON MULLARD FX 2249 > 2 mH
- TRANSISTORS
- NPN. 2N3904/BC108
- PNP. 2N3904/BCY 71

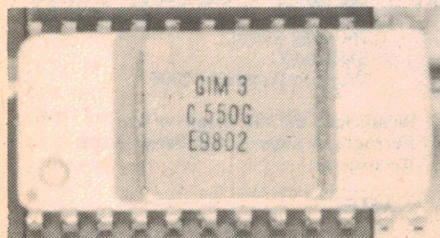


Fig. 1 (right): The power supply and clock generator circuitry required for the GIM C-550 calculator chip. All the parts are listed. Above is a view of the chip itself, about twice size.

* FOR USE WITH C550 ALL
RESISTORS SHOULD BE 220K OHM.

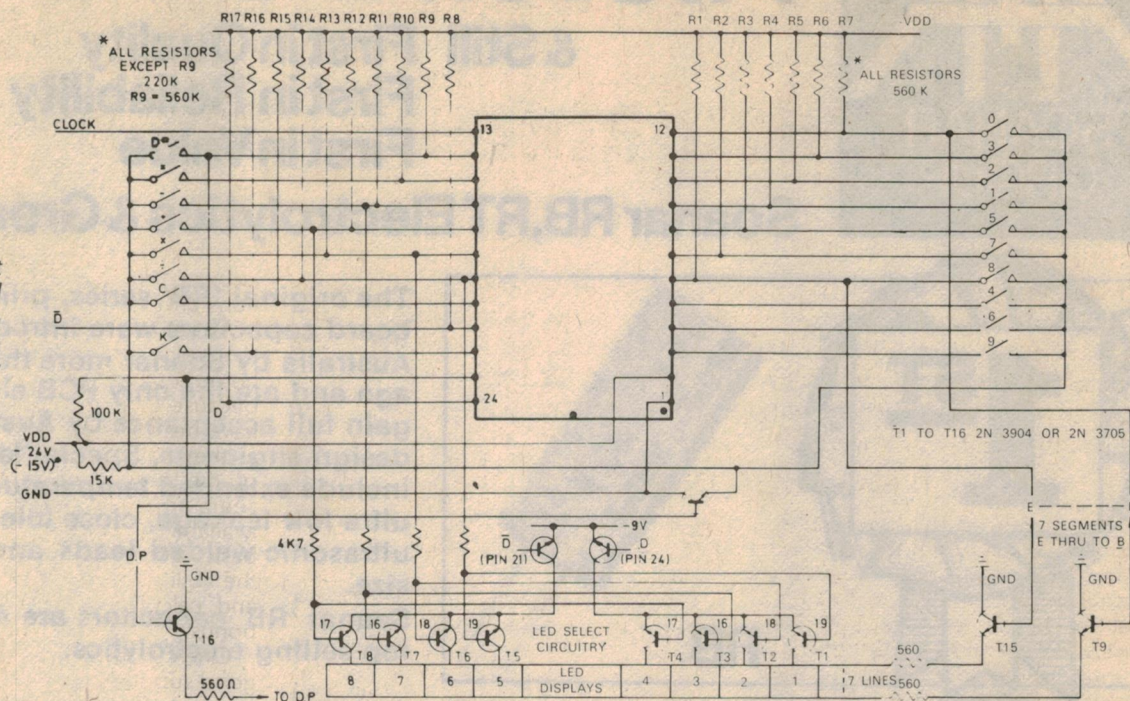


Fig. 2: The circuit for the keyboard and display wiring used with the C-550 calculator chip.

arithmetic is able to handle numbers varying in magnitude between 10^{-20} and 9.999999×10^{79} . The chip performs automatic overflow and underflow, so that any result within this range can be retrieved by multiplying or dividing by multiples of 10.

The chip is provided with integral protection against contact bounce in the input keyboard. It is capable of interfacing with a wide variety of displays, having an input/output multiplexing system whereby the multiplexed outputs for the display use the same device pins used by the input keyboard.

The C550 chip actually runs from 15V DC, drawing about 10mA. This is not directly compatible with the normal batteries used in portable or desk calculators, but the manufacturer suggests that this can be overcome by using a simple converter circuit. As the chip also needs an external 70kHz clock oscillator, the recommended scheme is to use a combined clock oscillator and converter, as shown in the circuit in Fig. 1.

As you can see, the circuit uses three NPN transistors (BC108 or similar), and two PNPs such as the BCY71 or similar. It uses a small inductor (L1) wound on a Philips FX 2249 ferrite core to develop the 15V clock pulses, which are rectified and regulated to provide the supply voltage to the C-550 chip. The circuit is designed to operate from a battery voltage of between 4 and 9V, with positive grounded.

The rest of the circuitry required to get the C550 going is shown in Fig. 2. Apart from the C550 chip itself, the display and the keyboard switches, the only other

components are 19 general-purpose NPN transistors (BC108 or similar) and 31 resistors. The transistors are used mainly as display drivers, with T1-T8 as digit drivers, T9-T15 as segment drivers, T16 as the decimal point driver and a further two for digit driver decoding. The final device is used for input-output strobing. Resistors R1-R17 are used as pullup loads for the multiplexed input-output lines, while the remaining resistors are used mainly as current limiters in the segment lines and digit driver base lines.

The input keys connect to pins 3-12, 14-20 and 22. Of these, pins 6-12 inclusive are also used for the seven segment multiplex outputs, and pins 16-19 inclusive for the four main digit output lines. Pins 21 and 24 are used for the digit group decoding outputs, while pin 23 is used for the input-output strobe gating output. This last signal gates the transistor which controls the keyboard switch common line, so that the key switches are disabled when the common multiplex pins are performing their output function.

To go with the C550 chip you will need a keyboard assembly with a compatible set of switches and inscriptions. As it happens, such a keyboard is also available from General Electronic Services, the type 19SK-6 made by the Flex-Key Corporation. The cost is currently \$18 plus tax (15%).

The 19SK-6 is a solidly made keyboard, featuring double-shot moulded keys. It has 18 keys, together with an on-off switch, and measures 71 x 91 x 15 mm overall. The contacts employed are of the conductive elastomer type, and are


completely sealed against dust and liquids. The switch connections are specifically made to suit the C-550 chip, so that the two are directly compatible.

The third essential item required for a calculator is the display, as mentioned earlier. Here you have a little more flexibility, with at least two approaches. If you want to spend the least money, the most attractive type of display will be the type expressly designed for calculator use, having all of the digits integrated into a single package. This also gives the most compact arrangement, and hence the most promising if you want your calculator to be of the "pocket" variety.

This type of display also tends to be fairly modest in terms of current drain, which is important if your calculator is to be run from batteries. On the other hand the digits are usually rather small, and not perhaps the most suitable for a desk-type calculator. Here you may prefer an alternative approach, using eight single-digit LED readouts.

For the first approach, a suitable integrated 8-digit display is available from Hewlett-Packard. This is the type 5082-7448, which features high efficiency GaAsP LEDs giving good readability at current levels as low as 250uA average per segment. The digits are 2.67 mm (0.105 inches) high, but have a built-in plastic magnifying lens system to make them appear larger.

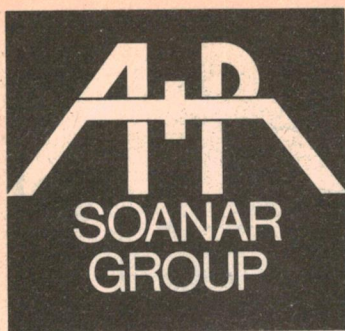
Current price of the 5082-7448 is \$14.04 plus tax, and they should be available through any of the H-P distributors, or o.i order from them via your usual parts supplier. At this price, the H-P device probably represents the cheapest display



First on the Market

**& Still First in Quality
First in Reliability
First in Value**


Soanar RB, RT Electrolytics & Greencaps

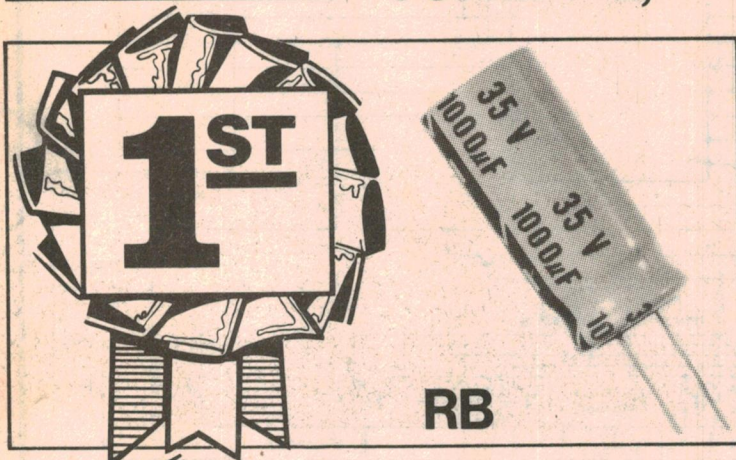

RB

The original 'RB' series, printed circuit board capacitors were introduced into Australia by Soanar more than 10 years ago and are the only PCB electrolytic to gain full acceptance by Australia's design engineers. Special features include extended temperature range, ultra low leakage, close tolerance limits, ultrasonic welded leads and very small size.

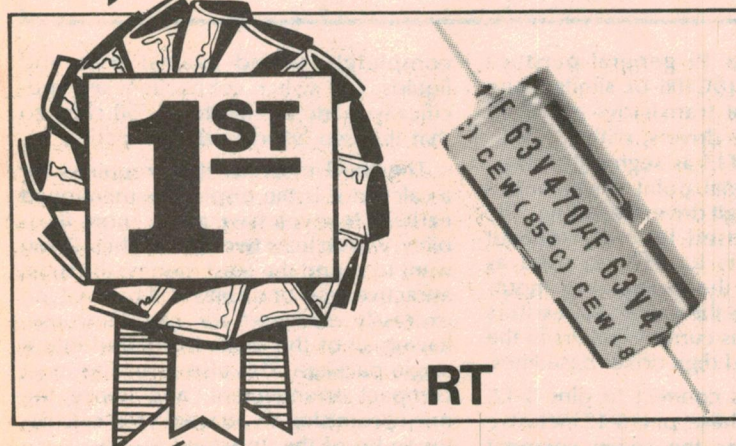
Soanar 'RB' capacitors are Australia's top selling electrolytics.



RT

Soanar 'RT' series, axial lead electrolytic capacitors have been accepted as the Industry Standard for high reliability and long operational life. They are used by practically every Australian manufacturer and government department.

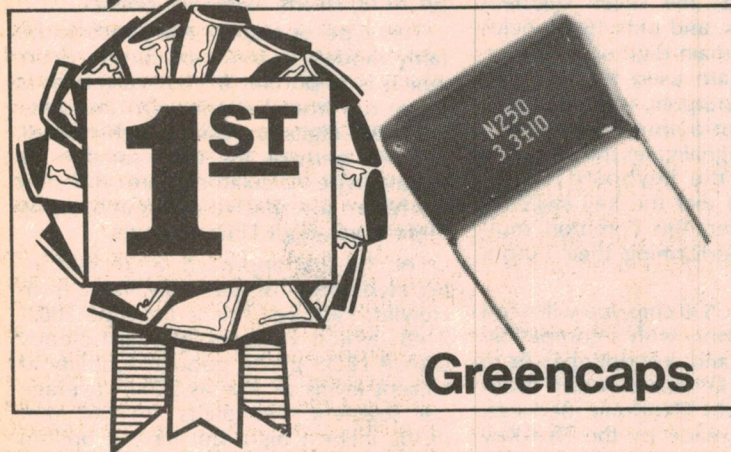The working characteristics of RT electrolytics closely approach those of the publicised and more expensive 'long life' types, yet cost only a fraction of their price.



Greencaps

These high quality sub-miniature polyester-film capacitors are ideally suited to transistor circuitry and a wide range of high voltage applications. They are also an ideal low-cost replacement for the older types of Polyester/Ceramic capacitors in the 25V to 630V range. Soanar GREENCAPS are highly stable over the -40°C to +85°C temperature range. They are Australia's largest selling polyester film capacitors and represent outstanding value for performance, reliability and appearance.

Technical literature available on request.


SOANAR ELECTRONICS PTY. LTD.
A MEMBER OF THE A & R-SOANAR ELECTRONICS GROUP



SALES OFFICES PHONES:
VICTORIA: 89 0238 89 1086
N.S.W.: 78 0281
S. AUST.: 51 6981
QUEENSLAND: 51 5421
W. AUST.: 81 5500
SOANAR (JAPAN) LTD. TOKYO

30-32 Lexton Road, Box Hill, Vic., 3128, Australia.

Telex: 32286.

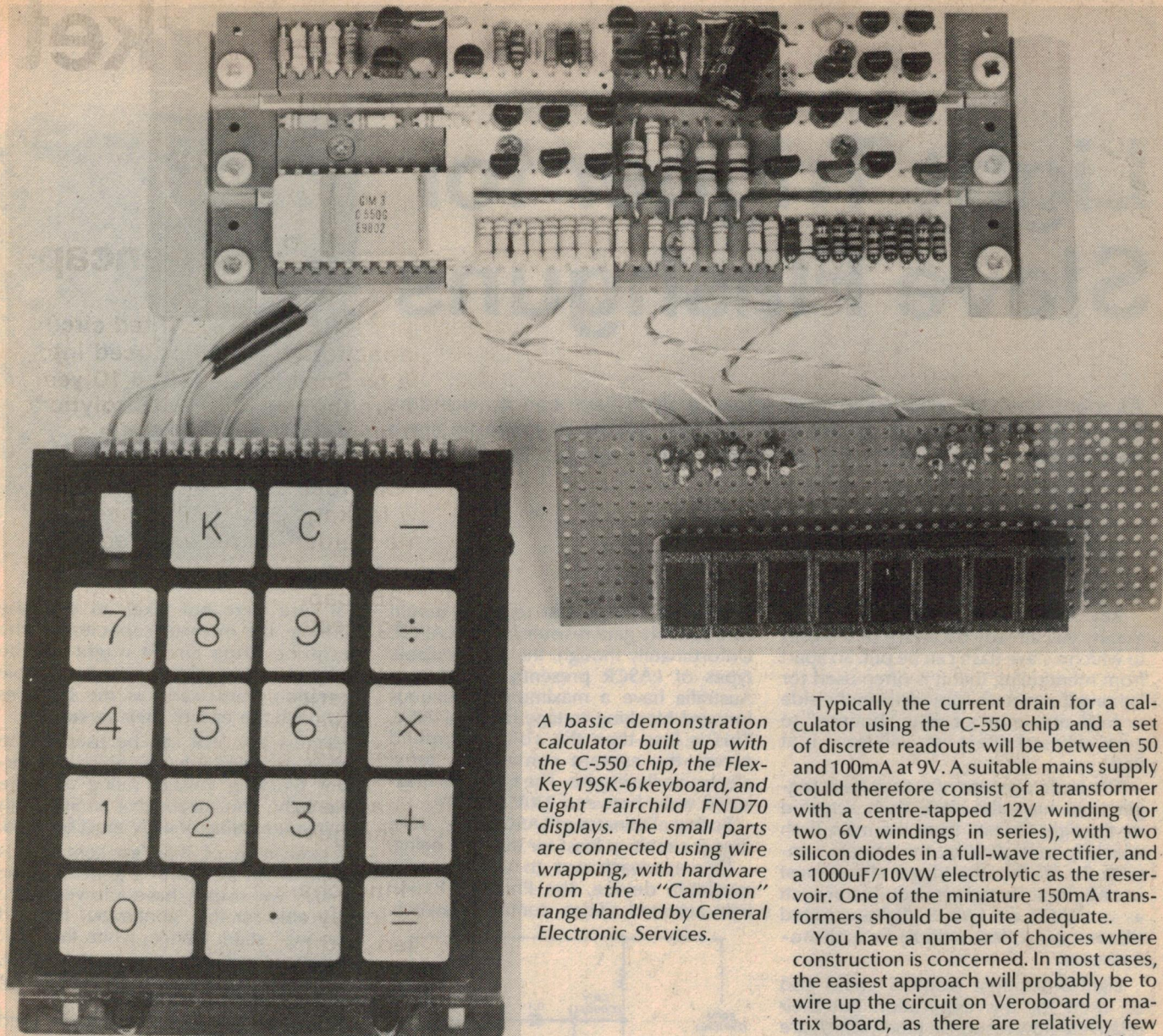

A basic demonstration calculator built up with the C-550 chip, the Flex-Key 19SK-6 keyboard, and eight Fairchild FND70 displays. The small parts are connected using wire wrapping, with hardware from the "Cambion" range handled by General Electronic Services.

for your calculator, by far—working out to about \$2 per digit.

Litronix apparently have a similar device, the DL-95, which is available from Cema Distributors Pty Ltd, of 21 Chandos St, Crows Nest, NSW 2065.

If you opt for the individual readouts, there are quite a wide range of devices available. If you want big digits—0.6in—then you could use the Litronix type DL750. These are also available from Cema Distributors.

Hewlett-Packard also make a family of high-efficiency readouts with digits 0.43in high, and with a choice of either yellow or green emission as well as the usual LED-red (although their red is not quite the same as others, having been modified for greater readability). The red device is designated type 5082-7653, the yellow type 5082-7663 and the green type 5082-7673. The green device is not quite as efficient as the other two, but all three would probably be equally suitable for use in a mains-powered desk calculator.

These devices should be available on order from H-P distributors shortly, having been released in the US only a few months ago. The anticipated price at the time of writing is \$4.56 each plus tax.

Another suitable readout device would be the Fairchild FND-70, as used in some of our digital instrument projects. This should be available ex stock from most parts suppliers, at a price of around \$4.50 including tax.

The remaining aspects of building a calculator are largely a matter of personal choice, such as power supply, the type of construction used, and a suitable case.

The power supply will depend at least partly on whether you want a pocket calculator or a desk type. If you want the former, a battery supply is virtually unavoidable, whereas with a desk type you can use whichever you prefer. Don't forget, though, that the larger readout units tend to need a fairly high current, so that battery operation may not be very practical.

Typically the current drain for a calculator using the C-550 chip and a set of discrete readouts will be between 50 and 100mA at 9V. A suitable mains supply could therefore consist of a transformer with a centre-tapped 12V winding (or two 6V windings in series), with two silicon diodes in a full-wave rectifier, and a 1000uF/10VW electrolytic as the reservoir. One of the miniature 150mA transformers should be quite adequate.

You have a number of choices where construction is concerned. In most cases, the easiest approach will probably be to wire up the circuit on Veroboard or matrix board, as there are relatively few parts involved. However you could try your hand at designing a suitable PC board pattern, and making up a board using one of the do-it-yourself etching kits. Yet another alternative is to use wire-wrapping, as shown in the photograph; General Electronic Services can supply the hardware you need for this, along with a simple manual wire-wrapping tool.

As for a case, you're going to be on your own. There don't seem to be any suitable cases available, although one of the metalwork manufacturers such as Wardrobe and Carroll Fabrications may be prepared to produce one if there is sufficient interest. Alternatively you could probably make up a simple case yourself, from a material such as Marvplate, or from wood covered with leatherette. ☺


Footnote: This article is intended only as a guide for those experienced readers intending to build a calculator, and is not a constructional project. No further information will be available via the information service.

Ideal for amateur or professional . . .

Light Trigger for Slave Flashguns

As many keen photographers will attest, a slave flash can do wonders for picture composition. So here we present details of a simple slave flash trigger circuit which can be made into a compact module.

by LEO SIMPSON

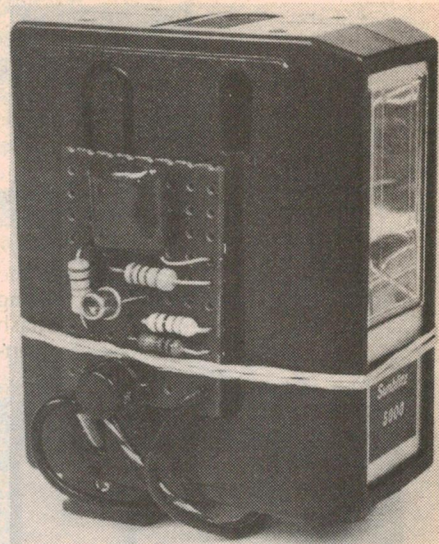

Any reader who is keen on photography will already be aware of the uses to which a slave flash can be put. So apart from mentioning that it is often used for lighting the picture subject from the side or from above by a ceiling "bounce" to get a diffused effect, we will leave it at that.

The basic concept of a slave flash trigger is to have the slave flash actuated by the light "burst" from the main flash which is controlled by the camera contacts. To do this, the trigger circuit must use a light-activated semiconductor such as a LASCR or LASCS (light-activated silicon controlled switch) or a photo-transistor.

Light-dependent resistors could also be used for this application but their relatively slow response times, which are generally of the order of a few milliseconds or so, may prove to be a disadvantage when rapid shutter speeds are required.

To understand the function of the slave trigger flash unit, which really substitutes for the camera contacts, one must be familiar with the circuit of a typical electronic flashgun. While these vary greatly in detail, they all use a transistor converter which changes the 3 to 12V battery voltage up to between 350 and 500V DC.

A typical electronic flash firing circuit is shown in Fig. 1.

A pulse transformer is used to fire the flash tube and this is energised in much the same way as the coil in an automotive capacitor-discharge ignition system. In the flash-gun though, the trigger capacitor is typically about 0.1 μ F. It is charged via the high-resistance voltage divider and then discharged by the camera contacts via the primary of the pulse transformer.

Perhaps the simplest slave flash trigger circuit could merely use a light-actuated SCR in place of the camera contacts. The

only other component required would be a suitable gate resistor for the LASCR. Unfortunately though, the few available types of LASCR presently available in Australia have a maximum continuous forward-blocking voltage rating of 200V. This is less than the voltage applied across the camera contacts by most electronic flash-guns. The types we measured were between 230V to 270V.

So that eliminates a "LASCR only" slave trigger circuit, at least for the time being.

Our approach was to use a readily available device, the Philips BPX66P light-actuated silicon controlled-switch.

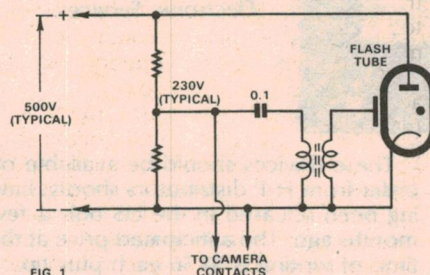


FIG. 1
A typical electronic flash firing circuit. Some use an SCR to discharge the capacitor, but the basic arrangement is the same.

Since this has an anode-cathode voltage rating of only 70V, it suffers from the same limitation as the LASCRs mentioned above—it cannot be used directly in place of camera flash contacts.

Instead, the BPX66P is used to discharge a small capacitor into the gate of a conventional SCR, which then in turn discharges the capacitor in the flashgun firing circuit.

A high resistance voltage divider comprising a 10 megohm and 1 megohm resistor is used to charge a 0.1 μ F capacitor from the 200-plus voltage impressed across the flashgun connector, while ensuring minimum loading (on that voltage).

If care were not taken to minimise loading, the internal capacitor in the flashtube firing circuit might not be charged sufficiently to ensure reliable operation, particularly as the batteries approach the end of their service life.

Almost any SCR can be used in the circuit, provided it has a continuous forward blocking voltage rating of more than 300V. This means that an SCR with a minimum rating of 400V must be used.

Clarification of that last sentence is required: An SCR with a general rating of 400V will usually have a lower figure applicable for the "continuous forward blocking" state. Hence, while the 300R version of the BT100A may seem suitable, for example, its continuous blocking voltage rating is only 200V.

If necessary, a 400V Triac can be used in this circuit in place of the SCR.

Construction of the trigger unit is not critical and several approaches may be used. Our prototype was assembled on a small section of Veroboard measuring 30 x 40mm, and used a 400V SCR in a TO-5 metal can.


Before wiring of the trigger circuit can be completed, the polarity of the voltage across the flashgun connector must be ascertained. Turn on the flashgun and measure the voltage and polarity across the socket using a multimeter switched to a high DC voltage range. Do not be surprised if the voltage is below 200V or conclude that use of a 200V SCR is permissible.

The apparently low voltage across the flashgun connector will be due to the loading effect of the meter. For example, a VTVM with a load resistance of 10M or a 20,000 ohm per volt meter on the 500V range (which results in a load of 10M) will reduce the voltage across typical flashgun connectors by 30 or 40 volts.


As noted above, a 400V Triac may be substituted for the SCR. Use a plastic

For this test, you can merely strap the trigger unit to the side of the flash using an elastic band. Check that the slave flash is triggered when in the vicinity of another flash (when it fires).

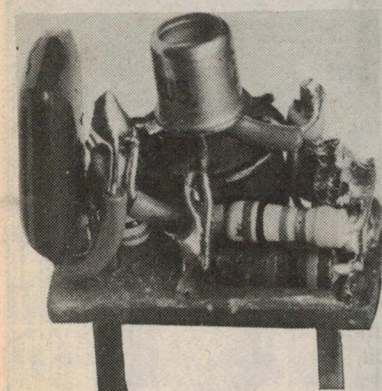Because the current available through the sync contacts of these units is so low,




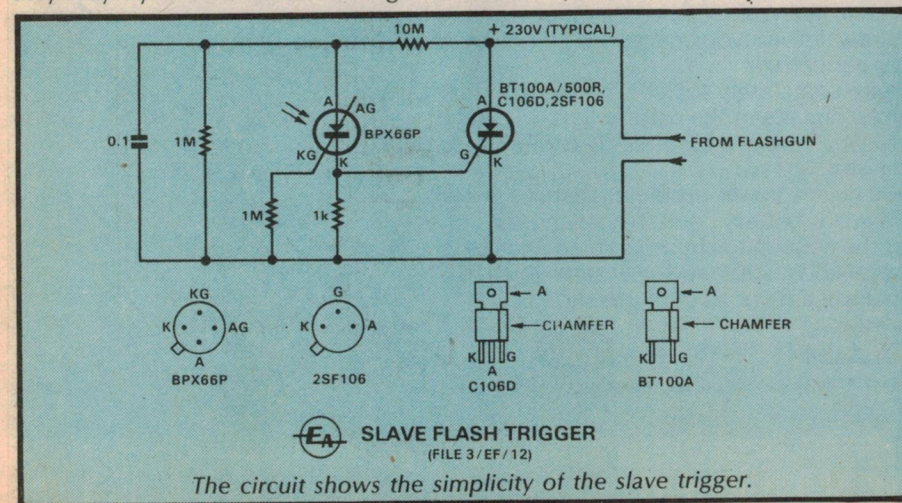There is no need to make this modification if you do not intend to use a flash



A variation of the method of assembly would be to wire the socket directly to the Veroboard and encapsulate it along with the rest of the components. Alternatively, if you have a "professional" flash with a two-pin socket on the side of the housing, the trigger circuit could be assembled on the back of the two-pin plug and then encapsulated in epoxy.

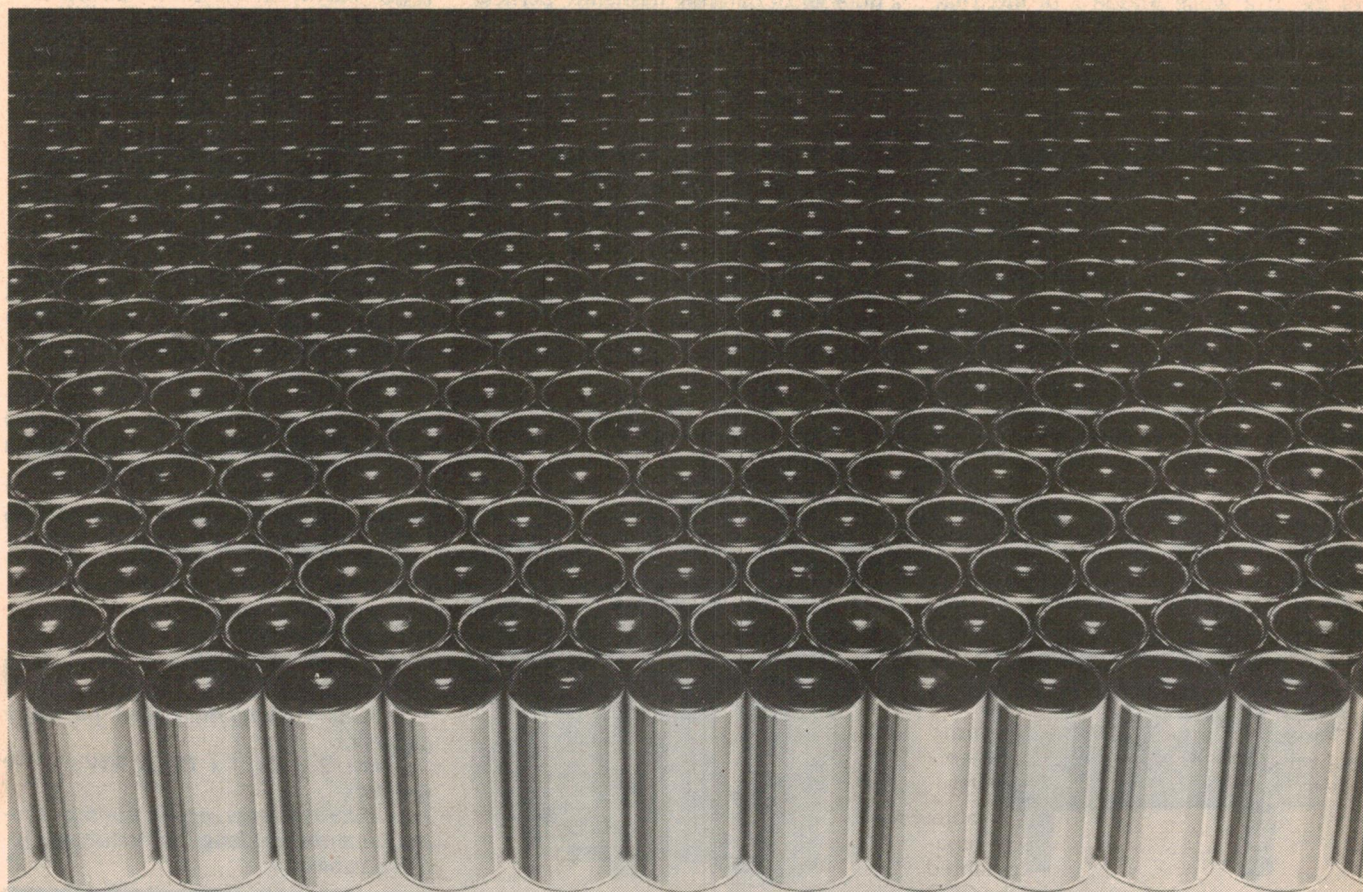1 small piece of Veroboard (optional)
1 flashgun connector socket
1 BPX66P LASCS
1 BT100A/500R, C106D or similar silicon controlled rectifier
1 x 0.1uF/100VW metallised polyester capacitor
1 x 10M, 2 x 1M, 1 x 1k, all ¼W or ½W resistors
Plus Velcro fastener, epoxy potting compound and short length of miniature figure-8 cable.



500 batteries in one.

When an 'Eveready' Nickel Cadmium battery runs down, you don't throw it away, you charge it up. And you can do that up to 500 times per battery.

They're completely sealed so they won't leak throughout the incredibly long life of the battery.

'Eveready' makes a range of "Nicad" batteries in all shapes and sizes.

If you have a power problem, chances are an 'Eveready' "Nicad" battery could be the answer.

Post the coupon to Union Carbide Aust. Ltd., P.O. Box 5322, Sydney, N.S.W. 2001, and we'll send you a brochure that will answer all your questions.

EVEREADY

BATTERIES Products of

**UNION
CARBIDE**

'Eveready' & 'Union Carbide' are registered Trade Marks.

Please send me a copy of your Nickel Cadmium
Battery Brochure.

Name _____

Address _____

Postcode _____

085.P.422



51


KITSETS

KIT'S KOLUMN

Woof. So much is happening I'm having trouble keeping up. First, we've got a new store opening in Melbourne at Box Hill which should please all the locals who have to trek miles to get what they want. And to all you studious types across the road at the Tech. College — come on in and say hello. Or drop me a line. (I didn't say hand me a line, Alfred E.).

You'll notice in this ad a bit about tools. Expense-account tells me good tools have been hard to come by and I'll have to accept his word for that. Although I've personally noticed no real shortage. However, when he showed me the new range, I saw what he meant. Beautiful solid stuff that should last for years. I only wish I could get eyebrow tweezers as good.

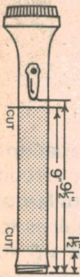Back to the torch conversion. For all of you who have been following our breathtaking in-depth and fearless investigation of Mom (also known as Yankee doodle) here at last is our special expose of how to cut down your enormous 5-cell flashlight into a more economical 2-cell version, and save yourself 60% on battery refills.



Scribe cutting lines on case as shown in diagram. Cut at switch end first, taking care not to damage metal strap. Cut other end of case. Align cut ends, then cement together. (Metal strap fits between case and pull-out metal ring.) Replace globe with 2.5 — 3V one, add 2 batteries and you're in business.

Had a nice letter from Richard H. Barton of Wellington New Zealand who seems to get marvellous circuit ideas in his bathtub. Love to see you if you're ever in Sydney, Richard. You sound like my type of experimenter.

Talking about New Zealand, and other nether parts of the world, it will be interesting to see where the best project ideas come from for our contest. (See details this ad.) But please, no black boxes — our friends at the APO would never forgive us.

Finally, to Alfred E. Neuman of Gore Hill, our special award of the Kitsets weeping handkerchief. Firstly, for maudlin nationalism, but mostly because he doesn't believe in me. Alf, how could you? (Autographed pic. sent free for S.A.E.) Until next month —

Keep your iron hot,

Kit



COMPLETE HI-FI SYSTEM: A BEAUTY FOR ONLY \$299

Not a kit, nothing to build. Just hook all units up, plug in, and you're in business. System consists of the Phodis C6000 amp which puts out 20W per channel RMS, has twin VU meters, 6 input jacks, 2 output jacks, and more features than we can list here. PLUS the BSR P128 turntable which has diecast platter and is fitted with a Shure M75 cartridge. Your choice of speakers—our 8" ready-made system or our kit with 12" twin cone and 1" dome speaker in each enclosure, which are both pre-assembled and veneered. P&P \$7

DON'T GUESS USE A METER!

If you're really serious, a good meter is about as important as a good soldering iron. These are all Japanese, and in our opinion some of the best value for money today.

Big daddy. Does just about everything except make coffee. 100,000 ohms per volt DC, 10,000 ohms per volt AC. Claimed burn-out proof. Instruction book, test leads. Has carry-handle, mirror scale. P&P \$1.50


\$49-50

Mini-pro. Angled scale for easy reading. Test transistors! 20,000 ohms per volt DC, 8,000 ohms per volt AC. Has all the usuals including zero adjust, instruction booklet, leads. P&P \$1.

\$29-50

Economy master. Fits big pockets, has quarter-circle scale, mirror back. 20,000 ohms per volt DC, 10,000 ohms per volt AC. With leads, instruction sheet. One of our best buys. P&P 75c

\$19-50

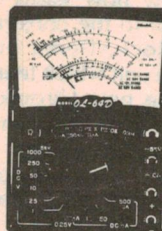

NOW FULL RANGE OF PHILIPS SPEAKERS



You know Philips. And you know Philips quality. Now we can offer you Philips speakers for virtually any sound system. Plenty in stock. Here's a sampling:

AD1060-T8 1" dome tweeter. **\$8.50.**

P&P \$1. AD8066-W8 8" woofer. **\$12.50.**

P&P \$1. AD1256-W8 12" woofer. **\$21.50.**

P&P \$2.

FAME AND FORTUNE ARE YOURS!

As we promised last month, here are details of our new contest where you can win big prizes for your favourite (own design) project. All you do is send us your original project design. Each month, we'll select a major prizewinner and runners-up. Winning projects will bear the entrants' names, and will be on sale as a kit through us. Get more details on the special entry form available from all Kitsets stores. If you can't call, write, and we'll send you one or how many you want. Grand prizewinner gets a full L&G colour plan Hi-Fi system at the end of the contest. This is your chance to lay your pet projects on us and maybe win a prize and see your name in print. No entry fee. Nothing to buy. Open to anyone. Get off your heat sink and get cracking — you'll never have a better chance!



NEW SQ DECODER KIT

Build this new 3ICSQ decoder—incorporating both full logic and wave-matching. Connected between the tape out and tape in on your existing amplifier, and connected to a rear channel stereo amplifier it provides you with a fully decoded SQ sound. Our kit comes complete with all parts, including power supply, and a case about 8" x 2½" x 5½" plus sleek blackface front panel. P&P \$2.50

\$59-50

Design for a PAL-S colour TV receiver—2

In response to the many favourable letters received since we published Mr Pierson's first article on the design of a PAL colour TV receiver, last June, we present here the first part of its sequel. In it, the author discusses various modifications and improvements to the original decoder design.

by **ANDREW PIERSON**

Following on from the information contained in the June 1974 issue, I have completed the design of the remaining colour recovery circuitry for a colour television receiver. As well as completing the (G-Y) matrix, luminance adding and sync facilities, I have taken advantage of a recent large price drop in the components market to make some very worthwhile improvements to the original decoder design—for a minimal increase in cost. The time which has elapsed since the appearance of the first article has been used to thoroughly research most of the possible circuit alternatives for a PAL-S decoder, whilst keeping within the constraints of the design philosophy outlined in part 1. It was felt that this time could be profitably put into research before the final circuit was committed to a PC card.

Coincident with this work was the development of an IF strip which could be simply aligned without using specialised equipment. Whilst this will be described in a later article, it is relevant to point out that the chroma information emerges at a much lower level (with respect to the luminance signal) than that found in conventional designs. The result of this is that the decoder must have higher chroma gain than normal, and also the chroma separation process must be carefully attended to, in order to minimise cross-colour interference.

Since regular test programs commenced, I have been able to carry out much more off-air testing. One of the most important things that I have learned is that a decoding system with immaculate specifications may be wasted in a domestic receiver, and, in fact, may be a definite hindrance. Take the chroma bandwidth, for instance—the wider it is, the more susceptible to noise and sound interference it becomes. So we make it narrower, but if we go too far, the coloured areas become visibly smeared.

With the above information in mind, I have now developed two separate colour recovery systems. The first (Mk II) has good specifications, and is intended for use with a colour camera chain, signal generator or a very clean off-air signal. The second system (Mk III) uses similar principles, but has lower chroma bandwidth and modified sync, ident and chroma blanking circuitry. This enables a subjectively better result to be obtained from off-air signals, and also allows the unit to operate from the simple IF strip.

This article will describe the Mk II system in detail, for the information of those readers

who require a circuit that can be used as a versatile model to demonstrate the principles of colour TV signal processing. All the classic parameters can be varied, including individual phasing of both vectors. The burst is not suppressed, so the results of demodulating it can be readily seen. The chroma bandwidth can be varied (by changing the resistive damping on TR1), and the luminance delay can also be shortened (by tapping down the delay line). The APC circuit can be disconnected without affecting subcarrier locking, so that the effects of phase errors can be studied.

If you are contemplating the construction of a vectorscope, the Mk II system would be the best choice. The addition of a simple electrostatic CRT and deflection amplifiers would produce a very effective and economical instrument, and more will be said about this in a later article.

It should be stressed that the article which follows is not primarily intended to be a constructional one, but sufficient information is given to enable the equipment described to be reproduced if necessary. The present discussion is intended to be a lead-in to further articles which put several years of experimentation into practice with the description of a low-cost colour recovery system.

Subsequent articles in the series will describe the Mk III system, which is the obvious choice

EDITOR'S NOTE

The design presented in these articles is intended purely as a guide for experienced amateurs wishing to build a colour TV receiver on their own initiative. A complete receiver of this type is a complex piece of equipment, whose construction involves not only components worth hundreds of dollars, but a large amount of time and effort. We do not recommend such a project to those without a solid grounding in both theory and practical electronic equipment construction. Because of the specialised nature of the articles, neither Electronics Australia nor the author will be able to supply information on colour TV receiver design or construction further to that published, or in advance of material which may be published in future issues. Similarly we regret that we will not be in a position to assist readers privately with problems they may meet in constructing a colour TV receiver based on the designs presented.

for a colour TV receiver project. This article will be constructional in nature, and the theory content will be limited to those sections which differ from the Mk II. It is worth noting that both the cost and complexity of the Mk III circuit have been considerably reduced.

THE Mk II SYSTEM

This equipment consists of a revised decoder design, plus the addition of the (G-Y) matrix, luminance delay line, luminance adders, and self-contained sync circuits. The result is a completely self-contained unit, i.e. 1V p-p composite video is fed in, and three 1V p-p signals corresponding to the red, green and blue components of the picture are available at the outputs. Since the subcarrier and ident recovery functions have been separated, the burst demodulation products are now meaningful, and may be very successfully used as an aid to alignment. As before, no special equipment is required for the alignment procedure, which may still be performed on ordinary program material. The power supply requirement is +12V at 380mA. It is true that the circuit employs more than 50 transistors, but it is also true that the devices specified are very inexpensive types. Also, bear in mind that the circuitry described represents a fair proportion of a complete colour TV receiver.

A description of the complete circuit now follows. Many sections are identical to the earlier design, and for detailed accounts of these the reader will be referred to part 1, in the June 1974 issue. A block diagram of the complete system is given in Fig 1, and this should be followed in conjunction with the circuit description.

CHROMA SEPARATION

Composite video is fed from the wiper of the CHROMA GAIN pot. RV1 to the base of the wide band amplifier Q1 via C1. The primary winding of the chroma bandpass transformer TR1 is included in the collector circuit of Q1, and the secondary winding is tuned to resonance at 4.43MHz by C2.

Since this circuit exhibits maximum impedance at its resonant frequency, the output signal amplitude will be maximum at 4.43MHz, the centre of the chroma passband. The Q of the circuit, and hence its bandwidth, is determined principally by the value of the damping resistor R5. The -6dB bandwidth is 1.6MHz.

Chroma signals from TR1 are passed to the amplifier stage Q2, which has a gain of 20dB and is DC coupled to Q3. A parallel-resonant 5.5MHz sound trap may be inserted here, but its presence has not been found necessary at this stage of development. Should it become desirable to include a filter at some later stage, the circuit designations L1 and C4 have been reserved for this purpose. Q3 is a unity gain amplifier, and is used to provide two signal paths—one for the synchronous demodulators and the other for the burst gating circuit. Its operation is described fully in part 1.

SYNC SYSTEM

Composite video is fed to the emitter follower Q4 via the low-pass filter R15-C7. The —6dB frequency of this network is approximately 600kHz, and it serves to prevent both sharp impulsive noise and the burst from reaching the sync separator. The purpose of Q4 is to buffer the low impedance input of the sync separator from the video input line.

Q5 is the sync separator, and is a PNP transistor biased in such a manner that collector current can flow only when the input signal is at or near its most negative excursions, i.e. during the sync pulse periods. Because the emitter is maintained at earth potential by C11 as far as the AC video signal is concerned, the base-emitter diode of Q5 acts with the input capacitor C9 to form a clamp circuit. This ensures that the sync tips are always maintained at approximately 650mV below the emitter voltage, regardless of the amplitude of the input signal. In this manner, correct operation of the sync separator circuit is maintained, even if the input signal amplitude should vary from its nominal 1V p-p.

The waveform available at the collector of Q5 is positive-going, and contains both line and frame information. The normal potential at this point is 0V, with positive excursions occurring during the line sync periods. However, during the frame sync period the collector goes positive, and returns to earth during the line sync periods. Half-line pre- and post-equalizing pulses are also present. This is known as a 'composite sync' waveform. Since the ident recovery circuit can reset the ident flip-flop on every second line, it is quite possible to clock the flip-flop from this waveform. Any spurious triggering which occurs during the frame sync period will be corrected as soon as the bursts begin to appear after the four-field burst blanking sequence. Tests have shown that this method of clocking will be suitable for all except very noisy signals. It has been used because of its simplicity and also because sync facilities may now be easily incorporated within the decoder unit itself. Since the flip-flop operates on the negative edge of its clock pulse, the positive-going sync pulses are inverted by Q7 which enables the change of state to be coincident with the start of the line sync pulse.

BURST GATING PULSE GENERATOR

Because a pulse is required for both the normal burst gate and the ALT-V burst switch, the gating pulse generator Q6-Q8 is employed. Q6 is maintained in a conducting state by RV2 and R23. The trailing (negative) edge of the separated line sync pulse from Q5 is differentiated via C12, and turns Q6 off for 3.6µs following the end of the line sync pulse. The amount of differentiation, and hence the Q5 'off' time, is made variable by means of RV2, so that the gate period may be correctly adjusted. Because the base of Q8 is connected to the collector of Q6 via R26 and C14, when Q6 is turned 'off' (i.e. during the burst period) Q8 is turned 'on', so producing a low impedance negative-going pulse at its collector.

BURST GATE

The waveform at the collector of Q8 is coupled to the base of Q9 via the components R28 and C15. The result of this action is that Q9 grounds the collector of Q3 at all times, except during the burst period. The resulting waveform is illustrated in Fig. 4. The burst amplitude is adjusted by RV1 to be 1V p-p. In the meantime, Q3 continues to function as an emitter follower.

Fig. 1 (at right) shows the block diagram for the Mk II colour recovery system. The complete circuit diagram is shown overleaf. Readily available discrete components are used throughout.


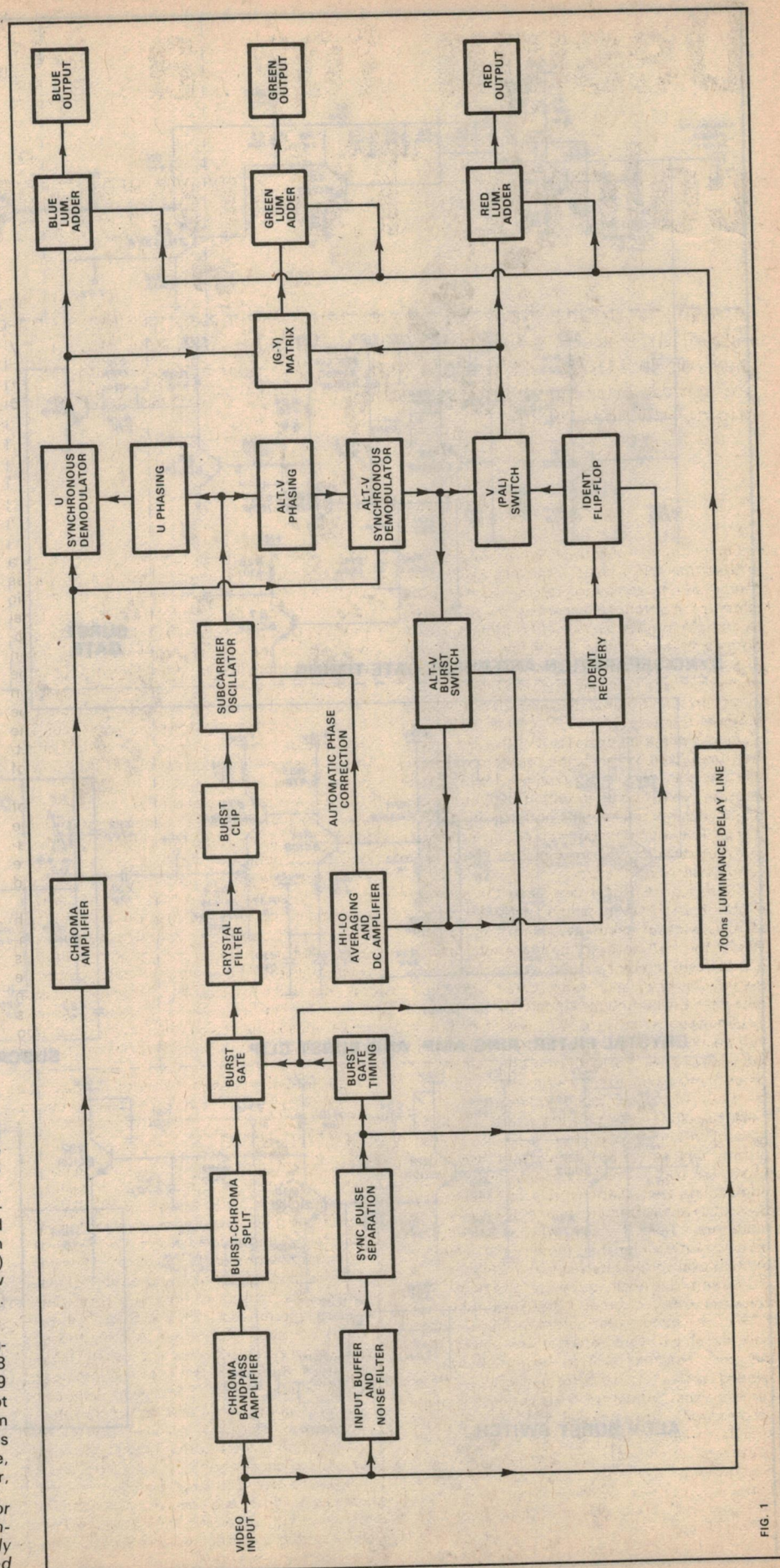


FIG. 1

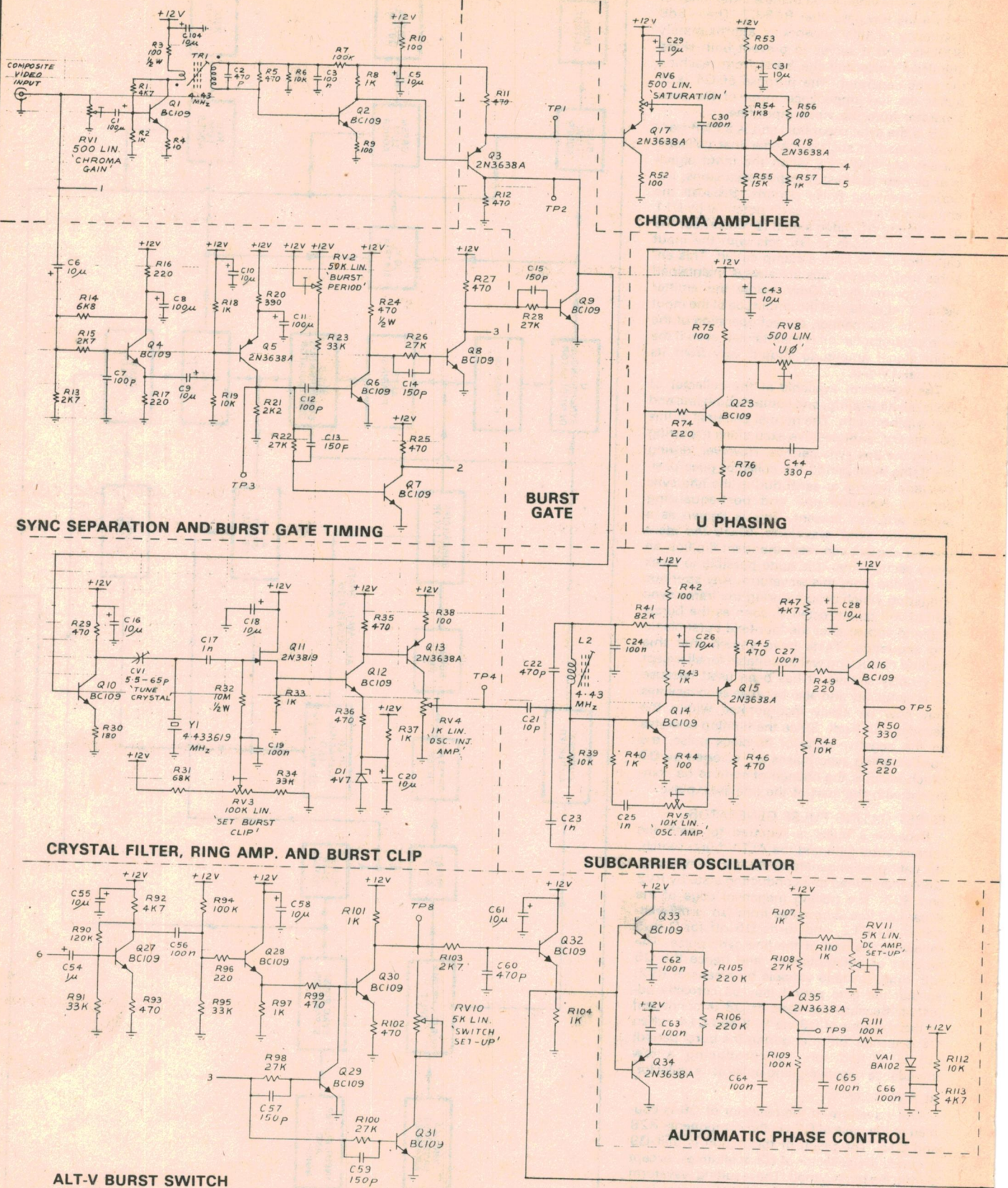

ALT-V PHASING

LUMINANCE DELAY LINE

ALT-V DEMODULATOR AND FILTERING

U DEMODULATOR AND FILTERING

BLUE LUMINANCE ADDER AND OUTPUT

RED LUMINANCE ADDER AND OUTPUT

GREEN LUMINANCE ADDER AND OUTPUT

IDENT RECOVERY

IDENT FLIP-FLOP

V (PAL) SWITCH

(G-Y) MATRIX

PAL-S COLOUR RECOVERY SYSTEM (MK. 2 DECODER)

PAL-S COLOUR TV RECEIVER

producing the chroma waveform in Fig. 3. Again, the burst amplitude is 1V p-p, but the phase is inverted.

CRYSTAL FILTER

Q10 is a DC coupled crystal driver amplifier which is identical to the circuit given in part 1. The crystal Y1 is tuned to resonance at 4.433619MHz by the trimmer CV1, and because of its very high Q, continues to ring with an almost undiminished amplitude between excitation by each burst (see Fig. 2). The crystal resonant circuit is unable to follow the alternate line $\pm 45^\circ$ phase shifts, and so takes up a nominal operating phase of 0° . However, static phase shifts inherent in the crystal filter operation produce an absolute phase shift between the nominal burst phase at the collector of Q3 (TP2) and the ring at the source of Q11 of approximately 95° .

Additional phase shifts are present in the subcarrier oscillator, ALT-V and U phasing stages, chroma amplifier and synchronous demodulators. The directions of these phase shifts are so engineered that the relative axes of the chroma information and the subcarrier drive signals are correct at their respective ALT-V and U demodulators. With minor differences, these phase shifts are common to the first decoder circuit but for the sake of simplicity mention of them was omitted from the earlier circuit description. One important point which was perhaps over-simplified was that if the sub-carrier oscillator is to act as a synchronous demodulator and so produce unequal burst demodulation products, then the oscillator signal must have an offset from the mean burst phase. This will be obvious when Fig. 17 is consulted. Note also that the oscillator phase differed from the new design because no U phasing stage was employed.

FET SOURCE FOLLOWER AND BURST CLIPPER

As in the first circuit, a FET is employed as a high input impedance buffer stage in order to obtain a maximum operating Q from the crystal. In this case, the signal at the source of Q11 is directly coupled to a 2-stage non-inverting amplifier Q12-Q13. During the burst period, the mean potential at the collector of Q3 is about 2.9V. The crystal is shocked into oscillation by the alternate phase bursts from Q10. However, when the burst gate closes (i.e., Q9 is saturated) Q10 is deprived of forward bias, and so its collector returns to rail potential. At this time, the crystal is also ringing, and this oscillation is superimposed onto the rail voltage. Because the burst is disposed $\pm 1.3V$ about 6.1V, and the ring is disposed about 12V, the two are separated by a 5.9V DC step, and the burst may be removed by arranging for the amplifier Q12-Q13 to conduct only on the positive excursions.

The emitter potential of Q12 is maintained at 4.7V by the zener diode, D1. Its base potential must therefore exceed 5.35V before the collector voltage can move downward. Since the gain provided by Q12 is unity, its base potential must exceed 6.0V before the collector voltage of Q13 can move upward. The burst is neatly clipped off by adjusting the bias on Q11 (and hence Q12) by means of RV3 so that just sufficient operating bias is supplied to handle the ring signal at the collector of Q13. The result of this operation can be seen in Fig. 2, although the ultimate adjustment is slightly different (see alignment procedure) so that in-

creases in ring signal amplitude may be accommodated. The collector load of Q13 is in the form of a potentiometer (RV4) so that the oscillator injection amplitude may be adjusted to a standard value (500mV p-p) regardless of the activity of the particular crystal in use. If necessary, Q13 can provide a maximum voltage gain of 20dB.

SUBCARRIER OSCILLATOR

The synchronized oscillator circuit is virtually identical to that used in the first decoder, and a description of its operation is given in the text of part 1. Incidentally, this oscillator is ideal for experimental and instrument use since it requires only a two terminal resonant circuit, has adjustable feedback and provides a buffered output signal.

The oscillator is injection locked to the sub-carrier frequency by feeding the signal present at the wiper RV4 into the base of Q14 via C21. During the burst periods, the oscillator is not supplied with a synchronizing signal. However, because of its high operating Q, it continues to run at the same frequency and maintains the same phase relationship which it had whilst being supplied with the ring signal from the crystal filter. The ratio of ring (sync) to burst (no sync) is 16.8:1, which means that the stability during the burst period is very high. Because the burst does not exert an influence on the oscillator's operation, the synchronous demodulators yield conventional burst demodulation products which are used for ident recovery, oscillator APC and assistance during the line-up procedure.

When the nominal free-run frequency of the oscillator is equal to the synchronizing frequency, the oscillator operates at a phase angle of approximately $+30^\circ$, which is due to the input coupling network. When the free-run frequency is swung above or below the input frequency, the oscillator remains locked, but its phase relationship to the synchronizing signal will 'skew'. The amount and polarity of the phase skew will depend on the magnitude and direction of the oscillator's frequency displacement. When this becomes too great, the oscillator will lose lock altogether.

Since the phase inversions produced by Q10 and the oscillator transistor Q14 cancel each other, the sum total of the phase leads produced by the crystal filter (approximately 95°) and the oscillator input circuit (approximately 30°) mean that the oscillator operates with an output phase lead of 125° from the average burst phase. (This is equivalent to 55° of Fig. 17). This relationship is illustrated by Fig. 8, and should be compared with Figs. 6 and 7 which show the phase skewing limits available from the synchronized oscillator ($+45^\circ$ and $+180^\circ$). The total phase variation available is 135° , and the magnitude of the phase shifts introduced by the ALT-V and U phasing stages is so chosen that the oscillator normally operates at or near the centre of its skewing range. This ensures optimum performance from the APC system, which makes use of the oscillator's phase skewing characteristic by controlling its free-run frequency via the varactor diode, VA1.

Q16 is an emitter follower stage, and is used to buffer the output of the oscillator from the input of the ALT-V and U phasing stages. Since the subcarrier drive required by the synchronous demodulators is 2V p-p, the necessary attenuation from the oscillator output

level (5V p-p) is provided by the resistive divider R50-R51. DC coupling is employed between Q16 and both phasing stages, so that their bias conditions are actually determined by the resistive divider R47-R48.

U AND ALT-V PHASING STAGES

Because of phase shifts present in the chroma amplifier and synchronous demodulators, the subcarrier phase angles (with respect to the nominal burst phase) required by the U and ALT-V demodulators are 170° and 80° respectively, i.e., $+$ and -45° from the oscillator output phase. These angles correspond to 10° (U) and 100° (V) on Fig. 17. The necessary shifts are provided by the phasing stages Q23 (U) and Q19 (ALT-V), which are driven by the oscillator buffer Q16. The U phasing stage is required to provide a phase advance of 45° , and its adjustment range is between $+15^\circ$ and $+180^\circ$. The ALT-V stage must also produce a 45° shift, but this time a phase retard is required, so that the difference between the U and ALT-V demodulation axes is 90° . The adjustment range of the ALT-V phasing stage is between -10° and -80° .

CHROMA AMP AND DEMODULATOR BUFFERS

The path from the chroma splitting stage (Q3) through the saturation control buffer (Q17), chroma amplifier (Q18) and the synchronous demodulator chroma buffers (Q20 and Q24) is identical to that found in the first decoder, and a full description of this is given in the June 1974 issue.

SYNCHRONOUS DEMODULATORS

Similarly, the synchronous demodulators have not been altered, but the subcarrier filters which follow them have been increased in complexity to provide improved colour difference bandwidth, together with much greater sampling frequency rejection.

Instead of the original R-C low pass filters, two-section L-C types have been substituted. Since the Zo (characteristic impedance) of these filters is 180ohms, the emitter follower stages Q26 (U) and Q22 (ALT-V) are required to effect the necessary impedance transformations from the demodulator outputs. The f_c (cut-off frequency) of these filters is 880kHz, and the 4.43MHz sampling frequency rejection is 47dB, i.e. from 440mV p-p to 2mV p-p.

The formulae used for the design of these filters is identical to those used for the luminance delay line, and will be found in the text dealing with that section.

U DEMODULATION

The U synchronous demodulator is Q25, and the recovered U vector is available at the output of the filter. The wiper of RV9 provides a source of (B-Y) information which is variable in amplitude (the BLUE AMP. control) for the blue luminance adder and output stages. R89 and RV9 together make up the necessary 180 ohm terminating resistance for the filter L5-C52-L6-C53.

Figs. 15 and 16 provide an interesting insight into the operation of the synchronous demodulators, and are the collector waveforms with all filtering components removed. Fig. 15 shows the classic sampling operation when the swinging bursts are demodulated by a subcarrier which is shifted by 90° with respect to the mean burst phase. Fig. 16 shows the actual gating operation at 4.43MHz effected by the subcarrier signal at the base of the demodulator. The 'angle of flow' is approximately 130° .

The standard output signal from both demodulators is set by the saturation control (RV6) to be 100mV peak (U) or 200mV p-p (ALT-V) on the demodulated burst.

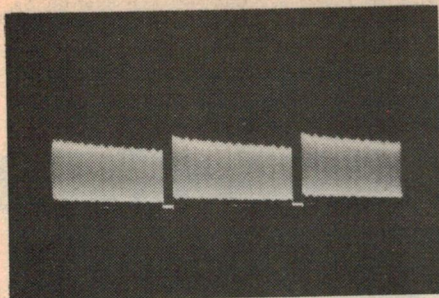


Fig. 2

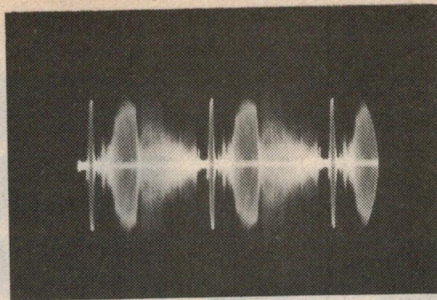


Fig. 3

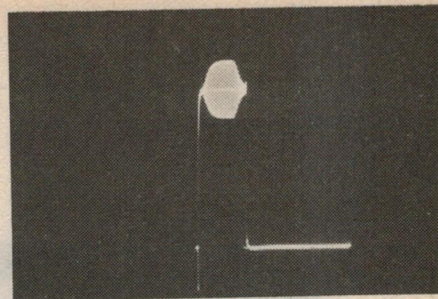


Fig. 4

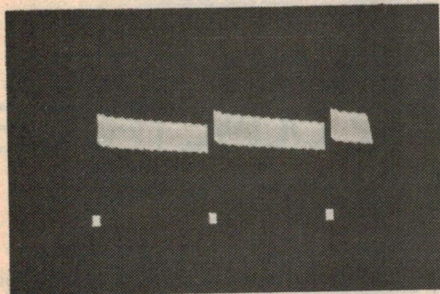


Fig. 5

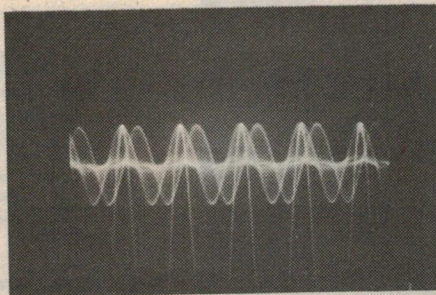


Fig. 6

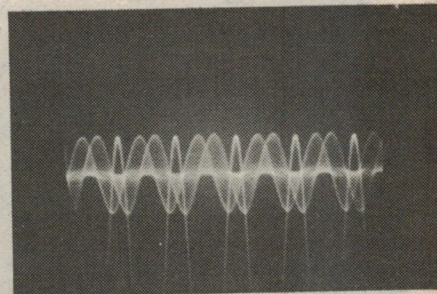


Fig. 7

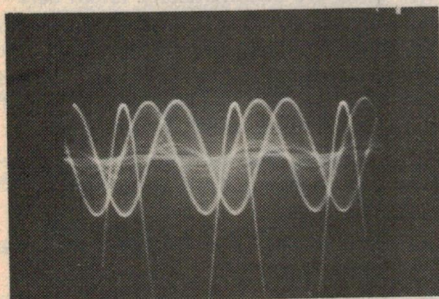


Fig. 8

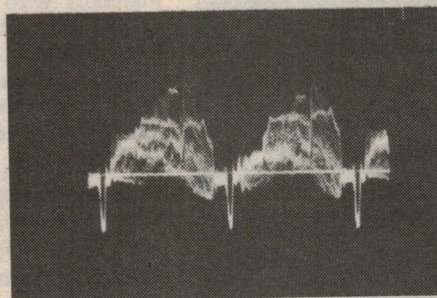


Fig. 9

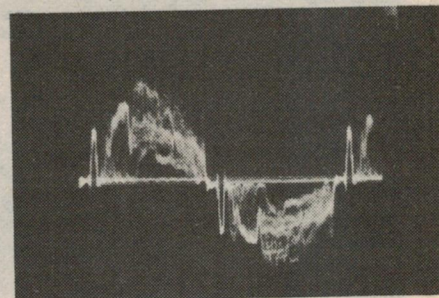


Fig. 10

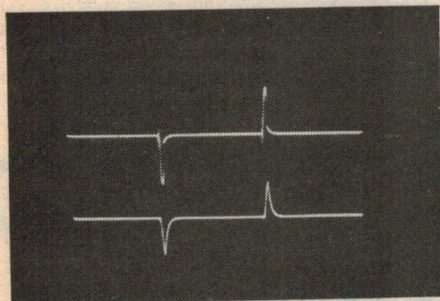


Fig. 11

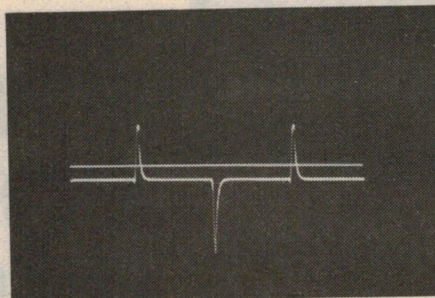


Fig. 12

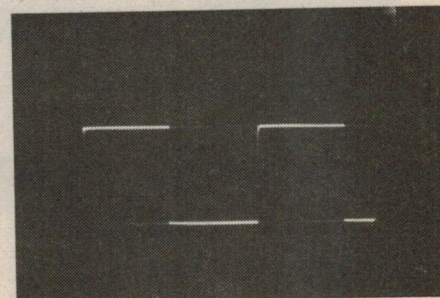


Fig. 13

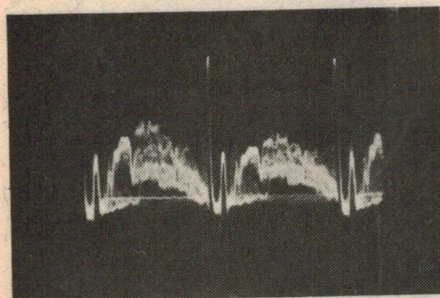


Fig. 14

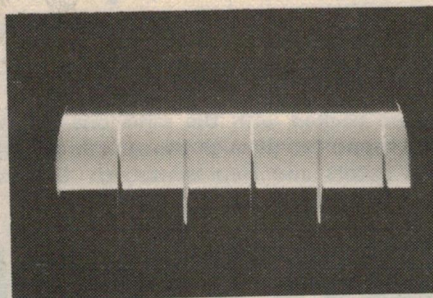


Fig. 15

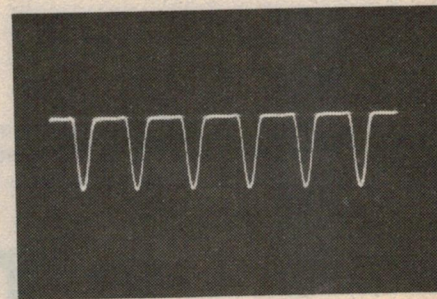


Fig. 16

Fig. 2: burst clipping action (see text) — Fig. 3: chroma at TP1; amplitude of burst = 1V p-p — Fig. 4: gated burst at TP2; burst amp = 1V p-p; burst gate period = 3.6 μ s — Fig. 5: signal at TP4 (see alignment procedure) — Fig. 6: oscillator phase skewing limit (+45° — see text) — Fig. 7: oscillator phase normal (+180° — see text) — Fig. 8: oscillator phase normal (+125° — see text) — Fig. 9: U vector output (TP7); amplitude of demodulated bursts = 100mV pk — Fig. 10: ALT-V vector output (TP6); amplitude of demodulated bursts =

+100mV pk — Fig. 11: ALT-V burst switch; output: top trace 3.25V p-p (TP8); bottom trace 2.5V p-p (after LP filter) — Fig. 12: ident recovery (at base of Q36); marker line is OV; amplitudes +0.7V, -1.55V — Fig. 13: ident signal at TP10; amplitude = 11V p-p — Fig. 14: V vector output (TP11); amplitude of demodulated and switched bursts = +100mV pk — Fig. 15: synchronous demodulator operation (see text) — Fig. 16: synchronous demodulator operation (see text). These oscillograms all taken from the author's Mk II decoder.

SPOT ON FOR COLOUR TV SERVICE



TEKTRONIX 10MHz DUAL TRACE OSCILLOSCOPE

Servicemen like the D61 because it's accurate, reliable and extremely easy to use. Functions that are normally selected manually with other units are automatically taken care of on the D61. It has performance high enough to tackle the most meticulous of pulse analyzing jobs on the bench and rugged construction and solid state circuitry so you can take it out on the road with confidence. The D61 has the specification you need to do TV servicing easier, faster.

HORIZONTAL — 0.1 μ s/cm to 500 ms/cm in 19 calibrated steps with magnifier. Full triggering facilities including TV line, TV frame and auto.

VERTICAL — Dual Trace, each DC to 10 MHz, calibrated from 10mV/cm to 5V/cm in 9 steps.

C.R.T. — 8 x 10cm operating at 3.5kV. Weight — 6.5Kg.

RIGHT ON FOR PRICE

\$399 DUTY
PAID

Optional x10 Probe \$14.70 each.

All TELEQUIPMENT scopes are backed with the same one-year warranty as other TEKTRONIX products and are marketed and supported through the same International network of Tektronix Field Offices, Service Centres, Distributors and Representatives. Call your nearest office, or write to:-



TEKTRONIX

Committed to technical excellence

Australia Pty. Limited, 80 Waterloo Rd., North Ryde, N.S.W. 2113
SYDNEY 888 7066 MELBOURNE 94 0229 ADELAIDE 223 2811

COLOUR TV RECEIVER

ALT-V DEMODULATION

For the V-signal recovery, the circuit techniques employed deviate sharply from those used in the first circuit. The chroma information is synchronously demodulated by a subcarrier on the V axis, but no alternate line phase switching is provided. Since the phase of the encoded V signal is changed by 180° on each alternate line, demodulation by a fixed phase subcarrier will produce a waveform in which each alternate line is reversed in phase (see Fig 10). This is known as an ALTERNATE-V signal. Whilst the polarity of the picture information is reversed from line to line, the $+45^\circ$ and -45° bursts also demodulate alternately positive and negative, as reference to the diagram in Fig. 17 will show.

If we pass the ALT-V signal through a switch which opens only during the burst period, the result is a series of pulses at line rate, each pulse having an alternate polarity. From this signal, two pieces of information may be gleaned. Firstly, since pulse polarity is directly related to burst phase, the ident may be recovered. Secondly, from the diagram in Fig. 17 we see that the amplitude ratio of the alternate line demodulated bursts depends on the subcarrier phase. The demodulated pulse amplitudes are only equal when the subcarrier phase is correct. This is the basis of the operating principle for the APC system, which detects a shift in the mean pulse level, and feeds a correction signal back to the subcarrier oscillator so that the phase returns to normal.

The V signal is reconstituted by inverting the phase of each alternate line of the ALT-V signal. A bistable multivibrator, guided by the ident information operates a switch which performs the polarity reversal. Because a wideband video switch usually cannot be produced as economically as one which has to handle only subcarrier or chroma information, post-demodulation PAL switching is generally not used in commercial decoders. However, because of the unusual signal paths employed in this decoder it was simpler to switch the ALT-V signal than to provide a separate switched-subcarrier V demodulator.

A great advantage inherent in post-demodulation V switching lies in its high phase accuracy. Phase shifts in a subcarrier or chroma switch will cause demodulation errors. However, when the same phase shifts are applied to the demodulated colour difference signal, they can only produce registration errors which are far too small to be noticeable. It is interesting to note that at least one high grade commercial colour monitor uses three demodulators: one each for the U, V and ALT-V signals.

The ALT-V synchronous demodulator is Q21, with the recovered ALT-V vector being available at the output of the filter L3-C41-L4-C42. This point is also fed to the ALT-V burst switch and the V switch.

ALT-V BURST SWITCH

The function of this stage is to remove the demodulated chroma from the ALT-V signal, so that only the demodulated bursts remain. Heart of the switch is Q30, which is connected as a common-emitter amplifier stage with a voltage gain of 6dB. Operating bias is supplied from the resistive divider chain R94-R95 via the emitter follower stage Q28 and the series resistor R99. When Q29 and Q31 are in the 'off' state, the operating conditions are such

that the DC potential at the collector of Q30 is approximately 8.6V. Any signal which is AC coupled to the base of Q28 via C56 will therefore appear (inverted and 6dB up) at the collector of Q30. This is the case during the burst period, but at all other times Q29 and Q31 are kept saturated. The immediate effect of grounding the base of Q30 is to remove both the bias and the signal, thus allowing its collector to rise to +12V. However, since Q31 is also saturated, a variable resistive potential divider is formed from R101 and RV10. The value of RV10 is adjusted so that the collector potential during the switch 'off' time is equal to the potential determined by R94 and R95 during the 'on' time.

In the interests of stability, it is desirable that the DC gain of Q30 be kept low, and that the signal amplitude applied to its base be relatively high. Accordingly, the 20dB amplifier stage Q27 has been inserted between the ALT-V demodulator output and the switch input.

The switched burst output can be seen in Fig. 11 (top trace). In order to minimise the effects of noise on ident recovery, the switched bursts are fed through a low-pass R-C filter

synchronous demodulators is correct. If errors are detected, a signal is developed and this is fed back to the subcarrier oscillator in order to correct its phase.

In this case, the demodulated ALT-V signal is used as the source of APC voltage. From Fig. 17, it can be seen that demodulation along the 90° axis with a CW subcarrier yields an ALT-V signal, in which the demodulated burst swings alternately positive and negative on successive lines. Furthermore, it can be seen that when the phase is correct, the positive and negative swings are equal. The ALT-V burst switch is used to gate out all other information except the demodulated bursts, and the result is averaged. If phase errors should occur, the alternate polarity demodulated burst from successive lines are no longer equal in amplitude, and will be predominantly positive or negative, depending on the direction of the error. The averaged output voltage will follow this change, and after DC amplification is applied to the subcarrier oscillator's frequency control circuit.

From the description of the subcarrier oscillator we have seen that when the oscillator is locked to the ring signal from the crystal filter,

Fig. 17: this diagram illustrates in practical terms what happens when the $\pm 45^\circ$ swinging burst is synchronously demodulated by a variable phase subcarrier signal as represented by the moving arrow.

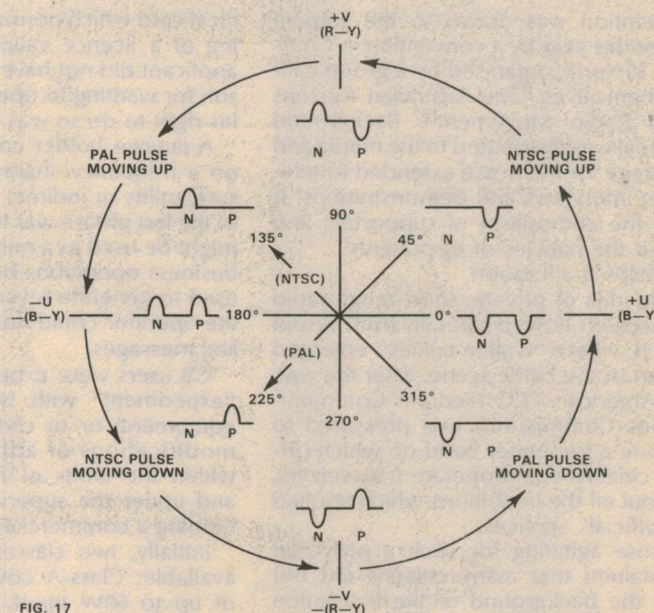


FIG. 17

R103-C60. The -6dB frequency of this network is 125kHz. An emitter follower Q32 is used to buffer the filter output from the remaining circuitry.

APC SYSTEM

In the decoder circuit described so far, there are two main sources of possible subcarrier phase errors. The first of these is a drift in the free-run frequency of the subcarrier oscillator, as this will result in the subcarrier phase being incorrect. The second source of error stems from the action of the crystal filter, and this disadvantage is common to all passive subcarrier regeneration circuits. The crystal behaves as a very high Q tuned circuit, and as such is phase sensitive. A phase shift of 90° will occur when the input frequency moves away from the circuit's resonant frequency by an amount equal to its -3dB bandwidth. If the subcarrier frequency is maintained within specification at $4.43361875\text{MHz} \pm 5\text{Hz}$, the phase shifts from this source will be very minor.

The function of the automatic phase control system is firstly to determine if the phase of the subcarrier signal supplied to the

a change in the nominal free-run frequency will result in a 'phase skew' between the input and output signals. This characteristic is exploited for the APC system. Phase errors are detected in the demodulated ALT-V signal, amplified, and then applied to the phase skewing circuit in such a manner that the original error is cancelled. In other words, the circuit is constantly 'seeking' to balance itself about the point where the ALT-V demodulation is symmetrical. A high order of overall stability is achieved, because the APC loop covers the entire ALT-V demodulation process. The U demodulator is individually phased by means of a very stable phase shifting stage (Q23), so that correct U demodulation can be achieved.

It may be noted that when the oscillator is off-lock, there are two influences tending to produce synchronism. These are firstly the basic injection locking process, and secondly the asymmetrical beat products from the APC system. In a conventional phase-locked loop, only the second influence is available for initial lock acquisition.

(To be continued)



Forum

Conducted by Neville Williams

Should Australia have a full-scale Citizens Band?

A subject likely to generate heat in certain circles is whether or not Australia should have citizens band radio on the American pattern. Argument becomes all the more pointed because the main contender groups—the “forers”, the “againsters” and the “statusquoers” can all make out a convincing case.

Attention was drawn to the subject earlier this year by a convention in Churchill, Victoria, organised by a group calling themselves “The Australian Citizens Band Radio Movement”. Background material was distributed to the media and coverage for their case extended to television interviews and demonstrations. It fired the enthusiasm of supporters and stirred the hackles of opponents.

What’s it all about?

The idea of private, short-range radio transceivers flowed naturally from World War II, where “walkie-talkies” emerged as part of the battle scene. After the war, the American FCC (Federal Communications Commission) was pressured to allocate a frequency band on which private citizens could operate transceivers, without all the inhibitions which applied to “official” services.

Those agitating for such a provision maintained that many citizens did not have the background or the inclination to secure an amateur style operator’s licence; nor did they want to experiment with equipment, talk technicalities, or communicate across the nation or across the world. They just wanted to use radio as a casual, personal and essentially local extension of their ability to communicate.

In 1947, the U.S. Congress acquiesced by making available a band of frequencies in the UHF region (460-470MHz) for the “Citizens Band Radio Service”.

Related regulations made it possible for any citizen of the United States, 18 years of age or over, to operate a radio transmitter/receiver, using equipment which had been approved for the purpose by the FCC.

While there seems to have been an early assumption that most of the messages passed would be of a brief, substantive nature between associated transceivers, the system did not obviously impose this as a condition. Applicants were required only to fill out a non-techni-

cal card which normally led to the issuing of a licence valid for 5 years. The applicant did not have to advance a reason for wanting to operate a transceiver; his right to do so was taken for granted.

A licence holder could communicate on a frequency sharing basis, for pleasure, utility or indirect profit. Implication of the last phrase was that the equipment might be used as a minor aid to ordinary business operations but it could not be used to generate revenue directly. Thus, the operator could not charge for handling messages.

CB users were expressly forbidden to “experiment” with type approved CB equipment, or to carry out extensions, modifications or adjustments, except within the limits of FCC specifications and under the supervision of a person holding a commercial operators licence.

Initially, two classes of licence were available: Class-A covering transmitters of up to 60W input, with a frequency stability within .02%; these could operate anywhere within the allocated band and with antennas subject only to building codes. Lower performance, class-B equipment, 5W maximum input and less stable oscillators, had to operate nominally at 465MHz into restricted antennas, and not drift more than 0.4%.

Subsequently, a third type of licence, class-C, was announced, intended primarily for remote control of models, garage doors, etc.

As matters transpired, use of the 460-470MHz band was inhibited by the cost and complexity of equipment and by the fact that signal coverage was limited to little more than an “optical” path. Following agitation, a proposal was advanced that part of the 11-metre amateur band be also allocated for CB use. This was implemented by the FCC during 1957-59 as a class-D licence, with 23 available channels, spaced 10kHz apart, between the band limits of 26.960 and

27.255MHz.

The response was immediate and overwhelming, with more than 50,000 licences issued within months of them becoming available. Class A and B stations were virtually rendered obsolete and the 460MHz band became largely the domain of class-C radio control.

By and large, the concept and conditions set down for the original class-A and class-B UHF citizens band were retained for class-D with the notable exception that the normal power limit was lowered to 5W. And because 27MHz had the potential for occasional ionospheric coverage, a ban was placed on contacts international or over distances greater than 150 miles.

Supporters of the 27MHz citizens band point to it as one of the success stories of the electronics industry, with licensees running into millions in the United States alone and an enormous turnover for equipment ranging from tiny hand-held transceivers to mobile and fixed installations. Most of these are privately owned but a very large number are operated by local utilities, small firms, business and professional men who find it more convenient to use CB equipment than face the expenditure and complications of an “official” 2-way radio installation.

But critics of the CB concept put an entirely different construction on the facts and figures. They see the huge number of CB users as posing an impossible administrative task. There is no way, they say, that the FCC or any other regulatory body can keep track of licensed and well-intentioned users, let alone the huge numbers who don’t bother with a licence or who abuse their licence either in a “merely illegal” or a positively anti-social manner.

“Merely illegal” operation would include the addition of high power linear amplifiers to transmitters, high gain beams for DX, “experimenting” without technical supervision, and the ultimate operation of the equipment as unlicensed amateur station, totally removed from the local, personal CB concept. Apart from anything else, the existence of such high power stations, engaged in lengthy DX or “net” activities, denies the channels to legitimate users.

The anti-social transgressions, which have been highlighted from time to time, are quite ugly: the transmission of false, mischievous or defamatory matter, obscenities, etc; standover tactics to block channels used as a business aid; and the use of CB equipment by groups and gangs to “set up” victims or crimes.

String together enough of these abuses and they will seem to outweigh any possible good, the community being better off without a facility so democratic but so open to abuse!

In fact, there are plenty of administrations around the world that think this way and, during the past decade, there has been evidence that the American FCC itself tended to share the view.

Opponents have often claimed that, if the FCC had its time over again, it would have vigorously resisted the proposals.

Initially, authorities in Australia took the hard line, affecting not to know the citizens band, or to recognise the existence of CB equipment. The importation or possession of transmitters for anything but the official allocations was effectively "discouraged".

The writer challenged this whole attitude in an editorial and a 3-page article in our August 1961 issue.

At the time, "experimental" FM stations in the capital cities had just been silenced on the grounds that the VHF FM band was needed for television and for additional communication channels.

We maintained that this was wrong thinking and that, with appropriate planning, FM broadcast stations and TV stations could share the 88-108MHz band. Further, that some of the pressure for two-way radio licences would be relieved if the authorities would take their heads out of the sand and encourage use of the citizens band and equipment being sold for it. We pointed out that applications in the USA were running at 12,000 per month, and that about 50 manufacturers were currently supplying equipment.

The articles produced an immediate response from readers and from industry, but scarcely a word from the authorities. Behind the scenes, however, it was evident that we had put a cat amongst the chickens.

In January, 1962, we were able to confirm that the PMG's Department, as the licensing authority, did have a frequency allocation around 27MHz for what they were choosing to call the "industrial" band. They had been remarkably reticent about it but were prepared to issue licences for operation in the band to people who had a "legitimate" need.

An interview with a Departmental representative at the time indicated typical "legitimate" users: bushwalkers; cave explorers; pastoralists; TV antenna jobbers; tug to dredge; boat to boat at sea (not boat to shore); sporting fixtures (officials only); medicos, surgery to vehicle; construction and maintenance work. There would be other possibilities but a basic consideration was that there must be no conflict with revenue-producing facilities, where available, already provided by the PMG or OTC. The frequency normally available was 27.24MHz and the power limit 1W ERP.

Applications for a licence involved the applicant's full name and address, an explanation of the business or activity with which the "fieldphone" would be associated, how and where it would be used, the number of fieldphones likely to be involved and the maximum likely communication distance; finally the precise brand and model of the equipment(s) to be used. The cost of a licence: one pound (or \$2).

Since then, a considerable number of

"industrial" band licences have been issued in Australia. Figures released in March 1974 indicated that about 20,000 hand-held transceivers had been licensed for "handphone mobile services", plus a number of special 5-watt "base stations. The gross figure now would be much higher.

A statement by the Postmaster-General indicates that the "CB" units are being used by private individuals and groups as indicated earlier, and also by utilities and departments for secondary communication links: police, fire brigades, forestry, civil defence. And, because the channels are not loaded up with trivial matter, those who have a legitimate need are better served.

The statement concludes with a reminder of a "long-standing Government policy in Australia that the public telephone and telegraph systems, which have been provided at considerable public expense, should be the normal means of communication between individuals residing in areas where these services are available".

A letter on behalf of the Australian Citizens Band Radio Movement brands the Postmaster-General's statement as "ridiculous". However one may disagree with it, I don't think it is. As I said at the outset, it is possible to advance sound argument in favour of the present Australian approach: namely to make communication facilities available to those who have an even modest need, and to exclude those who don't.

If anything is ridiculous in the Australian approach, it is the failure of other governmental bodies to help make it work. The simple fact is that people can bring into the country, or import and sell any number of citizen's band transceivers, ranging from highly developed units to junk. The stage has even been reached where they are given to children as birthday toys.

Officially, the vendors should seek type approval and warn the purchasers that a licence is required; and they should supply the PMG's Department with names and addresses of purchasers. But the simple fact is that it doesn't work this way and, alongside the 20,000 odd licensed units, we have a huge number of unlicensed transceivers.

It is intriguing to note that CB exports to Australia from Japan alone were more than 7000 units in 1973, and 16,000-plus in 1974. As we observed in an earlier issue, we are rapidly acquiring a full-scale citizens band in Australia—by default!

The case for a communications band freely open to all rests partly on the concept that denial of access to anyone is a denial of their basic right. A motorist has to conform to all kinds of laws but thus far, as a nation, we have not questioned his right to be a motorist!

Should the CB facility become overcrowded or difficult to administer, the protagonists say, it is a problem to be solved, as such. In any case, they con-

tend, CB tends to be self-levelling and self-correcting, with people using the channels to the extent that they think is worthwhile. And abuses? They have to be faced up to, as do the abuses of any other right or activity.

The other main line argument is that, problems notwithstanding, a CB facility can serve the interests of individuals and communities in a thousand isolated ways, most of them too transient ever to be documented.

Overall, the case for a freely accessible citizen band can certainly be built up to convincing proportions and it was the one accepted by the New Zealand Post Office back in the same 1961 era.

Whether New Zealand can be accepted as an example of a freely accessible CB situation is another matter. Severe exchange and import controls in the intervening years must surely have inhibited use of the band, and therefore the emergence of the "chaos" which is allegedly characteristic of American CB.

Curiously enough, there is some hint of a new and positive attitude to CB by the American FCC. Writing in "Popular Electronics" columnist Len Buckwalter says: "Unlike FCC documents of past years, which attacked CB as radio's black sheep, this one (No. 20120) is cause for celebration. It could more than triple the number of CB channels and ease the complaints about CB from the law-makers."

The new proposals would extend the existing band to include 30 channels 10kHz apart between 26.960 and 27.310MHz. There is some debate as to whether the channels would be retained for AM operation only or opened up for some SSB equipment. Also under consideration is revised allocation of channels: calling only, emergency only, intra (same call sign) and inter (different call signs).

A further extension of the present band—out to 27.505MHz—would accommodate 40 SSB channels at 5kHz spacing.

FCC docket no 19759 envisages a yet further expansion into a class-E licence, for operation in a band 222-224MHz.

This improved "accommodation", together with vigorous industry co-operation to stamp out the sale of illegal equipment, could go a long way to cleaning up the American CB scene.

Out of all this, one thing is patently clear about the Australian situation: we must put a stop to the present drift towards CB by default, or we will indeed end up in a mess. If we are to have a restricted situation, then government instrumentalities must co-operate to ensure that it is preserved. But if this co-operation is impractical, then the Radio Branch of the PMG Department should be empowered and equipped to turn what is almost a fait accompli into a properly supervised citizens band radio service, with channels, call signs, co-operative regulations... the whole bit! ☺

Using the Philips 10GHz Doppler module

Until recently, microwave radar systems and the range of applications they encompass have been relatively unavailable to the home constructor. This problem has now been overcome by the release of the CL8960 Doppler radar module by Philips Elcoma. In order to illustrate one possible area of application, Philips Elcoma built up a demonstration intruder alarm system, as described in this article.

by PHILIP TRACY*

Modern microwave radar modules such as the Philips CL8960 are based on a phenomenon known as the Gunn effect, an effect which causes a suitable semiconductor material to act as a microwave oscillator when operated under certain conditions. Costing far less than an equivalent klystron source, the Gunn oscillator, because of its inherent efficiency, reliability and compact size, is finding wide application in contactless object detection and observation equipment. Some of these applications include intruder detectors for security systems, aids for the blind, automobile anti-collision systems, contactless actuators, and speed and rotation measuring equipment.

Microwaves have many advantages over light, infrared and ultrasonic waves

for such duties. Principal among these is the relatively unpolluted section of the spectrum in which they operate—few natural phenomena or electrical machines generate incidental microwaves. In addition, conventional radio signal processing techniques are available for extracting information from the signal.

While these radar systems are essentially very simple in theory, the production of workable systems has been confined to a limited number of companies possessing the necessary know-how and resources. The two main limitations to date have been:

- the difficulty in separating the wanted signal from power supply spikes, ripple etc in commercially available devices using a common Gunn oscillator/mixer diode;
- the lack of commercially available mechanical hardware for a Gunn oscillator/separate mixer diode type of system.

The release of the CL8960 twin transmitter-receiver radar module assembly by Philips Elcoma is intended to overcome these problems and, by eliminating the need for microwave test equipment, to increase the number and range of potential users of microwave systems.



For those readers unfamiliar with the operation of Gunn devices, a brief theoretical discussion follows.

The Gunn effect was discovered in 1963 when J. B. Gunn first reported that he had obtained coherent oscillations by applying an electric field to a crystal of gallium arsenide. A power output of 0.5W at 1GHz was quoted for these early experiments. Since that time, a great deal of research and development effort has been devoted in producing a range of microwave generators with stable predictable properties.


Basically, a Gunn device consists of a sample of bulk semiconductor, moderately but uniformly doped, provided with ohmic contacts, and mounted in a suitable cavity. Under suitable pulse or DC bias conditions, the device will act as a microwave oscillator.

The effect may be explained in terms of the conduction mechanisms found in certain types of semiconductor compounds. Studies have revealed that the momentum of an electron travelling through a solid may only have certain

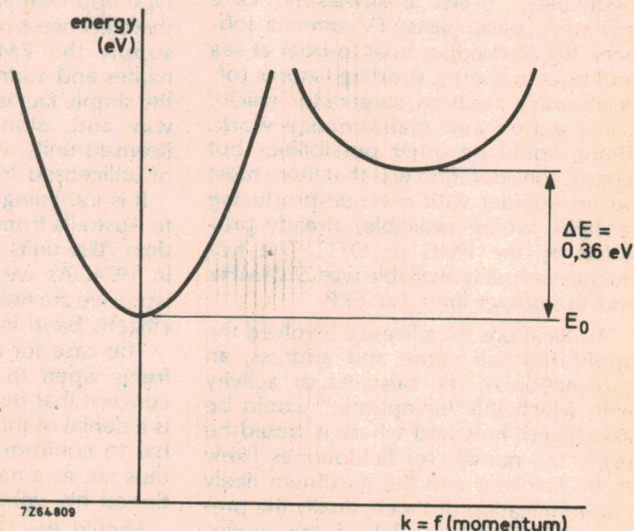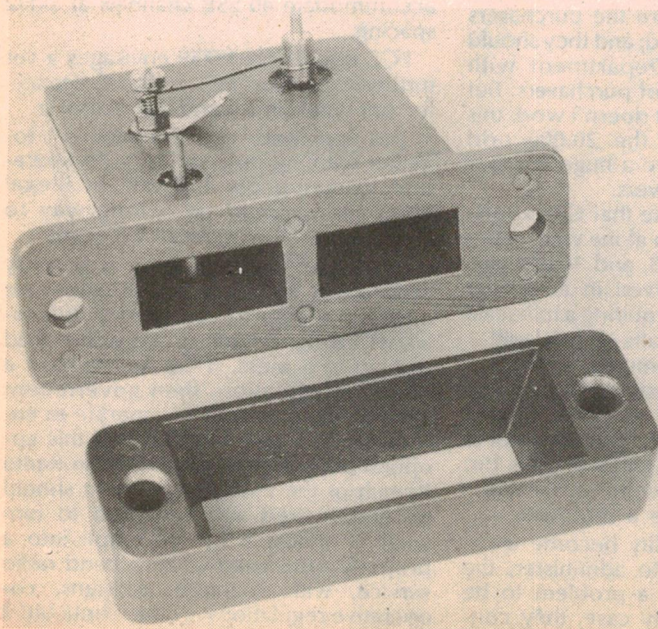*Product engineer with Elcoma, Division of Philips Industries Holdings Ltd.



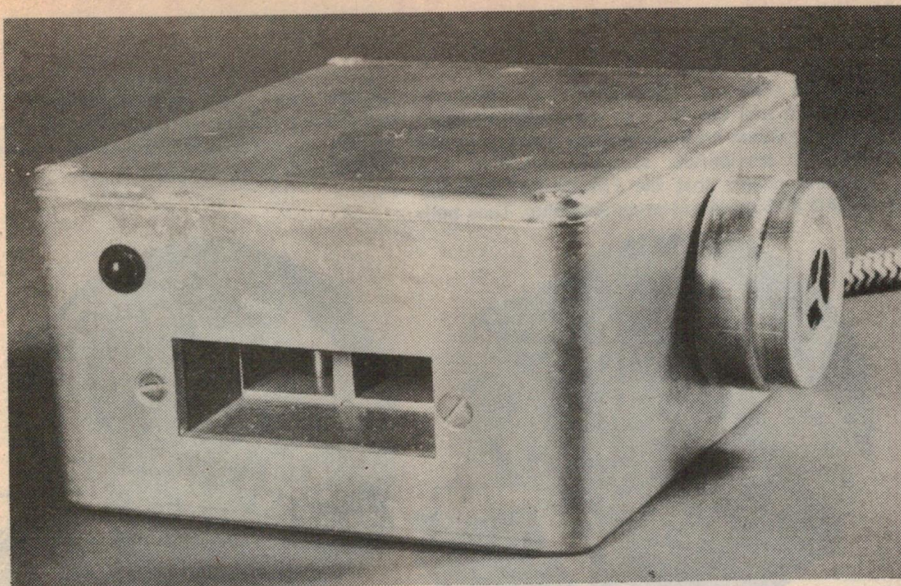At left is the Philips CL8960 X-band Doppler radar module, together with its 5dB gain antenna horn. Fig. 1 (above) depicts the energy band diagram of gallium arsenide.



Use of the CL8960 radar module in a practical situation—the demonstration microwave intruder alarm as built up by Philips Elcoma.

discrete values, which depend on the material itself. When an electron gains sufficient energy, its momentum may change from a low value to a higher value. A change in momentum corresponds to a change in effective mass and a change in mobility.

If the range of energies available to an electron in a particular solid is plotted against the wave vector k (where $k = 2(\pi)/\lambda$, λ being the wavelength and h Planck's constant) the resulting graph is called the energy band diagram for the material. The energy band diagram of gallium arsenide, the material used for the majority of Gunn devices, is shown in Fig. 1.

For electrons having energy of only a little more than E_0 , only the valley corresponding to the lower conduction band is available. If a sufficiently large electric field is applied across the material, some electrons will acquire sufficient energy ($E_0 + \Delta E$) to allow them to attain the upper conduction band. Since here their effective mass is much higher, and mobility appreciably lower, electrons reaching this band will slow down. Thus with increasing applied voltage electron velocity, and therefore current density, decreases, and the material exhibits "negative" resistance.

When a sample of gallium arsenide is biased to beyond its Gunn effect threshold of 3,500V/cm, electrons in the cathode region will enter the upper energy band, the current density will fall, and the electric field across the specimen will be concentrated into a "domain" in the vicinity of the high energy electrons. Since these electrons will be moved across the specimen by the remainder of the field, the domain will migrate at a characteristic drift velocity of about 10⁷cm/sec.

When the domain arrives at the cathode it will collapse, causing the field

strength across the specimen to once again exceed the critical level, and thus form a new domain at the cathode. The current through the specimen under these conditions thus consists of a quiescent DC current with a series of pulses superimposed on it. The frequency of these pulses varies inversely with the time taken for the individual domains to traverse a given specimen. With a drift velocity of about 10⁷cm/sec, this corresponds to about 10GHz for a sample about 10 μ m thick.

The receiving section of a Gunn microwave device consists of either a separate diode mixer, or a combined Gunn effect/mixer oscillator diode. The former type offers superior signal-to-noise ratio performance.

The Gunn diode can be made to oscillate in waveguide, coaxial or microstrip circuits by means of a resonator and DC power supplied through a low pass filter. The condition for oscillation is that the circuit impedance vanishes. A Gunn oscillator thus consists of a Gunn diode, of given "negative" resistance, together with a positive resistance of the same value.

The Philips CL8960 radar module used in the intruder alarm described here is of the separate Gunn oscillator/diode mixer type. Designed to operate at the X-band frequency of 10.687GHz, the CL8960 is supplied complete with a detachable 5dB gain antenna and costs around \$28.00 plus sales tax. Individual devices should be ordered direct from your regular supplier of Philips Elcoma components.

The transmitting section consists of a Gunn diode from the Philips CXY11 family mounted at a distance of one wavelength at the wanted transmit frequency (10.687GHz) away from the short circuited end of a tuned microwave cavity or waveguide. This ensures that the

diode is presented with a small amount of resistive impedance. Power output is typically 8mW when operated from a 7V DC supply.

In order to obtain a small range of frequency adjustment, a small screw is inserted about halfway along the cavity. Adjustment of this screw causes a change in the VSWR (voltage standing wave ratio) of the cavity thus changing the diode loading and causing a small change in operating frequency. This adjustment is preset during manufacture, and should not be tampered with.

The receiving section of the CL8690 consists of a Schottky diode from the BAV46 family. This device is mounted about 1/4 wavelength from the short circuited end of a waveguide cavity similar to the transmit cavity. The transmitter and receiver waveguides are sited together and coupled to a common transmitting and receiving aerial.

As supplied, the CL8960 module comes with a shorting strap between the mixer AF output terminal and earth. The mixer has a low junction capacitance and may be damaged by transients of quite short duration. It is therefore recommended that soldering appliances be isolated from mains supplies and that the shorting strap be left in position until all wiring has been completed.

The microwave intruder alarm system operates on the principle that the reflected RF signal from a moving target undergoes a Doppler frequency shift. In fact, a double frequency shift is observed by the receiver since the target will move in respect to both the transmitter and receiver, which are fixed at a common location. This Doppler shift is a function of the transmit carrier frequency and the speed of the reflecting object. For normal X-band systems (carrier 10.687GHz), a target speed of 1 metre/sec results in a Doppler frequency shift of about 70Hz.

RF energy reflected from a target is fed to the mixer diode where it is mixed with a sample of the transmitted frequency to produce a direct audio output voltage. If the target is stationary, the phase relationship between these two signals will be constant, giving a constant DC output voltage from the mixer. However, the Doppler frequency shift produced by a moving target results in a varying phase relationship between the reflected RF signal and the sample frequency, causing the mixer to produce a varying output voltage signal or Doppler signal.

The way in which the Doppler signal is processed is very much dependent on the personal opinions of the various security companies, as a result of their experiences. The systems may include either analog processing (filtering, level detecting) or digital processing (digital filtering, counting the number of times a given frequency is observed), or a combination of both.

In order to understand the reasons behind the choice of signal processing,

A CALCULATING TRIO

These days just about everyone seems to be using a calculator. The Farad Mini is designed and priced to suit the busy person who wants to keep pace with today's world of figures. Just glance at the features and the price, you'll realise immediately that this is a genuine offer. Why not

show the other two calculators to the men and women in your life. With so many features you'll have no trouble convincing those involved in the scientific disciplines, students, teachers and business people that the FARAD 807 and the FARAD 808 represent excellent value. They both


operate from rechargeable long-life nickel cadmium batteries and all three carry a 12 months manufacturer's guarantee. Instruction booklet with every machine.



Farad Mini II
Ideal for the calculating person

What fun you are going to have with this cleverly designed little calculator. It fits snugly into your pocket and neatly into the palm of your hand. It will do almost everything you want it to. The features include 8 digit red display, floating decimal point, percentage key, true credit balance (minus sign), counting facility, clear key, clear entry key, algebraic logic, division and multiplication keys. There's another cute little idea which helps save the batteries. If you accidentally leave the Mini switched on or you don't press the keys for 15 seconds, it automatically cuts off. Press button D and you're in business again. An instruction book is supplied and the unit is encased in a charming cover.

\$17.65 POST FREE

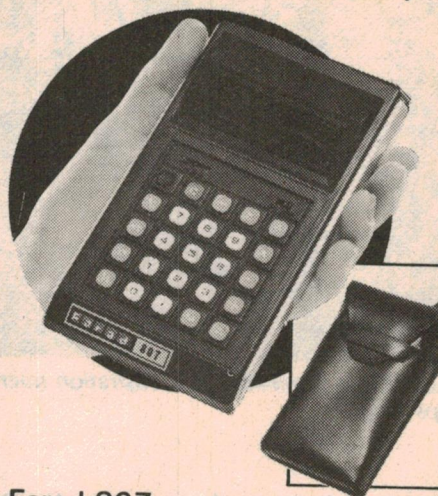


Farad 807
JUNIOR ELECTRONIC SLIDE RULE
Ideal for the businessman and student

Features include: • Large green 8 digit display • Wide viewing angle • Tilted display • Soft touch keyboard • Auto power-on clearing • Selectable full floating, four or two decimal round off, or dollar mode operation • Arithmetic mixed chain and repeat chain calculations • Automatic constant on multiplication and division operations • Negative number, positive and negative overflow, memory and low battery indications • Raising to positive and negative powers (whole numbers) plus squares, square roots and reciprocals • Percentage mark up, discount and percentage of calculations • Full access memory including algebraic calculation and negative and positive accumulation • Memory overflow protection • Charger/adaptor included • Rechargeable batteries included.

Capacity: 8 digits maximum for data entry. 16 digit maximum for results displaying 8 most significant figures. **Power:** DC by two Nicad rechargeable batteries. AC by adaptor/charger unit. **Power Consumption:** Approx. .30 watt. **Dimensions:** Approx. Width 85 mm. Length 155 mm. Height 27 mm. **Weight:** Approx. 210 gm with batteries.

\$44.85 POST FREE

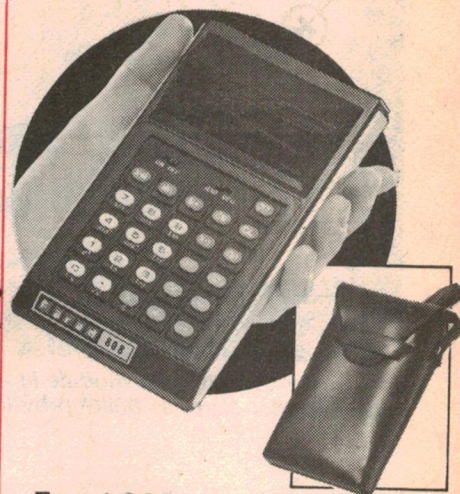

Farad 808
SENIOR ELECTRONIC SLIDE RULE
Ideal for the scientific disciplines and advanced students

Features include: Large green 8 digit display • Wide viewing angle • Tilted display • Soft-touch keyboard • Automatic power-on clearing • Full floating decimal point • Trig, inverse trig, logs, anti-logs, exponential, power, reciprocal, square root and pi functions • Deg or radian mode • Arithmetic, mixed chain and repeat chain calculations • Automatic constant on all four arithmetic operations • Negative number positive and negative overflow, function, low battery and erroneous operation indications • Full access memory including algebraic calculation and accumulation • Memory overflow protection • Charger/adaptor included • Rechargeable batteries included.

Capacity: Arithmetic Operations: 8 digit maximum for data entry. 16 digit maximum for results, displaying 8 most significant figures. Scientific functions: 8 digits maximum for entry. 8 digits maximum for results, with the sixth most significant digit accurate to plus or minus 1 or better. **Power:** DC by two Nicad rechargeable batteries. AC by adaptor/charger unit. **Power Consumption:** Approx. 0.35 watt. **Dimensions:** Approx. Width 85 mm. Length 155 mm. Height 27 mm. **Weight:** Approx. 210 gm with batteries.

\$67.85 POST FREE

HOW TO ORDER: Fill in the coupon below. Print your name and full postal address in block letters. If you are entitled to exemption from Sales Tax, fill in the coupon on the left. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to ELECTRONICS AUSTRALIA Reader Service (Calculators), P.O. Box 93, Beaconsfield, N.S.W. 2014. Cheques should be made payable to ELECTRONICS AUSTRALIA. This offer is open to readers in Australia only. Please allow four weeks for delivery.

SALES TAX (EXEMPTIONS AND CLASSIFICATIONS) ACT

To: The Commissioner of Taxation and The Commonwealth of Australia

I hereby certify that the Calculator/s purchased by me from on.....(date) is for use in.....(Name of University or School) in or directly and essentially in connection with, the production of facts, by means of observing, measuring, testing or otherwise experimenting with material phenomena, for the purpose of proving or illustrating natural principles or laws or in the study of pure or mixed mathematics. Exemption is accordingly claimed under item 63 (1) in the First Schedule to the Sales Tax (Exemptions and Classifications) Act.

Signature of official of University or School.....

Designation.....

Name of University or School.....

Date..... Signature of Student.....

Address of Student.....



Included in the price of the Farad 807 and 808 is a Special Adaptor/Charger Unit. This means you may operate directly from AC mains or recharge your batteries — thus ensuring longer battery life.

Name.....
Address.....
State.....
Postcode.....

Please send me.....(state quantity) Farad Calculator/s.

FARAD MINI II ☐ FARAD 807 ☐ FARAD 808 ☐ (tick appropriate square).

I enclose my cheque, postal/money order to the value of \$.....
Since I qualify for sales tax exemption and have completed the necessary certificate of exemption, I am entitled to the following deduction:

FARAD MINI II \$2.30 — FARAD 807 \$5.85 — FARAD 808 \$8.85, and have made this/these deductions from the prices shown in the advertisement. I enclose my cheque, postal/money order to the value of \$.....

ELECTRONICS AUSTRALIA "CALCULATOR OFFER No. 28/75"

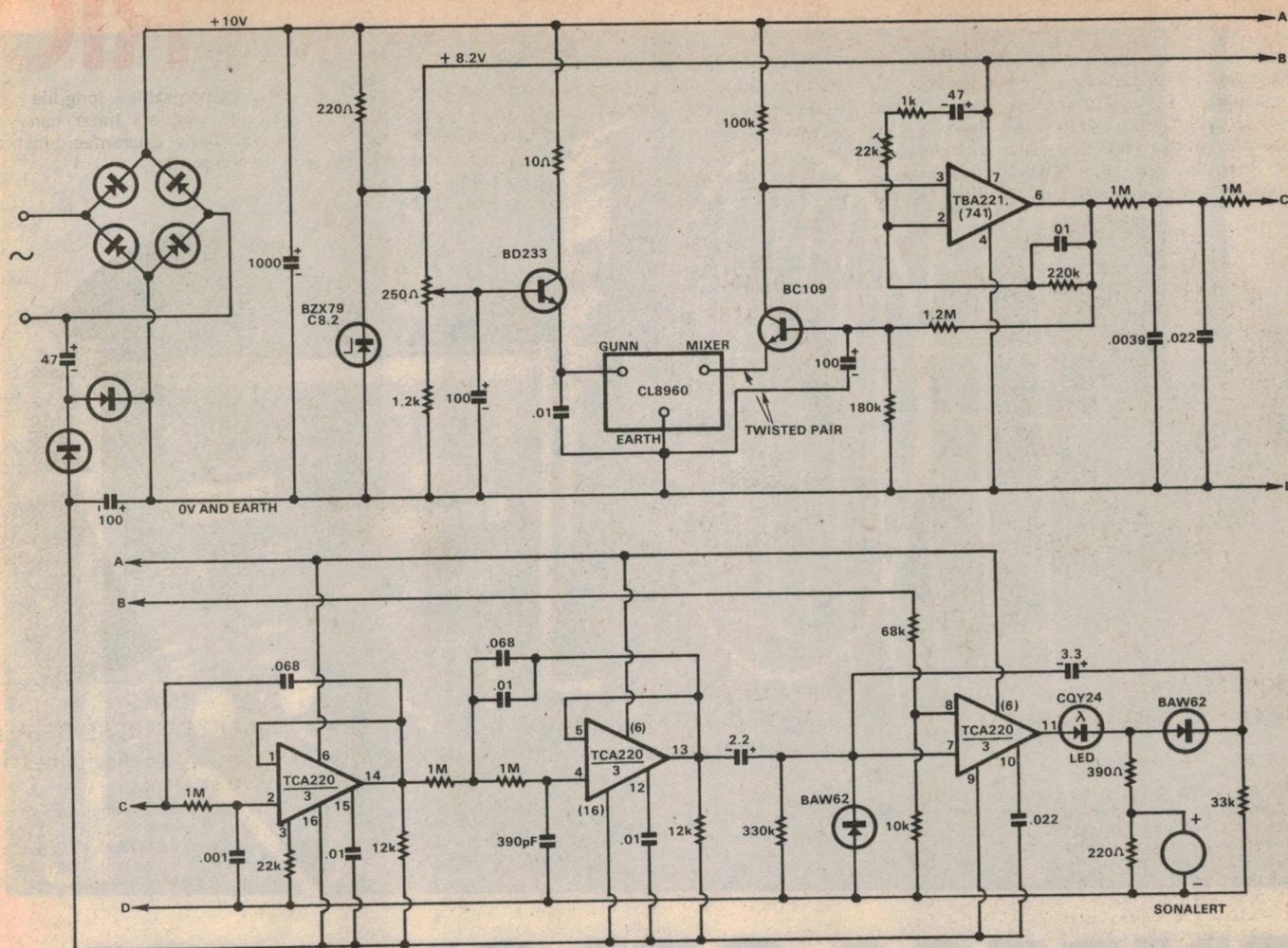


Fig. 2: the circuit diagram of the Philips Elcoma microwave intruder alarm.

it is worthwhile considering the environment in which a radar intruder detector will operate, and those signals which will indicate an intruder.

At first consideration, it would seem that the amplifier pass band should be centred on about 150Hz as this is the Doppler frequency generated by a medium walking pace of about 2 metres/sec (4MPH). However, when one looks more closely at the process of walking it is found that due to the hesitant movements of legs and arms, and swaying of the upper body, the actual Doppler spectrum is centred around 50Hz for a man walking slowly towards or away from the transmitter. This figure is reduced to around 10Hz for similar movement across the radar beam. In both cases, the frequency spectrum extends right down to a couple of Hertz.

Looking next at the sources of interference, one finds that the lower frequency limit is set by the $1/f$ noise generated in the mixer diode and preamplifier. Despite efforts to reduce this interference by special selection of mixer diodes to have low $1/f$ noise close to the carrier frequency (BAV46), and the use of low noise transistors (BC109), it has been found desirable to limit the low frequency response to about 5Hz.

Turning to the higher frequencies, the first major system problem occurs at 50Hz due to gas discharge lamps (fluorescent lights etc). Although their major effect is at 100Hz, due to asymmetrical conduction, they also cause 50Hz signals. Most practical intruder alarms contain circuitry to suppress 50Hz and 100Hz RF interference. Perhaps the simplest system is a low pass filter with a cut-off frequency below 50Hz. However, twin-T filters and complex digital filters are also in use.

It is also necessary to provide some means of controlling the range of a radar protection system, and the most common method is a simple gain control on the preamplifier. This method relies on the fact that the transmitted and reflected signals are each attenuated by 20dB for a 10 times increase in path length. A simple detector system also incorporates a level control to render it insensitive to small objects such as flying insects, etc.

In order to illustrate just how effective simple signal processing techniques can be, Philips Elcoma built up a demonstration unit according to the circuit depicted in Fig. 2. This circuit contains the recommended Gunn diode feed circuit together with a very effective preamplifier, but has only low pass filter-


ing plus level detection to initiate the alarm. Range control uses the simplest method, i.e., gain control.

As such, the design presented here was not originally intended as a practical proposition, although the prototype appears to function quite well within its design limitations. A practical intruder alarm device would probably require battery operation, and would certainly require a more effective alarm system than the Sonalert device used here. However, the basic circuitry is presented, and individual constructors are free to experiment along these lines. We turn now to the circuit details.

DC bias for the Gunn diode is obtained from a sample voltage regulator based on a zener reference diode. A 0.01uF capacitor is connected close to the +7V Gunn diode terminal and the earth terminal to suppress parasitic oscillations in the supply circuit.

A small amount of DC bias is also applied to the mixer diode, in order to increase its sensitivity as a mixer. The total bias under which the mixer operates is 42uA, which is the sum of the applied bias (35uA) and the bias from the coupled local oscillator supply (7uA).

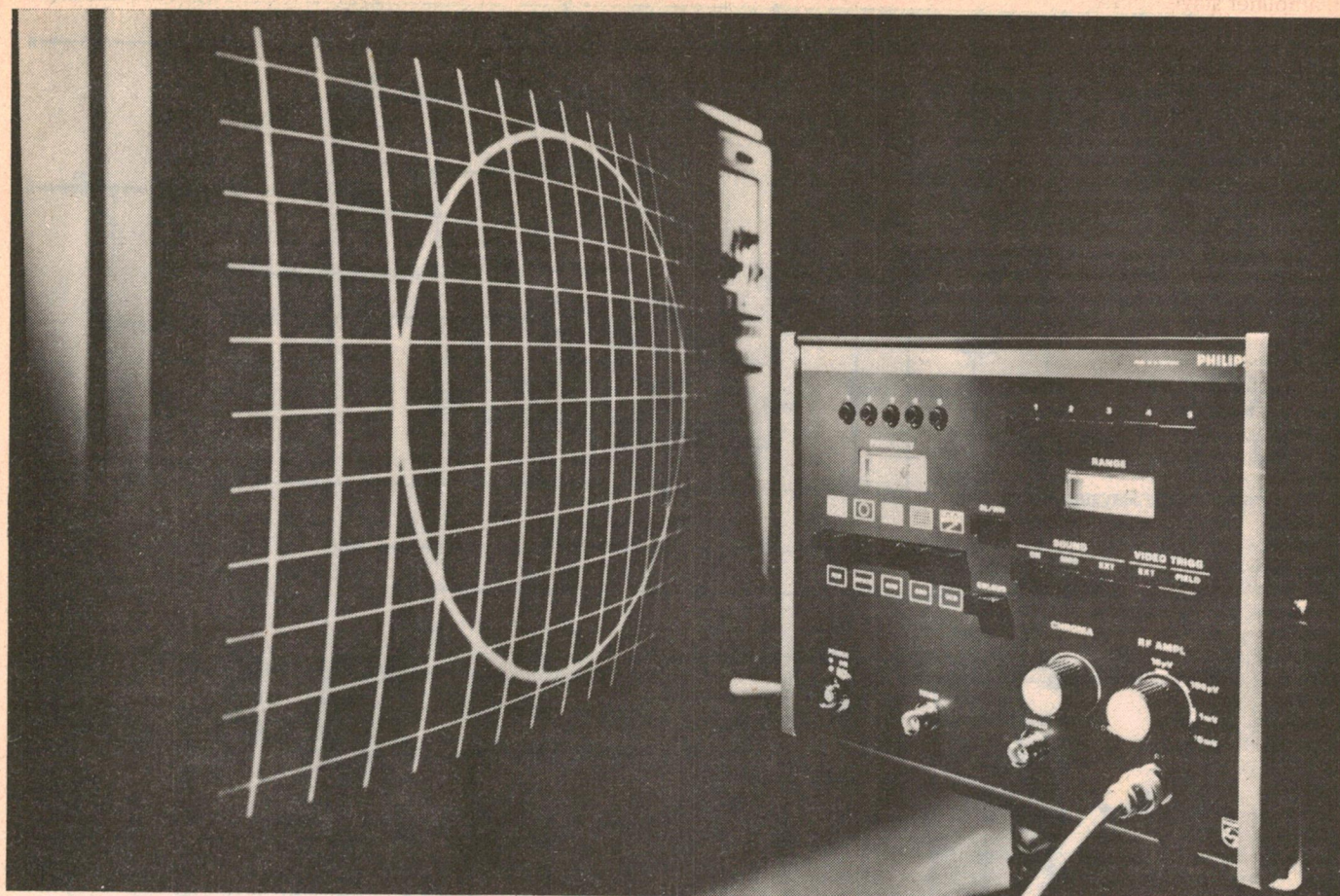Output from the mixer diode is fed into the emitter of a BC109 transistor



PM5509 COLOUR T.V. PATTERN GENERATOR NOW AVAILABLE EX STOCK.

For immediate delivery, contact:
Test & Measuring Instruments Dept.
Philips Scientific & Industrial Equipment
200 Goulburn Street, Darlinghurst 2010.

or phone Sydney 2 0223, Brisbane 44 2471, Canberra 95 0321,
Melbourne 69 0300, Adelaide 223 4022, Perth 21 3131, Hobart 28 0121.

PHILIPS

38.2467



preamplifier stage operating in common base configuration and providing a gain of 100. This stage is direct coupled to a Philips TBA221 (equivalent to 741) operational amplifier, the gain of which can be varied from 10 to 200 times by means of a 22k trimpot.

From here the signal is fed to a fifth order Chebyshev low pass active filter ($\frac{1}{3}$ TCA220) with nominal unity gain in the pass band, 3dB attenuation at 25Hz, and 50dB attenuation at 50Hz. The filter values were taken from the design tables for the TCA220 triple operational amplifier.

The remaining amplifier in the TCA220 is used as a simple level detector with monostable action and a hold time of about 3 seconds. As shown in the circuit, this amplifier is used to drive a LED and a Sonalert alarm device.




Because the demonstration unit is mains operated, a negative supply rail was included to simplify IC biasing. However, a practical unit would probably need to operate from a single 12V battery supply rail, and may need artificial centre point generation to bias the filter IC. Negative supply rail voltage in the demonstration unit is of the order of -10V.

The prototype unit was constructed on Veroboard and mounted in a standard diecast metal case as pictured. Constructional details are left to individual constructors, as are the power supply details and any circuit modification required for a more practical alarm system.

In practice, the demonstration unit has an adjustable range of between 2 and 9 metres, which agrees quite well with the theoretically calculated values. Greater range is best obtained by means of higher gain antennas, although this could also be achieved by increasing the amplifier gain. The theoretical range limit which gives a 20dB signal-to-noise ratio Doppler signal is around 15 metres when using the 5dB gain aerial supplied with the CL8960.

Designs are available for a 14dB gain antenna which provides an approximate three fold increase in range at the expense of a narrower beam angle. Beam dimensions are about 60° x 60° when using the 5dB antenna supplied, and about 50° x 24° when using a 14dB gain antenna. Polar diagrams of the free space radiation pattern for these two antennas are shown in Figs 3 & 4.

If, for environmental reasons, it is considered desirable to cover the antenna aperture, it is recommended that a thin plastic material (approximately 0.25 mm thick) be fixed to the metal plate with adhesive. Note however that this will result in an increase in the level of reference signal fed to the mixer from the Gunn diode, increasing the mixer bias current to approximately 60uA. The result will be an increase in AF output voltage for a given target, accompanied by a degradation in the signal-to-noise ratio. This should be acceptable for most

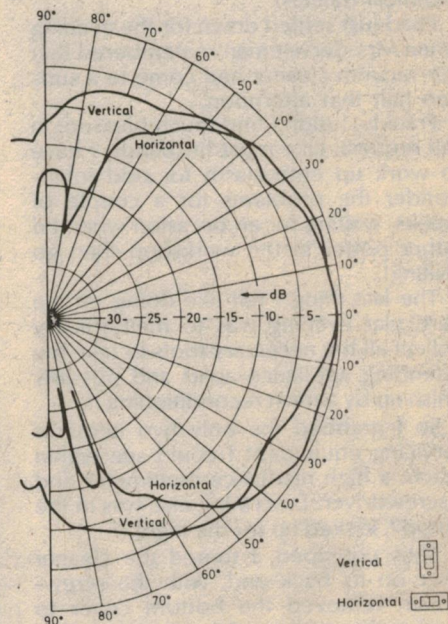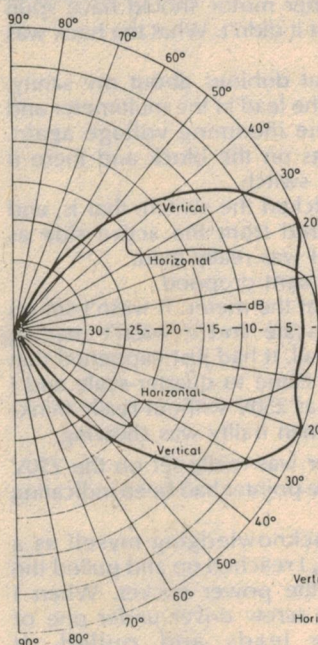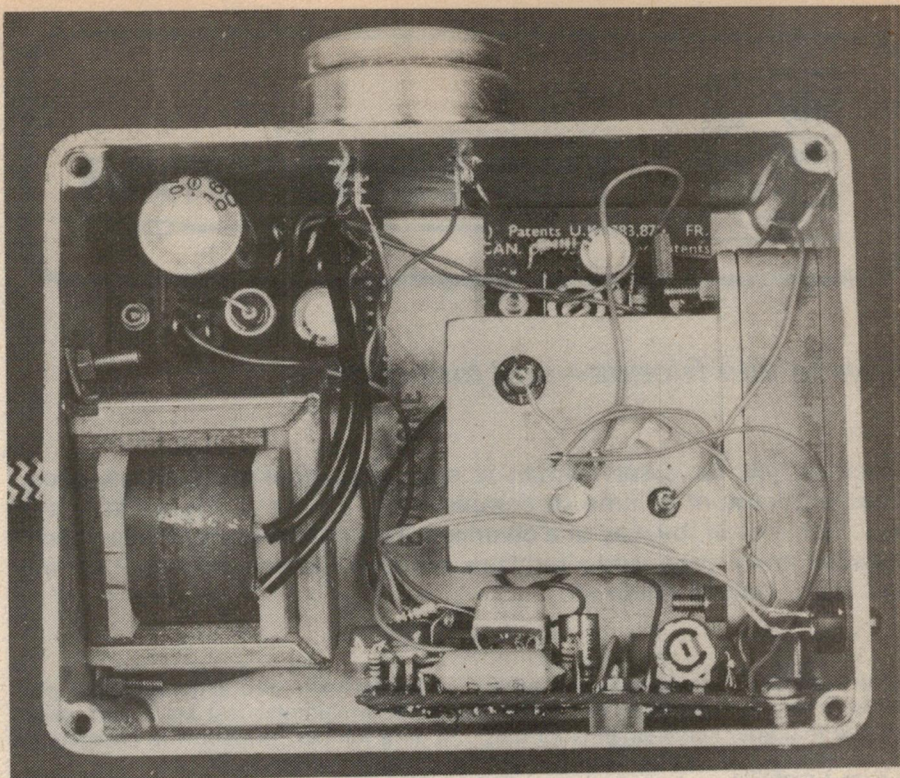

At top is an interior view of the microwave intruder alarm. Fig. 3 (above left) and Fig. 4 (above right) are polar diagrams depicting the free space radiation patterns of the 14dB gain antenna and the 5dB gain antenna respectively.


applications.

The use of other materials in this role will only serve to further degrade the signal-to-noise ratio and upset the operating conditions of the module. Their use should therefore be strictly avoided.

The intruder alarm unit described in the preceding paragraphs is intended to illustrate just one possible area of application for the CL8960 radar module. As indicated in the introductory paragraphs, a range of other possible applications

exists. To recapitulate briefly, these include speed measurement, range measurement, vibration measurement, and process control. Extension of the range measurement principle, to provide a measurement of range from two discrete modules appropriately located, can provide target location information.

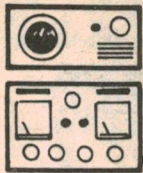However, it is beyond the scope of this article to give detailed design criteria for these application areas. Circuit details are left to those constructors possessing the necessary design experience.



The Serviceman

How to win friends—and lose money!

The ideal job for a serviceman is one which makes him look good, takes a minimum of time to complete and shows a tidy profit at the end. This month, by way of a diversion, I recount two situations which, between them, produced a red face, hours of talking and circuit tracing and not a cent of income!

The "red face" situation was a purely domestic one which will serve to demonstrate that your serviceman is a mere mortal, with a full share of human and technical frailties!

I had just settled down for the evening when Mrs. Serviceman remembered that her vacuum cleaner had come to a sudden halt that afternoon.

Frankly, I didn't find much pleasure in the request. Like most husbands, I have to work up enthusiasm for odd jobs—ponder the problems for a couple of weeks, waiting for an occasion when I'd rather potter in the workshop than go visiting!

The last thing I felt like doing on the particular evening was to methodically collect all the necessary tools to take the offending appliance apart and possibly finish up by almost reconditioning it.

So I grabbed the only two items of servicing equipment I could see within reach: a high resistance multimeter and a screwdriver. Everything else was in the "shop", locked up for the night.

Thus equipped, I turned the cleaner over on its back and, with the screwdriver, removed the bottom cover to expose the wiring and the foot-operated on-off switch.

I plugged the cleaner into the power point, turned it on and reached for the multimeter. Flicking around to the high voltage AC range, I measured across the incoming mains leads, which terminated at an insulating block. To my disappointment I got a quarter-scale reading—250V on the 1000V AC range.

Curses! I had hoped that the trouble would simply be an open power lead.

Next step was to check at the foot-operated switch. On one side I could measure volts; on the other side there were none, no matter how many times I operated the switch.

Curses again! I was faced with a faulty switch, which I couldn't replace on the spot because it was a special type.

Just to make sure of things, I took one of the multimeter test leads and, using it as a jumper, bridged the contacts of the faulty switch.

The cleaner motor should have spun into life, but it didn't. What the heck was going on?

Somewhat dubious about my sanity, I replaced the lead in the multimeter and checked the incoming voltage again. There it was on the block and there it was on the switch.

Until I clicked the switch, that is, and it disappeared from the active side as well! Now I was really mad.

Then the cent dropped.

I looked at the meter. It wasn't set on the 1000V scale and it wasn't reading 250V AC at all. It had just happened that the pointer came to quarter-scale and I had read it as 250V without really thinking. My human frailty was showing.

The meter was really set on the 250V scale and the pointer had been indicating about 80V.

Silently acknowledging myself as a dumb cluck, I reached up and pulled the plug from the power socket. When I hooked the screw driver under one of the active leads and pulled, it "stretched", or at least the rubber insulation did. The wire was broken in the most obvious place, just as it looped into the power plug.

Why the 80VAC reading?

Simply because there was enough capacitive coupling across the break to provide the very small amount of current necessary to deflect the multimeter.

Remember that I said it was a high resistance type?

The meter showed a reading whenever there was nothing else across the flex. The moment I closed the footswitch and connected the motor across the flex, the voltage disappeared.

The moral is simple: Next time you have to check an appliance, do it prop-

erly. Either use a lower resistance voltmeter or disconnect the appliance from the mains together and trace things through by measuring continuity and resistance. I have yet to see a stray capacitive path big enough to trick a DC measurement!

Red face? Well, it was a private sensation. I must have looked every inch a professional as I prodded around inside the cleaner with a multimeter and a puzzled frown. Why admit that I could have done the job much faster if I'd simply used the screwdriver in the first place to check the plug!

Perhaps the second story makes up for it, in a way, because I was able to correct an obscure fault without ever laying a hand on the equipment concerned. But the episode was notable for the time it took, and its lack of financial yield!

It began when a friend bought an electronic organ, of which he was duly proud. I gather that it was a slightly ageing design, but a good one, and he felt that he had got more than his money's worth.

But, one day, he expressed to me the conviction that the bass pedals seemed to be losing some of their punch. He had to advance the pedal volume control more to get the same level and, in addition, the response of the pedals seemed to be "a bit sluggish". Could I pop in and have a look at it some time?

Frankly, I needed to "pop in and have a look" about as much as I needed the usual hole in the head. I could imagine that, by the time I had picked my way through the circuit, found out how it all worked and where it was located in the organ, and then tried to work out what might be wrong, it would have been time for next morning's breakfast!

So I didn't encourage the idea, and weeks went by with my friend still presumably unhappy with his bass pedals.

It must have been months later that he made the next relevant observation: "Funny about that organ, but the bass seems okay again; just like it was when I bought the organ."

I gave a grateful grunt of satisfaction, though without too much conviction. I have been much too long in the electronics game to be easily convinced by faults that cure themselves.

And, sure enough, some months later, he was back on the old theme: the bass seemed down in level and sluggish, just as it had been on the previous occasion. Another "funny thing": he had noticed that it seemed normal enough at first switch-on, but deteriorated within the first few minutes of playing. It was a new piece of information and it gave me a possible clue.

I asked: "Does the organ use germanium transistors?"

"Transistors, yes. Germanium, I wouldn't know. Why do you ask?"

I explained that it could be a temperature effect, since germanium transistors in particular tend to change their characteristics with rising temperature.

And, as we chatted, we realised that he had bought the organ in the winter season. When he first noticed the loss of bass, it would almost certainly have been summer. Then it came right again—next winter—and now it was starting to misbehave as the warmer weather set in.

I felt quite proud of my powers of deduction, and even offered to have a look at the circuit and see whether I could pick out the offending stage.

At this point my friend suggested that the circuit might be "a bit complicated". He pointed out that, when you pressed a bass pedal, the organ played that note. But it had a "pedal sustain" system that would keep the note playing for a while after you took your foot off the pedal. But if you played another pedal shortly afterwards, it would cut the note that was being sustained, play the new note and sustain that!

Anyway next morning, over a cup of tea, I decided to take a quick look at the circuit, which he had dropped in.

Quick look indeed! There were multiple contacts to select notes, to bias transistors on, and bias transistors off; flip-flop frequency dividers, time constant circuits, and so on. You name it, it was there. Even the biasing arrangements of the transistors seemed completely crazy. So I gave it away until late that evening when Mrs Serviceman and the kids were safely in bed.

This circuit wasn't going to beat me if it took me till midnight to work it out. And it did just that!

Laboriously I figured out what would happen to this transistor and that as any given bass pedal was depressed, and released. I worked out the sustain circuit—a charged capacitor which kept a transistor gated on for a while, unless you depressed another pedal and discharged it abruptly.

And the queer bias? I realised that the pedal circuit was being fed with square waves from the generators in the main body of the instrument. The pedal circuitry simply had to pass a square wave of the required frequency, to be filtered or "voiced" later. The transistors therefore didn't need to operate as linear amplifiers. If they were overdriven and tended to square the already square wave input, what did it matter?

In fact, this realisation exonerated most of the circuitry from possible blame in regard to the changing signal level. The pedals were certainly selecting the right note and, in due course, it passed through a series of flip-flop frequency dividers to produce the necessary 4', 8' and 16' tones.

And, flip-flops being what they are, the output would be unlikely to vary unless with a variation in the supply voltage—and this could readily be checked.

But wait: Following the signals through, I realised that they did pass through one final stage which was subject to the keying or gating bias.

And here I struck oil. As I looked at the circuit, I realised that the gated transistor was virtually the bottom half of a signal voltage divider. When the transistor was turned on, and bottomed, virtually no signal would get through. When the bias was removed, and the transistor ceased to conduct, the divider would pass most of the signal to the amplifier.

What if that very obviously germanium transistor warmed up? Well, with zero bias, it would still conduct to some extent and attenuate the signal. And it could also have an effect on some of the time-constant skulduggery that was associated with it.

So, as the clock struck midnight, I reckoned I had found the culprit.

I was tempted to ring my friend there and then, as some kind of rough justice, but charity prevailed. Instead, I rang him next day and explained my theory, suggesting that he locate the particular circuit board and, if possible, the particular transistor. He could then put a weight on a bass note, wait till it faded down, and direct air from a fan on the board to see what happened.

In fact, I offered to lend him an output meter, if he called round, so that he wouldn't have to rely on his ears.

So it was, equipped with an output meter and a household fan, he duly attacked the job.

And with success!

He rang me later to say that, with the back off the organ and the fan playing on the board, the bass remained steady.

In fact, the circuitry was so sensitive that, even a finger resting on the metal can of the particular transistor would keep it cool enough to maintain the bass level. Yes even a warm finger!

The blade of a screwdriver had the same effect. What could he do to avoid the necessity for using a fan, or a finger or a screwdriver?

So, over the phone, I told him how to fashion a springy heat sink which he could clip on to the offending transistor, taking care that it did not contact any other part of the circuit. This he did—and played happily on the organ through the rest of the summer.

In fact, I gather that the word has since got around to owners of similar organs. It must have been a quite marginal effect, because some of them suffered with it to some extent, others not at all. It was all a matter of residual leakage of typical germanium transistors in the Australian summer.

But, apparently, the little heat sink did the trick in all cases.

So there you are: a "remote" service job that took a couple of years to complete and made happy the owners of at least three electronic organs.

And my reward? A grateful friend and no "bread"!

Know Where You are Going

Choose a career in the field of Electronics — the Nation's most progressive and fastest expanding industry.

Advancement in this modern science demands technical ability, a sound knowledge of basic principles and applications. *You can master the subject by training at the Marconi School, and be ready to grasp the opportunities that occur in the various branches of Radio Technology.*

BROADCASTING

A thorough grounding is available to students in the broadcasting field, leading up to the P.M.G. Broadcast Station Examination.

COMMUNICATIONS (Marine)

An extension to the Broadcast Operators course and extending into the fields of Navigation Aids and Electronic Devices used in mobile communications as required by the P.M.G. Certificates of Proficiency.

APPLIED SERVICING

Comprehensive training in the maintenance and repair of radio and television receivers offers substantial rewards to competent technicians. Marconi School training covers all aspects of radio and television receiver circuit applications, practical exercises in fault finding and alignment procedures.

The Marconi School Radio Servicing correspondence course is approved by the N.S.W. Apprenticeship Commission

*Classes are conducted at:
67 Lords Road, Leichhardt.
Day: 9 a.m. to 4 p.m.*

*Evenings: 6 p.m. to 8.30 p.m. or
by Home-Study Courses (except
practical instruction on equipment).*

SEND FOR PROSPECTUS

There is no obligation

.....

NAME.....

ADDRESS.....

.....

.....

.....

.....

A full ASCII-type input keyboard for EDUC-8

Continuing the description of suitable peripheral devices to interface with his EDUC-8 microcomputer project, the author here gives details of a full alphanumeric input keyboard unit. The logic is capable of fully encoding all 128 characters of the standard 7-bit ASCII code.

by JAMIESON ROWE

Although the simple 16-key input keyboard unit described earlier is likely to be adequate for many purposes, there will no doubt be some constructors who will want to provide their EDUC-8 microcomputer with a full typewriter-style keyboard unit. Apart from offering increased communication flexibility and convenience, a full keyboard also allows you to work with programs requiring full alphanumeric input, such as symbolic editors, assemblers and compilers.

With this in mind I have developed a design for a full ASCII-type input keyboard, which will be described here.

The logic circuit has been designed to work with any keyboard assembly having the required number of switches, providing these can be used as SPST or "form A" switches (normally open, but closed when the key is pressed). The switches need not be bounceless, as the logic will cope with any normal amount of contact bounce.

I have built up the design and checked it out with a surplus keyboard switch assembly, typical of the type available in obsolete key-punch equipment. This type of keyboard is likely to be that most accessible to you, at reasonable cost. Providing the switch contacts are in reasonable condition, such a keyboard should be quite suitable, although most will need a thorough dusting, lubrication and treatment with contact cleaning fluid before use.

You can, of course, elect to wire up the keyboard using a new keyswitch assembly, of which a number are available—at an appropriate price. For example General Electronic Services (99 Alexander St, Crows Nest, NSW

2065) can supply a 56-key keyboard assembly made by Mechanical Enterprises, Inc., of Virginia. Designated type AA-L2-R2, it has gold contacts, an 8-keylength space bar, and two 1½-keylength shift keys. The price is approximately \$130.

A new keyswitch assembly will undoubtedly give you a better looking keyboard, and ultimately greater reliability. However, as the cost of a surplus keyboard is unlikely to cost you more than about \$10-20, there is a considerable cost incentive in "making do" with one of these.

The keyboard unit shown in the pictures is from the same surplus keypunch station which provided the Welmec reader and punch units previously described. It is fairly typical of the sort of keyboard switch assembly you are likely to obtain from such sources, solid in construction and still quite serviceable despite many years of work.

The keyboard logic presented here is capable of encoding all 128 characters of the standard 7-bit ASCII code, in contrast with some of the alphanumeric keyboard designs published elsewhere. In addition, the logic incorporates reverse shift mode encoding, for those keys where this is normally used.

Incidentally, if you've forgotten what the acronym "ASCII" stands for, it is the American Standard Code for Information Interchange.

For the benefit of those not too familiar with the ASCII code, it is shown in Table 1. As you can see, the 128 characters are arranged in eight columns, each column having 16 rows. The 16 row positions are defined by the four least significant bits of the code, bits 0-3, while the three remaining bits are used to define the


columns. Each one of the 128 character cells in the array is therefore defined by a unique combination of the 7 encoding bits.

Columns 2, 3, 4 and 5 comprise the printing characters normally used on teletypewriters and printers (such as the Philips 60SR printer, for example). These columns include all of the upper-case alphabetic symbols, the decimal numerals, and all of the commonly used punctuation marks. The 64 characters concerned are often considered as a distinct sub-set of the full 128-character code, known as "6-bit ASCII".

As far as keyboards are concerned, the characters in columns 4 and 5 are normally provided with keys of their own, while those of columns 2 and 3 are usually arranged to share common keys, with a "shift" key used to change the encoding and distinguish between one column and the other. Usually the characters in column 3 are the "normal" characters for these keys, and those in column 2 the "shift" characters—except for the character pairs in rows 12, 13, 14 and 15. These usually follow the reverse convention, with comma, minus, fullstop and oblique the "normal" characters and their corresponding characters the "shift" equivalents.

This special treatment of the four keys concerned tends to complicate the logic, as we will see shortly. However it has apparently become standard because of the greater use normally given to the four characters in column 2, compared with those in column 3. It would be a nuisance having to press the shift key every time one wanted a comma or fullstop, for example.

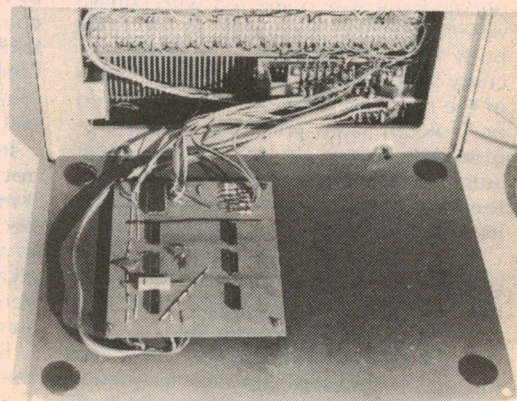Columns 6 and 7 of the table comprise the lower case alphabet and some infrequently used symbols and control codes. Many keyboards do not provide for these codes to be generated, apart from "del" (delete or rubout) and perhaps "alt mode". This is because lower case characters are not necessary in most communication, and are not even available on many printers. For




At left is the prototype keyboard unit, which is built inside the case of a surplus keypunch keyboard. The view above shows the logic board, mounted on the bottom plate of the case.

TABLE 1: ASCII CHARACTER CODE

								0	0	0	0	1	1	1	1
								0	0	1	1	0	0	1	1
								0	1	0	1	0	1	0	1
B 6	B 5	B 4	B 3	B 2	B 1	B 0	COLUMN → ROW ↓	0	1	2	3	4	5	6	7
			0	0	0	0	0	NUL	DLE	SPACE	0	@	P	\	p
			0	0	0	1	1	SOH	DC1	!	1	A	Q	a	q
			0	0	1	0	2	STX	DC2	"	2	B	R	b	r
			0	0	1	1	3	ETX	DC3	# (£)	3	C	S	c	s
			0	1	0	0	4	EOT	DC4	\$	4	D	T	d	t
			0	1	0	1	5	ENQ	NAK	%	5	E	U	e	u
			0	1	1	0	6	ACK	SYN	&	6	F	V	f	v
			0	1	1	1	7	BELL	ETB	'	7	G	W	g	w
			1	0	0	0	8	BACK SPACE	CAN	(8	H	X	h	x
			1	0	0	1	9	HOR. TAB	EM)	9	I	Y	i	y
			1	0	1	0	10	LINE FEED	SUB	*	:	J	Z	j	z
			1	0	1	1	11	VERT. TAB	ESCAPE	+	;	K	[k	{
			1	1	0	0	12	FORM FEED	FS	,	<	L	\	l	}
			1	1	0	1	13	CARRIAGE RETURN	GS	—	=	M]	m	} (ALT MODE)
			1	1	1	0	14	SHIFT OUT	RS	.	>	N	^ (†)	n	~
			1	1	1	1	15	SHIFT IN	US	/	?	O	—	o	DEL (RUB OUT)

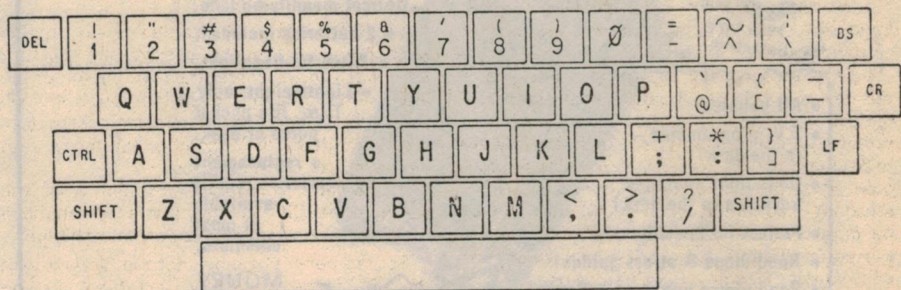Above is a table showing the 128 characters of the 7-bit ASCII code, with their coding. At right is the standard keyboard format used for this code.



the same reason it is usual for the upper case characters to be the "normal" characters, with the lower case characters in columns 6 and 7 encoded by using the shift key—just the opposite of the convention used with typewriters.

The characters in the remaining two columns, columns 0 and 1, are known as the non-printing or "control" characters. These are used to indicate changes in encoding mode, to control printer formatting, and for other facilities which may need to be controlled by "transparent" character codes—distinguishable from printing characters.

Generally most of the codes in columns 0 and 1 are generated using a "control" key, which acts rather like a second shift key. Any desired code in column 0 is generated by pressing the control key in conjunction with the key in column 4 corresponding to the desired row code. Thus "form feed" may be generated by pressing "control" and "L", while "horizontal tab" is equivalent to control-I.

In some cases special keys are provided for column 0 character codes, because they are used fairly frequently. This is generally done for "carriage return", "line feed", "back space" and "bell"—the last of these being used to activate the signalling bell of a teletypewriter.

The codes in column 1 are normally generated by using the control key in conjunction with the keys for columns 3/2, although some teletypewriters provide a special key for "escape".

Note that the characters in the ASCII code are not completely rigid, with certain codes

being used to represent two different characters on occasion. Thus the character in row 3 of column 2 is generally the "number" sign on American equipment, but the "pound" sign on machines of UK origin. Similarly the code in row 13 of column 7 is sometimes used to represent "wiggly closing bracket", and sometimes the non-printing control key "alt mode".

All of the character codes shown in the table may be generated using the logic circuit which will now be described. As many special keys as desired may be used to generate column 0 and 1 codes, depending upon the number of keys available on the keyboard you use. The remaining codes may be generated using the control key. Similarly the shift key may be used to generate the characters in columns 6 and 7, although "del" may be provided with a special key if you so desire.

As you can see from the circuit diagram, the main alphanumeric keyswitches are wired in an array, whose rows and columns correspond to those of columns 2, 3, 4 and 5 of Table 1. There are 16 "row" keylines, and three "column" keylines—two of which correspond directly to columns 4 and 5 of the table, while the last corresponds to both columns 2 and 3 (which use common keys).

At the heart of the encoding logic is an IC specially designed to perform keyboard encoding. This is the HD-0165, made by Harris Semiconductor in the USA. It is available on order through your usual parts supplier, from the local agents for Harris, Cema Distributors Pty Ltd of 21 Chandos Street, Crows Nest, NSW 2065. At the time of writing it costs about \$9, but performs a job which would otherwise involve many diodes, transistors and ICs.

The HD-0165 is a 16-line to 4-line binary encoder, which also generates both a "strobe" or "key pressed" signal and a "rollover" or "more than one key pressed" signal.

As you can see from the circuit, the HD-0165 is used to perform the basic encoding of the four least significant bits. As this corresponds to the row encoding for Table 1, its 16 inputs accordingly connect to the 16 "row" keylines of the keyswitch array.

Encoding of the remaining three bits of the ASCII code is performed by the logic circuitry involving gates G6, G7, G10-12, and inverters I1-6, using signals derived from the "column" keylines. The actual column keyline signals are generated by PNP transistors T1, T2 and T3.

amazing MAGNA-LITE®

lets you focus on
fine detail regardless
of lighting!

magnifier flashlight



**Illuminates and magnifies
whatever you are viewing!**

What a useful combination!
A concentrated light beam and
magnifier all in one! So compact
it fits in your hand, pocket,
purse or glove box.
Precision made in the United
States, amazing Magna-Lite
is yours for just \$5.95!
With a money back
guarantee! Hurry while
shipment lasts! Mail
no-risk coupon today!

- Optical magnifying lens.
- 2 batteries included.
- Powerful flashlight.
- Lightweight, only 1½ oz. fits pocket purse or desk.
- replacement batteries readily available at most chemists.

**MONEY
BACK
GUARANTEE**

HOW TO ORDER: Fill in BOTH sections of the coupon. In each section print your name and full postal address in block letters. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to Electronics Australia, Reader Service (Magna-Lite) P.O. Box 93, Beaconsfield, N.S.W., 2014. Cheques should be endorsed on the back with senders name and address and made payable to Electronics Australia. This offer is open to readers in Australia only.

CLIP COUPON — MAIL TODAY!

Name	
Address	
State	Postcode
Electronics Australia Magna-Lite Offer No. 36/75	
Name	
Address	
State	Postcode
Please send me (state quantity) Magna-Lite/s. I enclose my cheque, postal/money order to the value of \$	

EDUC-8 computer

These are wired so that when any of the keys in the associated keyline is pressed, the resulting input current drawn by the HD-0165 passes through the base-emitter junction, turning the transistor on.

Further logic signals are generated by the "shift" keyswitch, and the "control" keyswitch. Special keys such as "carriage return", "line feed" (LF), "back space" and "bell" are arranged to have the same effect as if the control key were pressed along with the corresponding column 4 alphabetic key, by means of diodes D3-D10. Thus D3 and D4 ensure that the carriage return key generates the "control" and "M" signals, as well as causing T3 to conduct.

As the "space bar" key is equivalent to "shift-0", diodes D1 and D2 are used to achieve a similar result when this key is pressed. Here the key causes activation of the "0" input of the HD-0165, generation of the "shift" signal, and conduction of T1—all three of which are needed to achieve the same result as shifted zero.

The actual encoding for bit 4 is generated at the commoned outputs of gate G6 and inverter I3. These are both open-collector elements, with their outputs tied together to achieve a wired-OR function. Similarly the bit 5 encoding is generated at the commoned outputs of G7-I4, and the bit 6 encoding at the commoned outputs of I5-I6.

The inputs of these elements are fed with the column keyline logic signals from T1, T2 and T3 together with the control and shift keyline signals, to achieve the correct encoding. For example I4 is fed with the control keyline signal, to ensure that bit 5 is false (0) whenever the control keyline is activated—corresponding to a column 0 or 1 character. Gate G7 is fed with the inverted shift keyline signal from I1, together with a wired-OR combination of the column 4 and 5 keyline signals from T3 and T2, so that bit 5 is again made false whenever a column 4 or 5 key is pressed without the shift key.


Similarly I5 and I6 are fed with the column 2/3 keyline signal from T1, and the control keyline signal, respectively, which ensures that bit 6 is false whenever a key or key combination corresponding to a character in columns 0, 1, 2 or 3.

Inverter I3 is fed with the column 4 keyline signal from transistor T3. As columns 0 and 7 are equivalent to column 4 characters combined with either the control or shift keys, this automatically ensures that bit 4 is always false for all column 0, 4 and 7 characters.

The signals fed to gate G6 are used to obtain the correct bit 4 encoding for columns 2 and 3. Because of the inverted shift mode operation of the row 12, 13, 14 and 15 keys, this is a little more complex than it might otherwise be. What must occur is that for the rows 0-11 keys, bit 4 must be false when the shift key is pressed, while for the rows 12-15 keys bit 4 must be false if the shift key is NOT pressed.

This is achieved by using gate G9 to monitor the bit 2 and bit 3 outputs from the HD-0165, so that its output is low whenever both these

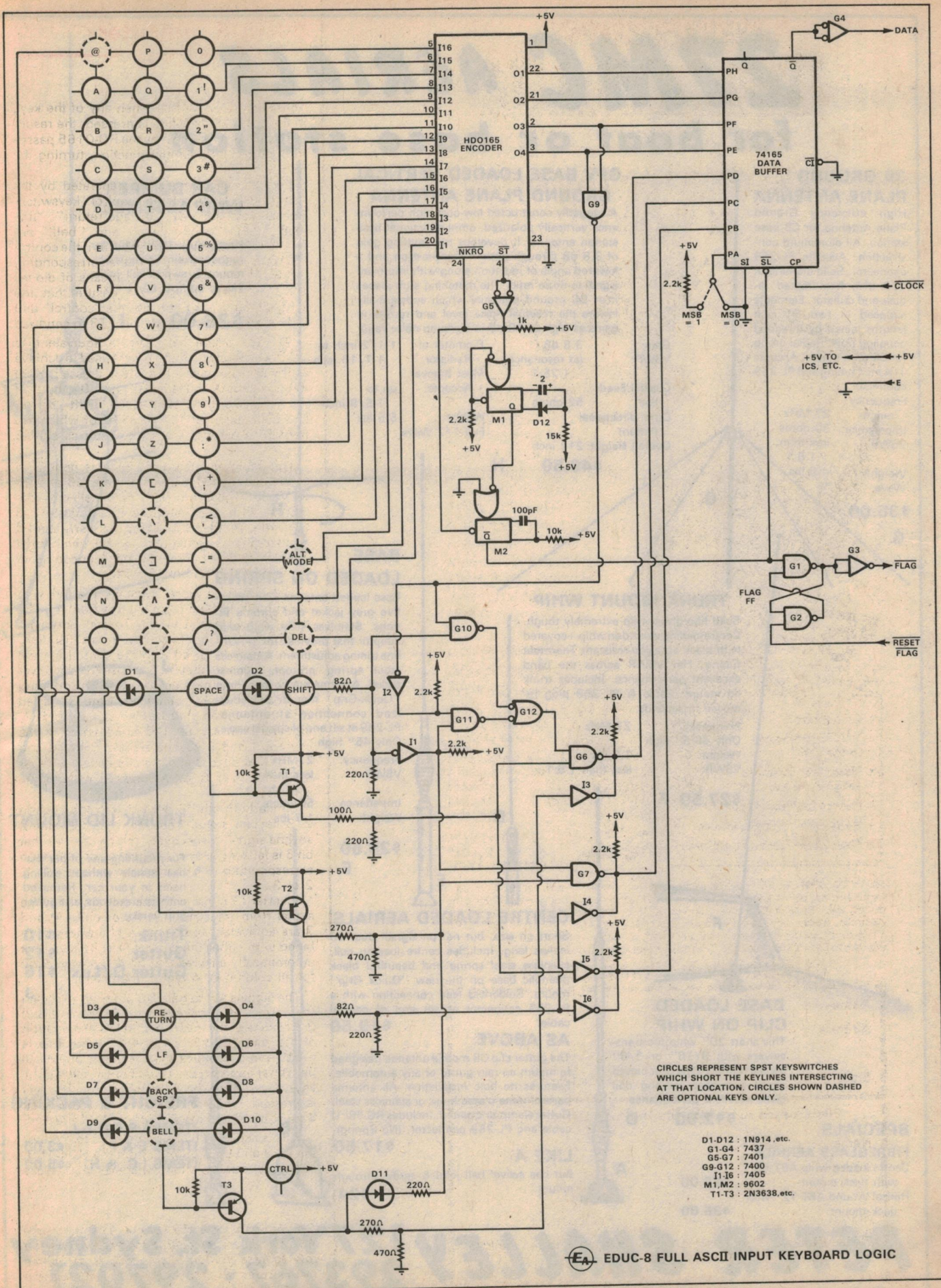Shown opposite is the complete circuit of the ASCII keyboard encoder. Encoding of the 4-bit row address portion of the code is performed by the Harris HD-0165 16-line to 4-bit encoder IC, at top centre.



CIRCLES REPRESENT SPST KEYSWITCHES WHICH SHORT THE KEYLINES INTERSECTING AT THAT LOCATION. CIRCLES SHOWN DASHED ARE OPTIONAL KEYS ONLY.

- D1-D12 : 1N914, etc.
- G1-G4 : 7437
- G5-G7 : 7401
- G9-G12 : 7400
- I1-I6 : 7405
- M1, M2 : 9602
- T1-T3 : 2N3638, etc.

EDUC-8 FULL ASCII INPUT KEYBOARD LOGIC

27MC AERIALS

for boat or base station

36 GROUND PLANE ANTENNA

High efficiency Ground Plane Antenna for CB base station. All aluminium construction. Accepts PL-259 connector. Solid aluminium 108 inch heat-treated radials and radiator. Elements supplied in two, 54 inch lengths joined by threaded coupling nuts. Radial droop for 50 ohm match. Accepts 1-1/4 inch tubing and PL-259 connector.

Frequency range: 27 MHz
Impedance: 50 ohms
VSWR: less than 1.5:1
Weight: 4.5 lbs
Wave: 1/4

\$35.00

G

GPV BASE LOADED VERTICAL GROUND PLANE ANTENNA

A ruggedly constructed low-cost high performance vertically polarized, omni-directional base station antenna. It develops transmitting gain of 3.8 dB through pattern compression and a lowered angle of radiation along with improved signal-to-noise ratio. The matching stub places it at DC ground potential which substantially lowers the residual noise level and results in gains as high as 19 dB in signal-to-noise ratio.

Gain: 3.8 dB
VSWR: (at resonance) 1.25:1
Coaxial Feed-line: 52 ohms
Omni-directional Pattern
Overall Height: 212 inch

Diameter of Radiator: 1-1/2 inch to 1-7/16 inch
Mast Bracket Accepts: up to 1-5/8 inch
Weight: 5.5 lbs
Full 1/2 Wave

\$49.50

H

CAR BUMPER WHIP ASSEMBLY

Heavy duty 102" whip for rugged terrain. Springshock mount & swivel ball joint. Fits to bumper bar.

\$28.00

I

TRUNK MOUNT WHIP

Solid fiberglass whip extremely tough. Centre loading wound on whip—covered with black abrasion-resistant Thermofit tubing. Flat VSWR across the band excellent performance. Includes trunk lid mount. Cable & PL 259 plug removed in seconds.

Frequency: 27 MHz
Only 48.5" high
Weight: 1.0 lbs
VSWR: less than 1.5:1

\$27.50

F

BASE LOADED ON SPRING

Base loaded antenna with attractive grey jacket and chrome fittings. Stainless steel whip with adaptor that provides for 1-1/4" fine tuning adjustment. A stainless steel spring protects against shock. Antenna easily snaps into "Quick-Grip" mount. Solderless lead connection at antenna. PL-259 at set end of coaxial cable. Only 46" high.

Frequency: 27MHz
VSWR: less than 1.5:1
Impedance: 50 ohms
Weight: 1.7 lbs

\$29.50

E

CENTRE LOADED AERIALS

Short on size, but not on signal! Just 20 inches long. Includes centre loading coil, stainless steel spring and beautiful black phenolic base on the new "Quick Grip" mount. Solderless lead connection with a PL-259 connector at set end of coaxial cable.

\$19.50

AS ABOVE


The gutter clip CB mobile antenna designed to mount on rain gutter of any automobile. Features no hole installation. All antenna parts chrome plated brass or stainless steel. Gutter clamp zinc plated. Includes RG 58/U cable and PL-259 connector. (No Spring).

\$17.50

LIKE A

But has swivel ball joint & screw through mount.

\$24

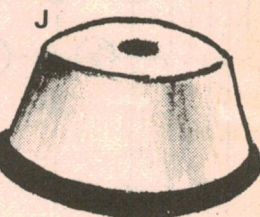

TRUNK LID MOUNT

For mounting any of our mobile aerials without drilling holes in your car. Removed or fitted in seconds, also gutter grip version.

Trunk \$10
Gutter \$12
Gutter D/Lux \$16

J

BASE LOADED CLIP ON WHIP

This short 20" whip fits transceivers with 9/16" or 3/8" aerials. Simply slips over closed aerial stub-base loading coil gives excellent performance.

\$12.00

D

SPECIALS

FIBREGLASS AERIALS

Centre loaded whip ABT 58" with deck mount
Helical Wound ABT 72" with deck mount

\$25.00

\$35.00

FREIGHT & PACKING

ITEMS A, B, C, D, & J

ITEMS E & F \$3.00

ITEMS I, G, & H \$5.00

PETER SHALLEY 127 York St, Sydney
293767 • 297021

bits are high — signifying a row 12, 13, 14 or 15 character. This signal and its complement are then gated with the shift signal and its complement, by gates G10 and G11. The outputs of these gates are then combined by G12, performing an OR function. Finally G5 gates the resulting logic signal with the column 2/3 keyline signal from T1. If you trace all this through, you'll find that it does the required job. Monostable elements M1 and M2 are used to generate a clean "key pressed" signal from the strobe (L) and N-key-rollover (L) outputs of the HD-0165. In the configuration shown, they both suppress key contact bounce, and also prevent encoding errors due to accidental pressing of more than one key.

Gate G5 is an open-collector element, used as an inverter for the HD-0165's strobe (L) signal. When a single key is pressed, the output of G5 thus goes high, and carries with it the trigger input of monostable M1. M1 thus triggers, and its output goes high for a period of approximately 20ms. This interval is set by the 2μF capacitor and 15k resistor, with diode D12 used to compensate for possible capacitor leakage. The 20ms delay is to allow for keyswitch contact bounce to die away, before further events are initiated.

The Q output of M1 is connected to the complementary trigger input of monostable M2, so that when the output of M1 falls back to the low state at the end of the 20ms delay, M2 is normally triggered — producing a clean "key pressed" (L) signal at its Q-bar output. However because the reset input of M2 is connected to the output of G5, and both are tied to the "N-key-rollover" (L) output of the HD-0165, triggering of M2 can only take place if a single key remains pressed. If a second key has been pressed accidentally, the reset input of M2 will be held low, and it will be prevented from triggering.

If this occurs, correct triggering will take place when the second key is released, assuming that the intended key remains pressed.

The clean "key pressed" (L) signal produced at the Q-bar output of M2 is a pulse of approximately 500ns duration. The pulse is used to perform two functions, one being to enable the parallel-load input of the data buffer register — a 74165 device. This causes the encoded 7-bit ASCII character to be loaded into the buffer, ready for despatch to the computer.

The second function performed by the key pressed pulse is to set the flag FF, formed by cross-connected gates G1 and G2. Buffer gate G3 is thus able to take the flag line low, indicating to the computer that a character is available.

As with the other input peripherals described, the computer itself performs the actual data transfer, sending clock pulses to the data buffer register and accepting the data via the inverter/driver G4.

Note that as the EDUC-8 input/output circuitry is designed to handle 8-bit numbers, the keyboard data buffer is an 8-bit register. This means that there is a spare bit, as only seven are used for the ASCII encoded characters. The eighth bit may be set permanently to either a high (H) or low (L), as desired, by tying the PA input of the 74165 either to +5V (via a protective resistor) or to ground, as desired.


In many minicomputer systems the eighth bit produced by an alphanumeric input keyboard unit is permanently set to high (1), as this allows

MODIFIED TAPE READER LOGIC—CORRECTION

There is an old rule in electronics publishing, that it is very unwise to publish a circuit you haven't actually tried. It is almost inevitable that if you do so, the circuit won't work! I have proved the rule still applies, much to my embarrassment. In the description of punched paper tape peripherals, the circuit I gave in Fig. 6 showing how to modify the program-controlled reader logic for use with a motor-clutch type reader mechanism had not actually been tried. Due to lack of time, I had deduced it by analogy from Fig. 4.

Needless to say, it won't work properly. The main problem is that there is no way for the computer to know when the clutch mechanism has incremented the tape.

Rather than attempt to patch up this circuit, I have started again from scratch. And the effort was worthwhile, because it turns out that the job can be done much more simply, using only three ICs—a 74165 as the data buffer, a 9602 dual monostable for timing, and a 7437 for the flag FF and line drivers. The circuit is shown below, and it should be fairly self-explanatory. It should be taken to replace the original Fig. 6. PLEASE NOTE ALSO that the parts list given for the program counter and adder board (main computer parts list 3) is in error. It should list only 4 x 7400 or 9002 quad 2-input gates, not 5, and it should list 1 x 7420 dual 4-input gate.

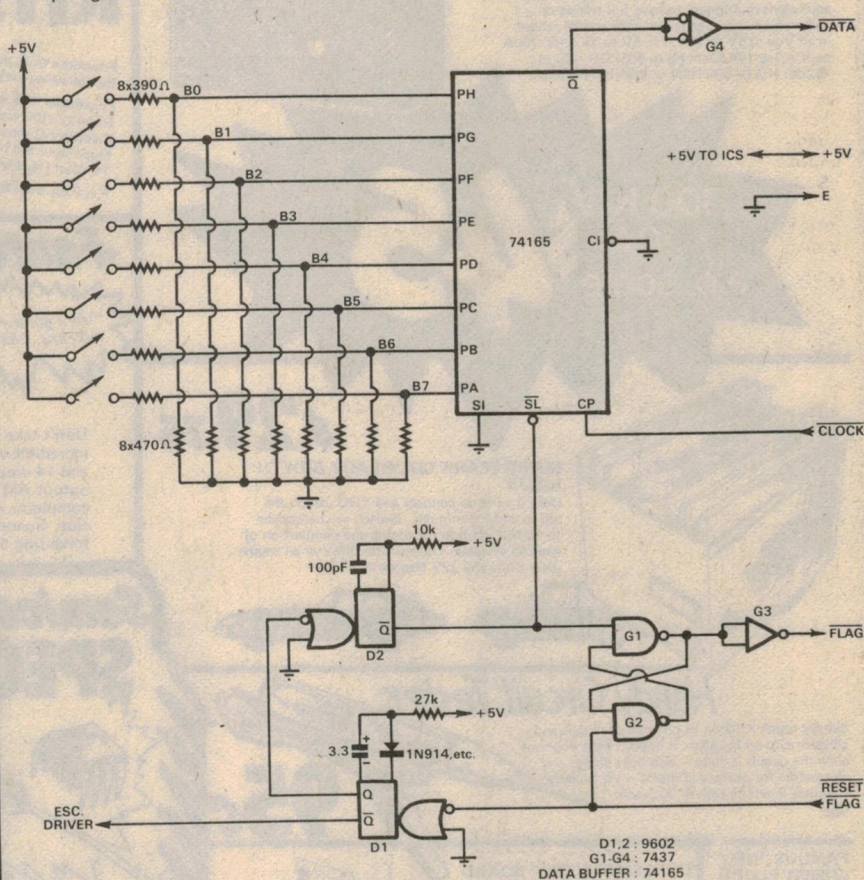

ready identification of alphanumeric or "symbolic" character strings. I have used the same convention, and I suggest you do too.

In the prototype keyboard unit shown in the photographs, most of the logic was wired up on one of our multi-DIP utility PC boards. This was then mounted on the bottom plate of the keyboard case, using suitable spacers. Pieces of flat multi-coloured cable were used to connect the board to the keyswitches, and to transistors T1, T2 and T3. These were mounted for convenience on some existing tagstrips inside the main keyswitch frame.

Before using the keyboard assembly, it was necessary to remove all of the existing switch wiring as this was arranged in a connection array quite different from the one required. Before wiring the switches according to the new array, the complete assembly was cleaned

thoroughly and the key contacts sprayed with one of the aerosol contact cleaning fluids.

At the same time, the opportunity was taken to re-arrange some of the keytops, so that the keyboard became closer to that used in a typewriter or teleprinter. You may care to do this also, as the keys on many keypunch keyboards have the keys in rather different positions. The keys and positions of a normal ASCII keyboard are shown in the diagram, to help you if you want to aim for an arrangement as close to this as possible. I recommend that you do this unless you have a good reason to do otherwise.

As before, the keyboard unit connects to the computer via a length of multi-way cable, and a 6-pin DIN plug. As well as performing the logic signal connections, the cable also supplies the keyboard logic with its 5V DC power.

Dick Smith Ele

Kamoden 360TR


KAMODEN 360TR COMBINED MULTIMETER/TRANSISTOR TESTER
You are literally paying only \$3.00 more than the equivalent multimeter to have full transistor testing facilities. Big mirror scale and 34 ranges in all Vdc, 0.5V to 1kV; Vac 5V to 1kV; Idc 10uA to 10A; Iac 10A; Ohm 5k to 50M; DB -10 to +62db; Hfe 0-500 NPN or PNP; Ico 0-50uA.



100 K/V
10A
a.c. scale

\$45

\$29.75

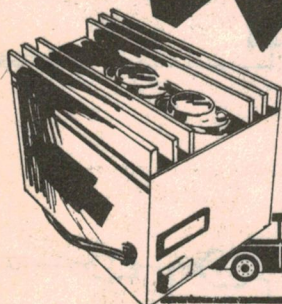

SUPER SPARK CDI. READY BUILT!! \$29.75

Only 4 wires to connect and YOU can do the job in under 5 minutes. Switch to changeover to normal ignition for tuning and comparison of ignition systems. Output over 30kV at all engine revs. Suits any 12V Neg earth vehicle.



Handy Circuit Tester

Simply touch PRD on to one side of circuit and alligator clip on to other: if in-built light does not glow the circuit is open - also tests diodes and alternators for opens and shorts - very handy (requires 2 penlite cells @ 20c each)
95c



FAMOUS "NEC" LD8051 FLURO READOUT

1 Volt.
Filament
20 Volt DC
Operation.
Large size
(4")
as used in
our digital
clock kit.

only **\$2.00**

10 Off \$1.75 each

DICK SMITH "DIL" BOARD

Fantastic little plug in printed circuit board measures 100mm x 60mm and takes dual in line IC's or transistors over 400 holes and copper lands, 24 way, 1" "plug" etched on board. Will take up to 14, 14pin or 16pin IC's or up to 20 "mini-dip" IC's. Ideal for hobbyists and professional engineers alike. ONLY 75c each, or 10 for \$5.00
24 way gold plated socket \$2.00




75c

NATIONAL MM5314N CLOCK I.C.

12 or 24 Hour, 50 or 60 Cycle. Complete with Circuit. Brand new - as used in our digital clock.
\$5.90, 10 off \$4.90.

CLOCK I.C.

\$5.90

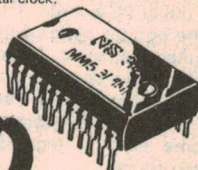

DOLBY CASSETTE DECK

\$189

Who ever heard of a top name Dolby deck as low as \$189.00?
DOLBY SWITCH • CHROME SWITCH
MEMORY REWIND • TWIN LEVEL
METERS • HEADPHONE JACK •
PAUSE BUTTON etc etc



KITS NEW LOWER PRICES!

Enormous bulk purchasing has allowed us to lower the following kit prices - Valid for May & June.

Playmaster 143 amp only	\$69.60
ETI 422 (100 watt) amp only	\$118.00
Capacitor Discharge Ignition	\$19.95
Musicolour MKII	\$49.00
TV Mast Head amp	\$26.00
P & P on amps \$3.00 other kits \$1.00	

PLESSEY 3+3 AMP KIT

COMPLETE - Only needs Transformer
Normally \$32.50
NOW \$29.50 (Save \$3.00)
P & P 75c 2155 TRANSFORMER \$4.75

FM ANTENNA SPECIALS

Manufactured by Hills (need we say more?) 3 element \$12.05. Long range 7 element \$29.55. (Both road freight only)

Fantastic F.M. Tuner


"Very good value indeed" Neville Williams, Electronics Australia, Feb. 75

Only \$75



Don't take our word for it, see the review in Feb. E.A. The Echosound Tuner is incredible value for money. Has separate AM and FM front ends. 10 transistors and 14 diodes. Covers FM 88 to 108 MHz AFC, 60db S/N, 35 db sepn. 600mV output AM 535 to 1605kHz, ferrite rod antenna. Features multiplex adaptor complete with built-in stereo indicator. 240V operation. Complete in Walnut case. Guaranteed for 12 months. Such has been the demand that we are air-freighting them in. Don't miss out at only \$75.00 (P & P Free).

Semiconductor SPECIALS

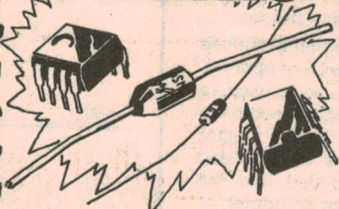

NE555 **\$1.00**

LM380N **\$1.75**

3A /1000V diodes **40c**

741 **\$1.00**

1N4148 (1N914A) **\$1.00**
10 for

Expo Stereo Tuner-Amp \$119

Don't pay over \$200! Yes a complete amp plus AM/FM stereo tuner for about the cost of amp alone.

26 Transistors, 18 diodes • AM: FM mpx • Phono, Aux, Tape Monitor • A & B speaker switch • Tuning Meter • Phone Jack • Stereo indicator.
COMPLETE system including Speakers and turntable from \$199.00

Only while stocks last!



PROJECT 250

See our ad in June 74 E.A. or review in May issue. Fully built - just add power supply and four pots! Philips and Motorola components. Heatsinked 10 transistor and 4 diode. Preamp and tone control board included. Kit A consists of fully built and tested amplifier and instructions. Add four pots 3 x 50k dual log and 1 x 50k single linear and a power supply of 24-30V at 1A. Yes, you've got a 25W (peak) amplifier for \$14.95 (P & P \$1.00). Kit B is as A above but has four rotary pots also. Just add power supply and a few wire links \$19.95 (P & P \$1.50). Kit C is as B above but also has components for power supply. Here is a COMPLETE kit for just \$29.95 (P & P \$2.)

Amp kit \$14.95

Head Office Mail Orders 160-162 Pacific Highway Gore Hill N.S.W. 2065
Tel: 439 5311
P&P 50c min

Electronics Centre

Fantastic Offer



TEN SETS TO
BE GIVEN
AWAY FREE

NEW
ICOM
IC22A

ONLY
\$200

Dick Smith has purchased a huge shipment of the very latest Icom transceivers.

Not only is this unit to be sold at a very competitive price but EVERY purchaser will help his Division of the WIA to obtain a FREE IC22A.

For every ten units purchased, Dick Smith will donate one to your nominated Division or Club. These units are ideal for repeater use or WICEN emergency activities.

Features:

- 146-148 MHz in 22 Channels
- RF Out 10W/1W Switchable
- Mode F3
- Deviation 3-16 KHz Adjustable
- Dynamic PTT Mic Supplied
- 5 Helical Resonators in Front End
- Receiver Sensitivity 0.4uV, 20dB Quieting
- Audio Output 1.5W into 8 Ohms
- Power Requirements 13.5V \pm 15%

The IC22A is Icom's new and improved version of the very popular IC22. The IC22A is ideally suitable for home or mobile use. We are offering this unit with 3 channels, i.e. channel 50 simplex and channels 42/54 and 48/60 repeat.

We have the IC22A INCLUDING 3 CHANNELS of crystals (normal price \$217) for only \$200.00 (P & P Insured anywhere in Australia \$3.00).

Sinclair DVM

AT LAST A DVM AT A REASONABLE PRICE.

3 1/2 digit 8mm bright led display gives readings up to 1.999. Specially developed MOS LSI dual slope integrating IC.22 ranges Vdc 1mV to 1kV; Vac 1mV to 500V; Idc 0.1uA to 1A; Iac 1uA to 1A; R 1ohm to 20M.

Battery operated and rugged construction for field use. Fully protected circuitry.



Unit including battery


\$139.00

Smart carrying case \$6.00 (P&P \$3.00).



TIE-CLIP ELECTRET MICROPHONE \$12.50

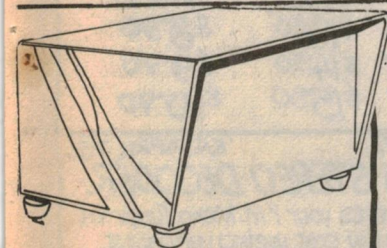Don't spend twice our price! This is a real electret job with FET preamp matching 600 ohms. Response from 50 to 16,000Hz. Measures 0.55" dia x 1.26" long. Battery will last around 1000h. Supplied with 10ft of shielded lead.




HAEGAR LMB GLAMOUR BOXES

First we gave you the extremely popular 'Zippy' boxes, now we have some posh metal cases that have a beaut enamel finish. Supplied complete with feet, no need to make front panels, these boxes will make even the dullest project look professional.

	HxWxL	
453	blue 4x5x3"	\$3.75
463	beige 4x6x3"	\$3.95
564	blue 5x6x4"	\$4.40

Trade enquiries invited.

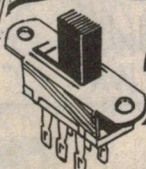


240V ac 1A slider switch DPDT high quality MSP switch with a thousand uses. Normally 85¢. Cut to 25¢ (or 10 for \$2.00).

only 25¢ each



Car Suppressor caps complete with heat resistant insulated wire (not plastic) and quick connector for alternators or generators. Normally 85¢. Now 25¢ or 10 for \$2.00.

only 25¢ each

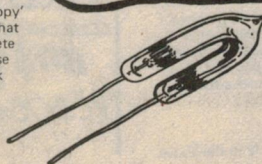

FANTASTIC XEON FLASH TUBES New Low Prices

MFT1210 Tube - normally \$4.54, NOW \$2.00.
TR4KM Transformer - normally \$3.40, NOW 90¢

QUANTITY ENQUIRIES WELCOME

Dick breaks the TIME~PRICE barrier!
See E.A. APRIL 75

Digital Clock Kit

with large fluoro readout

Even the basic beginner can build one in under an hour following our simple instructions. Full money-back guarantee so why not buy one, inspect it at home for 7 days and if not satisfied return the kit and we will refund your money.

Check these terrific features:

- Operates on 240V mains 50 or 60 cycle
- 12 or 24 hour display
- Full circuit board supplied
- Easy to understand instructions
- Power supply included - no extras
- Uses brand new National IC and semiconductors. Spares are available.
- 'Seconds' readout can be easily added

Basic kit \$24.90

OPTIONAL 'SECONDS' KIT \$5.00

OPTIONAL PLASTIC CASE \$9.50



SONY SPECIAL

Sporty 4-band portable FM, SW, MW & Marine

+60 min timer!!

Reduced from \$2650

FM 87.5 - 108MHz (3.42 - 2.77m)
MW 530 - 1,605kHz (566 - 187m)
Marine 1.6 - 4.5MHz (187 - 66.7m)
SW 4.5 - 12MHz (66.7 - 25m)
Power output: 2.8W (max.)
3 "C" size flashlight batteries, 5.6V in total, car/boat battery with car battery cord DCG-127 (optional) or
AC 100, 110 - 127 or 220 - 240V with AC power adaptor AC-3W (optional)
163(W)x204(H)x66.5mm(D) (6 1/4"x8"x2 3/4")
1.56kg (3 lb 7 oz)

\$114 (P&P \$2.00)



MAY SPECIALS

Extension speaker lead 18 feet of tough twin lead in grey with polarising stripe. Complete with 2 pin plug and Utilux speaker clips. Use them in the car or home. Was \$1.20 Now cut down to only 40¢. Get 10 for \$3.00

only 40¢ each




WATCHBIRD PL200 \$10.50

The Watchbird's sole function is to automatically turn on a light or lights (up to 1000W) at dusk and then turn it off at dawn. It contains only 3 parts and outperforms all the conventional electromagnetic or bimetallic type relay operated devices. Ideal for security lighting or when away on holiday etc. Easy to install and you need never worry whether essential lights have been switched on or off.



Also at 361 Hume Highway Bankstown Tel: 709 6600

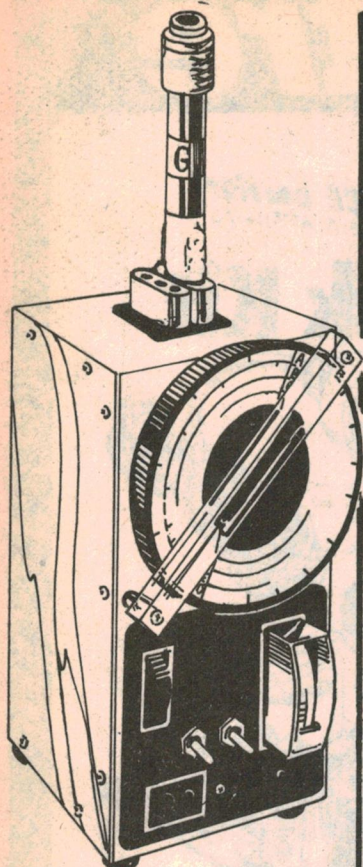& 125 York Street City 291126 opposite Queen Victoria Building 100yds from Town Hall.



**Genuine 200 MHZ
G.D.O. you won't
find a Better One!**

DELICA WB 200 GRID DIP METER
\$142.00 *P&P \$2.00*

FET transistorised GDM to beat all GDM's. This one works reliably on VHF to 200MHz. It is a really professional unit for those who seek the best. Covers 400kHz to 200MHz in 7 bands. Battery operated.

E.A. COMPUTER BOARDS \$4.75 each
P & P 50c

The following boards are now stock lines at \$4.75 each: E81, E8C, E8D, E8F, E8M, E8P, E8T, E810T. Special price for the full set of 8 boards: \$35.00 P & P \$2.00. We do not stock the optional boards E8K1, E8S, E8X.

E.A. COMPUTER TRANSFORMER
PF3798 10V @ 6A \$13.50 P & P \$1.50

**75 AOI Function
Gen Boards**
See Feb 75, 'EA' **\$1.50**
p&p 50c

SAVE ON AN INTERCOM

**PUT IN YOUR OWN INTERCOM &
SAVE A FORTUNE**

We have the Myphone systems which are easy to instal and offer excellent reliability. They use the French Isostat switches and operate on 6V batteries. Range up to 300m between units.

Three types are available:

TA3 MASTER is used in systems with one master working to up to 3 slaves. Only needs wires between units \$18.50

TAPR Remote units are used in conjunction with the TA3 and feature a privacy switch for unauthorised monitoring. \$7.50 each.

TA4M STATION MASTER is used in systems requiring 'all master' operation (any unit can call any unit). Maximum of 5 master stations. Called unit can answer hands-free. Requires 3 wires more than number of stations in system. Can be tied in with TAPR units as satellites. \$27.50

**A VERY EXPLICIT INSTRUCTION SHEET IS
SUPPLIED ENABLING ANYONE TO INSTALL
THESE UNITS**

Accessories Twin wire 12c/M. 12 pair 35c/M
AC power supply (6Vdc at 100mA) \$10.95

**TYPE 220 MAGNETIC HEAD
DEMAGNETIZER.**

Ideal for use with all tape recorders - cassette or reel-to-reel. Removes permanent magnetism, a major cause of noise, in seconds. 240V a.c. operated. Simply hold pole tip close to heads and remove slowly. Full instructions supplied \$6.25 (p & p 75c).

**Project 80 FM tuner
and stereo decoder**



• Twin dual vancap tuning
4 channel ceramic filter
switchable A.F.C.

• On the decoder, solid
state stereo indicating
LEDs on

See Sinclair Project 80 Tuner review in
'EA' April ONLY AVAILABLE FROM
US.

Mono FM Tuner
\$34.50
Decoder for above \$21.00

P&P \$1



\$7.50

p&p 75c




\$27.50

p&p 75c

CAR ENTHUSIASTS SPECIAL

Kamoden 77 Engine Analysers. can be used to check state of batteries, generators, alternators, regulators, starters, distributor, ignition circuit and wiring. In addition to its electrical functions it can also be used as a tachometer for tuning purposes and to accurately determine dwell angle of distributor. Suits any 4, 6 or 8 cylinder engine. Measures RPM on 2 scales to 1200 and 6000 rpm. Voltage from 0 to 3, 15 and 30V. Ohms to 100K. Checks diodes. Dwell angle to 90° in 4 cylinder engines. Current to 90A, yes 90A using shunt provided. Tests spark quality. Condenser substitution tool! Supplied with detailed 32 page manual describing all tests and giving circuit diagrams etc. 5 transistor circuit, large 4" meter for clearest readings. Complete with batteries (1.5V and 9V). This instrument could pay for itself the first time you use it and save costly garage bills. Hurry though, we are only bringing 30 in at this price \$49.00 (P & P \$2.00)

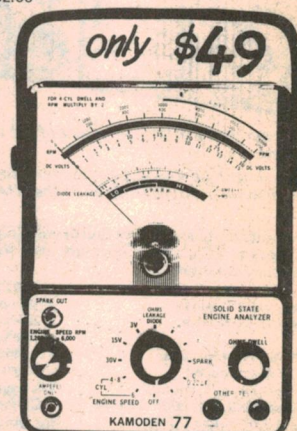

only \$49

FANTASTIC TAPE SPECIAL
Genuine BASF LH SM tape in C90's. Nothing but the best do not confuse with cheaper rainbow pack. Guaranteed low noise special mechanics non-jam tape. Orders may be assorted. C90SM normal list price \$3.99. Our special price 10 off \$2.20, 20 off \$2.00. C90SM (Cr2) Chromes normally \$5.60. 10 off \$2.75, 20 off \$2.50. P & P \$1.50 for 10, \$2.50 for 20.



**Heat Sink
Pliers**



\$1.90
P&P 50c

**TREMENDOUS LOW PRICE WALKIE TALKIE OFFER
CONTACT CT10**


Remember the famous Midland 13700 units in our last year's catalogue? We sold thousands of these units (and no wonder when you read the spec). The Midland is no longer available but we have located an absolutely IDENTICAL Unit. ONLY THE NAME HAS CHANGED. Check these features:

Provision for 2 channels (27.240MHz or 27.880 MHz). Tuned RF stage. One microvolt sensitivity. Mute control. Calling tone. Heavy duty aerial. Maximum power allowable. PMG APPROVED (licence required). Transmitter effectively converts its 1W output power into a high ratio output power by high level push-pull class B modulation. Rugged case. Supplied with one set of crystals (specify frequency). Other frequency available at \$4.50 pair.

Range: up to 10 miles depending on terrain
up to 50 miles over water
Frequency: 27.240 or 27.880 MHz
Freq. Stab: 0.005%
Tx: Crystal controlled 1W
Rx: Crystal locked superhet
Antenna: 13 section telescopic
Power: 8 x 1.5V UM3 cells
Size: 8 1/4 x 3 1/4 x 1 1/4"
Weight: 25 oz

We have the Contact CT10 at the same, YES SAME price as our old catalogue. It must be the cheapest, 1 Watt, fully approved unit in Australia at ONLY \$39.95. Buy 5 or more and save \$2.00 on each unit at only \$37.95 (P & P \$2.00 per unit).

\$39.95

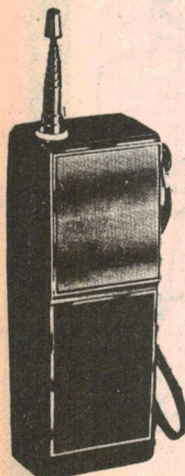

stop press

**MAGNAVOX
FOR
SOUND**

**FAMOUS MAGNAVOX TWIN CONE
SPEAKERS AT LESS THAN COST!**

-Now's your chance - Ideal for Hi-Fi

Extension Speakers -

Frequency range 30^{Hz} 16 KHZ

15 Watts wide range

All 8ohm Impedance

*P&P \$1.50 per
speaker*

8WR

10WR

12WR

8"

10"

12"

*NORMAL
RETAIL*

\$13.50

\$14.50

\$15.50

**OUR
SPECIAL
PRICE!**

\$8.90

\$9.90

\$10.90

FROM 3c each

**OA91 DIODES AT RIDICULOUSLY
LOW PRICES.**

As used by famous manufacturer, we have purchased a huge quantity of top quality OA91 Diodes from AWA. Ideal for manufacturers and service use. Don't pay 25c when you can buy in quantity and save a fortune. Pack of 200 8c each. Pack of 1,000 5c each. Pack of 5,000 3c each.

Fully guaranteed, only available in the above packs.

**KIT 78 'EA' APRIL 75
FM STEREO DECODER**

Converts your F.M. Mono Tuner at very low cost using very latest 'NO COILS' decoder I.C. All electronic components & P.C.B.

KIT \$10.75

Post 50c

P.C.B 75 sd 4 \$1.35

Circuit & Design Ideas


Conducted by Ian Pogson

Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

LEDs monitor supply voltage

Yet another use of LEDs turns up in an item by Marvin J. Moss in "Electronic Design". This is in the form of a voltage monitor for 12V supplies, indicating both over or under tolerance voltages. Using three LEDs the user can see at a glance whether power is on, over-voltage or under-voltage. This is achieved by means of a balanced bridge that uses zener diodes ZD1 and ZD2 in the bridge's opposite arms and back-to-back LEDs between the mid-points of the bridge arms.

If the input voltage does not exceed

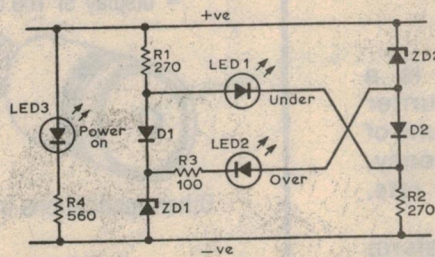


the two zener breakdown voltages ($2 \times 6.8V = 13.6V$), LED1 lights. But above 13.6V LED1 becomes reverse biased and

remains off. When the input voltage increases to the extent that at the junction of ZD2 and D2, it exceeds the zener voltage of ZD1, plus the LED voltage of 1.6V, then LED2 is turned on, with R3 limiting the current through the LED. By mixing of silicon and germanium diodes, etc, it might well be possible to decrease the voltage tolerance. The total drain of the circuit as shown is of the order of 50mA, which is not excessive for car batteries or mains units although would have to be considered for dry battery operation.

Motor reversing using silicon diodes

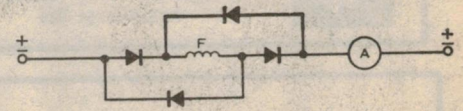C. Draper, G3TSK, two years ago built an aerial rotator using a 24V Meccano motor and some gears—and devised an interesting means of reversing the direction of the motor. Rather than put a relay in the motor box where it would be

subject to inclement weather conditions, he used the system shown in the diagram, based on diodes. These are arranged so that they effectively change over the armature winding depending on the polarity of the supply.




(From "Radio Communication".)

100-hour timer uses plating cell

A timer with output durations ranging from a few seconds to more than 100 hours can be built around a plating cell, thus avoiding the special low-leakage components or high resistances that such timers often require.

When the current direction in a plating cell is from reservoir electrode to working electrode, silver is plated onto the working electrode in an amount proportional to the charge passed through the cell. Conversely, when the current direction is from working electrode to reservoir electrode, silver is removed from the working electrode. As long as the electrode is plated, the impedance of the cell is only a few kilohms; but after all the plating is removed from the anode, the impedance across the cell increases to several megohms. When this happens, transistor Q1 is turned on; otherwise, when the cell is plated, Q1 is cut off.

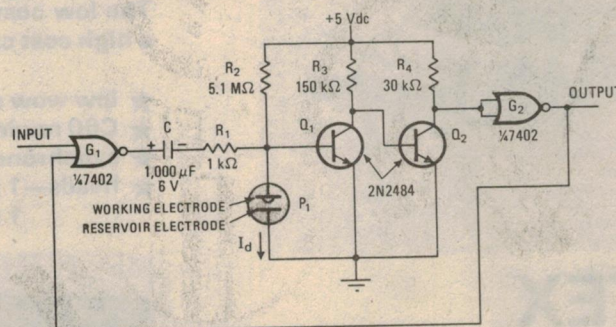The plating charge is the charge on capacitor C. When the input and output have both been low for a long time, C has charged fully to about 3.6V, and at 1000uF as shown, it holds 3.6×10^{-3} coulomb. Then, when the external input to gate G1 goes high, its output drops to ground and C discharges through the



Choice of RC time constant gives times from seconds to more than 100 hours. P1 is a Plessey E-Cell, type 560-0002.

plating cell. The current I_d , with the reference shown, is negative, causing the cell to be plated. The magnitude of the current is limited by resistor R1; the time constant for the values shown is about 1 second. Plating the cell drops the voltage at the base of Q1 below its threshold, thus turning Q1 off and Q2 on. The collector of Q2 drops almost to ground; this level is inverted by gate G2 and the output goes high. This output feeds back to gate G1 to make the circuit operation independent of the input line once the timing cycle has begun.

The deplating current flows continuously through R2; it is 1uA for the value of R2 shown. When deplating is nearly

completed, the impedance of the cell begins to increase gradually, Q1 turns back on, the timer output goes low, and if the timer input is low, capacitor C charges again.

The charge transferred during either plating or deplating is represented by $Q = CV = I_d T$. From this relationship, the time to transfer this charge is


$$T = CV/I_d$$

For a 1000uF capacitor, the time to deplate the cell is 3600 seconds, one hour. Other times can be obtained by using different values for the capacitor C or the resistor R2.

(By Ken Erickson, in "Electronics".)

"Perfection in Programming" with N.I.C.

8100 Series Counter/Timers

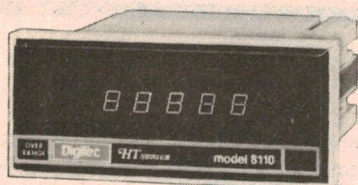

**Model 8110
Counter/Timer**

The Model illustrated (8110) is a Programmable Factoring Counter which can be read directly in any unit of rate measure, such as frequency, feet/minute, gallons/hours, draw rate, RPM, RPS, ratio . . . etc.

The instrument functions to transform the output of your frequency producing transducer (sine wave, pulse or any wave form) into desired units.

DISTRIBUTED THROUGHOUT AUSTRALIA BY:



N.I.C. INSTRUMENT COMPANY

A DIVISION OF ANSETT TRANSPORT INDUSTRIES (OPERATIONS) PTY. LTD.


MELBOURNE 338 3111 SYDNEY 51 8931 BRISBANE 44 2111

ADELAIDE 51 4935

PERTH 65 4655

Motor Speed is just one of the many applications of the 8110 Counter/Timer as illustrated below.

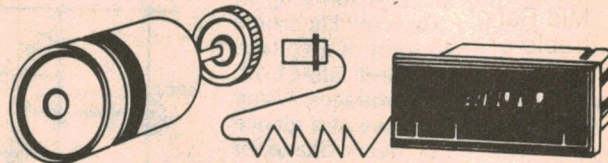- Convert output of transducer into RPM, RPS or other speed units.
- Convert output of transducer into custom units. Eg: 12,345 RPM = display of 100.00%




Other applications include Frequency, Rate, Flow and Ratio.

I would like to have further information on the Digitec 8100 Series Counter/Timers. Please have your representative contact us.

Name
Company
Address
.....
Postcode b/1

THE GOOD GUTS!

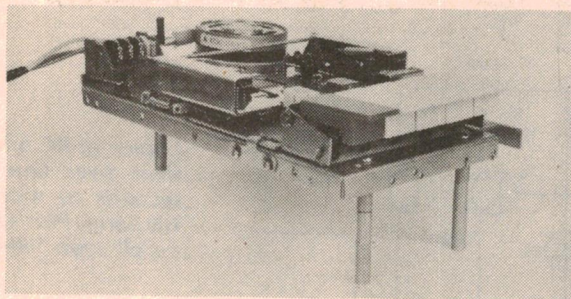


VORTEX

Cassette mechanism only \$29. Complete details of E.A.'s great Playmaster Project with every deck.

The low cost way (approx. \$99) to make a high cost cassette deck.

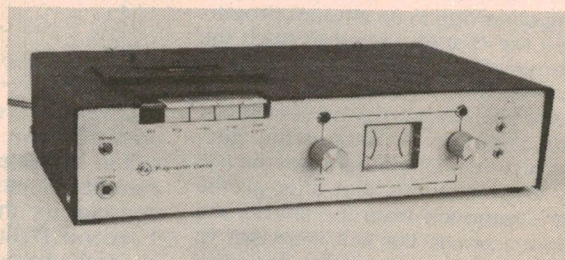- ★ low wow and flutter
- ★ C60 rewind time 90-100 sec
- ★ synchronous induction motor
- ★ heads—1 half track erase
- 1 stereo 1/4 track record/playback



Vortex decks available from:

N.S.W.

Alan Oliver Electronics, ph. 43 5305. J. V. Kinsman, ph. 328 2987.
Pre-Pak Electronics, ph. 797 6144. Radio Parts, ph. 329 7888.
M.S. Components, ph. 69 5922.

VIC.

S.A.: Jack Evans Agencies, ph. 223 1646.

W.A.: W. J. Moncrieff, ph. 25 5722.

QLD.: Electronic Components, ph. 36 5061.

Or from the
importers

Panel Parts, 16 Winbourne Rd., Brookvale 2100.


HI-FI SPEAKERS EXPLAINED:

Open up a Hi Fi speaker box and you will find one or more speaker cones. These cones are mounted on a board called a baffle. And attached to the back of each speaker cone is a coil of wire called a voice coil. This converts electrical signals from the amplifier into sound, by moving the speaker cone back and forth. Basically, speaker cones fall into three categories: Mid Range, which reproduce both treble and bass frequencies; Tweeters, which only reproduce treble or high frequency sounds; Woofers, which only reproduce bass or low frequencies. You can tell the difference between a cheap speaker and a true Hi Fi speaker by the price. And by using your ears. Ask to see the full range of Kenwood Hi Fi equipment at any good Hi Fi centre.



KL-333A**
2-way, 2-speaker system comprising 1 x 8" bass and 1 cone type high range. Maximum Input Power: 15 watts RMS. Frequency Response: 45 Hz-20,000 Hz. Sensitivity: 92 db/w at 1 metre distance.
\$220.00.*

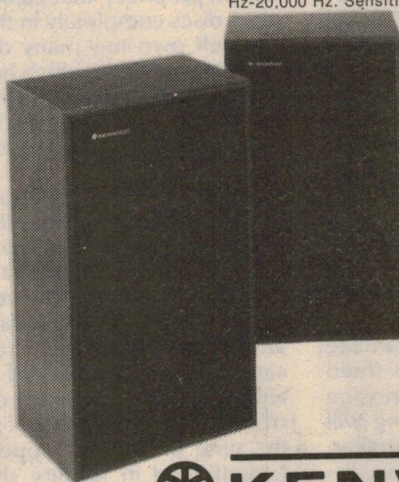KLX-10**
Full range single cone speaker 16 cm (6½"), 8 ohm. Maximum Input Power: 8 watts RMS. Frequency Response: 50 Hz-20,000 Hz. Sensitivity: 93 db/w at 1 metre distance.
\$89.00*



KL-444A**
3-way, 4-speaker system comprising 1 x 10" bass 1 x 5" mid range and 2 cone high range with tone selector. Maximum Input Power: 24 watts RMS. Frequency Response: 35 Hz-20,000 Hz. Sensitivity: 93 db/w at 1 metre distance.
\$370.00*



KENWOOD



**WE
WANT YOU TO KNOW
MORE ABOUT GOOD HI-FI**

**JACOBY
MITCHELL**

Distributed and serviced in Australia by Jacoby Mitchell.
Experts through experience.

We're giving you a **FREE 12-page booklet** to help you get to know more about good Hi-Fi.
All you have to do is send us the coupon and we will send you by return post "Hi-Fi Explained by Kenwood."

Name _____

Address _____

Post this coupon to
Jacoby Mitchell Sound Division
P.O. Box 2009
NORTH PARRAMATTA, N.S.W. 2151

*Recommended Retail Price.

**Averaged manufacturers' specifications subject to change without notice.

Classical Recordings

Reviewed by Julian Russell



A new batch of Dolby cassettes

All the cassettes reviewed in this column are Dolbyised—or wouldn't "Dolbyed" perhaps be a better word? When I reviewed my first batch of Dolbyised cassettes on Dolbyised equipment in last January's issue of "Electronics Australia", I wrote that, good as they were, they just failed to be as good as the very best disc recordings. I have since had occasion to change my mind. The recording of cassettes varies just as does the recording of discs; i.e., some are better than others. But the best of the cassettes I am reviewing this time are as good as any discs I have ever heard. I do not know if one would get an equally good result from a very weighty choral and orchestral work because I have so far heard none on this medium.

But I must reiterate another advantage of the cassette set-up. The user is freed from the nuisance of an inferior pressing from which no amount of cleaning will make the pops and crackles disappear. Dolbyised cassettes to which I have listened often have more stable stereo

separation than some by no means unimportant discs. Having set your balance there is seldom any need to readjust it, which is more than can be said about even the best recorded discs. I am reluctant to prophesy that cassettes will supplant discs completely in the near future. I myself own too many discs to which I am attached and which have long since been deleted from circulation to wish this to happen. But I consider I am perfectly safe in predicting a fast widening market for the Dolbyised cassette.

By the way I must apologise to any of my readers who found some of the cassettes I reviewed in the January issue unobtainable in Australia. Phonogram Ltd., the distributors allowed me to pick those I wanted from a large collection and unfortunately I chose some that were samples, not yet issued in Australia, although they are already on the market overseas. However I now learn that, by the time this review appears, all those I mentioned in January should be obtainable here.

MOZART—Symphonies Nos. 25 in G Minor (K. 183), 26 in E Flat (K. 184) and 27 in G Major (K. 199). Berlin Philharmonic Orchestra conducted by Karl Bohm. DGG stereo cassette No. 3300 337.

No one could wish for better sound than they will hear in these three early Mozart symphonies. It is beautifully transparent, not a note of detail is missing and the tonal quality of the Berlin Philharmonic superb. There is, too, the unrivalled Mozart conducting of Karl Bohm. These symphonies were composed after Mozart's third and last visit to Italy. Despite the Kochel numbering, No. 184 was written before No. 183 and shows a stronger Italian influence, so much so that it may be described as in the Italian Overture style. In keeping with this style you will find little formal development in the first and third movements, although Mozart provided a deeply felt contrast in the Andante, putting it in a minor key and introducing many novelties—of genius even at that early age—in his use of dialogues between different instruments.

Although only 17 years old, he already

showed extraordinary precociousness in his firm grasp of the orchestral medium. The combination of Bohm's superb conducting and the peerless playing of the Berlin Philharmonic makes it a memorable performance. To some, Bohm's tempos might seem a little on the slow side at times but this is well within the central European tradition. And there is ample compensation even to those who prefer slightly faster tempos in the compelling drive behind everything Bohm plays.

The K. 183 in G Minor will promote inevitable comparisons with the later "big" G Minor, one of the last three symphonies Mozart composed before his early unhappy and completely wasteful death. In this it is the slow movement that is in a major key and provides comforting balm after the grief-laden G Minor first movement.

It is a movement of quite seraphic serenity. You will find lighter relief still in the menuetto and Bohm takes the Finale with its wonderfully lucent part writing very seriously; some might think a trifle too seriously. But although I can appreciate their point of view, I find

Bohm's reading absolutely right,

K. 199, is a still earlier work although even here you might marvel at the originality of the instrumental dialogues over a pizzicato bass in the slow movement. The fast Finale has a most delicious lilt. I can think of nothing but the highest praise for the whole production.



MOZART—Concerto for Two Pianos (K. 365) Emil and Elena Gilels (pianos) with the Vienna Philharmonic Orchestra conducted by Karl Bohm. Concerto for Piano and Orchestra (K. 595). Emil Gilels and the VPO conducted by Karl Bohm. DGG Stereo Cassette No. 3300 406.

Although Gilels is one of the finest pianists playing today, this is the first time I have ever heard him in Mozart. From his very first bars there is never a doubt that he is as great a performer of the music of this composer as he is of so many others. In the Double Concerto Gilels is joined by his gifted daughter Elena. The rapport between the two is complete, both players showing the same engaging fluency and nuancing. Their tempos always sound just right and the tricky job of balancing the two pianos against the orchestra is always completely successful. The concerto is a happy, some times even joyous work, the creation of a young genius who had risen above the bitterness and humiliations suffered during his Paris visit. Soon to be followed by pain at the loss of his mother. The contribution of Bohm and the VPO adds to the triumph of the soloists.

In the K. 595—Mozart's last piano concerto—the light-heartedness of the earlier work has gone but it is again an example of other disappointments conquered by an indomitable spirit. This concerto—one of the greatest—is renowned for its almost entire lack of emphasis and point making. Here is true serenity untroubled except on rare occasions by a slightly raised voice. Yet as played by Gilels, and Bohm, there is no sense of monotony of emotion or greyness of texture. Only considerations of space prevent me from continuing my unqualified praise of the work and its performance. So I confine my remarks to the advice—don't miss it.



BRAHMS—Piano Concerto No. 1 in D Minor. Alfred Brendel (piano) and the Concertgebouw Orchestra of Amsterdam conducted by Hans Schmidt-Isserstedt. Philips Stereo Cassette No. 7300 281.

I must confess to considerable disappointment in this cassette, although this is limited to the manner of performance and not its engineering. For instance, the usually potent Schmidt-Isserstedt begins the first movement introduction with, here and there, a surprising lack of vitality. It sounds in fact very, very ordinary. When the piano enters its tone is at first

a little dry and percussive though this is corrected further on the tape. Brendel's reading is characteristically studious but there is an unsmiling atmosphere about his playing, even in the feminine second subject, that I found less than attractive. To me he comes perilously close to sounding irritatingly metronomic—I nearly wrote wooden. There are, of course, some very beautifully played passages, pianissimo figurations of delicious delicacy and fluidity. But elsewhere in this movement I had to concentrate hard to prevent my attention from wandering. Correct it undoubtedly is, but oh so starchy. And this might explain Schmidt-Isserstedt's reflection of Brendel's unexciting playing by accommodating these moods in the orchestral part.

In the slow movement the conductor starts warmly although his tempo is nearer to largo than adagio, which latter is the way Brahms marked his score. But, judging by the way Brendel continues the movement, this is the way he wanted it. On the other hand, one important point in Brendel's favour throughout the concerto is the exhibition of unforced power he has at his command. And in the Finale all lethargy vanishes. It is played right up to tempo and produces a very spirited performance from both soloist and orchestra with moments of enchanting delicacy by way of contrasts. There is, too, an admirably sustained balance between pianist and orchestra, no matter how soft or loud the sound issuing from the speakers.

★ ★ ★

SIBELIUS—Symphony No. 1 in E Minor. Symphonic Poem. The Bard. Radio Symphony Orchestra of Helsinki conducted by Okko Kamu. DGG Stereo cassette No. 3300 401.

I enjoyed both the playing and recording of this cassette immensely. The opening lonely clarinet solo establishes the right atmosphere instantly. Then the rest of the fine Finnish orchestra enters with alluring warmth of tone in the strings and a fine cutting edge on the brass. The conductor's reading of this turbulent score is unabashedly romantic. It differs slightly in detail from that of his great Finnish predecessor, Kajanus, who recorded the symphony on 78s back in the 1930s, especially in his treatment of the almost whispered pianissimos. But otherwise I found Kamu's interpretation of the stormy first movement just as exciting. The sound is outstandingly impressive with its very wide range of dynamics and frequencies. Kamu uses the many climaxes to fine effect without obscuring any of the finer details of the score.

He starts the first subject of the slow movement with quite ravishing tenderness sustained throughout and the end fades firmly but exquisitely into silence. Kajanus perhaps got a little more devil into the scherzo—so, too, did that other fine Sibelius conductor, Collins—but

Kamu's reading will still do very well. There is not an untidy bar anywhere. True this Helsinki orchestra must know the piece so well that they could probably make a good job of it in complete darkness. But this is not meant to detract from Kamu's performance in any way. He makes the Finale as majestic a conclusion as that of any romantic symphony, taking it all with impressive breadth.

No information about the second item on the cassette, The Bard, also by Sibelius, is included in the cassette notes though the fact that the music is so self-explanatory makes their omission unimportant even to those who are hearing the piece for the first time. The Bardic atmosphere is created by a series of harp passages in the accompaniment to its solemn but haunting melody. But even without this association, the music in itself is no less than superb and Kamu does it full justice observing every shade of expression. Sibelius wrote many symphonic poems but none—even Tapiola—better than The Bard. I can only describe it as supremely eloquent in its sad, narrative beauty. Very strongly recommended to those with a romantic bent who are meeting Sibelius for the first time.

★ ★ ★

TCHAIKOVSKY—Symphony No. 6 in B Minor (Pathétique). Vienna Philharmonic Orchestra conducted by Claudio Abbado. DGG Stereo Cassette No. 3300 405.

Here is another romantic symphony that I can recommend in every way to those who have enough sense not to affect scorn of the composer. For there exist, or did until recently, people—even critics—who profess contempt for one of the world's greatest writers of melodies, whatever formal delinquencies are to be found in his symphonies. But not everyone looks for the closely dovetailed workmanship of Beethoven in symphonic literature, nor the long, rambling, often mystical and still more frequently banal neurotic compositions of the composer of the minute, Gustav Mahler. Tchaikovsky has often been accused of writing clumsy fast passages for strings. Perhaps he did. My instrument was the piano so I cannot confirm or deny this. But one thing I know for sure, and that is that Tchaikovsky's string passages, fast and slow, sound glorious as played by the Vienna Philharmonic under Abbado on this cassette. For this is still another that has my unqualified recommendation. Abbado offers an excellently proportioned first movement, the intro one of solitary sadness followed by an allegro non troppo at first restrained, almost dainty in its string phrasing. Even the famous second subject, popularised some years ago under the title of, I think, Starry Night (yuk) is slightly underplayed emotionally. It is not until you reach the hoarse-voiced brass in the great climax that you realise just how carefully and

effectively Abbado has laid out the music. It is an agonised yet never undignified statement in which self-pity is kept to a minimum.

The movement closes in a mood of exhausted despair with the melody supported by giant pizzicato footsteps in the bass that somehow express—at any rate to me—the peace which comes with death.

Abbado uses the 5/4 time of the second movement to win a line of the most sensitive fluidity. Despite its time signature it never sounds the slightest bit lop-sided. And in the second subject he makes subtle uses of its repeats which are never taken as mirror copies of the original. The whole movement, despite its grace, has about it the languour of hopelessness.

The VPO strings start the scherzo with unmatched delicacy which would never prompt one to guess at the martial character of the music that follows later in the movement. If you play this movement as a sample, it will give you a good idea of the resources of modern cassette recording techniques. You will find it at the beginning of Side 2. And if this doesn't convince you of the superb standard of the playing and recording go on to the Finale with its great contrasts between the two moving subjects. Here is no Bernstein heart-on-sleeve showiness but deeply felt expression of the music without any hint of self-advertisement by the conductor. The grandeur of tone of the VPO has to be heard to be believed.

TANNOY

GOLD MONITOR

SPEAKERS

12" and 15"
THE ULTIMATE
IN HI-FI SOUND

Buy as components
or fully made up.
Hear them today.

Stockist of the full
range of Dutch
Philips speakers.

G.H.E.

GEORGE HAWTHORN ELECTRONICS

966-968 High St., Armadale
Victoria, 3143

Phone: 509 0374, 509 9725



Variety Fare

Reviews of other recordings

Devotional Records

DINO PLAYS FOLK MUSICAL THEMES.

With the Ralph Carmichael Orchestra and Chorus. Stereo, Light LS-5635-LP. Also on cassette. (From Sacred Productions Aust, 181 Clarence St, Sydney and other capitals.)

Identified only by his christian name, Dino is a young man with precisely what it takes to provide a very pleasant and entertaining sound on the piano. And Ralph Carmichael supports him with some fine arrangements and a generous orchestral backing.

The folk themes are taken from recent Christian musicals, from the pen of Ralph Carmichael, Kurt Kaiser, Jimmy Owens and others. Although the program is predominantly instrumental the words are given on the jacket, for those who may desire to follow them: My Little World — Jesus Never Forgets — He That Overcomes — Holy, Holy — Let It Ring/God Is Here Right Now — Joy Is The Centre of His Will — New Wine — Trusting Is Believing — Pass It On — My One Aspiration/Thank You Lord.

Whether or not the titles are familiar, I venture to suggest that you'll enjoy the big sound — melodic piano, full orchestra and touches of chorus. Those with a critical ear may detect a faint edge here and there on the strings and chorus but, all told, it's a highly successful album. (W.N.W.)



THAT THE WORLD MAY KNOW. Paul Johnson Singers. Stereo, Word WST-8623-LP. (From Sacred Productions Aust, 181 Clarence Street, Sydney and other capitals).

In some albums, hymns are presented more or less straight. In others they are so drastically rearranged that little of the original melody remains. The Paul Johnson singers and instrumentalists plot their course about midway between the two. The words and melodies remain substantially intact but the tempos and accompaniments are based on the current pop idiom: drums, bass, keyboards, percussion, guitars, electronic organ — and repeated lines.

The hymns: No One Ever Cared For

Me Like Jesus — Then Jesus Came — In The Garden — When I Come To The End Of The Road — I Need Jesus — That The World May Know — The Old Rugged Cross — He Lives — Beyond The Sunset — Living For Jesus.

The sound is full and clean and the basic melodies are as recognisable as the hymns themselves are familiar, but individuals will vary in their reaction to the mod. get-up. On the happy, boisterous hymns the format sits naturally enough but, when "The Old Rugged Cross" receives the same treatment, I wonder whether the tune merchants gave even the slightest thought to the words.

Provided you don't suffer hang-ups of this nature, the Paul Johnson Singers

Instrumental, Vocal and Humour

REVERIE. The Royal Liverpool Philharmonic Orchestra World Record Club Stereo WRC S/4799

This delightful record is most aptly named, for it certainly creates a mood of reverie. There are eight tracks covering a range of classical composers. From Chopin we have The Nocturne from "Les Sylphides"; from Massenet the Meditation from "Thais"; Nocturne by Borodin; Nocturne from "A Midsummer Night's Dream" by Mendelssohn; Adagio in G minor for strings and Organ by Albinoni-Giazotto; Gluck's Dance Of The Blessed Spirits; Pavane By Faure; and from Gounod we are offered the Judex from "Mors et Vita".

The quality and stereo image are excellent, making the record an excellent buy at club prices. (N.J.M.)



MELODY FAIR. The Soundtrack Orchestra. Quadraphonic, Mastersonic (W&G) WG-35/Q/5626.

Another one from Melbourne-based W&G, this album comes originally from the Nippon Columbia Co, Japan. Perhaps hinting at the shape of things to come, it has been encoded according to the RM matrix system and prominently marked "QX", which isn't all that far in

would go over well enough in the average mixed-family situation. (W.N.W.)



CLOSE TO THEE. George Beverly Shea. Stereo, RCA Victor APL1-0471.

If evidence is needed of the popularity of Gospel singer Bev Shea, one would need only to recall the number of albums he has released over the years. I remember counting up about fourteen on an earlier occasion and there have been others since then. Although recorded at the Nashville studios of RCA, I get the impression that the vocal and orchestral backing is less generous than usual, throwing a heavier load on a soloist who is no longer a young man. The titles: Close To Thee — Every Time I Feel The Spirit — Hope In God — Reach Out To Jesus — Whispering Hope — Where Could I Go — By And By — He's Everywhere — The Lord's Prayer — Fill My Cup, Lord.

The quality is a trifle patchy, generally clear on the voice but with a suggestion of roughness here and there on the backing orchestra and chorus. There have been better Bev Shea albums but, if you already have them and you're a Bev Shea fan, then the above reservations certainly won't stop you enjoying the contents of this new one. (W.N.W.)

practice and terminology from "QMX" which Nippon Columbia have used to describe their new UD-4 discrete format (See "HiFi News" March issue). Sufficient to say that it decodes very nicely through the E.A. Stereo 2/4 adaptor.

The music itself is just about as smooth and easy on the ear as music can be and the film theme selections add their own attraction: Melody Fair — The Marriage Waltz — Alfie — Both Sides Now — The Cad — The April Fool — Swedish Love Story — The Red Tent, Main Title — Love Story — We Love You Underground — Romeo and Juliet — The Particular Lesson.

Technically, the sound is very smooth due, in part, so the jacket claims, to the American developed "Mastersonic" cutting technique. Very smooth; very pleasant! (W.N.W.)



LA HARPE DES ANDES. Gerardo Servin. Barclay stereo L 35237.

The harp of the Andes is played by Gerardo Servin and is backed by guitars and percussion. Servin plays in virtuoso style with plenty of glissandos to make the music really bright. Sound quality is excellent, so we can recommend this disc.

Fourteen tunes are featured: El Tren Lechero—Amalia Rosa—La Canahuatera—Reyes Morenos—Costa Brava—La Troppilla El Triunfo—El Negrito Del

Reviews in this section are by Neville Williams (W.N.W.), Harry Tyrer (H.A.T.), Leo Simpson (L.D.S.), Gil Wahlquist (G.W.) and Norman Marks (N.J.M.).

Batey—Chacareando—Hay Quien Pudiera—Luna De Maracay—Mitacunami—Palo, Palo, Palito—Nueva Piel—El Canaveral. (L.D.S.)

★ ★ ★

YE OLDE MOOG. Synthesonic Sounds, arranged, conducted and produced by Mike Batt. Stereo 4D series, Astor SPLP-1429.

If you want to know more about this album, you'll look in vain for jacket notes. I would judge it to be a mix of sounds from traditional instruments and from a Moog synthesiser but there's plenty of room for argument about what is which, and who does what. The sound is clean and varied but my own reaction is that sixteen tracks of Moog is a bit much for straight listening. A few tracks at a time would go down much better.

Going to make up "Ye Old Moog" theme is: English Country Garden—Riddle Song—Scarborough Fair—Ash Grove—Drunken Sailor—Danny Boy—Morning Has Broken—Oh No John—Strawberry Fair—Streets Of Laredo—Amazing Grace—Early One Morning—Greensleeves—Cockles and Muscles—Loch Lomond—House Of The Rising Sun.

The endorsement "Stereo 4D" could mean conventional stereo, quadraphonic or compatible; the label gives no hint. All I can say is that it sounds okay either way—clean, different, and pleasant a few tracks at a time. (W.N.W.)

★ ★ ★

CHARLIE McCOY. The Nashville Hit Man Monument Records L35305 Festival release.

I automatically except high technical quality to come from the various studios in Nashville and this collection of numbers with a mainly western theme certainly shines, with clean, driving bass and a generally superb sound.

About the only person not listed on the sleeve notes must be the tea lady. The eleven tracks are: Silver Threads And Golden Needles—Help Me—Fireball Mail—The Way We Were—Keep On Harpin'—You Win Again—Boogie Woogie—I Can't Help It—Heart Over

Recommended for your quadraphonic collection

BIG BAND HITS OF THE 30's. Volume 2. Enoch Light and the Light Brigade. Quadraphonic, Project 3 (Festival) LQ-35,308.

Technically, this new recording by Enoch Light is right out of the top drawer. Recorded originally on 35mm magnetically coated film, it is completely free from any suggestion of background noise, peak overload or limitation on frequency response. But, curiously, with all the emphasis on technical excellence, there is no hint on the jacket of the matrix format. I simply played it as SQ and it sounded fine!

As to the musical content, Enoch Light

researched the original big-band arrangements and set out to recreate them, featuring those of his musicians who, by talent and past association, were best qualified to cope with the leads.

Numbers and arrangements featured are as follows: Benny Goodman: Stardust, Bugle Call Rag, King Porter Stomp. Glenn Miller: Little Brown Jug, American Patrol. Duke Ellington: Caravan, Solitude. Artie Shaw: What Is This Thing Called Love, Softly As In A Morning Sunrise. Clyde McCoy: Sugar Blues. Tommy Dorsey: Boogie Woogie. Glen Gray: Smoke Rings.

Technically, musically, it's a beauty. Recommended. (W.N.W.)

Mind—Ruby.—Let Me Be There. The cover photo depicts a scene reminiscent of an underworld 'hit' of the prohibition era, with bodies strewn around. Even the feet get a credit! There is lots of good steel guitar and harmonica playing as well as a very good rhythm section, in all a very enjoyable record. (N.J.M.)

★ ★ ★

JACK DANIEL'S ORIGINAL SILVER CORNET BAND. Paramount Stereo L 25115

If you fancy some whimsical, nonsensical tunes played by an amateur brass band of another era, then I cannot suggest a better album than this. A great deal of time and money has gone into the re-creation of the original Jack Daniel's Silver Cornet Band from Lynchburg, Tennessee, and it has been thoroughly worthwhile. Recording quality is generally good though a trifle edgy at times and there is some surface "prickle" and tape hiss. But unless you're very fussy in this regard, it can be recommended.

Some of the tunes presented on the disc are: The Bear Went Over The Mountain—Hail Hail The Gang's All Here—Ta Ra Ra Boom Te A—The Whistler And His Dog—Listen To The Mocking Bird—Shenandoah—Row, Row, Row—Waiting For The Robert E. Lee. (L.D.S.)

MY HEART REMINDS ME. The Paul Robinson Players Good Earth Records WG/S5611 W&G Release.

To be honest, I had never heard of this group of musicians; more to my sorrow as they produce a very pleasing sound, something akin to a scaled down Mantovani. They make their tuneful way through ten fairly standard numbers as follows: A Man Without Love—Somewhere My Love—Ode To Billy Joe—Softly As I Leave You—The Girl From Ipanema—Autumn Concerto—The Shadow Of Your Smile—I've Grown Accustomed To Her Face—By The Time I Get To Phoenix—I Left My Heart In San Francisco.

The sound quality is excellent and the stereo facility is skillfully used, making an ideal record for dinner background or dancing. (N.J.M.)

★ ★ ★

THE ROYAL TOURNAMENT 1974—"TRAFALGAR" Columbia Stereo, SCXO 6568.

I cannot imagine who in Australia would want a recording of a military pageant held in London, but if you have a place in your collection for a record of this type, this one is certainly exciting enough and well recorded. Various British military bands provide a high standard

DECCA record brush

1,000,000 CONDUCTIVE BRISTLES

no anti-static fluids needed

The new DECCA Record Brush consists of a million tiny fibre 'bristles'. As you brush the record surface, upward of a thousand 'bristles' enter each groove and remove more dust and grit than any other product available. In addition, each 'bristle' is *electrically conductive*. Static on the record is removed as you clean, without the aid of special fluids.

* \$12.50 at leading Hi-Fi stores & record bars.

Australian Agent: British Merchandising Pty. Ltd., 49-51 York St., Sydney. Ph. 29-1571.

* Recommended retail price.



3 Dimensional

A fascinating game...a decorative talking piece!




Feeling tired? . . . Overworked? . . . Here's a way to relax and enjoy a new concept of good old noughts and crosses.

Yes, noughts and crosses but with a new 3-dimensional twist . . . noughts and crosses in the horizontal, vertical and oblique planes . . . and all at the same time. It's a new international pastime . . . it's fun and keeps your mind active.

And when you're not playing, its smart modern appearance provides an intriguing decoration in the lounge or study.

\$9.95

Including postage

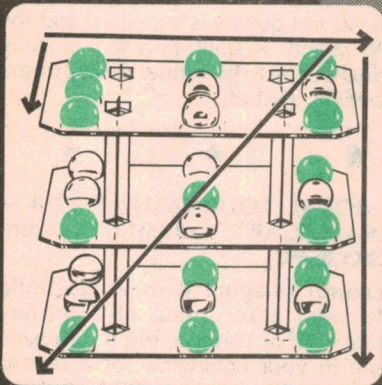

* An Electronics Australia Offer

ELECTRONICS AUSTRALIA Reader Service (3-Dimensional O's & X's), P.O. Box 162, Beaconsfield, N.S.W. 2014. Cheque should be endorsed on the back with sender's name and address and made payable to ELECTRONICS AUSTRALIA. This offer is open to readers in Australia only.

HOW TO ORDER: Fill in BOTH sections of the coupon. In each section print your name and full postal address in block letters. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to

Name.....

Address.....

State.....Postcode.....

ELECTRONICS AUSTRALIA 3-Dimensional O's & X's

Name.....

Address.....

State.....Postcode.....

Please send me..... (state quantity) your sets of Trimula. I enclose my cheque, postal/money order to the value of.....

VARIETY FARE

of band music and an exotic touch is provided by the drums of the Sri Lanka Police Reserve. A large part of side 2 is devoted to the main theme of the 1974 Tournament — "Trafalgar". Presumably the audience present on the occasion were treated to an impressive visual spectacle, but the sound only presentation has a considerable amount of interest when heard in conjunction with the sleeve note. (H.A.T.)

★ ★ ★

JERRY SMITH, RAG TIME. Interfusion, Harlequin series L 25153. Astor release.

Excellent ragtime piano playing with an occasional touch of 'boogie' style makes up this record with a dozen all-time piano hits. As the titles show, most of the tracks fall into the singalong category: Johnson Rag—The Old Piano Roll Blues—Baby Face—Ragtime Cowboy Joe—Music Music Music—Give The World A Smile—Rattle Trap—12th Street Rag—Down Yonder—Red River Valley—Swanee River—Laura's Living Room. The quality presents no problems and the backing group does a competent job to make up an enjoyable party record. (N.J.M.)

★ ★ ★

THE GREAT RAGTIME CLASSICS. Paul Hersh and David Montgomery. RCA Victrola stereo AVL1-0364.

To listen to this album is to learn the meaning of the expression "tickle the ivories". The arrangements for dual ragtime pianos (hony-tonk?) are very lively and make cheerful listening. For the finicky listener there is an edginess to the sound which tends to irritate after a short while. With this reservation, it's still a good album.

Rag titles are as follows: Bohemia—The Music Box—Swipsey Cakewalk—Shreveport Stomp—The Entertainer—Maple Leaf Rag—Wall Street Rag King Porter Stomp—Grampa's Spells—Castle House Rag—Cleopatra Rag. (L.D.S.)

★ ★ ★

DUTCH SWING COLLEGE BAND. 25th Anniversary Concert Parlophone PCSO 7572 Stereo EMI Release

The Dutch Swing College Band has been a part of the European Jazz scene since it was formed in 1945 and their professional, crisp Dixieland brand of playing has earned them a loyal following right through the world. This record was made during a concert and ball to celebrate the Band's 25th anniversary in 1970 and includes these titles: Way Down Yonder In New Orleans — There'll Come A Time — Strange Peach — Silver Jubilee

Blues — King Porter Stomp — Livery Stables Blues — Henry Hudson — Yesterdays — I'm Crazy 'Bout My Baby — Mississippi Mud — Rose Room — Rose Of The Rio Grande.

The quality is really good; a must for Dixieland fans! (N.J.M.)

★ ★ ★

THE MAN WITH THE GOLDEN GUN. Movie Sound Track United Artists L 35370 Festival Release.

My thoughts on sound track records I have made known before: unless you have seen the film and are really crazy about it, why buy a souvenir of some of the music? This record has the redeeming grace of technical brilliance that puts it in the demonstration disc class to show off your new electronic furniture. All the tracks carry the main theme, with instrumental and tempo changes to break the monotony.

Try to listen before you buy. (N.J.M.)

★ ★ ★

FAMILIAR FAVOURITES. Joseph Seal at the Wurlitzer. Stereo, Astor GGS-1441. Also on cassette.

Joseph Seal is certainly making his presence felt with albums on the pipe Wurlitzer: an old-time organist on an old-time instrument, playing music in the traditional theatre manner. And the numbers on this disc are among those which were often performed by way of

a change from the usual round of current hits and music hall favourites: Knightsbridge March — Beautiful Dreamer — Ballet Egyptian No. 1 — Chanson De Matin — Valse Caprice — Thrill Of The Pipes — Trees — Beautiful Spring — In A Monastery Garden — Can-Can (Orpheus In The Underworld).

Listen carefully and you'll notice a certain amount of auditorium noise in the background. And, here and there some of the detail suffers as pipes come in a split second late or chop off a fraction too soon. For these and other reasons many don't like the big cinema organs but, if you're one of the large band of enthusiasts, you enjoy this latest offering from the well known English organist recorded, I would assume, at the ABC Theatre, Kingston on Thames. (W.N.W.)

★ ★ ★

THE WORLD'S GREATEST OPERATIC ARIAS. Harry Secombe, tenor, with orchestra directed by Peter Knight. Philips Stereo, 6308 203.

Harry Secombe is a first rate comic and entertainer who also happens to have a fine tenor voice, but this does not qualify him for a purely operatic program. There are numerous discs of this kind recorded by the leading tenors singing today, and Harry Secombe simply cannot compare with them in interpretative depth. Therefore, if you need a good recording of the great arias recorded here look elsewhere. If you want a disc to show



COLOUR BAR GENERATOR

PUSH BUTTON MODEL COLROSE —PBC III

- ★ Provides the **THREE COLOUR BAR STANDARDS** as used in Aust. (100% Amp. 100% Sat., 100% Amp. 95% Sat., & 75% Amp. 100% Sat.)
- ★ Provides **THREE 8 STEP GREYSCALE PATTERNS**
- ★ Accurately centred **CROSSHATCH** patterns for precise adjustment of picture height, width and linearity.

Other features include: ★ **DOTS** ★ **VERTICAL LINES** ★ **HORIZONTAL LINES** ★ **VERTICAL BARS** ★ **RED SCREEN** ★ **WHITE SCREEN** ★ **PAL/NTSC COLOUR BARS** ★ **PAL/NTSC RED GREYSCALES** ★ **VARIABLE BURST AMPLITUDE** ★ **VARIABLE VIDEO OUTPUT** — pos. or neg. polarity ★ **VHF OUTPUT** — tunable ★ **SOUND CARRIER** — modulated (1KHz) or unmodulated ★ **CANCEL Y** (Luminance) U (B-Y) and V (R-Y) switches ★ **SYNC OUTPUT** for triggering C.R.O. ★ **ALL PATTERNS ACCURATELY CENTRED**

Introductory Price:

ONLY \$350.00 + 15% S/T.

COLROSE ELECTRONICS

13 FRED A STREET, NETLEY, S.A. 5037 Phone 293 5617

ELECTRONICS Australia, May, 1975

NEW ALL-TRANSISTOR STEREO AMPLIFIERS ULTIMATE IN DESIGN—LONG DEPENDABILITY

Using all silicon transistors 50 WATTS—RMS

SPECIFICATIONS

POWER OUTPUT:

25 watts per channel R.M.S. Total output 50 watts R.M.S. 8 Ohms.

FREQUENCY RESPONSE:
20 cycles to 40,000 \pm 1dB

HUM & NOISE:

Aux. 70dB. Mag. 60dB.

INPUT SENSITIVITY:
Mag. 2mv. Aux. 250mv.

EQUALISED:

Mag. RIAA.

TONE CONTROLS:

Bass 50 c/s \pm 13dB. Treble 10kc s 15dB.

HARMONIC DISTORTION:

Less than .05 per cent.

LOUDNESS CONTROL:

50 c/s 10dB.

SCRATCH FILTER:

(high filter) at 10kc s 5dB.

RUMBLE FILTER:

(low filter) at 50 c/s 5dB.

PROVISION FOR TAPE RECORDER:

Record or playback with din plug connector.

SPEAKER SWITCHING:

Two sets of speakers can be connected and selected by switch on front panel; they can also be driven together.

HEADPHONES:

Headphone jack is situated on front panel.

DIMENSIONS:


16 1/2 in. x 11 in. deep x 5 in. high. Weight 16lbs.

POWER SUPPLY:

Regulated power supply with switching protection for output transistors.

SEMICONDUCTORS:

30 Silicon transistors plus 7 diodes.

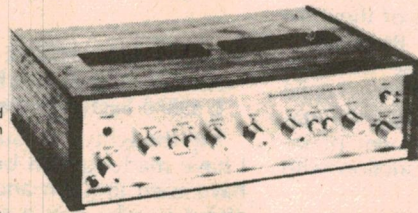

\$140.00

**CABINET
EXTRA
PLUS
FREIGHT**

— MODEL C.700 —

Cabinet available in teak or oiled walnut finish with matching metal trim. \$12.00 extra.

PROVISION FOR 4 CHANNEL. All units wired with sockets & control for simulated 4 channel only requires the addition of two extra speakers.

MAGNAVOX & PHILIPS SPEAKER KITS

NEW MAGNAVOX-PHILIPS 3 WAY SPEAKER SYSTEM

FREQUENCY RESPONSE 35Hz to 25KHz
POWER HANDLING CAPACITY 30 Watts R.M.S.

DRIVE UNITS:

Magnavox 8-30 High Performance
8in. Bass Unit o Magnavox 6J

—6in. Mid Range Speaker Philips

High Fidelity Dome Tweeter.

SPEAKER KIT: (less cabinet) comprising 1 8-30 speaker, 1 6J

speaker, 1 Philips dome tweeter,

1 1mh. inductance, 1 8 mfd. & 1

4 mfd. polyester condenser, 1 3" & 1 6" tube, innabond & speaker silk, plans for cabinet.

\$40.00. Reg. Post & Packing \$3 Extra.

CABINET AVAILABLE

— MAGNAVOX PHILIPS 2 WAY —

AS FEATURED IN JAN 75
ELECTRONICS AUST.
COMPLETE KIT OF PARTS.
Less cabinet.

\$35.00

post & packing \$3.00 extra.
CABINET AVAILABLE.

— PHILIPS 2 WAY —

AS FEATURES IN MARCH 75
ELECTRONICS AUST.
COMPLETE KIT OF PARTS.
Less cabinet.

\$32.00


post & packing \$3.00 extra.
CABINET AVAILABLE.

24 WATT R.M.S. HI-FI SYSTEM \$229.00



EXPO 1212 AMPLIFIER 24 WATTS R.M.S. (12 watts r.m.s. per channel) IN WALNUT FINISHED CABINET WITH HIGH FILTER, LOUDNESS CONTROL & TAPE MONITOR. FREQUENCY RESPONSE 20 TO 25,000 CYCLES, DISTORTION BETTER THAN 0.5% AT FULL RATED OUTPUT. GARRARD 6-300 CHANGER WITH SHURE MAG. CART. WITH BASE & COVER. TWO FOUR WAY SPEAKER SYSTEMS; TWO PHILIPS 8" & TWO PHILIPS TWEETERS IN EACH SYSTEM. WALNUT FINISH. (regret no mail orders).

NEW PLAYMASTER 143 AMPLIFIER

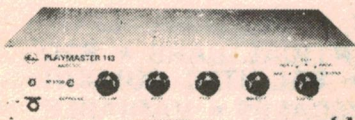

As featured in Sept & Oct.
issues of *Electronics
Australia*.

\$72.00

Complete kit of parts including all transistors for this high fidelity 25 watt amplifier, silver anodised panel with black lettering and matching silver anodised knobs & special transformer with electrostatic shield. Reg. post & packing \$3.00 extra.


De luxe version of the 143 amp. with high & low filters as used in the 140 playmaster plus loudness control **\$7.80 extra.**

NEW N.C. 310 DELUXE TRANSCEIVER

For 27240 or 27880 KHz operation (state which required) with switch position for additional two-channels tone call signal, noise squelch control, circuit contains 13 transistors, diode and thermistor. Transmitter stability crystal controlled. .005 Ceramic filter. Aerial 9 section telescopic powered by 8 1.5v UM3 batteries. Range up to 10 miles depending on conditions. Battery check meter. Attractive and durable die cast case with provision for external speaker, aerial and power supply. **\$49.50**

REG. POST \$2.00 EXTRA

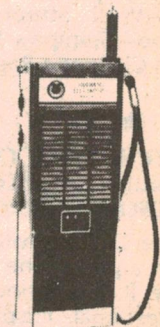At last a breakthrough in the cost for high quality portable radio transceivers of the walkie-talkie hand-held type. We are introducing and offering for sale a fully PMG approved transceiver.



CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045
PHONES 798 7145, 798 6507

VARIETY FARE

the versatility of genial Harry Secombe, singing fine music, this could well be worth your attention. The titles include such well known tenor arias as Flower Song from "Carmen"—Strange Harmony of Contrasts, and When the Stars were Brightly Shining, both from "Tosca"—woman is Fickle from "Rigoletto"—None Shall Sleep from "Turandot"—On with the Motley from "I Pagliacci"—and others from "Manon Lescaut", "L'Africana", "Martha", "L'Arlesiana", "Fair Maid of Perth". The recording is of satisfactory standard. (H.A.T.)

★ ★ ★

ALFONS BAUER. Sonic stereo 9075

The manufacturers of Astor and allied record labels are doing themselves a disservice in the marketing of this record. They could have at least translated the track titles and then perhaps provided a few explanatory notes to sell what is a very well recorded and thoroughly pleasant album.

Alfons Bauer is portrayed on the cover as a rather bemused gent in Austrian national dress and playing a zither. Accompanying him with piano accordion is an attractive lass also in national dress. They play some very lively and cheerful music with a suitable complement of yodelling on some tracks.

There is little point in listing the tunes played as they are all in a very foreign language. (L.D.S.)

★ ★ ★

SONGS SUNG BLUE (AND OTHER COLOURS). Val Doonican. Philips 6326 600 Stereo. Phonogram release.

I always enjoy Val Doonican's performances, whether on record or TV and this recent release from the Philips label only reinforces the view. Twelve of the top tunes of recent years make up the content: Sing—There Ya Go—It's Four In The Morning—Faces And Places—Amazing Grace—If You Could Read My Mind—Song Sung Blue—Spanish Eyes—Tie A Yellow Ribbon Round The Old Oak Tree—Sweet Caroline—Children—Oh Babe, What Would You Say.

The orchestra and chorus directed by Ken Woodman do a good job and, with good quality and sound, make an excellent buy for anyone that enjoys a ballad. (N.J.M.)

★ ★ ★

JUDITH DURHAM & THE HOTTEST BAND IN TOWN. Volume 2. Interfusion stereo L 35331.

Women's Libbers would be cheered to know that I find Judith Durham overpowering. Judy puts every last gram of effort into her songs on this album and the result is a sort of female Tom Jones.

Add the big brassy accompanying orchestra and the result is unbearably loud with the volume turned anything above a whisper. Please sing a little more softly, next time!

Thirteen tracks are featured: Basin Street Blues—Papa If You Can't Do Better—The Man I Love—Nobody's Blues But Mine—The Hottest Band In Town—Coney Island Washband—Down By The Riverside—What'll I Do—Louisville Lou—It's Goin' To Be A Beautiful Day—The Entertainer—Chase Those Blues Away—On Revival Day. (L.D.S.)

★ ★ ★

FIRST IMPRESSIONS. Olivia Newton-John. Interfusion stereo L 35375.

Olivia Newton-John deserves to do well in her singing career. Her songs are well chosen and she sings them in a straightforward way that is refreshing to listen to after some of the garbage that is passed off as talent in popular music. On the other side of the coin, the sound quality on this disc is on the rough side. Let us hope that Olivia follows the lead taken by some other successful pop artists in demanding quality recordings.

Tracks include all her recent hits: If Not For You—Banks Of The Ohio—Winterwood—Take Me Home, Country Road—Amoureuse—Let Me Be There—I Love You, I Honestly Love You—Long Live Love—If You Love Me Let Me Know—What Is Life—If We Try—Music Makes My Day. (L.D.S.)

"INNERBOND"

(Regd.)

BONDED ACETATE FIBRES

FOR PACKING IN
SPEAKER ENCLOSURES

A new resilient Bonded Wadding made from ultra fine Cellulose Acetate Fibres that gives high efficiency for sound absorption. "INNERBOND" is light, clean, dust-free and easy to handle. Because all the fibres are bonded "INNERBOND" will hang as a "curtain" and will not fracture or break down due to vibration. "INNERBOND" is odourless, highly resistant to attack by bacteria or fungus and is vermin repellent. "INNERBOND" at 1602 sq. yd. has a normal thickness of 1" and at this density is recommended as a packing in speaker enclosures for sound absorption.

If unobtainable

For 1 sq. yd. as above send \$2.00
For 2 sq. yds. as above send \$3.75
For 4 sq. yds. as above send \$6.50

+ POSTAGE AS APPLICABLE

WONDER WOOL

PTY LTD

87 JAMES STREET, LEICHHARDT
NSW 2040

Box 548 — GPO, Sydney 2001
Phone 56 2780

For fine detail work — a hands free magnifier



The **Magna-Sighter** is a precision 3-D binocular magnifier that leaves your hands completely free for work. It has hundreds of applications, and is invaluable for scientists, technicians, craftsmen, toolmakers, hobbyists, etc. Slips easily over the head—over glasses, too. Proved and used by many U.S. universities, space research bureaux, government departments and major industrial organisations. Available in 3 different magnifications. Price \$18.00

MAGNA-SIGHTER

For further information send this coupon today:

STOTT TECHNICAL SERVICES MEA 575
(Division of Stott's

Technical Correspondence College Pty. Ltd.)

159 Flinders Lane, Melbourne, Vic., 3000

Please send me full information on the 3-D Magna-Sighter. I understand that no Sales Representative will call.

Name.....

Address.....

Postcode.....

STC 721

LARGEST RANGE IN AUSTRALIA OF ELECTRONIC AND RADIO BOOKS

Mail orders available, prompt attention. See below for this month's new publications.


Now available 1975 Edition	
World Radio TV Handbook	\$8.95
Philips 1974 Pocketbook	\$2.75
Diodes Equivalents	
by De Muiderkring	\$5.95
Electrical Calculations	
by A. Mychael	\$4.45
How to Use Vectorscopes,	
Oscilloscopes & Sweep-Signal	
Generators	
by Stan Prentiss	\$6.15
Solid-State Devices and	
Applications	
by Rhys Lewis	\$6.60
IC OP-AMP Cookbook	
by Walter Jung	\$14.90
United States Callbook	
1975 Edition	\$15.95
Foreign Radio Amateur Callbook	
1975 Edition	\$14.95

Postage 45c Local
Postage 65c Interstate

McGILLS

Authorised Newsagency Pty. Ltd.

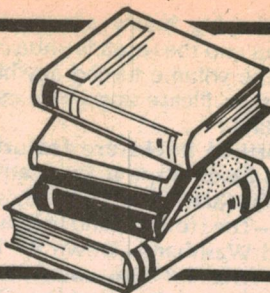187 Elizabeth Street
MELBOURNE, VIC. 3000
Phone 60 1475



Books & Literature

Amplifier design

WIDEBAND VOLTAGE AMPLIFIERS, by C. W. DAVIDSON. Published by Intertext Publishing Ltd, Aylesbury, UK, 1975. Soft covers, 150 x 228mm, 112pp, many circuits and diagrams. Price in UK £1.95.

This is a brief but thorough little text, or more properly a monograph, on the operation and design of solid state amplifiers dealing with signals up to about 10MHz. It is intended for the undergraduate engineering student and for the practising design engineer and technician.

The flow of thought is logical, starting with basic principles of devices and circuits, and progressing through considerations of feedback, noise, distortion, output capabilities, etc, to various types of amplifier and their application.

The text is written in clear, concise

language, and is well served by illustrations.

In short, while only modest in size and price, it gives just about all the detail information needed for any reasonably competent technician or engineer to design amplifiers using either discrete transistors (bipolar or FET) or ICs.

The review copy came direct from the publisher, with no information as to local price and availability. (J.R.)

Broadcasting

1975 WORLD RADIO AND TELEVISION HANDBOOK, 29th edition, published by World Radio and Television Handbook Co Ltd, Denmark, edited by Jans Frost.

The 29th edition is the biggest in size yet, with 440 pages crammed full of information on radio and television stations throughout the world.

In the past few years the major complaints have been the poor binding and the small print. The publication this year was printed and bound in the United States and uses a much bolder print.

The Handbook has come a long way since the first issue in 1947 with its 80 pages of information. Today radio listeners, professional monitors, broadcasters and the radio industry look on the World Radio Handbook as the complete directory of broadcasting and television world wide.

This year they should not be disappointed with the edition. It has many new features, and its information on stations in interesting countries like the USSR and Indonesia is the most comprehensive yet. The USSR details have been gathered mainly from monitoring.

As well as the details on every radio and television station under alphabetical country, listing schedules with power, frequency, addresses and other relevant information, this issue includes articles on the New Plan of Long Wave and Medium Wave, Solar activity in 1975, International regulations of the Broadcasting Service, How will Shortwave reception be today, and other articles on similar lines. At the back there is a full list of every station in order of frequency, so that cross reference is available.

As one who has handled the Handbook since its first edition, and watched the growth of this publication into the only reference manual of its type, and with my understanding of the work in-

KENWOOD



QR-666

the ALL-band

COMMUNICATIONS RECEIVER

that gives
you the world
and an FM
option, too.

All-band/all-mode reception on frequencies 170 kHz to 30 MHz covered by 6 bands. Receives broadcasts in any mode AM, SSB, CW or FM—with the optional accessory QR6-FM. Super sensitivity from dual gate MOS types FET's, double signal selectivity and AGC characteristics. IF circuit with mechanical and ceramic filters designed for high selectivity, resistance to interference; single button selection of wide band (5 kHz/6dB) or narrow band 2.5 kHz/6dB. Altogether a high performance compact, smartly styled unit of advanced design at a suggested 'Today' price of \$332.20.



—Mail coupon NOW!—

Weston Electronics Company
215 North Rocks Rd., North Rocks, N.S.W. 2151 Phone 630-7400

Please send details of
the Kenwood QR-666

NAME.....

ADDRESS.....

POSTCODE.....

volved in contacting thousands of stations for information, I can only express the gratitude of listeners everywhere to Jans Frost for another excellent edition.

The Handbook is available from technical bookstores or from Arthur Cushen, 212 Earn Street, Invercargill, New Zealand from whom a free brochure is available. (A.T.C.)

Amateur radio

AMATEUR RADIO TECHNIQUES by Pat Hawker, G3VA, 5th edition. Published by the Radio Society of Great Britain. Light card cover 245 x 185mm, 304pp, many circuits.

Now in its 5th edition, Pat Hawker's "Amateur Radio Techniques" is becoming something of a tradition in the field of amateur radio. For those who are unfamiliar with it, the author stresses that it is in no sense a textbook of radio theory, although it does, in fact, contain a lot of helpful discussion. It aims rather to be a companion volume providing hundreds of practical ideas and circuits to supplement normal theoretical study.

For the most part, the material has been adapted from items prepared for publication in the "RSGB Bulletin" (now "Radio Communication") so that its authenticity and relevance to the amateur scene is never in doubt.

The material has been grouped under general headings as follow: Semiconductors; Components and Construction; Receiver Topics; Transmitter Topics; Audio and Modulation; Power Supplies; Aerial Topics; Fault Finding and Test Units; Appendix; Index.

For those familiar with earlier editions, the natural question is how much of the material is new. The publisher's answer is: "... a considerable amount, in addition to revision and expansion of many sections." Those with a fifth (1974) edition may conceivably debate the investment but readers with older editions should be in no doubt. There really is a lot of material in Pat Hawker's book.

Our copy came direct from the publishers but supplies should be available by now through technical bookshops. (W.N.W.)

ATTENTION STUDENTS

Our handbooks are now basic texts or recommended reading for many courses. Have you got yours?

- **Fundamentals of Solid State**
Semiconductor theory \$3.00
- **Introduction to Digital Electronics**
Digital theory & practice \$3.00
- **Basic Electronics**
Starts from beginning \$3.00

Plus 60 cents each post/package.

BIG REWARDS WAIT FOR YOU IN COLOUR TELEVISION SERVICING -if you're trained for it!

Colour TV is the exciting breakthrough for the electronics service industry. It offers a great future for the service man who's gained the knowledge necessary to do the job.

Stott's introduce a brand new course designed to take you, step by step, all the way from basic electronic theory through to colour television receiver servicing techniques.

If you're a beginner, it can teach you everything you need to know about television principles and receiver circuitry.

If you are already working in the field or have already successfully completed some studies in electronics, you may be eligible to commence the course at an advanced stage.


Divided into three sections, the Stott's course covers:

- Part 1 — Introduction to Electronics (theory and practice)
- Part 2 — Monochrome Television Receivers.
- Part 3 — Colour Television including fundamentals, colour processing circuitry, servicing techniques and faults.

Like all Stott's courses, you will work with your own instructor, an expert in this exciting field, at your own pace, in your own home. Whether you intend to enter the television service industry, or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course to help you make it.

Other electronic courses offered by Stott's include:
Radio for Amateurs — Amateur Operator's Certificate

For full information mail this coupon today:

Stotts 

159 Flinders La, Melb., 3000
383 George St, Sydney, 2000
290 Adelaide St, Brisbane, 4000
66 King William St, Kent Town 5067
89 St. George's Tce, Perth, 6000
P.O. Box 3396, Singapore 1

TECHNICAL CORRESPONDENCE COLLEGE

The name to trust in correspondence education

Please send me free, and without obligation, full details of the following courses

.....

Stott's undertake that no sales counsellor will call

Mr, Mrs, Miss..... Age.....

Address.....

..... Postcode.....

EA 375

STC761

New Products

General Electric TC20T1 colour receiver

One of the latest colour TV sets to appear on the Australian market is the General Electric model TC20T1, marketed by General Electric-Kirby Appliances Ltd. It uses a 500mm (20in) picture tube and features an "instant on" facility, whereby both picture and sound are available immediately the set is switched on.

In greater detail the tube is a 110° deflection type, with a delta gun configuration and a black matrix screen. It is designed to present a correct 3 to 4 aspect ratio picture.

The 500mm tube would seem to be a good compromise between size and cost. As a guide, it is somewhat wider (406mm) and higher (304mm) than the old 17 in screen. Add to this the straighter sides, sharper corners, and correct aspect ratio and the result is a very satisfying picture area.

The cabinet measures 639mm x 448 mm x 469mm (W x H x D) and the complete set weighs 34kg (75lbs). The

model submitted to us was finished with a teak pattern vinyl covering with a chrome surround on the front. It was well finished and had considerable eye appeal, particularly for the ladies.

The set is fully isolated from the mains,

sion and contraction associated with the heating and cooling cycles. By reducing changes in temperature to a minimum the risk of failure from this cause is also minimised. An additional switch allows the set to be switched off completely during holidays, etc.

The set submitted to us was taken at random from stock and delivered in its original packing. It was simply unpacked and connected to mains and aerial without adjustment of any kind. It produced first class pictures immediately, the convergence being well within tolerance.

Subsequently some herringbone pattern was noticed on channel 2, but we had been forewarned about this, and adjustment of the AGC control was all that was needed to control it.

The set has ample reserve of brightness, contrast, and colour intensity—more than could be used in most cases—and gives good results even in well lit rooms.

The set is made up from 11 modules, all of which may be replaced without the need for a soldering iron. General Electric are providing a board exchange service for dealers not equipped to repair their own boards. On the other hand,

The attractive styling of the General Electric colour TV set is seen in this picture. A combined "on-off" and volume control is alongside the channel selector, and the brightness, contrast, and colour controls are slide types alongside the speaker grill.



UNITED TRADE SALES PTY LTD

280 LONSDALE STREET.
MELBOURNE, 3000
TELEPHONE: 663 3815


THIS MONTH'S SPECIAL

TAPE PUNCHES as illustrated featured in E.A. March '75 only \$12 ea. freight forward.

TAPE READERS \$12 ea. F/F.

KEYBOARDS only \$4 ea. F/F.

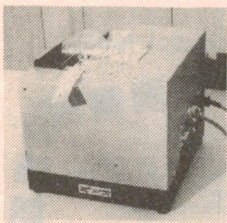POWER SUPPLY for above 120V. DC—240 AC Input \$10 ea. F/F.



COMPUTER TAPE 1/2" Diameter on 10 1/2" reels in plastic boxes. \$1 each P/P \$1.

COMPUTER BOARDS. Approx. 10 transistors. Plus 30 Diodes and resistors on each board. All components have long leads. 6 boards for \$6. Plus \$1 P/P.

COMPUTER RELAYS. Silver wire type. 4 sets changeover contacts. Size 2 1/2" x 1" x 1/2". Complete with socket. 50c each P/P 20c. As above, but with latching coil assembly. 75c each P/P 20c.

CASSETTE TAPE HEADS. Mono. 300 ohms. \$1.50 each P/P 15c.

using a double wound 50Hz transformer, has a 13 channel tuner, uses a PAL-D (delay) circuit, and in all other respects conforms to the ABCB standards.

The tuner is equipped to take either 300 ohm ribbon or 75 ohm coax. It is fitted with a memory type fine tuning control, whereby the control is pushed in to set the tuning, after which this setting is selected automatically.

The "instant on" feature is achieved by running the picture tube heater continuously, at a reduced voltage. When the remainder of the set is switched on and full heater voltage restored, it requires only about one second for the heater to reach operating temperature.

While this may sound like a gimmick, it proved more convenient in practice than one would imagine. More importantly, the makers claim that this actually increases the tube life. Heater failure is normally caused by the repeated expan-


the boards are of open construction and readily repairable. The set carries a 90 day warranty and the picture tube a 12 month warranty.

The convergence controls, 14 in all, are mounted on a sub-panel near the top of the cabinet. It is designed to be easily demounted and placed on top of the cabinet so that the technician can face the screen while working.

We had the opportunity to use the set in a typical domestic environment over a period of several days, and our reaction is that it appears to be an excellent set in its size class. On live material and good quality tapes it produced pictures which can only be described as superb—and this with virtually no setting up adjustments of any kind.

Recommended price is \$669.00 without a stand. A mobile stand, on castors, is available for an additional \$30.00, making the total price \$699.00. (P.G.W.)

Portable DMM/CRO combination

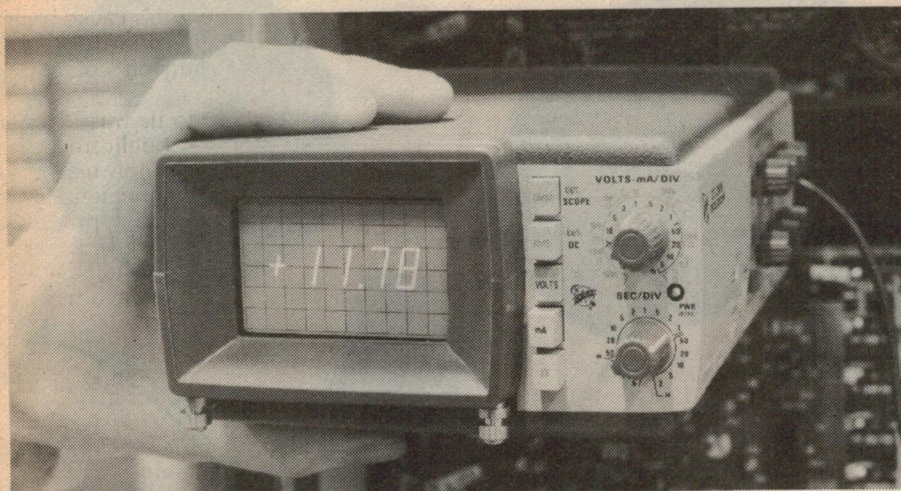

This new Tektronix instrument measures only 7.6 x 13.2 x 22.6cm, and weighs only 1.7kg. Yet it combines probably the two most useful measuring instruments of modern electronics: an oscilloscope and a digital multimeter. In addition, it runs from an internal, rechargeable battery and is thus truly portable.

Designated the model 213, it is ideal for precision servicing and field measurements. As a DMM, it provides DC and AC measurement ranges from 0.1V to 1000V, DC and AC current ranges from 0.1mA to 1A and resistance ranges from 1k to 10M. The AC ranges include a true RMS measurement capability, making it suitable for non-sinusoidal measurements.

In oscilloscope mode the 213 provides calibrated deflection factors from 20mV/div to 100V/div at DC-1MHz bandwidth, with an extension down to 5mV/div at 400kHz bandwidth. Current waveforms can also be displayed easily, with deflection factors from 5uA to 100mA/div. Sweep rates are from 2us to 500ms/div, with a variable magnifier providing up to 0.4us/div.


Readout for both DMM and CRO functions is via the CRT, with a 3 x 5cm screen. The 3½ digit DMM display occupies an area 1 x 4cm, giving easy readability.

Enquiries to Tektronix Australia Pty Ltd, with offices in each state.

"Zippy" boxes


To dress up those small projects without spending too much money, Dick Smith Electronics can supply these "zippy" boxes. The boxes themselves are moulded in ABS plastic, and normally come complete with a flush fitting aluminium panel, attaching via four self-tapping screws. There are two sizes, UB1 at 15 x 9 x 5cm (price \$2.00) and UB3 at 12.5 x 6 x 4cm (price \$1.65). Optional alternative panels are available.

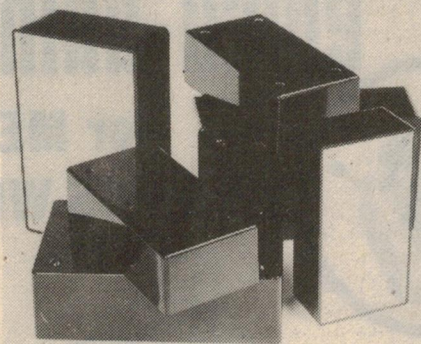Enquiries to Dick Smith Electronics at 162 Pacific Hwy, Gore Hill 2065.



Flyback transistors

Finding replacement horizontal output transistors for imported solid-state TV receivers can present problems. Those involved in the servicing of such equipment may therefore be interested to know that Paris Radio and Electronics have good stocks of the type 2SC643A, an NPN silicon device with Pt rating of 50W, BVceo rating of 800V, BVcbo rating of 1500V, and Ic rating of 2.5A. Hfe range is 7-50 at 2A. With these ratings it should be suitable for replacement purposes in many receivers.

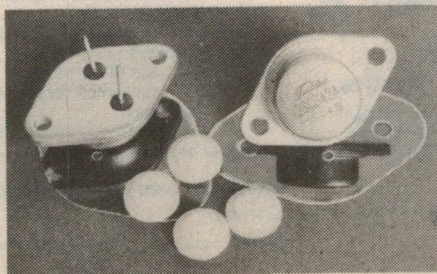

For further details on these and other components handled by Paris Radio, readers should contact them at P.O. Box 380, Darlinghurst 2010.

E-Z-HOOK SCOPE CABLES LET YOU CUSTOMIZE

The best way to fully extend the use of your scope. Simple spring-loaded hook attaches with a single contact point. Frees your hands, while making a safe, short-free connection. Inner terminal board comes connected as a direct probe with a removable link for the addition of circuitry, permitting customizing of probe to your specific needs. Strain relief adds to life of cable or lead.

Cable shown: No. 5420.


Specify probe color and cable length. When ordering

Durable, featherweight construction features:


Nylon slide, tenite body (removable for easy access to terminal board), Stainless steel spring, G-10 terminal board, Regular or gold-plated conductor.

Available in Red, Black, Blue, Green, Orange and Silver.

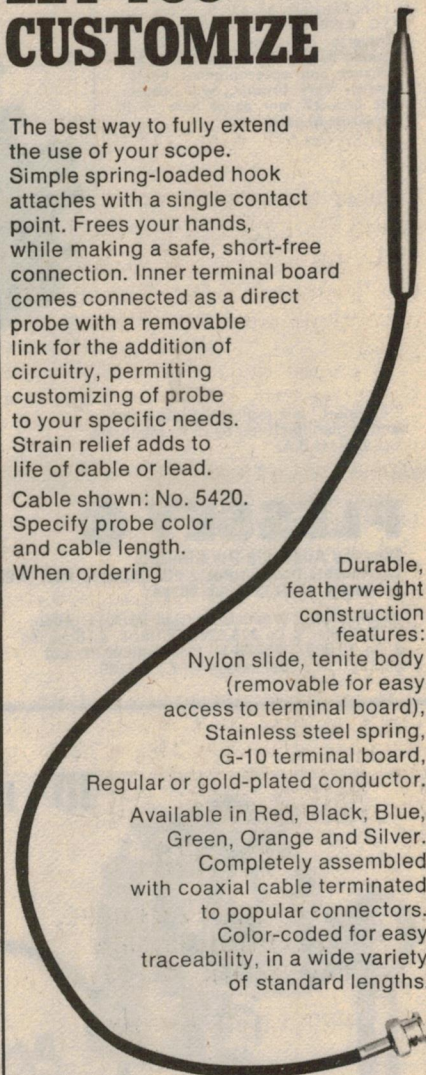Completely assembled with coaxial cable terminated to popular connectors. Color-coded for easy traceability, in a wide variety of standard lengths.



EXCLUSIVE FIELD SERVICEABLE FEATURE

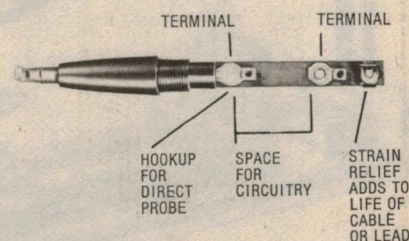

99 ALEXANDER STREET
CROWS NEST
NEW SOUTH WALES
Telephone: 439 2488, 439 2399

BIRTHS


SONALERT (Plessey). — February, 1975. To the Professional Components Division, a baby electronic signal with a big voice. Weight $\frac{1}{2}$ oz. (also less than 21 mm thick). Eagerly welcomed by big brothers Mini Sonalert, SC 628 Sonalert and SC 628P Sonalert. This low silhouette newcomer is seeking a good home in automotive, appliance and entertainment equipment. Very lovable, will snap-in fit into 27 mm panel hole with greatest of ease.

"Sonalert" is a registered trademark and is manufactured by P. R. Mallory & Co. Inc., U.S.A.

PLESSEY 

Plessey Australia Pty Limited
Components Division Box 2 PO Villawood NSW 2163
Telephone 72 0133 Telex 20384

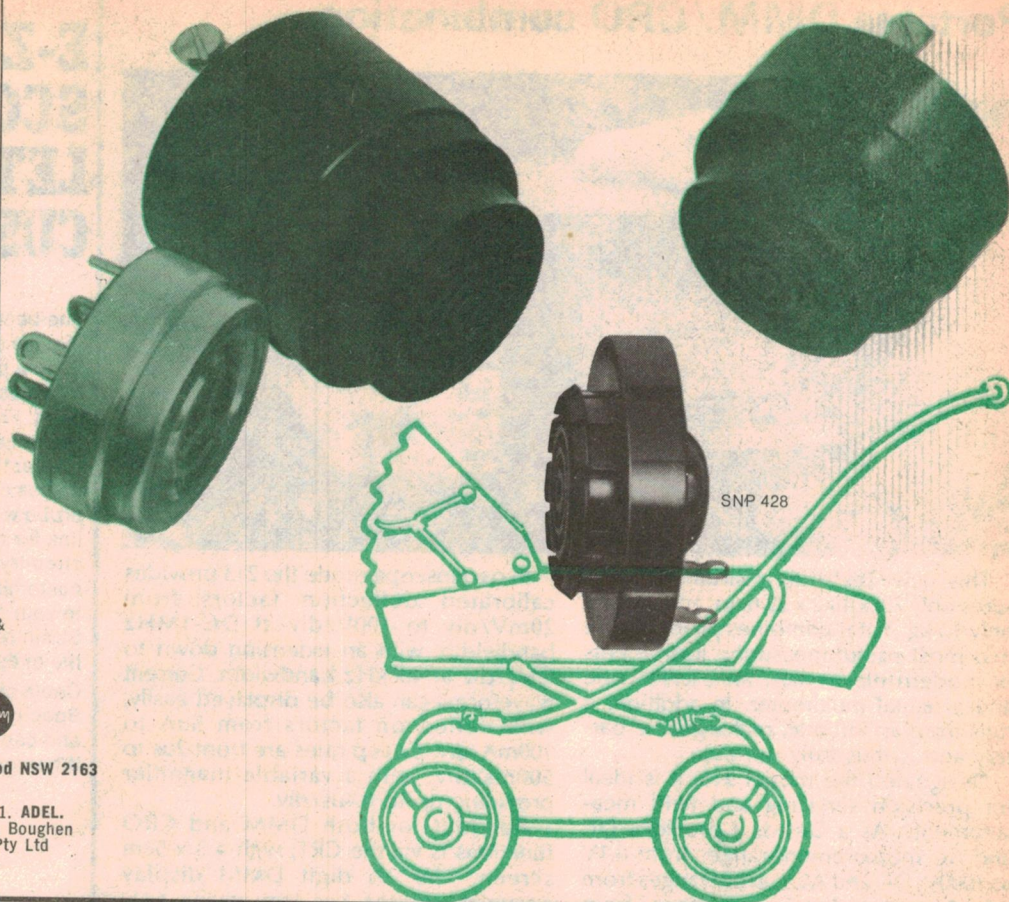MELB. Zephyr Products Pty Ltd 56 7231. ADEL.
K. D. Fisher & Co 223 6294. BRIS. L. E. Boughen
& Co 70 8097. PERTH H. J. McQuillan Pty Ltd
68 7111. N.Z. Henderson (N.Z.) 6 4189.




AC120/RI

10 - IN - 1 MINIATURE MACHINE SHOP

emco-unimat

for METAL PLASTICS WOOD

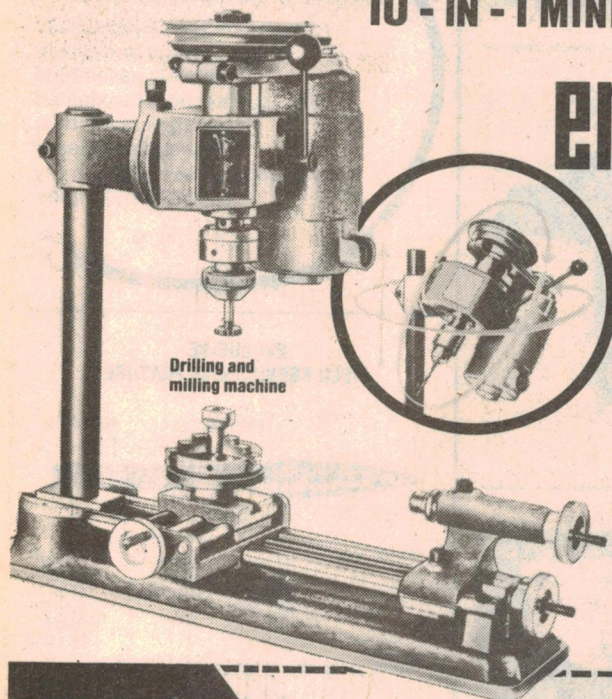

Drilling and
milling machine

The basic unit performs:

1. Turning
2. Drilling
3. Milling
4. Surface grinding
5. Tool grinding


Special unimat features:

- Pre-loaded ball bearing spindle
- 11 spindle speeds
- Detachable rotating headstock
- Motorized, ready-to-run.
- Radio and TV suppressed
- Easily convertible for the various operations
- Performs to very close limits


CONVERTS IN SECONDS TO:




Lathe

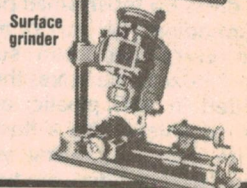

Surface
grinder

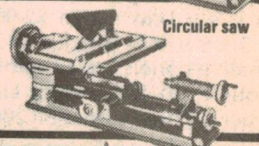

Circular saw

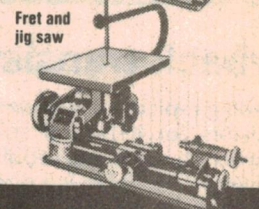

Fret and
jig saw

**MAIL
COUPON
NOW!**

ELLIOTT MACHINE TOOLS
Pty Ltd.

32 Barcoo St, East Roseville,
N.S.W. 2069

Please forward literature on Emco
Unimat.

Name


Address

.....P/C.....EA

emco-unimat

NEW PRODUCTS


Photo-etched panels

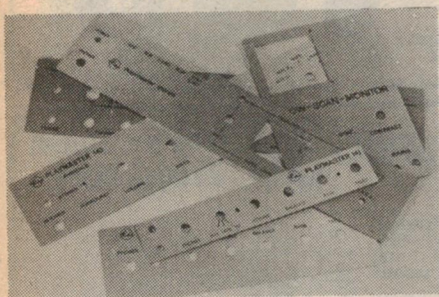

Pictured above is a selection of photo-etched front panels for several recent EA projects. Included are panels for the Playmaster 140, 141, 142 and 143 amplifier projects, the Slow-scan TV Monitor, and the Playmaster 144 Stereo Cassette Deck.

Interested readers should contact Wardrope and Carroll Fabrications Pty Ltd, PO Box 330, Caringbah, NSW 2229.

New plastic case range

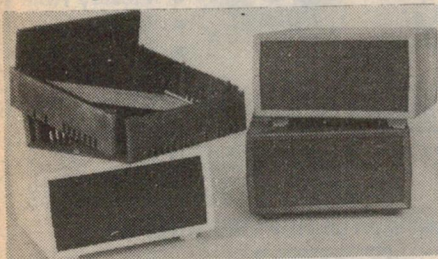

Manufactured by A & R Soanar is this new range of high impact plastic cases, available in a variety of colours. Of modular design, the new cases feature three sets of interior slots for printed circuit card mounting, together with a rear fourth slot for mounting an additional panel (bracket, heat sink etc).

Other features include integral feet, and generous ventilation slits for cooling heat generating components. Interior dimensions are 120 mm x 120 mm x 60 mm.

Write to A & R Soanar Electronics at the address given elsewhere on this page.

"OXFORD"

RADIO CHASSIS
INSTRUMENT CASES
ENGRAVED & PRINTED PANELS
"MINI BOXES" (Aluminium)
Speaker Cases
Rack & Panels (To Order)
Stainless Steel Work (To Order)

Wardrope and Carroll
Fabrications Pty. Ltd.
Box 330 Caringbah 2229
Phone 525 5222

Degaussing wand, battery charger from A & R Soanar


An essential part of every colour TV serviceman's tool kit is a degaussing wand, and this requirement is taken care of by the recently released XT8150 Degaussing Wand from the A & R Soanar Electronics Group. The new servicing aid is designed to demagnetise colour TV receivers which have become magnetised due to the earth's magnetic field, or some other extraneous cause.

A magnetised colour TV set is characterised by distorted colour balance and loss of colour saturation. These defects cannot be corrected for by use of the manual controls.

In use, the Degaussing Wand is simply pointed at the centre of the picture tube from a distance of 30-50 mm, switched on, and then gently moved with a circular motion of the wrist to trace the perimeter of the tube. The wand is then slowly withdrawn to a distance of 3 metres or more from the set, and switched off.

Also just released by A & R Soanar Electronics Group is the PS241 Nickel Cadmium Battery Charger. This unit is designed to charge heavy duty nickel cadmium batteries of the type used in emergency lighting systems, portable TV sets, amplifiers, electronic flashguns, electric tools, and the larger types of portable radios, electronic calculators, and tape recorders.

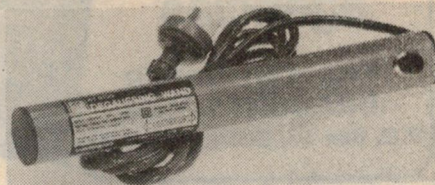The PS241 is a constant current unit capable of charging 1-10 cells in series



At top is the XT8150 Degaussing Wand, while directly above is the PS241 Nickel Cadmium Battery Charger. The battery charger is housed in A & R's new plastic case, featured elsewhere on this page.

simultaneously. The unit is provided with a switch for selecting six charging rates between 22 and 600mA. Output voltage is 15VDC.

For further information contact A & R Soanar Electronics Group, 30 Lexton Road, Box Hill, Victoria 3128.

CRYSTALS FAST DELIVERIES

OF ALL YOUR REQUIREMENTS

D Type 1 to 110MHz, J Type 5 to 110MHz, K Type 5 to 110MHz from \$7.00
Send S.A.E. for free comprehensive price list

- * 36 year's experience
- * Preferred by leading manufacturers throughout the country for: Accuracy-stability-activity-output
- * Consult us for crystals for any mobile radio
- * All types available
- * Discount for quantity orders
- * Amateur aircraft and ultrasonic crystals also available
- * Prompt delivery
- * Devoted exclusively to the manufacture of Piez electric crystals
- * Interstate customers please contact your local agent for fast service

W. J. MONCRIEF PTY LTD.
176 Wittenoom St, East Perth 6000.
Phone 25 5722, 25 5902.
PO Box 6057, Hay St, East.

FRED HOE & SONS P.L.
246 Evans Road, Salisbury North,
Brisbane, Queensland.
Phone 47 4311.

ROGERS ELECTRONICS
PO Box 3.
Modbury Nth SA.
Phone 64 3296.

PARIS RADIO ELECTRONICS
7a Burton Street,
Darlinghurst, NSW.
Phone 31 3273.

* TASMANIAN REPRESENTATION REQUIRED

BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA. 546 5076

electronic agencies

THE MAIL ORDER
DISCOUNT HOUSE
P.O. Box E5, CONCORD 2137

Your money
cheerfully
REFUNDED
if not fully
satisfied.
(less post/pack)

115-117 Parramatta Rd,
(Cnr Lloyd George Ave.)
CONCORD NSW 2137
TELEPHONE (02) 747-6472


Trading Hours: 12:00 to 6 pm Mon-Fri.
8:30 to 1pm Sat.

NOTE: Add postage, rated 10% order
value. C.O.D.'s send \$2.00 prepayment.




SANYO CC TV

it's cheaper than you think

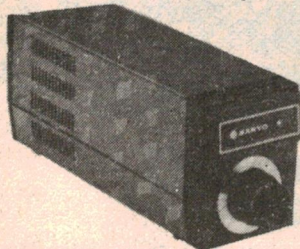

CAMERA VC1120

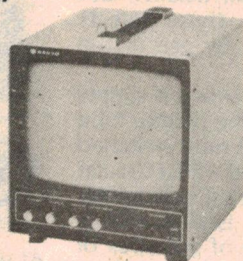- Monitoring with ordinary home TV — switchable RF/VIDEO output.
- Automatically adjusts to a wide range of light conditions
- Low noise, wide band amplifier equipped with FET for razor-sharp picture with a high resolution of more than 500 lines.
- Uses standard interchangeable lenses
- Compact, lightweight, easy-to-install, 240V mains powered.
- Proven, tested and guaranteed.



MONITOR VM4092

- Solid state 9" screen video monitor T.V.
- A.C. mains or D.C. 12V operation.
- Ideal for carrying into lecture halls for business presentations, for visual learning techniques, installing in shops as a deterrent to shoplifting, use at home to keep an eye on children playing, use in factory or warehouse to check incoming and outgoing goods or for observation of progress of production line etc, etc.

OUR SPECIAL
PRICE ONLY **\$185**

OUR SPECIAL
PRICE ONLY **\$199**

"CAMERA TALK" C.C.T.V. SYSTEM

Complete — ready
to install!

\$350



- Simplified sight and sound communications with other locations in the company, factory, hospital or home.
- Fully equipped with Automatic Gain Control (AGC). Minimum required light is only 40 lux (4 footcandles). Suitable for security and surveillance.
- Picture and sound transmitted by simply depressing the interphone button. Picture and sound hold for 40-60 seconds, then automatically cut out.
- Tremolo Call System for 2-way conversations.
- Corner-to-corner brilliance and detail on 7" monitor TV.
- Can be expanded to include three cameras and interphones, with optional camera selector (Model VCS 3K).
- Includes selected IC and FET circuitry for trouble-free service year after year.
- Compact dimensions. Easy to install.

Compact, Lightweight

VIDEO TAPE RECORDER

Model
VTR
2000 **\$550**

- Completely portable. Weighs less than 29 pounds.
- Recording and playback with sharp, clear signal.
- Auto Level Control (ALC) for both the video and audio.
- Sound-after recording for background music, narrations, commentaries etc.
- Extra-long life and stable signal with Perfect Ferrite Crystal (P.F.C.) head assembly.
- Precision interlacing with built-in sync signal generator. Horizontal resolution: more than 300 lines.




30 Watts
for \$30

STEREO 30 Quality Sound Budget Price

Kit includes transformer, labelled and numbered P.C. Board, all Resistors and Capacitors, 4 pages instructions.

Amazing offer for "hi-fi-ers" — Stereo amplifier kit giving 15W RMS in 4 ohms, 10W rms in 8 ohms (per channel) with 5 mV magnetic cartridge input VOLUME, BALANCE, BASS and TREBLE controls supplied — latest integrated circuit pre-amp and driver stages, complementary "flat-pack" output transistors — all on one P.C. Board for easy assembly. Hi-Fi performance with 20Hz to 50kHz response, low distortion and low hum level ensure compatibility and the best turntables and speakers.

Complete Kit \$30 + post.

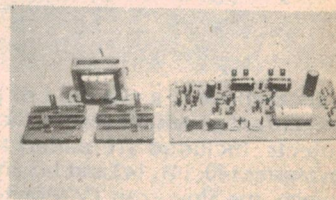

Over 5000 Brand New
QUALITY SPEAKERS
available ex stock at
FANTASTIC SAVINGS



Famous Brands

- Magnavox
- Plessey Rola
- MSP
- CTS — USA



Don't miss out on these SPECIALS.

2 1/4" 25 Ohm	\$1.00	5" x 4" 15 Ohm	\$2.75
3" 3.5 Ohm	\$2.50	6" x 4" 15 Ohm	\$2.90
4" 15 Ohm	\$2.50	7" x 3" 3.5 Ohm	\$2.90
5" 15 Ohm	\$2.75	7" x 3" 15 Ohm	\$2.90

Unbeatable deals on all HI-FI SPEAKERS.

HI-FI/TWIN CONE

6" 8, 15 Ohm	\$6.50
8" 8, 15 Ohm	\$7.50
12" 8, 15 Ohm	\$10.50
6WR 8, 15 Ohm	\$9.95
8WR 8, 15 Ohm	\$10.75
12WR 8, 15 Ohm	\$13.50
8-30 8 Ohm	\$16.50
3TC 8, 15 Ohm	\$3.75
3UC 8, 15 Ohm	\$4.20
1" Philips Dome, 8 ohm	\$9.00

LARGEST
RANGE in
Australia,
CHEAPEST
prices,
FASTEST
MAIL
ORDER
SERVICE.

WOOFERS AND TWEETERS

Plessey 1" Dome, 8 ohm	\$7.50
C80, 8", 8 ohm	\$12.50
C12P, 12", 8 ohm	\$19.50
C12PX, 12", 8 ohm	\$21.00
C6MR, 8 or 15 ohm	\$7.50
8" roll-surround T.C.	\$9.50
8" roll-surround T.C.	\$31.00
12" roll-surround	\$4.50
6" mid-range	\$4.50
3" Tweeter	\$2.50

VU STEREO METERS

1 3/8" Scales.

\$6.95

Dual Meters in one case — will "dress-up" any amplifier or tape recorder — for amateur or professional use.

ROLA 2 1/4" MINIATURE SPEAKER



□ \$1.00 ea or 10 for \$9.00.

Popular replacement speaker for local and imported transistor radios. Model 225A, 300 Hz to 5 kHz.

5 inch T.V. TUBE

Brand new, sealed in manufacturer's carton
SPECIAL PRICE
\$11.95.

Ideal for servicemen, amateurs and experimenters. Specifications: Electromagnetic deflection, 70 deg. angle, filament 12 Volt 70mA, Anode voltage 8KV at 50mA, 2nd grid voltage 300V, 1st grid cut-off voltage -25V, electrostatic focusing, size 5 1/2" x 4" x 7" long.

Price \$11.95. (plus \$1.00 registered post)

A limited quantity of yokes is available to suit above T.V. tube. Price \$7.50

VHF TRANSISTOR T.V. TUNER

12 Channels

A high sensitivity transistorized T.V. tuner suit Australian Stations. Operates from 12 V D.C. and output goes to IF section. Suit hobbyists, amateurs, T.V. servicemen etc. **\$8.50 ea.** □

MINIATURE TUNING CAPACITOR

Most popular type suit imported radios. Size 1/4" x 1/4", 200pf per gang with inbuilt trimmers, □ \$1.00 ea, or 10 for \$8.00.

DE-LUXE TUNER MODULE 304

A high sensitivity 4 transistor AM tuner with tuned RF amplifier and two IF stages for extra selectivity and sensitivity. The Module is ready assembled and operates from 9V DC at approximately 3mA. A permeability type tuner and push-button On-Off switch are supplied together with circuit and application diagrams. As the module may be used with a ferrite rod type aerial OR an external wire type antenna, it is ideally suited to car, portable or home use. Size 5 1/2" long x 1 1/2" wide x 7/8" deep. Ferrite rod aerial \$1.25ea, **\$12.99** □

DIGITAL CLOCK KIT

4 DIGIT
"NIXIE"
DISPLAY
\$45.00

Build your own case!

A complete, easy-to-assemble kit ready to install in your own cabinet. All top quality fully branded, full spec. parts incl. Printed Circuit Board, Mullard Display Tubes, transformer, I.C.'s, resistors, capacitors etc.

The Amateur Bands

by Pierce Healy, VK2APQ



IARU—Region III Conference

In March 1925, the concept of an International Amateur Radio Union was born. The aim was to coordinate worldwide amateur activities. Here, a half a century later, is a report on the third Region III conference held during March 1975 in Hong Kong.

During the past 50 years the IARU has flourished and is recognised as an official organisation by the International Telecommunication Union. It represents amateurs and their societies throughout the world.

The invitation to hold the third Region III conference in Hong Kong was extended by the Hong Kong Amateur Radio Transmitting Society (HARTS). The conference ran from the 4th March to the 8th March, 1975, and was held in the Lee Gardens Hotel, Hong Kong. All facilities for documentation of the proceedings were arranged by the host society.

Representatives of nine member societies, the president of the IARU, three directors and secretary of the Region III Association attended. They were:

IARU	President	Noel Eaton	VE3CJ
Region III	Directors	Michael Owen	VK3KI
		Tom Clarkson	ZL2AZ
		Kan Mizoguchi	JA1BK
Region III	Secretary	David Rankin	VK3QV
ARRL		Dick Baldwin	W1RU
HARTS		George Flenner	VS6AI
		Bob McCurrach	VS6BL
		Dan Douglas	VS6DD
		Phil Wight	VS6DR
		Bob Norcross	VS6AF
		Mal Hamilton	VS6HI
JARL		Drake Drakeford	VS6EK
		Shozo Hara	JA1AN
		Sammy Saitoi (Dr)	JH3PJE
		Junko Kiso (Miss)	JR1ANP
MARTS		Ron Fisk	9M2CJ
NZART		Doug Gorman	ZL2IY
		Fred Johnson	ZL2AMJ
PARA		Joe Gonzalez	DU1JMC
		Ed Reyes (Dr)	DU1OR
		Jose Tupas	DU1JIT
RAST		Kam Chotikul (Col)	HS1WR
SARTS		Tan Lian Huat	9V10D
WIA		David Wardlow	(Dr) VK3ADW
Observer		Maurice Caplan	VS5MC

The WIA also acted as proxy for the Radio Society Sri Lanka. All HARTS representatives were not present at the same time and John YB7AAA in addition to being assistant secretary also participated in the discussions.

The conference was opened by an address of welcome by the HARTS president, George Flenner, VS6AI. The IARU president, Noel Eaton, VE3CJ then addressed the gathering, stressing the importance of the work to be done by the Region III Association. Particularly in regard to the approaching ITU—World Administrative Radio Conference at Geneva in 1979.

The officers appointed for the conference were:

Chairman Michael Owen VK3KI

Secretary David Rankin VK3QV
Asst. Sec. John Van Lear YB7AAA
Convener of credentials committee David Rankin
Convener of editorial committee Tom Clarkson ZL2AZ

In addition to reports from the secretary, directors, and societies' representatives, the agenda contained a wide range of items for discussion. After preliminary discussions these were referred to working committees, whose reports, with some later amendments, became the official conclusions of the conference. Among these were:

Policy on Frequency Provisions:

1. Amateur activity is likely to have a world wide total of one million stations by 1982; the foreseen date of implementing the 1979-ITU-WARC decisions.

2. The increasing use of telephony justifies wider bands.

3. Increased frequency privileges should be sought as follows:

- The return of the 1800-2000kHz band.
- Eliminate sharing of the 3500-4000kHz band.
- Expand the 7MHz band to 7.0MHz to 7.5MHz and eliminate sharing with broadcasting services.
- Establish a new amateur band in the vicinity of 10.5MHz.
- Expand the 14MHz band to 14.0MHz to 14.5MHz.
- Establish a new amateur band in the vicinity of 18.5MHz.
- Expand the 21MHz band to 21.0MHz to 21.5MHz.
- Establish a new amateur band in the vicinity of 24MHz.
- All the above to be the same for all regions.

4. Article 41 of the ITU regulations should be amended to improve the official pronouncements describing the amateur service.

5. The amateur satellite service should merge with the amateur service so that there is freedom to use all bands in space communications.

6. Allocations should be sought in all parts of the spectrum up to 275GHz.

7. World wide allocations on 220MHz should be sought, if necessary on a shared basis.

8. While band plans are necessary in individual countries, coordination is not considered necessary or practical for VHF and UHF. But agreement will be needed to avoid conflict in space operations.

Societies urged to participate in a regionally coordinated intruder watch scheme. A WIA offer to nominate a regional coordinator was accepted. Greater occupancy of amateur bands to be encouraged.

To implement the policies, the proposals provide for:

- Better communications between societies and

administrations.

2. Better communications between societies.

3. Better communications between IARU headquarters and societies.

4. Coordination of travel liaison.

5. A meeting of Region III directors before the next conference.

6. A director from Region III should attend the Region II conference in 1976.

7. A booklet to be produced in suitable languages to advocate amateur radio throughout Region III.

8. Societies and IARU HQ to be urged to consider the conclusions of the Region III conference, in view of the personal discussions held there.

9. Societies to seek inclusion of an amateur on official delegations to the WARC or, alternatively, to have an amateur liaison officer on the delegation.

Financial Matters: A budget for three years (to the next conference) was prepared to carry out the Region III Association aims and the implementation of the policies set down. It was decided not to alter societies' subscription rates.

On this basis, in the third year, there would be a deficit of Aus. \$6270. After considerable discussion the matter was resolved by a proposal from the Japan Amateur Radio League.

The JARL undertook to subscribe an additional amount, for each of the three years, of Aus. \$2120. The payment was for the defence of frequencies used by the amateur service.

This very generous action of the JARL was emphasised by the conference.

Region III News: An offer by the JARL to publish a "Region III News" was accepted. Initially this will come out twice a year. Details are yet to be completed between the JARL and the secretary. Material for publication will be sought from member societies.

Region III Association Officers:

Directors	T. R. Clarkson	ZL2AZ
	M. J. Owen	VK3KI
	Tan Lian Huat	9V10D
	Dr. S. Saito	JH3PJE
Secretary	D. Rankin	VK3QV

Next Conference: Invitations were extended by PARA (Philippines), RAST (Thailand) and NZART (New Zealand). The voting was Thailand, Philippines and New Zealand in that order. It is therefore proposed to hold the next conference in Bangkok, about October 1978.

LOCAL & OVERSEAS NEWS

IARU REGION I. Writing in the February, 1975 issue of the "Radio Communication", Roy Stevens, G2BVN, secretary Region I Division IARU, refers to that division's conference to be held in Warsaw commencing on 14th April, 1975; the same date as the first IARU conference held 50 years ago in Paris.

The Region I Division was formed 25 years later, on the 18th May, 1950. At the time that division consisted of 15 member societies; today there are 41 member societies.

Referring to the IARU, Roy writes:

"An international body, united in aim and purpose, is essential if amateur radio is to continue. No longer is the future controlled by the votes of those nations who have always held a traditionally friendly attitude towards the amateur service.

"Today, and in the future, ITU conference decisions will depend on the votes of nations who are, at the best, unco-operative with the amateur movement.

"The amateur service does not intend to be on the defensive. A logical plan for the expansion of amateur frequencies, in accordance with the conditions of the time, has already been considered in regional committee meetings. To be successful such a plan must be basically acceptable to many national administrations who will be prepared to support it at the ITU with positive votes.

"Only the IARU is in a position to prepare a plan and then to propagate it world-wide".

IARU REGION II. In the U.S.A. on 1st March, 1975, the basic fee for a new, renewed or modified-and-renewed amateur licence drops from \$9 (US) to a new rate of \$4 (US), equivalent to \$2.95 (Aust).

In 1974 the FCC proposed to increase the fee to \$10 (US) but, following a protest by the ARRL, the US Supreme Court ruled that the FCC had authority

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent direct to Pierce Healy at 69 Taylor Street, Bankstown 2200.

FERGUSON

Manufacturers of:
Electrical / electronic
equipment, wound
components and
lighting control
equipment.

BRANCHES IN ALL STATES

Ferguson Transformers
Pty Ltd.

Head Office
331 High Street, Chatswood
NSW 2067

PO Box 301 Chatswood,
NSW, Australia 2067

Phone: 02-407-0261

AMATEUR BANDS

to reclaim only part of its expenses, that part which represented the "value to the recipient" of the service received from the FCC.

Accordingly a new basic fee of \$6 (US) was proposed. Again the ARRL protested, pointing out that there was no tangible benefit to the recipient, as he could not use his licence for pecuniary gain. Also, in view of that fact, such licences should be issued without fee.

The FCC has now clarified its interpretation of the Supreme Court ruling to mean "value of what the recipient receives, as its cost to the government", rather than the actual cash value to the recipient. ("QST" March 1975.)

(This is a very different approach to that taken in Australia by the PMG's Dept. in reply to the WIA protest against the 100% increase to \$12 for an Australian amateur licence.)

AN E-M-E FIRST. What is believed to be the first SSB moonbounce contact between Australia and the USA, has been achieved by Chris Skeer, VK5MC on 144.107MHz.

Contact was made on the 30th December, 1974, at 1117GMT with W8PKY, initially on CW. A report R5-S4-T9 was sent by Chris and he received R4-S4-T9. On changing to SSB the reports were: sent R5-S4, received R4-S4. W8PKY was running 1kW to a yagi antenna and VK5MC 250 watts to a rhombic antenna. VK5NC and VK3AKC were visiting Chris at the time.

On 23rd February, 1975, at 0738GMT Chris worked K1WHS on CW. Reports: sent R4-S3-T9, received R3-S3-T9, also K2RTH at R4-S4-T9 and R4-S3-T9.

Eight stations in North America have now been worked via E-M-E by Chris.

At 1335GMT on the 22nd February on 1296MHz, Ron Wilkinson, VK3AKC worked PA0SSB on CW. Reports: sent R5-S3-T9, received R5-S2-T9.

On the 23rd February, 1975, between 1430GMT and 1525GMT Ron worked OZ9CR and between 1525GMT and 1542GMT again worked PA0SSB. In all cases the E-M-E signal report code "O" was

exchanged. PA0SSB uses a 4 metre dish antenna with 1kW input and OZ9CR an 8.5 metre dish antenna, also 1kW input.

RADIO CLUB NEWS

TOWNSVILLE AMATEUR RADIO CLUB: The club will hold its second bi-ennial North Queensland Convention in Townsville over the weekend 26th and 27th July, 1975. Visitors from the cold southern states will be particularly welcome.

Registration forms and further details may be obtained from the NQC Convenor, TARC, PO Box 964, Townsville, Q. 4810. The closing date for registrations is 18th July. Registrations received up to this date will be eligible for a prize decided by ballot.

Further details will be given over the VK4WIA news broadcasts at 0900EST on Sundays. Intending visitors are invited to join the VK4WIT net on 3605kHz, each Sunday at 1945EST.

The official convention frequency will be channel 50 (146.5MHz) and a new repeater (channel 1) will be in operation by the convention date.

CENTRAL COAST AMATEUR RADIO CLUB: At the annual meeting the following officers were appointed. President—Bill Smith, VK2TS; Vice-president—Ray Wells, VK2ZSX; Secretary—Susan Wells; Treasurer—Leon Brett, VK2ZEC; Committee—Bob Leane, VK2ZLV; Ross Mudie, VK2ZRQ; Peter Ward, VK2YAA; Don Crutcher, VK2ZCC; Stan Dogger, VK2ZRD, and John Tanner, VK2ZXQ. Public relations—Dick Maitland, VK2BBK.

With a favourable bank balance, a motion passed at the February meeting to transistorise the repeater can now be implemented. There is also further progress towards obtaining a new repeater site.

A refinement will be a Morse clock. As well as the call sign (VK2RAG) in Morse, as at present, it will also give the location and time when first activated. The time will also be transmitted at intervals while the transmitter is in operation.

In spite of the bad weather 475 people attended the 18th annual field day on Sunday, 23rd February, 1975.

All the field events were keenly contested and excellent prizes for the winners were donated by

Atlas-210

NO TRANSMITTER TUNING.


MODULAR CONSTRUCTION.

SIDE BAND TRANSCEIVER

5 Band — 200 Watts

SOLID STATE

10, 15, 20, 40 and 80 meters

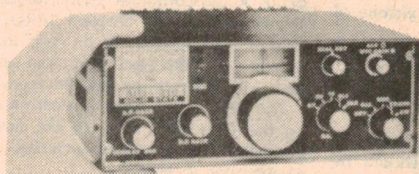

\$570

The Sensational ATLAS-210/215

PRICE LIST

Atlas-210/215	
SSB Transceiver	\$570
Atlas 210M/215M	
(Mars Model)	\$585
AR-230 Power Supply	\$150
AR-200 Portable AC	
Power Supply	\$96
Mobile Mounting Bracket	
Deluxe Plug-in Model	\$47
DC Battery Cable	free
Mobile Bracket Kit	\$6

OTHER HF GEAR

YAESU FT101B	160/10m
AC-DC transceiver	Avl EX-
STOCK at \$585	
YAESU FV-101B VFO for	
FT101B	\$102
YAESU FT75B 80w pep trans-	
ceiver	\$245
AC power supply \$65, DC	
power supply	\$75
TRIO TS-520 all band transceiver	
— \$550	
external VFO \$80	
YAESU FT-201 \$505	
YAESU FT-2100B Linear \$388	



The gear you want may not appear in this ad. Vicom can procure any amateur equipment available overseas through our Telex service. As all imports are air-freighted your order should be available in about 10-14 days.

WRITE FOR DETAILS

VICOM INTERNATIONAL PTY LIMITED

139 Auburn Rd, Auburn, Vic., 3123. Phone: (03) 825398
378 Pacific Hwy (near Hume St.) Growns Nest, NSW, 2065.

Open Friday nights and Saturdays.

Queensland agent: db Electronics, 21 Christine Ave, Miami Qld, 4220. Phone: (075) 35-1798.

HAM HEADQUARTERS!

VICOM INTERNATIONAL PTY. LIMITED

AUSTRALIA'S BEST SELLING 2M FM rig — the IC-22A

IC22A 2M FM TRANSCEIVER replaces the IC22 and is identical electronically, but features a redesigned front panel with easier-to-read channel selection. It features switchable power 1 or 10 watts, 22 channels, solid state T/R relay, built-in PA protection, filtered d.c. voltages. The unit comes complete with mounting brackets, microphone, cables, etc., and three channels — 1/4/50. Price is \$210 incl. tax and VICOM 90-day warranty. Extra crystals \$7.80 pair.

TEST GEAR

TRIO CS1557 CRO	DC-10MHz	\$340
TRIO VT108 FET VOM	8 ranges 0.5 to 1.5kv, 11 meg input, ohms 0.1 to 1000 meg, memory feature \$85	
TRIO AG202A AUDIO GENERATOR	covers 20Hz to 200 KHz, 10v rms output, sine and sq wave, ext sync \$94	
TRIO 75mm scope	20mv cm sens, dc to 1.5 MHz \$170	
TRIO SG402 RF GENERATOR	covers 100KHz to 30MHz	\$78
D-60 FREQUENCY COUNTER	including 2 metre precaler \$360	
GILCO 275	0-15 MHz frequency counter	\$210
VICOM 24 or 12 hr digital (electronic) clock		\$39.90

6 METRES SSB

YAESU TS-620B transceiver (new release)	\$435
TRIO TRANSVERTER TV-506	\$212
ICOM IC-501 TRANSCEIVER	\$445

2 METRES SSB

YAESU FT-220 SSB/CW/FM	solid state transceiver \$480
TRIO TRANSVERTER TV-502	\$243



CRYSTAL OVENS

pcb mount proportional control crystal ovens can be supplied for standard temperatures and voltages. Model PCL1-12 clip type oven for Hc-25/u crystal \$19.80. Model PCL2-21 slip-on oven for Hc-6/u crystals \$19.80.



IC21A - \$298 DV-21 - \$298
BOTH FOR \$570

DV-21 DIGITAL VFO employs a PLL synthesised system with 59 ICs, 34 transistors, 1 FET and 37 diodes. It can be INTERFACED with the IC22 or any 2m transceiver with 44-45 MHz rx 18 MHz tx, 10.7MHz i.f., lwr side heterodyne, 8 x basic freq. for tx and 3 or 9 x basic freq. for rx. Only a slight modification is required for such equipment and is detailed in the operating manual. It operates in 5 or 10 KHz steps from 146 to 148 MHz and can scan either empty frequencies, or the frequencies being used, whichever you select. Complete separate selection of the transmit and receive frequencies is as simple as touching the keys. When you transmit, bright easy to read LEDs display your frequency. Release the mic switch and the receive frequency is displayed. These are two programmable memories for your favorite frequencies. You won't believe the features and versatility of the DV-21 until you've tried it. Price \$298 includes VICOM 90-day warranty. THE IC21A is the 10w base station or mobile (146-148 MHz) with variable power control, adjustable deviation, 24 channels, built-in discriminator meter, S meter, SWR meter, PA protection, modular circuitry, runs from 13v DC or 240v AC. Complete with three channels. Price \$298, extra crystals \$7.80 pair.

RAC ANTENNA

	Model	Imp	Freq	VSWR	PRICE \$
BALUNS	BL-50A	52	1.8 - 38MHz	1.3:1	14.90
	BL-70A	75	1.8 - 38MHz	1.3:1	14.90
COAX SWITCHES (2 & 6 pos)	CS-2A	52	to 300MHz	1.3:1	21.00
	CX-6A(A)	52	to 500MHz	1.3:1	54.00
	CX-6A(B)	75	to 500 MHz	1.3:1	54.00
TRAP DIPOLES	III-N	52	7 to 28MHz	1.2:1	31.00
	AL48DXN	53	3.5 & 7MHz	1.2:1	31.00
	AL24DXN	52	7 & 14MHz	1.2:1	24.00
	A-4VPN	52	3.5MHz	1.2:1	24.00
	A-8VPN	52	7MHz	1.2:1	26.50
LISTENER	L1	75	3 to 30MHz	—	14.90
BALANCED FEEDER	BTF-1	600	—	—	12.00

We do not sell "C.B." equipment.

various business houses. Several provided trade displays of the latest amateur equipment.

The club wishes to thank those who provided the prizes and displays, and all who attended and made the day such a success.

BLUE MOUNTAINS BRANCH NSW DIVISION WIA: The annual meeting was held on Friday night, 14th March, 1975, in the Springwood Primary School. The officers elected were:

President: D. Clift, VK2DC; Vice-presidents: N. Thyrd, VK2AUS and N. Walker, VK2ZNS; Secretary: R. Lopez, VK2BRL; Treasurer: A. Griffard, VK2AGN; Publicity officer, Rex Black, VK2YA; Catering officer, W. Moore, VK2HZ; Education officers, H. Smit, VK2BHS and J. Oxley, VK2YCO.

Preliminary plans were formulated for the 1975 Blue Mountains Branch field day and for an "out-reach" demonstration of amateur radio to introduce the branch's activities to more people in the area.

Those interested in gaining an amateur licence are invited to join the classes each Friday night in the Springwood Primary School, at 8.00 p.m.

The branch has offered a book prize to the student who performs best during the year in the new electronic course at the Katoomba High School. This is being conducted by Brian Kleinschafer, of the science staff, on a three lessons per week basis. Branch members hope to provide the school with radio equipment and components.

ILLAWARRA BRANCH NSW DIVISION WIA: A moonbounce test with WA6LET using a 45 metre dish antenna was held on 22nd February, 1975. VK2AMW was operated by Charles Proctor, VK2ZEN and Roger Evans, VK2BRE. Signals were heard from WA6LET from 0800GMT to 0845GMT at 8dB above the noise, but repeated calls from VK2AMW were not acknowledged.

Work is proceeding at VK2AMW on the quarter wave filter in front of the receive preamp.

The Board of Senior School Studies has approved a proposed two unit course at the Wollongong Technical College for 5th and 6th forms.

This course is to provide a broad theoretical and practical introduction to electronics circuits, for students interested in electronics as a hobby or as a career.

High School students in 5th form may take this course for the Higher School Certificate. Other persons may also attend.

Enquiries should be directed to Bruce Carroll, VK2ZIC, School of General Studies, telephone Wollongong 299 9611 ext 271. Classes—6.00 to 9.00 p.m. Room 6, Science Block, Wollongong Technical College.

GEELONG AMATEUR RADIO-TV CLUB: Details of repeaters in Victoria appeared in the GARC Newsletter, March, 1975. This was the result of a repeater committee meeting held in the WIA rooms, Melbourne on 15th February, 1975.

Repeater standards:

- Deviation + and - 10kHz.
- Transmitter power (to suit area) 150W max.
- FSK identification.
- Tail length: silent—1 second long.
- Timers 2½ minutes.

Call signs and channel locations:

VK3 — RAP Mt Arapiles	Ch. 1*
RAM Mt Alexander	2
RSH Swan Hill	1+
RMW Mt William	3
RMM Mt Macedon	6 or 7*
RML Mt Dandenong	1
RGL Mt Anakie	4
RLV Mt Tassi	2
REG Mt Sugarloaf	3*
RBA Ballarat	5*
RMA Mildura	4*
? Albury-Wodonga	4*

* Proposed; + pending licence.


Members of the Victorian repeater executive elected at the meeting were:

Chairman	Peter Linden	VK3BX
Vice-chairman	Peter Mill	VK3ZPP
Secretary	Ken Jewell	VK3ZNI
Publicity officer	George Francis	VK3ASV

IONOSPHERIC PREDICTIONS FOR MAY

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.

5.75

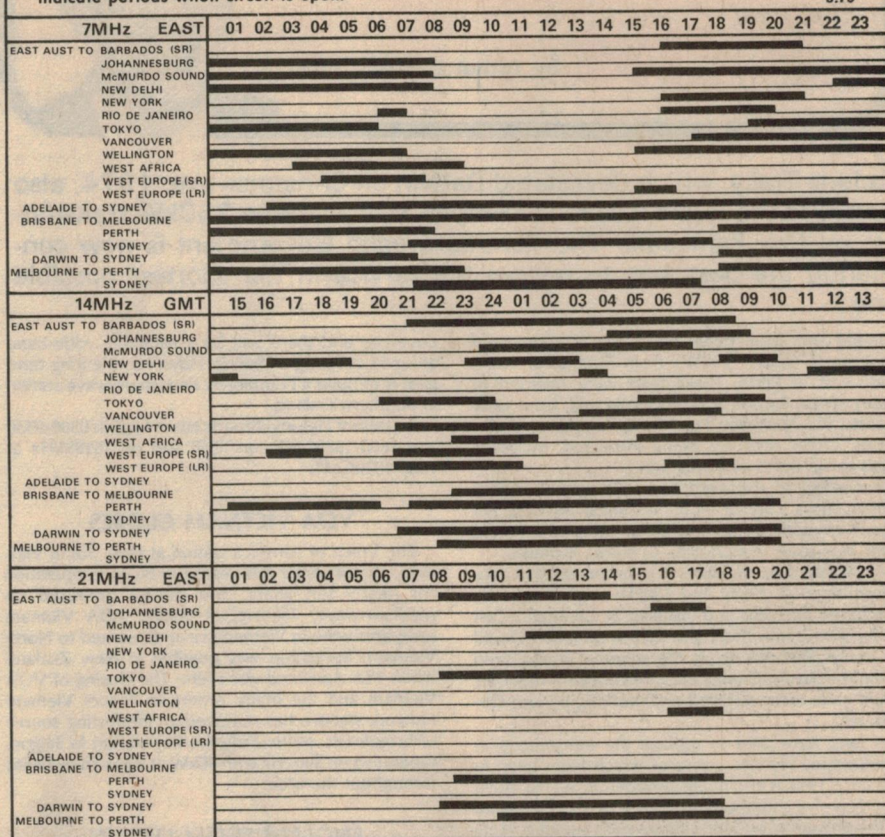

The GARC conducts a wide range of activities associated with amateur radio. For details write to the Secretary, PO Box 520, Geelong, Vic. 3220.

GOLD COAST RADIO CLUB: Material for a new repeater antenna has been received and construction is under way. A higher power final has been installed and reports are that the signal is being received a little better in the more difficult areas. One report came from Dalby around 200km distance.

A GCRC net on 3650KHz at 8.00 p.m. on Sunday evenings is popular with listeners in southern states. Anybody, member or not, is invited to join in. Visiting the Gold Coast? Then let the club know through PO Box 588, Southport, Qld, 4215. Members will be pleased to see you.

UNIVERSITY OF NSW AMATEUR RADIO SOCIETY: The society held a successful demonstration of amateur radio during university orientation week. Several new members were recruited and a good start for 1975 seems assured. Contacts were made on all HF bands, including all states and a number of interesting overseas stations. The equipment was the club's FT101B and an 18AVT antenna on top of the Roundhouse.

After submitting an idea for a WIA educational hobby station on the FM broadcast band to the council of the NSW Division, the society has been asked to conduct a feasibility study.

The study will examine such issues as ownership, equipment, staffing, and finance. The society was also requested to submit the proposal to the WIA federal convention.

For information write to UNSWARS, Union Box 57, PO Box 1, Kensington, 2033 or call at the society's club room, Room 601, Electrical Engineering Building, University of NSW, Kensington.

WINDSOR YMCA RADIO CLUB: A radio club for high school students at the Windsor YMCA centre in Brisbane, was formed on 14th February, 1975. The club is jointly sponsored by the YMCA and the

Queensland Division of the WIA.

First year membership will be limited to 50. Activities will range from building simple radio receivers to an amateur radio station. In 1976 the course will be expanded to cover the AOCIP.

The WIA is providing a number of instructors to lecture on radio and electronic theory, job opportunities in electronics, amateur radio, satellites, digital computers and associated subjects.

Inquiries may be directed to the YMCA centre. **EDENHOPE HIGH SCHOOL RADIO CLUB:** An enthusiastic group of students have formed a radio club. Their immediate aim is to study for their amateur licence. The long-term goal is to help others to do likewise.

Like all new clubs any assistance to help them to achieve their aims would be appreciated. The secretary is Tracey Evans, EHSRC, PO Box 117, Edenhope, Vic. 3318.

SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to:

**THE COURSE SUPERVISOR,
W.I.A.
14 ATCHISON STREET,
CROWS NEST, N.S.W. 2065**

Shortwave Scene

by Arthur Cushen, MBE



Cyclone Tracy, which devastated Darwin on Christmas eve, 1974, also destroyed the Radio Australia Complex with its three 250kW transmitters on Cox Peninsula. The Commonwealth Government is now considering the best way to restore the service in the shortest possible time.

Initial tests have been made with low powered equipment (under 10kW) from Gnargara, 40km north-east of Perth. These tests were beamed to South Africa, Europe and Indonesia and, from early reports, the Australian Post Office is making evaluations. Other sites are being inspected, including areas as far north as Carnarvon.

According to the April issue of "Australian Post Office News", senior PMG technical advisers are against re-establishing the Darwin complex at its old level, due to its vulnerability to storm damage.

As a stop gap measure it is proposed that two transmitters, of 25kW and 100kW respectively, be purchased overseas and installed at Gnargara. Cost of the two transmitters and their installation would be about \$2.9 million. If the scheme is approved without delay PMG engineers are confident that they could have them installed and working by late December.

A long term plan to replace the transmitters at Shepparton, Victoria, some of which have been in use since 1943, is also being considered. Such a move could involve a total expenditure of up to \$45 million. In the present economic climate such a plan is likely to be treated as long term project, rather than one of urgency.

BRAZIL EXTENDS SERVICE

Radio Nacional at Brazilia, as well as operating the international service now broadcasts 24 hours a day with a relay of the internal service. According to the station the internal transmissions are on 6065, 9665, 11720 and 15445kHz, and the power on all frequencies is 10kW. These transmitters are located within the city limits of Brazilia.

The international service has been assigned 9605, 11780 and 15245kHz, at 250kW, and these transmitters are 50km from Brazilia. The station broadcasts in Portuguese at 1900GMT followed by German at 2000 and English at 2100GMT. At 2200GMT the program "A Voz do Brasil" is carried. The station address is: Radio Nacional De Brasilia, P.O. Box 07/0173, Brasilia, D.F., Brazil. The verification card shows a map of Brazil and the various states.

FINLAND INCREASES POWER

The Finnish Broadcasting Company is to be provided with a 250kW transmitter for world wide broadcasting, and this should be in operation next year. In the meantime, according to the New Zealand DX Times, Radio Finland currently has one 100kW, two 15kW and one 1kW transmitter at the Pori short-wave station. Also a 15kW transmitter relays the full home service on 6120kHz. There are 19 and 31 metre dipole antennas beamed to Europe, and a 25 metre antenna beamed to Mediterranean areas. The new 250kW transmitter will have full short-wave

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT, add 9 hours for West Aust. Summer time, 11 hours for East Aust. Summer time and 13 hours for NZ Summer time.

coverage and there will be a rotatable wide-band antenna covering all bands. However, the long term goal is to build a completely new short-wave station in Southern Finland.

At present Helsinki Broadcasts in English 0300-0330 and 1600-1630GMT, on 9550 and on 15185kHz at 1800-1830GMT.

VOA VIETNAM CLOSES

The Voice of America station at Hue, South Vietnam, closed earlier this year after being in operation for nearly ten years. The station operated on medium-wave, 760kHz, at 50kW. VOA Vietnam programs were in Vietnamese and beamed to North Vietnam. Reception was possible in New Zealand when 1YA Auckland was silent. The closing of VOA Vietnam and the many American Forces Vietnam network stations has removed an interesting source of broadcasts, particularly the key station in Saigon. Operating on 540kHz with 50kW, it was widely heard throughout the area.

ENGLISH FROM LISBON

Major changes have taken place in Portugal and these have been reflected in the short-wave service. Broadcasts of the Voice of the West have been cancelled and all transmissions are now conducted with the slogan "Emissora Nacional Lisbon". Programs in English are now as follows:

GMT	kHz
0230-0300	11935
0430-0500	6025, 11935
1400-1430	21495
1600-1630	17895
1800-1830	11875, 21495
2030-2100	9740

RBI ON 6060kHz

Radio Berlin International has been heard with a new transmitter on 6040kHz, with a Spanish program at 0345-0500GMT. Previous to this is a service in Portuguese from 0300GMT. Reception is fair, but suffers interference from the Voice of America on the same frequency.

According to a report from North America, additional tests have been observed and these include Portuguese to Brazil at 2315-2400 on 6040 and 6065kHz in parallel with 5955, 6010, 9500 and 9600kHz. Spanish is broadcast at 0000 until sign-off at 0045GMT. Further transmissions in Portuguese to Brazil are broadcast at 0300-0345 on 6040, 6070, 9500 and 9600kHz.

RELAYS FROM MALTA

Reception of the Deutsche Welle relay station at Malta has been widely reported on short-wave, but our reception of the medium-wave signals on 1570kHz last year, seems to be the first indication of reception at this distance. Since then the station has been widely received by readers around dawn, and the New Zealand DX Times has given additional information on this station. The station is principally intended for countries surrounding the Mediterranean and the Middle East, but we understand the beam is strongest in the "general direction" of New

Zealand. Three 100 metre masts are linked together for the 1570kHz antenna. The current schedule includes: 1400-1750 in German to Near East and Asia, 1800-1850 in Turkish to Southern Europe, 1900-2055 in Arabic to Near East, North Africa.

WINB ON 1518kHz

The Red Lion station WINB which broadcasts gospel programs to Europe has been heard on 15185kHz closing at 2245GMT. This frequency replaces 11775kHz which carried the transmission in the past, but suffered interference from Madrid on the same frequency. The broadcast commences at 1745GMT on 17720kHz and changes to 15185kHz at 1930GMT. The station address is: P.O. Box 88, Red Lion, Pa. U.S.A., 17356.

ENGLISH FROM DELHI

All India Radio provides good reception during the morning listening in this area with a special transmission to Australia and New Zealand from 2045-2215GMT. The frequencies are 7260, 9912 and 11740kHz. A previous broadcast to North Africa at 1945-2045 is now on 9755 and 11880kHz. The transmission from 1000-1100GMT provides best reception on 11755 and 15205kHz. All India Radio welcomes reports from listeners. The address is: P.O. Box 500, Delhi, India.

MEDIUM WAVE NEWS

HAWAII: Station KIOE in Honolulu on 1080kHz has closed, according to Tim Hendel of Honolulu. The station formerly operated on 1090kHz as KHAI. Another Hawaiian Station KPOI on 1380kHz is expected to change to 990kHz shortly, the frequency formerly used by KTRG, which has also closed.

AUSTRALIA: The University of Adelaide station 5UV which tested on 1560kHz when granted its licence, has moved to 530kHz according to Keith Barton of Adelaide. The transmissions are 0830-1130GMT and the program consist of educational instruction. The transmitter power is 600W. The station address is: Radio University, Department of Adult Education, The University of Adelaide, Adelaide, South Australia.

NEW ZEALAND: Since April 1 broadcasting in New Zealand has been under the control of Radio New Zealand after the NZBC was split into three corporations, one for radio and two for television. Major changes have already been announced with the extension of hours of some stations, and a Polynesian radio station to be established in Auckland. Earlier this year two new repeaters came into operation, 4YQ Queenstown on 1120kHz and 2YM Palmerston North on 1410kHz.

The commercial network is now known as Network 1, the former national program is now Network 2, while the former YC program is Network 3. Network 3 will carry good music and has been extended in hours with a breakfast session 1800-2230GMT, on 1YC 880, 2YC 660, 3YC 960 and 4YC 900kHz.

LISTENING BRIEFS EUROPE

DENMARK: According to "Sweden Calling DXers", after 25 years' service the antennas and masts of Radio Denmark at Herstedvester have deteriorated badly and, since February 15, only two remain in service. These are beamed to Africa, and Greenland/North America, and backwards to the Middle East. Radio Denmark is at present broadcasting on only 15165kHz. In these circumstances reception reports are highly appreciated. The address is: Radio Denmark, Short-wave Department, Broadcasting House, DK-1999 Copenhagen V., Denmark.

HUNGARY: Radio Budapest continues to be heard on its new frequency, 6000kHz, with an English program to sign-off at 0440GMT. Transmitter power is understood to be 500kW. Our reception has been spoilt by other stations on the same frequency.

SWEDEN: Radio Sweden in Stockholm has recently been using 11735kHz with English from 1830-1900GMT beamed to South Asia. The frequency is also used by Radio France and interference is rather severe. Two other frequencies, 11705 and 15240kHz, carry the same program.

E.D.&E. (SALES) PTY. LTD.

EDUC-8 COMPUTER—COMPLETE KIT

(OCT-NOV-DEC 1974)

\$368.75 (Plus Tax)

OR INDIVIDUAL COMPONENTS
AS REQUIRED

K
I
T
S

K
I
T
S

MAJOR STOCKISTS OF ALL GENERAL RADIO & ELECTRONIC COMPONENT PARTS — YOU NAME IT — WE WILL QUOTE

Valves — Transistors — Zener & Power Diodes — Semi-Conductors — Diacs — Triacs — S.C.R.'s — I/C's. Speakers — Microphones
— Coils — IFT's. Transformers — Inst Cases — Metalwork. Players & Changers — Meters — Relays — Condensers — Resistors
— Bezels — Styli — Cartridges — Recording Tape — Probes — Instruments — Potentiometers — Crystals — Ferrite Beads —
Cores — Baluns — Terminals — Co-Axial Plugs & Sockets — Multi Connectors — Printed Circuit Boards — Copper Winding
— Wire — Etc. — Etc.

POPULAR KITS — TOP QUALITY — LOWEST PRICES

AUDIO

- 1 Direct Reading A.F. Gen.
- 2 SQ Wave Gen-10Hz-1MHz.
- 3 Solid State A.F. Gen.
- 4 Additive Freq Meter.
- 5 A.F. Tone Burst Gen.
- 6 Laboratory Solid State A.F. Gen.
- 7 Scaler/Divider Unit.
- 8 Crystal Freq Calibrator.
- 9 Direct Reading A.F. Meter (0-200KHz — 10MV-2V).
- 10 High Performance A.F. Gen.
- 11 White Noise Gen.
- 12 —
- 13 —
- 14 —

AUTOMOTIVE UNITS

- 15 Tacho & Dwell Angle for Service Stations.
- 16 Dwell Extender Unit.
- 17 Solid State — CDI.
- 18 All Electronic Ignition System.
- 19 Windscreen Wiper.
- 20 Tacho & Dwell Unit.
- 21 Brake Light Warning.
- 22 Emergency Flasher.
- 23 High Efficiency Flasher.
- 24 Solid State Volt Reg.
- 25 Car Theft Alarm System.
- 26 Ignition Analyser & Tachometer Unit.
- 27 Strobe Adaptor for Ignition Analyser.
- 28 Car Burglar Alarm.
- 29 —

BATTERY CHARGERS

- 30 6 Volt — 1 Amp.
- 31 12 Volt — 1 Amp.
- 32 Automatic H/Duty.
- 33 1-14 Volt — 4 Amp.
- 34 1973 Automatic Unit.
- 35 Constant Current Unit.
- 36 —
- 37 —

CONVERTERS — INVERTERS

- 38 12 VDC 300/600V 100W.
- 39 12 VDC 240 VAC 20W.
- 40 12 VDC 240 VAC 50W.
- 41 24 VDC 300 VDC 140W.
- 42 24 VDC 800 VDC 160W.
- 43 —
- 44 —

C.R.O. UNITS

- 45 1963 3" Calibrated.
- 46 1966 3" C.R.O.
- 47 1968 3" Audio C.R.O.
- 48 C.R.O. Electronic Switch.
- 49 C.R.O. Wideband P/Amp.
- 50 C.R.O. Calibrator.
- 51 —
- 52 —

INTRUDER WARNING SYSTEM

- 53 Electronic Thief Trap.
- 54 Infrared Alarm System.
- 55 Simple Burglar Alarm.
- 56 Light Beam Relay.
- 57 Car Burglar Alarm.

MULTIMETERS & V.O.M.

- 58 Protected D.C. Multimeter.
- 59 Meterless Voltmeter.
- 60 Wide Range Voltmeter.
- 61 F.E.T. D.C.
- 62 1966 V.T.V.M.
- 63 1968 Solid State V.O.M.
- 64 1973 Digital V.O.M. (1).
- 65 1973 Digital V.O.M. (2).
- 66 High Linearity A.C. Millivoltmeter.
- 67 —
- 68 —

PHOTOGRAPHIC UNITS

- 69 50 Day Delay Timer.
- 70 Regulated Enlarger Line.
- 71 Slave Flash Unit.
- 72 Sound Triggered Flash.
- 73 Solid State Timer.
- 74 Auto Trigger For Time Lapse Movies.
- 75 —
- 76 —

REGULATED POWER SUPPLIES

- 77 Laboratory Type 30/1 Unit.
- 78 Laboratory Type Dual Power Supply.
- 79 Serviceman's Power Supply.
- 80 Solid State H.V. Unit.
- 81 IC Variable Supply Unit.
- 82 1972IC Unit (E/T)
- 83 Simple 5V 1A Unit.
- 84 Simple 3-6V 3.5A Unit.
- 85 S/C Proof 0.30 VDC at 1A.
- 86 Reg 0-30VDC at 3A O/L Protected.
- 87 Variable Reg 12V-05A.
- 88 Reg O/Load & S/C Protection 60 VDC at 2A (1973) — EA.
- 89 —
- 90 —

R.F. INSTRUMENTS

- 91 Solid State Test Osc.
- 92 Signal Injector & R/C Bridge.
- 93 Solid State Dip Osc.
- 94 "Q" Meter.
- 95 Laser Unit.
- 96 Digital Freq Meter 200KHz.
- 97 Digital Freq Meter 70MHz.
- 98 IF Alignment Osc.
- 99 27MHz Field Strength Meter.
- 100 100KHz Crystal Cal.
- 101 1MHz Crystal Cal.
- 102 Solid State Dip Osc.
- 103 V.H.F. Dip Osc.
- 104 V.H.F. Powermatch.

- 105 V.H.F. F/S Detector.
- 106 S.W.R. Reflectometer.
- 107 R.F. Impedance Bridge.
- 108 Signal Injector.
- 109 1972 FET Dipper.
- 110 Digital Freq Meter.
- 111 Simple Logic Probe.
- 112 Frequency Counter & DVM Adaptor.
- 113 Improved Logic Probe.
- 114 Digital Logic Trainer.
- 115 Digital Scaler/Preamp.
- 116 Digital Pulser Probe.
- 117 Antenna Noise Bridge.
- 118 Solid State Signal Tracer.
- 119 1973 Signal Injector.
- 120 Silicon Diode Sweep Gen.

TRAIN CONTROL UNITS

- 124 Model Control 1967.
- 125 Model Control with Simulated Inertia.
- 126 Hi-Power unit 1968.
- 127 Power Supply Unit.
- 128 SCR-PUT Unit 1971.
- 129 SCR-PUT Unit with Simulated Inertia 1971.
- 130 Electronic Steam Whistle.
- 131 Electronic Chuffer.

TV INSTRUMENTS

- 134 Silicon Diode Sweep Gen.
- 135 Silicon Diode Noise Gen.
- 136 Transistor Pattern Gen.
- 137 TV Synch & Pattern Gen.

VOLTAGE CURRENT CONTROL UNITS

- 142 Auto Light Control.
- 143 Bright/Dim Unit 1971.
- 144 S.C.R. Speed Controller.
- 145 Fluorescent Light Dimmer.
- 146 Autodim-Triac 6 Amp.
- 147 Vari-Light 1973.
- 148 Stage, etc. Autodimmer 2KW.
- 149 Auto Dimmer 4 & 6KW.

RECEIVERS—TRANSMITTERS—CONVERTERS

- 153 3 Band 2 Valve.
- 154 3 Band 3 Valve.
- 155 1967 All Wave 2.
- 156 1967 All Wave 3.
- 157 1967 All Wave 4.
- 158 1967 All Wave 5.
- 159 1967 All Wave 6.
- 160 1967 All Wave 7.
- 161 Solid State FET 3 B/C.
- 162 Solid State FET 3 S/W.
- 163 240 Communications RX.
- 164 27 MHz Radio Control RX.
- 165 All Wave IC2.
- 166 Fremodyne 4-1970.
- 167 Fremodyne 4-1970.
- 168 110 Communications RX.
- 169 160 Communications RX.

- 170 3 Band Preselector.
- 171 Radio Control Line RX.
- 172 Deltahet MK2 Solid State Communications RX.
- 173 Interstate 1 Transistor Receiver.
- 174 Crystal Locked H.F. RX.
- 175 E/A 130 Receiver.
- 176 E.A. 138 Tuner/Receiver.
- 177 Ferranti IC Receiver.
- 178 Ferranti IC Rec/Amp.
- 179 7 Transistor Rec.
- 180 —
- 181 —

TRANSMITTERS

- 182 52MHz AM.
- 183 52MHz Handset.
- 184 144MHz Handset.

CONVERTERS

- 187 MOSFET 52MHz.
- 188 2-6MHz.
- 189 6-19 MHz.
- 190 V.H.F.
- 191 Crystal Locked HF & VHF.

AMPLIFIERS PREAMPS & CONTROL UNITS MONAURAL.

- 194 Mullard 3-3.
- 195 Modular 5-10 & 25 Watt.

STEREO

- 196 1972 PM 129 3 Watt.
- 197 Philips Twin 10-10W.
- 198 PM 10 + 10W.
- 199 PM 128-1970.
- 200 PM 132-1971.
- 201 ETI-425 Amp & Preamp.
- 202 ETI-425 Complete System.
- 203 ETI-416 Amp.
- 204 PM 136 Amp 1972.
- 205 PM 137 Amp 1973.

GUITAR UNITS

- 209 P/M 125 50W.
- 210 E/T 100 100W.
- 211 P/M 134 21W.
- 212 P/M 138 20W.
- 213 Modular 200W.
- 214 Reverb Unit.
- 215 Waa-Waa Unit.
- 216 Fuzz Box.

PUBLIC ADDRESS UNITS

- 219 Loud Hailer Unit.
- 220 P.A. Amp & Mixer.
- 221 P/M 135 12W.
- 222 Modular 25W.
- 223 Modular 50W.

CONTROL UNITS

- 225 P/M 112.
- 226 P/M 120.
- 227 P/M 127.

MIXER UNITS

- 229 FET 4 Channel.
- 230 ETI Master Mixer.
- 231 Simple 3 Channel.

TUNER UNITS

- 232 P/M 122.
- 233 P/M 123.
- 234 P/M 138.
- 235 Simple B/C.

PREAMPLIFIERS

- 237 Silicon Mono.
- 238 Silicon Stereo.
- 239 FET Mono.
- 240 Dynamic Mic Mono.
- 241 Dynamic Mic Stereo.
- 242 P/M 115 Stereo.
- 243 —

MISCELLANEOUS KITS


- 244 Geiger Counter.
- 245 Direct Reading Impedance Meter.
- 246 —
- 247 Electronic Anemometer.
- 248 Simple Proximity Alarm.
- 249 Pipe & Wiring Locator.
- 250 Resonance Meter.
- 251 Electric Fence.
- 252 Metronome Ace Beat.
- 253 Transistor Test Set.
- 254 Electronic Thermometer.
- 255 Flasher Unit.
- 256 Lie Detector.
- 257 Metal Locator.
- 258 Stroboscope Unit.
- 259 Electronic Canary.
- 260 240V Lamp Flasher.
- 261 Electronic Siren.
- 262 Probe Capacitance Meter.
- 263 Moisture Alarm.
- 264 AC Line Filter.
- 265 Proximity Switch.
- 266 Silicon Probe Electronic Thermometer.
- 267 Transistor/FET Tester.
- 268 Touch Alarm.
- 269 Intercom Unit.
- 270 Light Operated Switch.
- 271 Audio/Visual Metronome.
- 272 Capacitance Leakage.
- 273 Audio Continuity Checker.
- 274 Bongo Drums.
- 275 Simple Metal Locator.
- 276 Keyless Organ.
- 277 Musicolour.
- 278 Stereo H/Phone Adaptor.
- 279 Attack Decay Unit.
- 280 Tape Recorder Vox Relay.
- 281 Tape Slide Synchroniser.
- 282 Tape Actuated Relay.
- 283 Auto Drums.
- 284 IC Vol Compressor.
- 285 Audio Attenuator.
- 286 Thermocouple Meter.
- 287 Door Monitor.
- 288 Earth "R" Meter.
- 289 Shorted Turns Tester.
- 290 Zenor Diode Tester.
- 291 Morse Code Osc.
- 292 Simple Electronic Organ.
- 293 Pollution & Gas Analyser.
- 294 Universal H/Phone Adaptor.
- 295 Super Stereo ETI 410.
- 296 "Q" Multiplier.

PHONE
662-3506

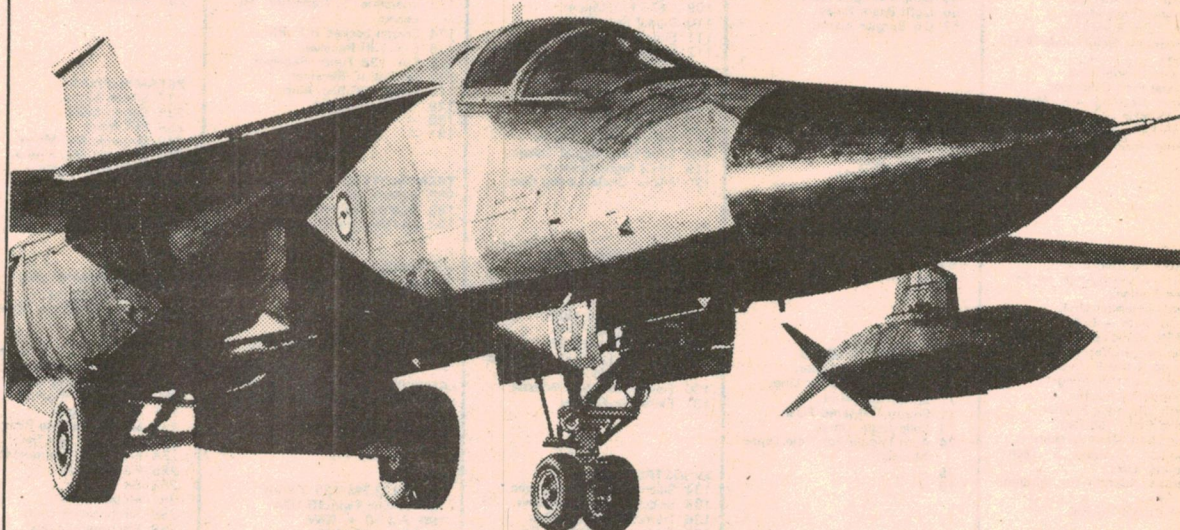E. D. & E. (SALES) PTY. LTD.
118 LONSDALE STREET, MELBOURNE — 3000 — VIC.

PHONE
662-3506

WE GIVE OUR ELECTRONICS ENGINEERS THE TIME AND OPPORTUNITY TO GO AS HIGH AS THEY LIKE.



As an engineer in the Air Force it's really up to you how far you want to go with your profession. For a start you'll have a wide range of advanced techniques and technology with which to work and learn and it will add enormously to your store of knowledge.

As well as this, we'll give you the time and opportunity to develop your skills. In whatever branch of engineering you serve: mechanical, electrical, aeronautical, electronics or communications. And you can do it all without having to worry about the financial traumas of the commercial world. You can devote your entire effort to becoming a better engineer. Which is just another advantage service life has over civilian life. Also you can become eligible to apply for a low interest Defence Force home loan.

QUALIFICATIONS Graduates who hold a University Degree or a Technical College Diploma in Mechanical, Electrical, Electronics, Communications or Aeronautical Engineering.

Undergraduates are eligible after one year of a three or four-year, or two years of a five-year Tertiary course or upon commencement of final year Technical College Diploma Course.



RAAF

The Air Force Careers Officer,
G.P.O. Box XYZ,
Your nearest State capital city.

Please send me further details of appointment as
an Engineering Officer in the Air Force.

Name _____

Address _____

Postcode _____

☐ Graduate ☐ Undergraduate ☐ Diploma Student

Adelaide 223 2891, Brisbane 31 1031, Canberra 65 2225,
Hobart 34 4116, Melbourne 61 3731, Perth 22 4355,
Sydney 212 1011.

INFORMATION CENTRE

ELECTRONIC ANIMALS: I have been a reader of Electronics Australia for some time now, and have enjoyed constructing many of the excellent projects that have been presented in the magazine.

However, as I am primarily interested in bionics (electronic animals etc.), I have noticed the lack of projects along that line in Electronics Australia. The only source material I have been able to obtain is from English magazines.

Unfortunately, back issues of these magazines are often hard to obtain, not to mention the problems involving Australian equivalents for English components. Because of this, do you think you could include some "electronic animal" projects in your magazine in future?

My colleagues and I are in unanimous agreement that Electronics Australia is an excellent magazine. (D.K., Willetton, WA).

Thank you for your comments about the magazine. We are pleased to see that our projects have been to your satisfaction. We have no plans at the present time to develop projects along the lines that you mention, although if interest is sufficiently high, we will certainly consider this possibility.

REPLACEMENT TRANSISTORS: In the December 1973 issue of E.A., Mr. H.B. of Dunolly wanted a replacement transistor for a 2SB494. In the Tandy Electronics Guide (Archer) the replacement listed is a 276-2006 power transistor in a TO-3 case. It retails for \$2.30.

I also have transistor troubles—could you tell me of any substitutes for Sanyo 2SB474. It comes out of the output of a Monarch SA616 and is in a PT-1 case. Is it PNP or NPN? Does it have any equivalents? Wedderspoon, the importers of Monarch gear, do not know of any SA616, do you? Would it be possible to work out power output from the (four) power transistors mentioned?

Would it be possible to supply me with some data about the 2SB474? Is it silicon or germanium? Have you published a transistor tester for power types such as the 2N3055? Your mag. is great, keep up the good work. (I.K., Dundas, NSW.)

Thank you for your comments about the magazine. As you can see, we have published the data on the 2SB494, for the information of Mr. H.B. We are unable to help with your transistor problem, as

it is not listed in any of our data books. We suggest that you contact one of the local transistor manufacturers, who may be able to provide a replacement.

We have not to date published a circuit for a transistor tester expressly for use with power transistors, but you can perform good-bad tests with our Transistor-FET checker of August 1971 (File No. 7/VT/9).

COMPUTER PARTS LIST: I wonder if it is possible to obtain a bulk parts list for the computer project—especially the semiconductors. (C.V., Lindfield, NSW).

By the time this letter appears in print, the computer will have been completed, and all parts lists for the various boards and sections will have been published. Simply collate all the parts lists, and you will have what you require.

IONOSPHERIC PREDICTIONS: I have always been of the opinion that the pictorial representation of ionospheric predictions is by far the best. The old method of representing the predictions of MUF and ALF in graphical form seems to have gone forever due, no doubt, to various reasons. However, these did convey a larger amount of information than the bar graph method. For example: since the ALF is not a sharp cut-off, one could estimate how much loss of signal strength there would be when working below it.

While it is impossible to convey the same amount of information on your bar graph predictions, I would like to suggest an improvement. Where the particular path on a particular frequency is below the MUF, but just below the ALF, the bar could be shown dotted. This would allow the user to discover the difference between a cut-out due to loss of F layer reflection and E layer absorption. (J.A., Preston, Vic.)

The points raised in your letter are similar to those raised several times in the past by both staff and readers. Unfortunately, we are unable to follow this suggestion for a number of reasons.

As you may readily appreciate, the preparation of the ionospheric prediction graph involves a fair amount of time, both for the staff member who does the initial preparation, and for the draughtsman. The graph as it appears in the magazine is not as presented to us by the Ionospheric Prediction Service.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Actual size dyeline transparencies: \$2 each. Specify positive or negative. We do not sell PC boards.

REPLIES BY POST: Limited to advice concerning projects published within the past 2 years. Charge \$2. We cannot provide lengthy answers, undertake special research or discuss design changes.

BACK NUMBERS: Only as available. Within last 6 months, face value. 7-12 months, add 5c surcharge; 13 months or older, add 10c surcharge. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

jaycar

PTY. LTD.

ELECTRONIC COMPONENTS DIVISION OF
JOHN CARR & COMPANY PTY LTD.


405 SUSSEX STREET
SYDNEY 2000
P.O. BOX K39, HAYMARKET

211-5077

211-5077

A professional system at a domestic price

ETI 427 GRAPHIC EQUALISER

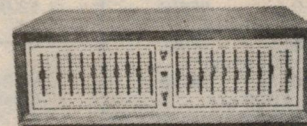


Features:

- 9 filters at octave intervals in each of two channels.
- Level control for each channel.
- $\pm 13\text{dB}$ range on each filter.
- Input voltage up to 3 volts.
- Output voltage up to 2 volts at less than .1% distortion.
- Frequency response 1.5Hz to 30KHz.

Comes with all coils prewound and a choice of either a timber cabinet or an attractive Marvplate cover making this kit ideal for professional P.A. or domestic Hi-Fi use. Complete kit (with Marvplate cover) **\$96.00** P&P \$3.00


ETI 422 STEREO AMPLIFIER

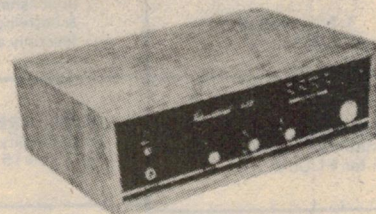

High power — 50w RMS per channel less than .2% distortion. Complete Kit only **\$118.00**

P&P \$3.00



ETI 420 4-CHANNEL AMPLIFIER

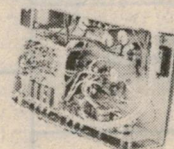

features 15watts per channel with SQ decoding. Complete kit **\$129.00**

P&P \$2.50

ETI 423 ADD ON DECODER AMP

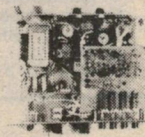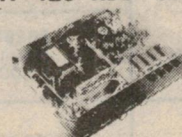

adapt your stereo to full 4 channel SQ operation **\$65.00** P&P \$2.00

332 PARRAMATTA RD, STANMORE, NSW 2040. PH. 56-7398.

106 ELECTRONICS Australia, May, 1975

It is prepared from a series of individual graphs contained in booklets and from a number of computer printouts. As this service appeals to only a limited number of readers, we cannot justify additional time spent expanding its format.

In addition, there is a further practical consideration to be made to your suggestion. Where do we select the cut-off point if we were to expand the format along the lines suggested? Such a cut-off point would, at best, be subjective, and could only be made after extensive field investigations. These difficulties would be compounded by the fact that ionospheric prediction is not an exact science anyway.

Obviously, we must have some cut-off point, and for the present format we have chosen those time intervals when it is predicted that the circuit will be open for at least 50 per cent of the month.

200MHz DIGITAL FREQUENCY COUNTER (EA December 1973): I shall be very grateful if you could clarify through your columns the pin connections of ICs 10 and 24 of the above project.

The connections on the printed board (73/c12) appear to be at variance with the circuit diagram on pages 42-43. It has been noted that pins 3 and 14 of IC10 have been transposed in the circuit diagram compared to the printed board. Similarly, pin 2 and pins 10 and 12 of IC24 have been transposed.

I have checked the above with the technical information provided for the ICs, but I am still confused. Perhaps the above does not disturb the function of the instrument, but the counter I built did not function, despite changing the bias resistors. The overflow IC has been connected as per technical data of IC 7473.

Thanking you and awaiting your reply in your good magazine. (P.L., Wondai, Qld.)

⊕ The differences that you have detected between the board pattern and the circuit diagram are illusory rather than real. Since the reset function is not being used on IC10, the J and K inputs may be interchanged, the Q and Q-bar outputs also being interchanged to restore the logic function.

This was done to simplify the printed circuit board pattern. As the logic function is not affected, there is no reason why the change should be shown in the circuit.

As you have not supplied any symptoms of the actual faults displayed by your counter, we are unable to provide a positive diagnosis. However, we would like to draw your attention to the errata for this project which were published in the April and June 1974 issues.

VARIABLE FREQUENCY SPEED CONTROL: Could you supply me with a circuit for a variable frequency supply to be used as a speed control on a synchronous motor. I have looked through past editions of the magazine without success. I need a supply rated at 200W, 240V. (K.B., Port Macquarie, NSW).

⊕ The reason you couldn't find one is because such a supply has never been published. K.B. However, a tip published in Circuit & Design Ideas some time ago may help: An audio oscillator connected to a very high power audio amplifier thence through a suitable voltage transformer is often useful in applications such as this. ⊕

Notes & Errata

DAUBLE (January 1975, File No. 3/MS/50). The parts list contains the following errors. The 120 ohm resistor should be 15 ohms, 1 x 6.8k should read 2 x 6.8k, and 2 x 68k should read 1 x 68k.

FUNCTION GENERATOR (February 1975, File No. 7/AO/22). In the diagram on page 53, the numbering of the wires to the range switch is incorrect. Leads 2 and 5 should be interchanged, as should leads 3 and 4.

MSA

No information is disclosed to clients until candidates have given permission during personal discussion.

GENERAL MANAGER

Electronics

To co-ordinate and lead the activities of a group of small companies involved in the manufacture, marketing and servicing of advanced electronic equipment —sold to a range of industries and to government, and directly to the general public. Location: Sydney.

The Managing Director, to whom the General Manager will report, is developing considerable other interests and seeks someone capable of taking the day-to-day control of the present group off his shoulders. With the right leadership, the combined sales of the companies concerned should soon reach \$10 million p.a. with some 500 employed. There are strong international affiliations.

The remuneration package, which includes company car and superannuation provision, will attract someone currently earning a basic salary in the area of \$15,000 to \$20,000 p.a.—and there are real promotion prospects.

Applicants, probably in their 40's, will be well qualified technically. More importantly their experience will have involved them in all facets of this industry, ideally including development work, marketing and long-term contract negotiation. A knowledge of modern management methods and a keen business sense are key requirements.

Applications should be addressed to:

Ian F. Rose

MANAGEMENT SELECTION AUSTRALIA

1st Floor, Royal Exchange Building, 56 Pitt Street, Sydney, NSW 2000

MSA2084

CALCOMP AUDIBLE CONTINUITY TESTER

SAFE

LIGHTWEIGHT



EFFECTIVE

COMPACT

- ★ Replaces buzzer and bells and danger of inductive kickback
- ★ Audio tone varies with resistance (0 to 50 OHM)
- ★ Open circuit 9V at the probes
- ★ Short circuit current 6mA
- ★ Fits your hand and your tool box
- ★ Safe for semiconductors
- ★ Measures only 70mm x 35mm x 95mm

★ \$12.93 including sales-tax plus P & P \$1.00

AUSTRALIAN TIME EQUIPMENT PTY LTD
192 Princes Highway, Arncliffe, N.S.W. 2205
Phone: 59 0291

A precision switch for those who can't afford a failure.



This is a precision switch for those who can't afford a failure.
We wanted a switch which met the highest industry standards of reliability, a switch that was perhaps extravagant in its structure, in the raw materials employed and in its mechanical and electrical life expectancy.
It would be machined out of a single piece of brass, finished in nickel plating, be insulated with Hostaform C and with contacts of rolled gold on silver.
It would be a miniature illuminated type with interchangeable lens caps of varying colours.
It would be at home in the most sophisticated professional or conventional equipment, but essentially where dependability was a foremost requirement.
It would probably be Swiss made.
Only Sloan met all our requirements.
This quality switch is now available from Plessey.


PLESSEY 

Plessey Australia Pty Limited Components Division Box 2 PO Villawood NSW 2163 Telephone 72 0133 Telex 20384
MELBOURNE: Zephyr Products Pty Ltd 56 7231 ADELAIDE: K. D. Fisher & Co. 223 6294 PERTH: H. J. McQuillan Pty Ltd 68 7111 N.Z.: Henderson (N.Z.) 6 4189

AC118 HOLT

TELE-TENNIS

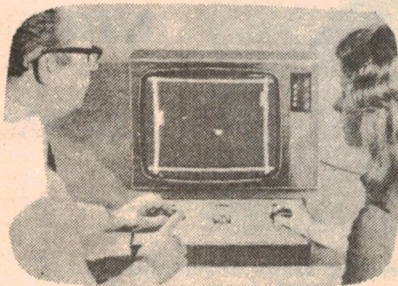THE POPULAR NEW ELECTRONIC GAME PLAYED ON THE TELEVISION SCREEN. AS DESCRIBED IN PRACTICAL WIRELESS.



PLAY THE GAME THAT'S SWEEPING THE NATION. YOU'VE SEEN IT IN PUBS, CLUBS AND ARCADES. NOW YOU CAN PLAY IT IN THE COMFORT OF YOUR OWN HOME. PLUGS INTO THE AERIAL OF YOUR VHF BLACK & WHITE OR COLOUR TELEVISION. DOES NOT INTERFERE WITH OTHER TV PROGRAMS. BUILT FROM 7 NEAT SUBSECTIONS. PURCHASE A COMPLETE KIT OR SUB-SECTION AT A TIME. WITH FULL INSTRUCTIONS.

Complete kit \$99.50 + P&P \$2.00

◆ NOTE.—WE HAVE MOVED TO LARGER PREMISES. (7000 SQ. FEET) AT 429 MURRAY ST.

NOVUS PORTABLE CALCULATORS

from \$15.95
ELECTRONIC SLIDE
RULE MODEL 4510

- Arithmetic
- Logarithmic
- Trigonometric
- Conversions
- Square Roots

\$79.50 + Postage
includes Sales Tax
WITH
CASE




NEW MODELS




7 TRANSISTOR RADIO KIT
Silicon transistors, complete with instruction book, carrying case and earphones.
Special Price \$8.75

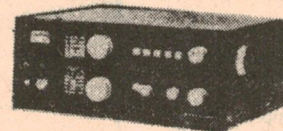10 TRANSISTOR RADIO KIT
With RF stage \$14.50
Post & Pack, 75c.



Trio Kenwood solid state communications receiver \$335 P/P \$4.

BARLOW-WADLEY RECEIVERS

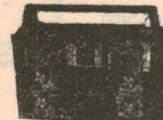

Model XCR-30 Mk II 500kHz to 31 MHz continuous coverage, crystal controlled reception of AM/USB/LSB/CW. Price \$260 + P & P.


- 1 Watt 3 channel C.B. transceiver
- With call system
- External aerial

Provision for external speaker, aerial and power supply \$49.50.
Post \$1 extra.

NC310 1 WATT
TRANSCIVER



A PROFESSIONAL TYPE SOUND LEVEL METER

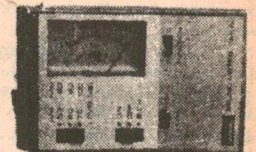

Check stereo speaker systems, Industrial noise, Group sound

\$69.00 + P&P

VHF CONVERTER TUNER



110-136 MHz couples to broadcast receiver, \$14.95 P & P 55c



New VORTEX STEREO CASSETTE DECK
AS USED IN EAP/M 144
— \$29.50

WILLIS TRADING CO.

PERTH G.P.O. Box No. X2217, W.A. 6001

429 MURRAY ST.,
PERTH, W.A.
21 7609 21 7600

Marketplace

FOR SALE

NEW COMPONENTS. Resistors $\frac{1}{4}$ & $\frac{1}{2}$ W, 5% range 10 to 10M ohm 3.5c each or \$3 per 100 mixed. Capacitors 'Green Caps' .001 to .022uF 10c. .033 & .047 11c. 0.1uF 13c. 0.22uF 17c. All 100 volt. 630 volt .001 to .0047 12c. .01uF 14c. .022 15c. .033 18c. .047 20c. 0.1 22c. Electro all 25V PCB mount 5, 10 & 25uF 12c. 50uF 16c. 100uF 18c. 220uF 25c. 470uF 32c. 1000uF 58c. Min order \$2. P&P 30c. GH Components. PO Box 378, Glen Waverley 3150.

EASY COLOUR PROCESSING. Kits available, neg & print chemicals, equiv. to C-22, C41, E3/4, Ektaprint 3, Agfa 82, etc., for Kodak, Agfa, Fuji, Ansco and others. Send SAE for price list or our product range and information service. Transcolor Services, PO Box 212 Newport, 2106.

100pF 5kV DISC CAPS 10 for \$2.50. Pair National Transceivers \$40. Ryan, 26 Underwood Cres, Qld. 4350.

SEMICONDUCTOR & COMPONENT BULK BUY SPECIALS: BC107/8/9 metal can 10 of one type \$2.40. EM402 1 Amp diodes 10 for \$1.20. 2N3055 power transistors 4 for \$5, 10 for \$9.90. Mixed resistors 100 for \$1, mixed capacitors 100 for \$1.50. 3.5mm plugs 10 for \$1.30. RCA plugs 10 for \$1.50. Minimum order \$2, post & packing 30 cents. SAE for free comprehensive price list. Grove Electronics, Box 158, Elizabeth, SA 5112.

BATTERY SAVER OR POWER SUPPLY basic kits. Comprising 1A tapped transformer 1.2V to 15V range, bridge rectifier, filter capacitor. \$7.70, P&P 80c. ECM Industries, Box 309 Hawthorn, Vic. 3122.

CALIBRATION SERVICE:


Haltronics offer a calibration service for digital meters and frequency counters to the following guaranteed standards: DC voltage to 0.05%; AC voltage to 0.1%; DC current to 0.1%; Resistance to 0.1%; Frequency to 1 part in 10^6 ie. 0.1Hz at 10MHz. Both commercial or magazine project instruments handled. Charges on an hourly rate. Haltronics Pty Ltd, 57 Sinclair St, Crows Nest, NSW. Ph. 02.92 0845.

TV REPAIR COURSE

This well designed black and white course has been designed by servicemen who know. Learn at home at your own rate. First set of lessons and tests \$10 inc. postage. All tests are corrected by your instructor.

MITCHELL'S TV SCHOOL,
35 Rosewarne Ave,
Cheltenham 3192.

TIME CLOCKS

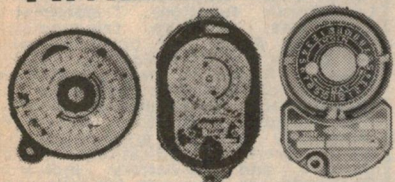

SANGAMO \$15
DAY OMIT DEVICE
VENNER \$12
Now with spring reserve
HORSTMANN \$12

240V 50 cs 15A Contacts
Used tested and guaranteed

PACK & POST \$1.00
Vic. & QLD. \$1.20 W.A. \$1.50

CLOCK DISPOSAL CO.
P.O. Box 147
LINDFIELD. N.S.W. 2070

VINTAGE RADIO COLLECTION: valves, books, speakers, etc. \$250 the lot, also comm Rx's—B28, 60KCS—30MCS \$75; Bendix BC348, \$50. Compass MN26C \$25. M. Smith, 99 Semaphore Road, SA 5019.

OPERATIONAL AMPLIFIER: 301 TO-5 80c. 307 TO-5 or MDIP 85c; 709 TO-5 or DIP 75c. 741 TO-5 or MDIP 80c. 747 (dual 741) TO-5 or DIP \$2.35. 748 (freq. adj. 741) MDIP \$1.15. Digital clock chips MM5311 28 pin BCD 6 digit mux \$16.90; MM5312 24 pin ipps BCD 4 digit mux \$13.90; MM5313 28 pin ipps BCD 6 digit mux \$15.90; MM5314 24 pin 6 digit mux \$17.90; MM5316 40 pin alarm 6 digit \$17.90. Data sheets for clock chips supplied on request with order. Worldwide Electronics, P.O. Box 308, Hornsby N.S.W. 2077.

AIRMEC WAVE ANALYSER type 248: Covers 2.5—300 MHz. Has 70dB dynamic range, 3 bandwidths of 20kHz, 17kHz, and 500kHz. Has AM and FM monitor. Measurements accurate to .25dB. Rangemaster Electronics, Brisbane. Ph. 91 3597.

WE SELL Construction plans. TELEVISION: 3D converter, \$25 camera, Kinescoping recorder, VTR Colour Converter. HOBBYIST: Electronic Microscope, 96-hour music system, voice typewriter, Morse Code to typewriter copier, solid state Teletype. TELEPHONE: Answering machine, pushbutton dialer, phonevision, Autodialer, Car Telephone Extension, legal connector. BROADCAST: Special effects Gen, Time Base Corrector. Plans \$7.50, air shipped from our USA research labs. COURSES: Telephone Engineering \$52. Security Electronics \$33. Investigative Electronics \$29.50. Super Hobby Catalog plus 1 year's Electronic Newsletter, air mailed \$1.00. Don Britton Enterprises, Suite 28, 280 Pitt St., Sydney, AUSTRALIA.

1 CENT SPECIAL FOR THIS MONTH ONLY FROM MICRONICS. .1uF/300VAC DUCON HERMASEAL CAPACITORS—1 CENT EACH (Limit of 20 to each customer at this price).

Polyester Greencaps .001uF/100v—20 for \$1. .01uF/100v—20 for \$1.20. Electrolytics SPECIAL 1000uF/18v Top Brand Pigtail—5 for \$2. COPPER CLAD BOARD SPECIAL 6" x 3"—5 for \$1. THE ABOVE SPECIALS FOR THIS MONTH ONLY! Act Now! Order yours before they sell out.

TRANSISTORS: BC108(BC548)—10 for \$1.80, BC179, BC157—6 for \$2, AS205(BC107)—10 for \$1.80, BC328, AS147—6 for \$2. **DIODES:** OA91—10 for \$1.50, OA95—10 for \$1.80, 1N914—10 for \$1.40, EM402 (200v, 1A)—10 for \$1.20, 1N4007 (1000v, 1A)—10 for \$1.95. **GERMANIUM TRANSISTORS:** 2N2613(AC126), 2N270(AC128), 2N410(2N1638), 2N412(2N1639)—10 for \$2.50, 2N1110(OC45), XB103(OC71), XA101(OC45), XA102(OC44)—10 for \$2. **INTEGRATED CIRCUITS** at GENUINELY BARGAIN PRICES—DIGITAL T.T.L. 7400, 7401, 7402, 7410, 7420, 7430, 7440—40c ea., 7404—45c, 7408—50c, 7413—80c, 7473, 7474, 7475—\$1.05 ea., 7441, 7442—\$1.75 ea., 7447—\$2.20. **LINEAR OP AMPS** 709 (D.I.P.)—80c, 741 (D.I.P.)—85c. **AUDIO AMP** PA234 1w R.M.S. incl. Cct Diagram—95c ea. **VALVE SOCKETS** (7 pin)—10 for 50c. **SLIDE SWITCHES** (18 pin)—4 for \$1. **TUNING CAPACITORS**—Larger type 2-gang—\$1.50, 3-gang—\$1.75. **ELECTROLYTICS AMAZING DISCOUNTS:** Top Quality Pigtails 47uF/10v—10 for 60c, 2uF/40v—10 for 90c, 2uF/300v—10 for \$2.50, 10uF/65v—10 for \$1.20, 40uF/70v—10 for \$2, 50uF/125v—6 for \$2, 100uF/200v—3 for \$2, 200uF/70v—4 for \$2, 500uF/25v—10 for \$2.50, 1000uF/6.5v—6 for \$2, 1000uF/18v—5 for \$2, 2000uF/18v—4 for \$2.50.

SUPER BARGAIN PACKS. A MUST FOR THE AMATEUR, HOBBYIST or SERVICEMAN. THESE are assorted mixed packs at sometimes $\frac{1}{4}$ of the normal price. **TRANSISTORS.** NEW, BRANDED pnp and npn germanium types (Mixed)—10 for \$1.75. **POWER RESISTORS:** 3w-7w, 5%, 10%. Top quality (Mixed)—25 for \$1.75. **ELECTROLYTICS:** Top quality Pigtails incl. low volt. and high volt.—25 for \$1.90. **CERAMIC CAPS:** Excellent quality low and high volt. types—50 for \$1. **TANTALUMS:** Miniature types at incredible price of 20 for \$1.90. **ZENER DIODES:** Consisting of 5 x 1w and 5 x 10w types—10 for \$2.95. **TAG STRIPS:** Including 11-pin with 2 securing lugs—40 for \$1.95. **COILS:** Miniature coils Osc. I.F. (Mixed) unmarked—20 for \$1.50. **STYROSEALS:** Including 630v types. Top grade—25 for \$1. **POTENTIOMETERS:** Including dual, single, switch and preset pots—20 for \$2.95. **SWITCHES:** Including rotary, slide and P.B. switches. Real value—10 for \$3.50. **SILICON DOUBLE DIODES:** (20v, 30ma) TD772, ideal for making up "AND" GATES—20 for \$1. Post and Pack 30c or extra for heavy parcels. MICRONICS, P.O. Box 175, Randwick, N.S.W. 2031.

Electronics & Hi Fi Enthusiasts ring HOBBY HIRE for

- oscilloscopes, dual and single trace
- signal generators
- function generators
- frequency counters
- VTVM's and VOM's
- auto-transformers and isolating transformers
- complete audio testing equipments
- TV tuning equipments
- high speed drill presses for PC boards
- hand-operated guillotines
- many others
- technical advice

Very reasonable rates. Free delivery and pick-up 7 days a week (50 km from Sydney GPO only). Please phone (02) 50 4361 after 6 p.m.

C.C.T.V. CLEARANCE SALE C.C.T.V.

Ideal for Hams, Experimenters or Security.



Concord cctv camera with 5" inbuilt electronic viewfinder. Features... 500lines resolution, RF or video output (switchable), std. C mount for lens, auto or manual light compensation, internal sync generation, high output signal.

Retails at \$650.00 Limited stock only at \$425.00 inc tax

HI-FI HOUSE
127 Forest Rd, HURSTVILLE
N.S.W. 579-4673
118 Keira St, WOLLONGONG N.S.W. 28-6661

MARKETPLACE — Cont.

ELECTRONIC EQUIPMENT: UV recorder, TV test gear, many other items, \$450 the lot. B. Haley, Flat 1, 43 Blair Street, North Bondi 2026.

BIG IC CLEARANCE:—74 series 00, 02, 03, 04, 06, 08, 10, 20, 30, 40, all 40c ea.; 7473, 75c; 7413, 7474, 7476, 80c; 7490, 85c; 709, 95c; 723, \$1.50; 741, 85c; 555, \$1.50; LM309K, \$3.15; TBA810 Amp. Module (E.A. Jan, 1975) \$6.20, power supply \$10.00, MJE340 \$1.97. P&P extra. Send S.A.E. for lists to:— Oliver Electronics Pty. Ltd., P.O. Box 4, St. Leonards, N.S.W. 2065.

BACK ISSUES ELECT. AUST: Elect. Today. Complete 1972-1973-1974. Offers please, 421 Forest Rd, Bexley, N.S.W. 2207.

NOVUS MATHEMATICIAN 4510 imm. del. \$81 pp. stud. T/Ex. NORSTATE ELECTRONICS, Box 582, Shepparton 3630.

AUDIO AMP IC'S. TBA 641 B 5W RMS with pc board and details... \$3.95. TBA 810 S 7W RMS with details \$3.35. Numerical indicators... 1/2" LED... \$3.15. 1/4" LED... \$2.80. Decoder driver and latch... \$2.45. LED's: Red... \$0.37, Green... \$0.95, Yellow... \$0.95. BC107, BC108, BC109... 25c. IN914... 15c. IN4004 1A. 400V. DIODES... 15c. IN4148... 15c. 709 DIL... \$0.56. 741 DIL... \$0.82. LM309K V. REG... \$3.85. 7800 Series v. regs. 5V. 8V. 12V. 15V. 18V. 24V. AT 1.0A... \$2.25.

Desolder tools, min switches, panel meters etc. Send for details by return service. All goods are ex-stock and by top manufacture with no hassle money back guarantee.

ELEKTRON DEVELOPMENTS, Box 305, Cloverdale, W.A. 6105.

BRIDGE RECTIFIERS 400V 10A \$3.50 ea. Zener diodes 6.2V 1W 30c ea. Timer IC NE555 \$1.50 ea., NE556 \$2.50 ea. Leds large red with mounting 35c ea., green 45c ea. P & P 30c. Dalby Electronics, P.O. Box 1, ERMINGTON 2115.

ELECTROLYTIC CAPS. (upright): 16v: 1, 4.7, 10uf — 8c, 30uf — 10c, 47uf — 11c, 100uf — 13c, 220uf — 24c, 470uf — 27c. 25v: 1uf — 9c, 4.7, 10uf — 10c, 30uf

— 12c, 47uf — 13c, 100uf — 17c, 220uf — 29c, 470uf — 30c, 1000/25v — 69c, 1000/15v — 45c, 1000/50v — \$1.09. Pigtaills arrive soon. JUMBO leds: red — 28c, grn. or yellow — 47c, Min. red — 21c. SN7400 — 30c g teed. Many other components at similar low prices. Send S.A.E. for full price lists. All items top quality & new. P & P — 35c. Return of post service. DIGGERMAN ELECTRONICS, Box 33, Coramba, N.S.W. 2466.

READER SERVICE

AUSTRALIAN RADIO DX CLUB: For overseas and long distance shortwave and medium wave reception for serious DX monitors. Monthly bulletin. Send 20c stamp for membership details to ARDXC, PO Box 227, Box Hill, Vic 3128.

PRINTED CIRCUIT BOARDS: Design, layout and artwork for PCB negatives or finished boards supplied. For further information phone 878 8945 or write to G. Sampson, 7 Homewood Street, Nunawading 3131.

PENFRIENDS: Have friends throughout the world. Start now, all ages welcome. Write to: The Pen Society, (Y.12), Chorley, Lancs, England.


WANTED

VALVE CHECKER, do older type valves. Particulars to J. Cooper, Hartley Street, Cowra, N.S.W. 2794.

ACOS REPLACEMENT LONG LIFE CARTRIDGES

Acos 90 Series — a family of pick-up cartridges covering all the main types needed today, each fitted with Diamond Stylus at no extra cost.

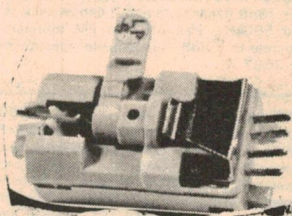- GP91-1 MONO CRYSTAL Stereo Compatible \$6.95
- GP91-2 HIGH OUTPUT MONO CRYSTAL Stereo Compatible \$6.95
- GP92 MONO CERAMIC Stereo Compatible \$7.55
- GP93 STEREO CRYSTAL \$8.55
- GP94-1 STEREO CERAMIC \$8.95
- GP94-5 STEREO CERAMIC FOR TRANSISTOR AMPLIFIERS \$9.95
- GP104 MINI STEREO CERAMIC \$9.95




All cartridges fitted with DIAMOND STYLUS at no extra cost

TECHNICAL DATA SHEETS SENT FREE ON REQUEST

Sole Australian Agents

AMPLION (A'ASIA) PTY. LTD.

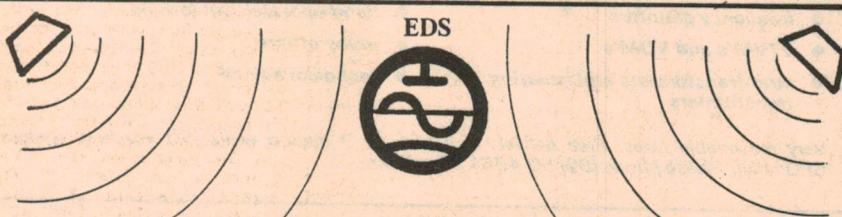31 Majors Bay Rd., Concord, Sydney, NSW. Phone 73 1227




- | | | |
|------------|---|-------|
| ★ MRX 25 | RADAR UNIT | \$145 |
| ★ CL 8960 | DOPPLER RADAR MODULE | \$28 |
| ★ CL 8960B | DOPPLER BURGLAR ALARM | \$75 |
| ★ CL 8960D | DOOR OPENER/CLOSER
(Automatically & selectively opens doors etc.) | \$90 |
| ★ CL 8960K | Burglar Alarm Kit
Case, D/R Module, Relay, P.C.B., all you need to build an equivalent to CL 8960B | \$49 |

● IN Development; Miniature Doppler Radar module the size of 2 cigarette packets ●

Electronic Developments & Service Pty Ltd
27 Buckley Street, Marrickville N.S.W. 2204

EMONA
best value in
Electronic
Calculators

MODEL SC40 POCKET SIZE

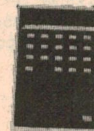

SCIENTIFIC COMPUTOR

— \$104. +15% sales tax if applicable, including: carry case, type 12, 240 V A.C. adaptor/charger.

Data entry and display in range of $\pm 1 \times 10^{-99}$ to $\pm 10 - 10^{99} \times 10^{99}$.

Answer in ten significant mantissa and two exponent digits. Floating decimal point or scientific notation. Double entry proof. $\times 2$, \sqrt{x} and $1/x$ functions. Exponential functions. Logarithmic functions. Trigonometric functions. Inverse trigonometric functions. Angle unit both in radian and degree. Fixed memory for 10-digit precision π and e . Two sub-memory registers for automatic bracketing and parenthesizing. Extra memory register. Radian-degree Indicator. Automatic busy/ready indicator, error indication, result overflow indication, display shut-off and Lo-battery indicator. Dual-sectioned keyboard for arithmetic and scientific functions. 14-digit LED display. Built-in computer-controlled energy saving circuit. Built-in rechargeable battery

Package & Postage By

Registered Airmail \$3.50 extra.

OTHER MODELS ALSO AVAILABLE

EMONA ENTERPRISES,
21 Judge St., Randwick,
N.S.W. 2031. Phone: 399-9061.

SOCKET SPANNER SET

32 piece metric brand new 1/2", 3/8" + 1/4" drive ratchet ext bar, T bar plug spanner etc in metal case only \$5.95 set. Post A 95c, B \$1.10, C \$1.25, C \$1.35.

CIRCULAR SLIDE RULE

3 3/4 in diameter. Will do the same work as the conventional slide rule. Instruction book included from \$1.60 each P & P 20c.

P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

\$26.00

(2 TELEPHONE SETS)

\$1 cartage to rail. Freight payable at nearest attended railway station.

ALTIMETERS

Sensitive type ex Air-Force, made by Pioneer USA. \$37.50. Post: A \$1.50, B \$1.60, C \$1.95, D \$2.75.

TEN CHANNELS VHF TRANSCEIVER

Types TR 1934 100-125 MHz and TR 1936 125-150 MHz. 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator. \$33.00

MINIATURE ELECTRIC MOTORS

1 1/2 to 3 volts DC. Ideal for model boats, cars, planes, etc. Strong torque. Only

75c each or 10 for \$5
P & P 20c ea. or 10 for 55c.

AIRCRAFT CLOCKS

Genuine Eight Day Jewelled movement, sweep second hand and start of trip indicator. Dash mountings. Ideal for car rallies.

\$22.50 P & P \$1.05.**ILFORD 17.5 mm SPROCKETED MAGNETIC TAPE**

1000 ft reels brand new original packing \$4.00 ea. quantity available

Post A 79c, B \$1.20,

C \$1.40, D \$1.70

TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$35 per drum \$1 cartage to rail freight payable at destination.

PRISMATIC COMPASSES

Genuine ex-army Mk 3, liquid damped, as new \$35.00 P & P \$1.05

MORSE KEY | MORSE KEY BUZZERS**\$1.40**

Post 20c.

\$4.25

Post 55c.

HALF INCH RECORDING TAPE

Top Grade 2400' on 10 1/2" reels. Ideal Video Experimenting. Only **\$3.50** per reel.

P & P A. \$1.55, B \$1.60
C. \$1.95, D. \$2.75.

UNI-SELECTORS

4 bank 25 position \$4 each.
P & P A. 70c, B. 85c, C. \$1, D. \$1.10.

ADLER FREQUENCY METER100KHz 20MHz **\$95****4 DIGIT RELAY COUNTERS**

50 volt DC, suit slot car Lap counters, etc.

\$1.25 each. P & P 30c.**NIBBLING TOOL**

Cuts sheet metal like a punch and die, trims, notches and cuts to any size or shape over 7/16 in.

ONLY \$7.85

Post 55c

NIFE CELLS

1.2 Volt, fully charged, 4in x 3in x 1in 4 AH.

\$1.50 each P & P 30c.**BC221**


Frequency Meters.

\$35.00**HANDY SIGNAL INJECTOR**

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On-Off Switch and indicator lamp. Size 1 1/2" Diam. 5" Long. Only

\$6.50 Post 55c**P.M.G. TYPE KEY SWITCHES.****45c** P & P 20c**TELESCOPES ZOOM FOCUSING**

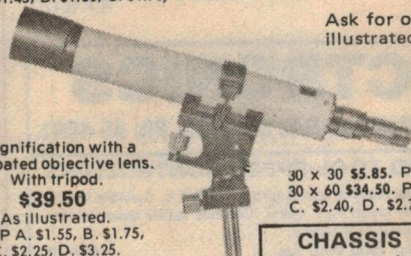25 x 30 **\$19.95** — 40 x 40 **\$28.95**
50 x 50 **\$37.50**. 60 x 60 **\$75.00** as illustrated.
P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$1.85.



60 magnification with a 60mm coated objective lens. With tripod.

\$39.50

As illustrated.

P & P A. \$1.55, B. \$1.75,
C. \$2.25, D. \$3.25.

WALKIE TALKIES

2-way radio, 7 transistor, PMG approved, set of 2 only **\$48.50**

1 watt, 11 transistor \$130.00 set of 2.

P & P A. \$1.45, B. \$1.60, C. \$1.75,
D. \$1.85.

SMALL COMPUTER PANELS

3in x 2in containing 2 valves, qty. of resistors, etc.

ONLY 75c P & P 30c.**ELECTRONIC FREQUENCY COUNTER**

Austronic type DFC-4 240V 50 cycle 0-100KHz **\$150**

IMPELLER PUMPS

New gunmetal body, Stainless Steel Shaft. Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sillage drains, etc. Approx size 8" x 5"

3/8" **\$19.95**1/2" **\$22.75**3/4" **\$27.50**

P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$2.

FREQUENCY METERS

AN URM 32 A 120 KHz to 1000 MHz, with two 40V power supply, \$125.00. \$1.00 cartage to rail, freight payable at nearest attended railway station.

CONDENSER LENS

2 1/2 in DIAM. 2in FL. \$1.50 each. Or \$2.50 per pair. P & P 20c.

522 Transceivers 100-150M CS

\$35.00

5" CRO TUBE 5 BPI **\$6.50** each.
Post: A 85c, B \$1.10, C \$1.25, D \$1.35.

LOUD HAILER

Battery operated, transistorised. In good used condition \$27.50 Post A 70c, B 85c, C \$1, D \$1.25.

POSTAGE KEY:

A: NSW.
B: Vic, Qld.
C: SA, NT, Tas, New Guinea,
D: WA.

VALVES**BRAND NEW IN CARTONS**

807	\$1.50	CV850	\$1.50
65N7GT	95c	1H6G	75c
5U4G	95c	832	\$5.00
EF50	75c	6AG5	80c
5Y3	\$1.99	6X4	\$2.25
2 x 2	75c	VR64	75c
		VT4C	75c

P & P 30c

PARABOLIC REFLECTORS PYREX MIRROR

36" dia. Ideal solar radio optical experimenting also decorating purposes. \$37.50 Sorry shop sales only.

RADAR TRANSCEIVER

X BAND WITH KLYSTRON ETC. **\$45.00**

Ask for our illustrated leaflets

30 x 30 \$5.85. P & P 55c.
30 x 60 \$34.50. P & P A. \$1.79, B. \$2.20, C. \$2.40, D. \$2.70.

CHASSIS PUNCH SET

Five sizes: 1/8 inch, 3/4 inch, 7/8 inch 1 inch and 1 1/8 inches. With taper reamer. **\$21.00**

P & P A. \$1.45, B. \$1.60, C. \$1.75
D. \$1.85.

SELSYN MOTORS MAGSLIP

Md. 11.....\$5.25 ea.
No. 19 TWO-WAY RADIOS.
Power supply, accessories, etc., \$35.

BINOCULARS

PRISMATIC Coated Lenses. Brand new. Complete with case.

7 x 35 Wide Angle.....	\$35.50
8 x 40 Wide Angle.....	\$39.50
7 x 50.....	\$31.50
10 x 50.....	\$32.50
12 x 50.....	\$33.65
20 x 50.....	\$37.95

P & P A. \$1.45, B. \$1.60, C. \$1.75,
D. \$1.85.

3000 TYPE RELAYS

P.M.G. 200Ohms — 1'500Ohm
Coils \$2.50 each. P & P 30c.

SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8". Only \$3.50 each, post 55c.

Cintel Oscillator and Electronic Counter, type 388.

\$250

SPECIAL lucky dip valve offer, 15 new valves in cartons for only \$2.95. We haven't got time to sort them, so you reap the benefit.

P & P A. 60c, B. 85c, C. \$1, D. \$1.10.

CONDENSER LENS

1 1/2 in diam. 1 1/2 FL. 50c each.
P & P 20c

MULTIMETER

A compact and handy tester for workshop or lab where quick circuit checks are required
DC Voltage 5-2.5K (20,000 OHMS per volt) AC Voltage 10-1000V (10,000 OHMS per volt) DC Current 0-50 UA. 0-2.5 MA. 0-250 MA. Resistance 0-6 Megohms Capacitance 100 UUF to 1UF. Decibels — 20 to plus 22 DB. Complete with instructions.

Only **\$15.95** ea. Post \$1.05.**EX ABC RECORDING TAPES TOP BRANDS**1/4" x 1200' on 7" reels. **\$2.50**1/4" x 2400' on 10 1/2" reels. **\$4.95**

P & P A. 72c, B. \$1.05, C. \$1.15, D. \$1.30

SOLENOIDS

Plunger Type 12V 300MA. Suit electric camera control, miniature trains, radio, etc.

\$2.50 P & P 20c200 MA 24 volt, 1/2 in push movement. **\$2.50** P & P 20c.**ZOOM FOCUSING MICROSCOPE**

Battery and mirror illuminated 600x magnification. Complete with dissecting kit slides etc.

P & P A. \$1.45, B. \$1.60,
C. \$1.75, D. \$1.85.

\$15.00**TRANSCEIVERS****Ex Army**

No 10 set, 38 to 55MHz with hand piece \$22.50. Battery to suit \$3.50 extra.
No C42 set, 36 to 40 MHz complete with 24V power supply, headphone, mic, leads etc \$65.00.
No C45 set, 23 to 38 MHz complete with mast, headphones, mic 24V power supply etc. \$95.00.
\$1.00 cartage to rail, freight payable at nearest railway station.

Crystal Earphone **75c** P & P 20cCassette head cleaners **\$1.50** P & P 20c**5" SPEAKERS**

6 OHMS 5 watts flush mounting with attractive bakelite cover plate mounting screws and off connecting wire \$4.50 ea or two for \$8.50.
P & P A. \$1.02, B. \$1.35, C. \$1.45, D. \$1.60.

COMMUNICATIONS RECEIVER

TCA R5223 Communications Receivers. These receivers don't cost as much as a R390 A or a RACAL but give you the opportunity of having a unit with a similar performance at a fraction of the cost. Continuous tuning from 1.5 to 30.5 Mhz. bands. First conversion is crystal locked into a 2.5 to 3.5 Mhz tunable second IF. 1 uV sensitivity. Drift from switch on to fully warmed up less than 3 Khz. Dial reset to less than 1 Khz. Calibration to within 3 Khz. (typically within 1 Khz.). Operation from 240V, 110V AC or 24V DC with inbuilt power supplies. 19 inch rack mounting. Accepts coaxial 50 or 75 ohm antennas. Diversity operation possible IF output for panadaptors etc. Complete with leads, headphones a bargain at \$295.00 Cartage to rail \$1. Freight payable at nearest attended railway station.

ALLIGATOR CLIPS

Sets of two with 14" connecting wire. 5 sets for \$1. Post 24c.

Deitch Bros.
70 OXFORD STREET, SYDNEY 2010

SORRY. NO C.O.D.

ELECTROLUBE FREEZER SPRAY

For isolating faults in transistors, diodes and other semi conductors, finding dry joints and bad contacts. Protecting heat sensitive components whilst soldering, checking thermostats and thermal cut-outs.


Electrolube is non-toxic and will not affect any paints, plastics, or rubbers.

Available from leading electrical wholesalers.



Information on FREEZER SPRAY and other ELECTROLUBE products is available from Australian agents:

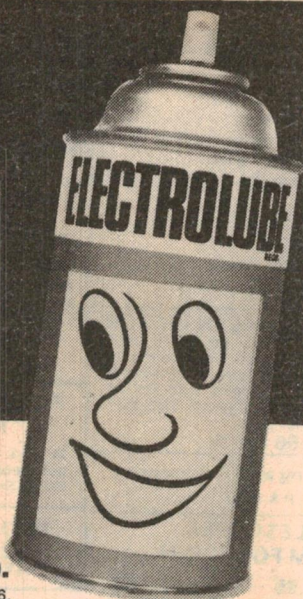RICHARD FOOT (AUSTRALIA) PTY. LTD.
63 HUME STREET, CROWS NEST, N.S.W. 2065. Telephone: 43-0326.



Advertising Index

A & R-Soanar Group	46
Akai	8
Amalgamated Wireless (A'sia) Ltd	36
Amplion (A'sia) Pty Ltd	110
Arlunya Pty Ltd	12
Audio Engineers Pty Ltd	18
Australian Time Equipment Pty Ltd	107
Bright Star Crystals Pty Ltd	97
British Merchandising Pty Ltd	41,87
BWD Electronics Pty Ltd	11
John Carr Pty Ltd	105
Maurice Chapman Pty Ltd	5
Classic Radio Service	90
Clock Disposal Co	109
Colrose Electronics	89
Deitch Bros	111
Dick Smith Electronics Pty Ltd	78,79,80
Directorate of Recruiting	104
E D & E (Sales) Pty Ltd	103
Electronic Agencies	98
Electronic Developments & Services	110
Elliot Machine Tools Pty Ltd	96
Emona Enterprises	110
Ferguson Transformers Pty Ltd	100
Richard Foot (Aust) Pty Ltd	112
General Electronic Services Pty Ltd	95
George Hawthorn Electronics	85
Haco Distributing Agencies Pty Ltd	OBC
Hi-Fi House	109
Hobby Hire	109
IRH Natronics Pty Ltd	42
Jacoby, Mitchell & Co Pty Ltd	30,83
Kenelec Systems	38
Kits Australia Pty Ltd	52,53
Lanthur Electronics	112
Leroia Industries Pty Ltd	7,43
Management Section Australia Ltd	107
Marconi School of Wireless	71
McGills Newsagency Pty Ltd	92
Mitchell's TV School	109
National Radio Supplies	106
NIC Instrument Coy	82
Panel Parts Pty Ltd	82
Philips Industries Ltd	2,26,27,68
Plessey Australia Pty Ltd	32,96,108
Radio Despatch Service	49
Rank Industries Ltd	IBC,6,13
Rose Music	16
Sanwa Electric Instrument Co	4
Peter Shalley Electronics Pty Ltd	76
Sony Kemtron Pty Ltd	IFC,20
Stott's Magna Sighter	91
Stott's Tech Correspondence College	93
Sungavure Pty Ltd	66,74,88
Tektronics Pty Ltd	60
Union Carbide Australia Ltd	50
United Trade Sales Pty Ltd	94
Vicom International	100
Wardrope & Carroll Fabrications Pty Ltd	107
Weston Electronics Pty Ltd	92
Willis Trading Co	108
Wireless Institution of Australia (NSW)	101
Wonder Wool Pty Ltd	91

LANTHUR ELECTRONICS

69 Buchanan Avenue, North Balwyn. 3104. Victoria. P.O. Box 162. Ph. 85 4061

TELEPHONE PLUGS

Standard 6.5 mm. Grey plastic handle.	0.35 each
Five for	\$1.50
Also as above but stereo type.	0.50 each
Five for	\$2.25
Above prices include postage.	

CRYSTAL EARPIECES

With cord & either 2.5 or 3.5 mm plug.	0.90 each
Six for \$5.00 including postage.	

BASIC ELECTRIC MOTOR SPEED CONTROLLER KIT

Suitable ac/dc or brush type motors only. Hand tools especially.	
Three amp. size	\$7.50
Ten amp size	\$8.50
Kit consists of—triac, resistor, pot, knob, diodes, 3 pin plug & base, & circuit	
Plastic cabinet suitable for above.	\$1.35
Prices include postage.	

BASIC LAMP DIMMER KIT

Will control incandescent lamps up to 1000 watts. Consists of—triac, diac, pot, knob, ferrite rod inductor, capacitors, resistors & circuit.	
	\$6.50
Plastic cabinet suitable for above.	\$1.35
Prices include postage.	

HAND TOOL SPEED CONTROLLERS

Complete ready to use. Approved by S.E.C. Suitable for any ac/dc or brush type motor. Controls speed down to stop with little loss of torque.	
Two amp. (500 watt) size.	\$15.75
Ten amp. (2400 watt) size.	\$25.00
Prices include certified post.	

METAL BOXES

Detachable top & bottom. Grey hammertone finish. Size 5½ x 5½ x 4¼ inches. One side has a 1½" and a ½" hole. Unused and suitable many uses.	
Four for \$3.95 including postage. Quantity discounts available.	

AMMETERS

Moving coil type. 0-10 amp. dc.	
Clear plastic face 65 x 55 mm.	
\$4.50 including postage.	

FERRITE RODS

Eight inches long by three-eighths inches diameter.	
Four for \$2.50 including postage.	0.75 each

DIN PLUGS

Five pin 180 degree stereo type.	0.35 each.
Five for \$1.50 including postage.	

SUBSCRIPTION SERVICE



**ELECTRONICS
Australia**

Subscription Rates

\$A12.00 per year
within Australia.
\$A15.00 per year
elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance, to Subscription Dept, PO Box M204, Sydney Mail Exchange, 2012. Subscription will start with first available issue.

Name

Address

Postcode Enclosed is.....for..... years

MUSICALITY.

As Japan's leading audio-only manufacturer, Sansui has always provided the vanguard in amplifier technology, design and development.

Three new models — the AU-5500, AU-6600 and the AU-7700 — combine the latest developments in design with electronic circuitry which produces an audio transparency — **musicality** — impossible to write into technical specifications. This abstract quality must be **heard**.

Power output of the three models range from 70 to 110 watts RMS into 8 ohm speaker systems. Total harmonic distortion is less than 0.15% — the figure for the AU-7700 being less than 0.1%. Frequency response figures are equally outstanding.

Your hi-fi specialist will gladly tell you of all the technical innovations in the new Sansui AU range. Listen **critically** to these new Sansui amplifiers. **Please be quite analytical.** We believe you will confidently select Sansui.

Here are abridged technical specifications:

SANSUI — AU-5500.

Output: 35 watts RMS per channel into 8 ohm speaker systems. THD: Less than 0.15%. Frequency response: 10-35,000 Hz. +0.5, -1 dB. Sensitivity suits magnetic cartridges, tuners, tape decks, etc. Recommended list price: \$419.

SANSUI — AU-6600.


Output: 45 watts RMS per channel into 8 ohm speaker systems. THD: Less than 0.15%. Frequency response: 10-40,000 Hz. +0.5, -1 dB. Sensitivity suits magnetic cartridges, tuners, tape decks, etc. Recommended list price: \$469.

SANSUI — AU-7700.

Output: 55 watts RMS per channel into 8 ohm speaker systems. THD: Less than 0.1%. Frequency response: 10-50,000 Hz. +0.5, -1 dB. Sensitivity suits magnetic cartridges, tuners, tape decks, etc. Recommended list price: \$549.

TWO YEAR WARRANTY. All Sansui amplifiers carry a full 2 year warranty. Effective service facilities are available throughout Australia.

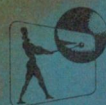The key to
the Success
of **SANSUI's**
New **AU.**
Series Stereo
Amplifiers.



**RANK INDUSTRIES
AUSTRALIA
PTY. LIMITED.**

Sydney Office: 12 Barcoo St., East Roseville, N.S.W. Tel. 406 5666. Melbourne Office: 68 Queensbridge St., South Melbourne, Vic. Tel. 62 0031. Canberra Office: 25 Molonglo Mall, Fyshwick, A.C.T. Tel. 95 2144. Adelaide Office: 2 Bowen St., Kensington, S.A. Tel. 332 4288. Brisbane Office: 14 Proe St., Fortitude Valley, Qld. Tel. 52 7333. Perth Office: 27 Oxford St., Leederville, W.A. Tel. 81 4988. INTERSTATE REPRESENTATIVE: N. T. Pfitzner's Music House, Smith St., Darwin, Tel. 3801.
W.A. Distributors for Sansui:
Atkins Carlyle Limited, 1-9 Milligan St., Perth, 6000. Tel. 22 0191.
Sansui equipment is manufactured by:
Sansui Electric Co. Ltd., 14-1, 2-chome, Izumi, Suginami-ku, Tokyo, Japan.



Sansui

RIA—SSAX3

Low distortion Excellent frequency response and all the power you need

Unquestionably, the SU3500 from TECHNICS is one of the most eyebrow-raising stereo amplifiers on the market today.

Elegant and functional design.

The SU3500 houses all the latest advances in audio amplification starting with an ultra low distortion of 0.08% THD.

Advanced Direct coupled differential OCL/CCT circuitry allow this unit to boast of a very wide frequency response and a power bandwidth of 5-70,000 Hz.


A full 86 watts RMS output gives you all the power you need.

The front panel houses controls such as 2 tape monitor, 2 speaker systems, click stop tone controls, pre-set volume and tone defeat switch are just some of the advanced features.

But don't rely on mere words when you can experience one of the best sounding amplifiers.

Visit your Technics dealer.

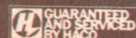There allow your ears and pocket to do the testing.



Technics